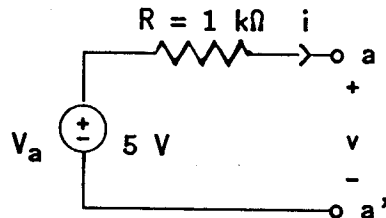



Chapter 1
Review of Linear Circuit Theory

- 1.1 Plot the v - i characteristic of the following circuit when $V_a = 5$ V.




- 1.2 A 2 kΩ resistor is connected across the terminals a - a' in the circuit shown above. Find the operating point of the resistor using the graphical method. Verify the result using Ohm's Law.

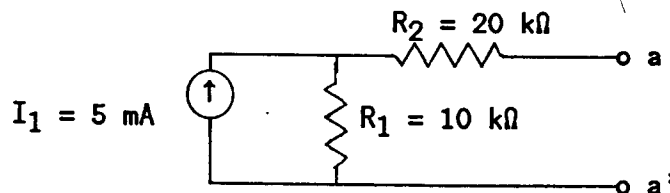
- 1.3 Find the Thevenin equivalent of the circuit shown below, as seen from the terminals a - a' .



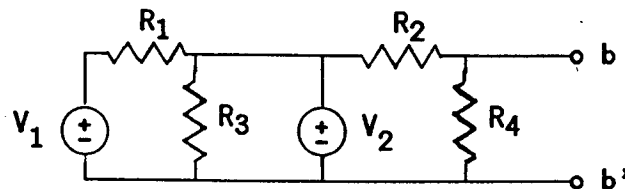
- 1.4 In the following circuit, use superposition to find the Thevenin equivalent seen at the terminals b - b' .



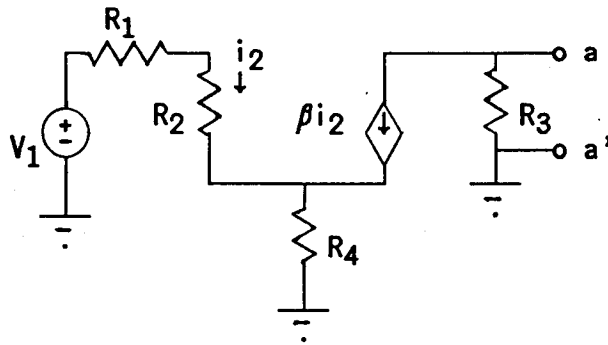
- 1.5 The circuit shown below contains a dependent source. Find the Thevenin equivalent of the circuit as seen at the terminals a - a' .



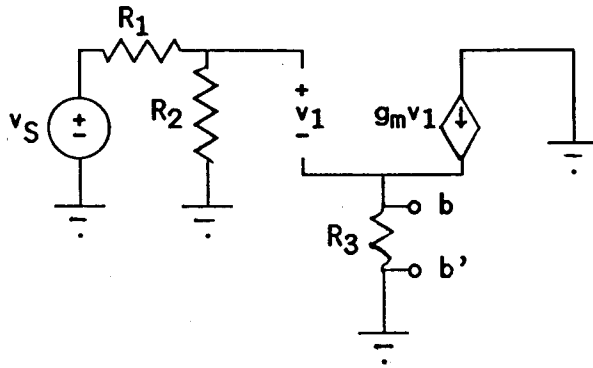
- 1.6 The circuit shown below contains a dependent source. Find the Thevenin equivalent of the circuit as seen at the terminals b-b'. Use the "test source" method to find R_{Th} .



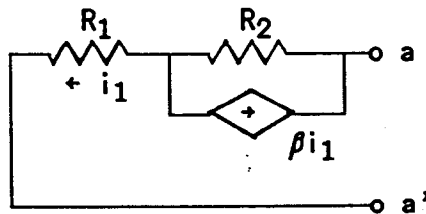
- 1.7 The circuit shown below contains a current-dependent current source. Find the equivalent resistance seen looking into the terminals a-a'. Use the "test source" method.



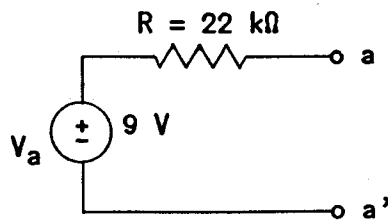
- 1.8 Find the Norton equivalent of the circuit shown below.



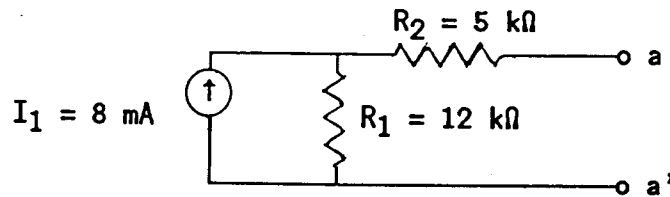
- 1.9 Find the Norton equivalent of the following circuit:



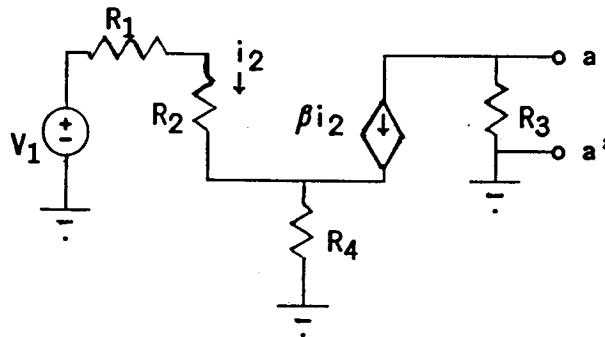- 1.10 The circuit shown below contains a dependent source. Find the Norton equivalent of the circuit as seen at terminals a-a'. This circuit is the same one analyzed in Prob. 1.5.



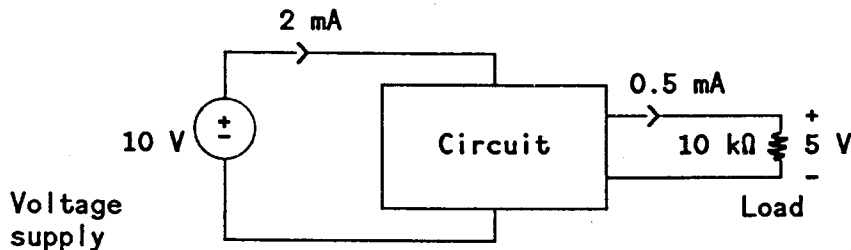- 1.11 Measurements with a voltmeter are made at the terminals of a circuit that contains only resistors, dc current sources, and fixed voltage sources. The meter has an internal resistance of $1\text{ M}\Omega$. With no other loads applied, the measured voltage is 12 V. With an additional external $1\text{ M}\Omega$ resistance connected in parallel with the meter, the measured voltage is 10 V. Find the Thevenin equivalent of the resistive circuit as seen at the measured terminals.
- 1.12 A circuit is powered from a 10-V voltage supply, as shown below. When the circuit drives a $10\text{ k}\Omega$ resistive load at 5 V, it draws 2 mA from this supply. Find the power dissipated in the load; find the power dissipated in the circuit.




SOLUTIONS TO PROBLEMS


Chapter 1

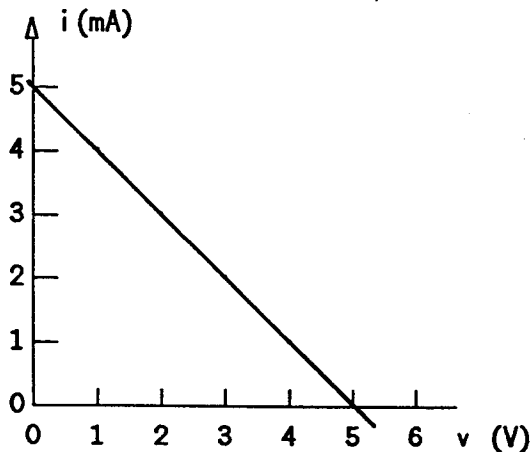1.1 Since the circuit is resistive (i.e., contains only a resistor and a constant voltage source), its v - i characteristic is a straight line. The v - i characteristic can be plotted by finding two points.

For $i = 0$ (open circuit), $v = V_a = 5$ V (v -axis intercept of the v - i characteristic). For $v = 0$ (short circuit), $i = V_a/R = 5$ mA (i -axis intercept). The resulting v - i characteristic is shown below.



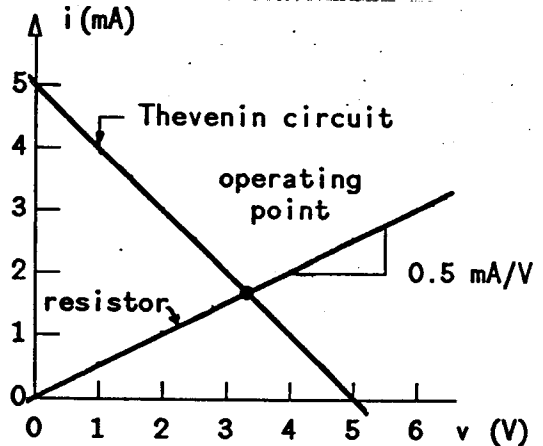1.2 The v - i characteristic of a 2 k Ω resistor consists of a straight line with slope $(1 \text{ mA})/(2 \text{ V}) = 0.5$ mA/V passing through the origin:



The point of intersection, i.e., the operating point, is seen to be 3.3 V; 1.6 mA. An analytical solution confirms this result. From Ohm's Law:


$$i = \frac{5 \text{ V}}{1 \text{ k}\Omega + 2 \text{ k}\Omega} = 1.67 \text{ mA}$$

$$v = (1.66 \text{ mA})(2 \text{ k}\Omega) = 3.33 \text{ V}$$

Alternatively, from the voltage divider relation:


$$v = 5 \text{ V} \frac{2 \text{ k}\Omega}{1 \text{ k}\Omega + 2 \text{ k}\Omega} = 3.33 \text{ V}$$

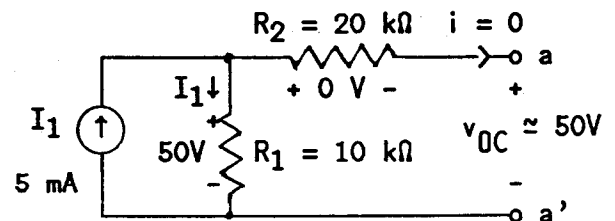1.3 The Thevenin voltage is equal to the voltage at the terminals a - a' under open-circuit conditions (i.e., with no other elements connected to the terminals):



Under open circuit conditions, all of the current I_1 flows through R_1 , causing a voltage drop

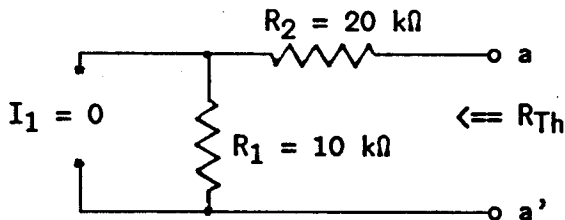
$I_1 R_1 = (5\text{mA})(10\text{k}\Omega) = 50\text{ V}$ to develop across R_1 . No voltage drop is developed across R_2 , since the current through it is zero. Thus, $v_{OC} = 50\text{ V}$. The Thevenin resistance is equal to the resistance seen at the terminals a-a' with I_1 set to zero (open circuit):



By inspection, $R_{Th} = R_1 + R_2 = 30\text{ k}\Omega$.

• Alternative method for finding R_{Th} :

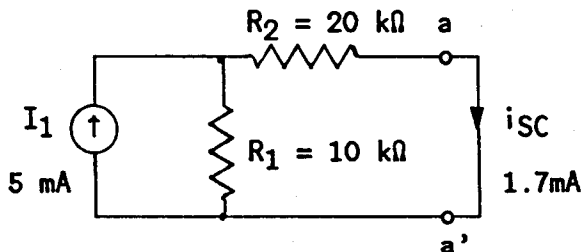Find the current flowing through a short-circuit applied to the terminals a-a':




The current flowing through the short-circuit is also equal to the current flowing through R_2 . From the current divider relation:

$$i_{SC} = I_1 \frac{R_1}{R_1 + R_2}$$

$$= 5\text{ mA} \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 20\text{ k}\Omega} = 1.67\text{ mA}$$

$$R_{Th} = \frac{v_{OC}}{i_{SC}} = \frac{50\text{ V}}{1.67\text{ mA}} = 30\text{ k}\Omega$$

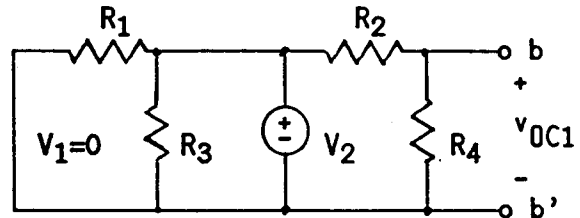
1.4 To find v_{Th} , find the separate contributions of V_1 and V_2 to v_{OC} . Here is the circuit with V_1 set to zero and V_2 "on":



From the voltage divider relation

$$v_{OC1} = V_2 \frac{R_4}{R_2 + R_4}$$

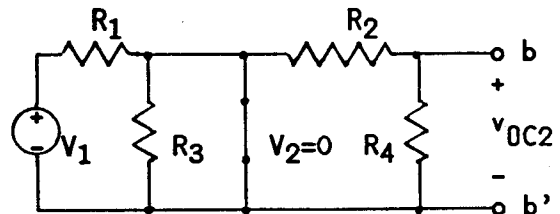
Here is the circuit with V_2 set to zero and V_1 "on":



Because a short circuit appears directly across the series combination of R_2 and R_4 (voltage drop equal to zero), $v_{OC2} = 0$. Thus v_{Th} is equal to v_{OC1} alone:

$$v_{Th} = v_{OC1} = V_2 \frac{R_4}{R_2 + R_4}$$

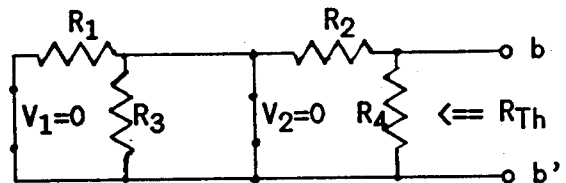
To find R_{Th} , set both V_1 and V_2 to zero (short circuits) and find the resistance seen at the terminals b-b'



By inspection, $R_{Th} = R_4 || R_2$. Note that the $R_3 || R_1$ combination is bypassed by the $V_2=0$ short circuit.

Alternatively, R_{Th} could be found by applying a short circuit to the terminals b-b' and using superposition to find the contributions of V_1 and V_2 to i_{SC} .

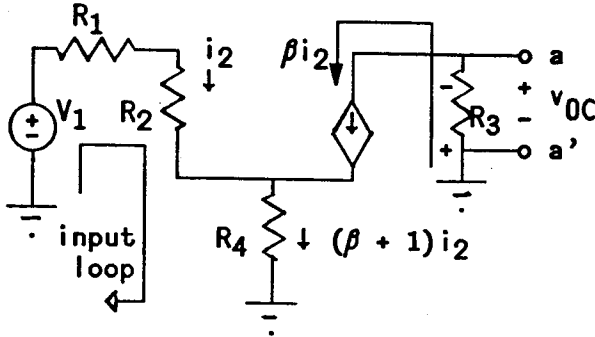1.5 Find the open-circuit voltage at the terminals a-a'.



The dependent source pulls a current βi_2 up from ground through R_3 , so that $v_{OC} = -\beta i_2 R_3$. Find i_2 by applying KVL to the "input loop" of the circuit. Note that a total current of $(\beta + 1)i_2$ flows through R_4 , with i_2 entering R_4 via R_2 and βi_2 entering R_4 via the dependent source. From KVL:

$$V_1 = (R_1 + R_2)i_2 + R_4(\beta + 1)i_2$$

Solving for i_2 yields


$$i_2 = \frac{V_1}{R_1 + R_2 + (\beta + 1)R_4}$$

so that

$$v_{OC} = -\beta i_2 R_3 = V_1 \frac{-\beta R_3}{R_1 + R_2 + (\beta + 1)R_4}$$

where $v_{Th} \equiv v_{OC}$.

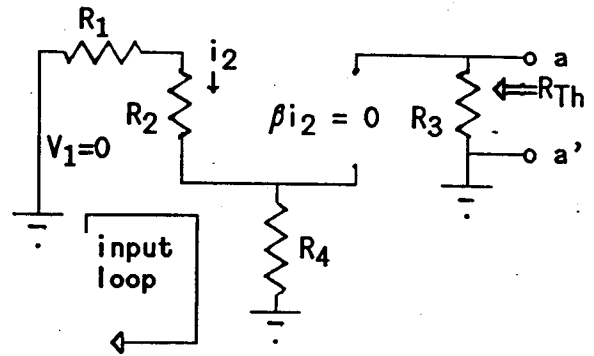To find R_{Th} , set V_1 to zero (short circuit) and find the resistance seen looking into the terminals a-a'.



From KVL around the input loop,

$$(R_1 + R_2)i_2 + R_4(\beta + 1)i_2 = 0$$


Solving for i_2 yields $i_2 = 0$. Consequently, the dependent source is set to zero as well (open circuit), and R_{Th} in the remaining circuit becomes just R_3 .

• Alternative method:

With V_1 on, the current flowing through a short circuit applied to the a-a' terminals becomes $-\beta i_2$, so that

$$R_{Th} = \frac{v_{OC}}{i_{SC}} = \frac{-\beta i_2 R_3}{-\beta i_2} = R_3$$

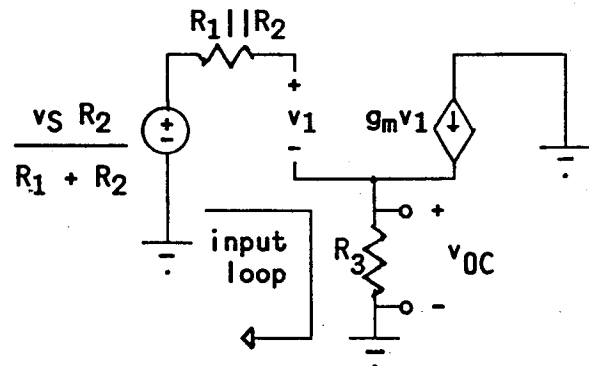1.6 Step 1: Represent v_S , R_1 , and R_2 by a simpler Thevenin circuit consisting of one resistor and one voltage source:



Next find v_{OC} (i.e., v_{Th} at the terminals b-b') by applying KVL to the "input loop". Note that no current flows through the open

circuit at the terminals where v_1 is defined, hence no current flows through $R_1 || R_2$, and the voltage drop across the resistance $R_1 || R_2$ is zero. Applying KVL yields

$$v_S \frac{R_2}{R_1 + R_2} = v_1 + g_m v_1 R_3$$


or

$$v_1 = v_S \frac{R_2}{R_1 + R_2} \frac{1}{1 + g_m R_3}$$

The open-circuit voltage thus becomes

$$v_{OC} = g_m v_1 R_3 = v_S \frac{R_2}{R_1 + R_2} \frac{g_m R_3}{1 + g_m R_3}$$

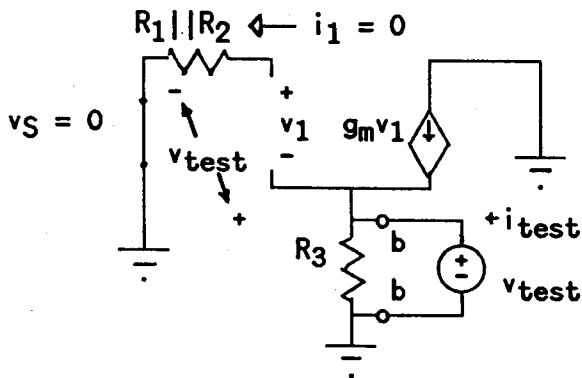To find R_{Th} , set v_S to zero and apply a "test" voltage source to $b-b'$. The value of R_{Th} is determined by v_{test}/i_{test} . Note that a test current source could also be used, but a test voltage source simplifies the computation because it directly fixes v_1 to a known value.



Since $i_1 = 0$, the voltage drop across $R_1 || R_2$ is zero, so that $v_1 = -v_{test}$.


The current i_{test} has two components, one through R_3 and one through the dependent source:

$$i_{test} = \frac{v_{test}}{R_3} - g_m v_1 = \frac{v_{test}}{R_3} + g_m v_{test}$$

The ratio of v_{test} to i_{test} can be computed from this equation, i.e.,

$$R_{Th} = \frac{v_{test}}{i_{test}} = \left[\frac{1}{R_3} + g_m \right]^{-1} \equiv R_3 || \frac{1}{g_m}$$

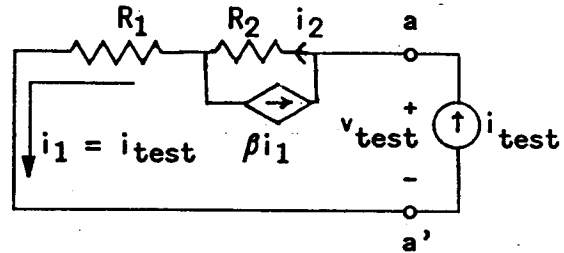1.7 Find R_{Th} by applying a test source to the terminals $a-a'$. In this case, a test current source works best because it directly fixes i_1 to the value i_{test} .



Applying KCL to node "a" yields

$$i_{test} = i_2 - \beta i_1 = i_2 - \beta i_{test}$$

Solving for i_2 results in

$$i_2 = (\beta + 1) i_{test}$$

Adding up the drops across R_1 and R_2 yields


$$v_{test} = i_1 R_1 + i_2 R_2 = i_{test} R_1 + (\beta + 1) i_{test} R_2$$

so that

$$R_{Th} = \frac{v_{test}}{i_{test}} = R_1 + (\beta + 1) R_2$$


The value of R_2 as seen from $a-a'$ has essentially been multiplied by the factor $(\beta + 1)$ via the action of the dependent source.

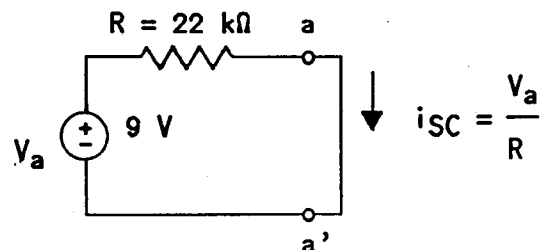1.8 The Norton equivalent consists of a current source and parallel resistance. The value of the source is equal to the short-circuit current measured at terminals $a-a'$:




where $i_{SC} = V_a/R = (9 \text{ V})/(22 \text{ k}\Omega) = 0.41 \text{ mA/V}$. The Norton resistance is found by setting the V_a source to zero (short circuit), yielding $R_N = R = 22 \text{ k}\Omega$.

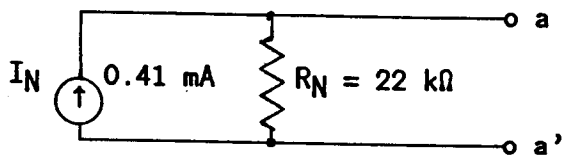The complete Norton equivalent circuit is shown below.



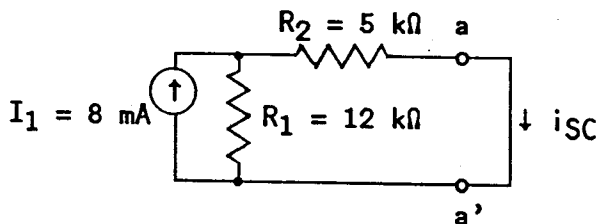
1.9 The Norton current is found by applying a short-circuit to the a-a' terminals:




From current division:

$$i_{SC} = \frac{R_1}{R_1 + R_2} I_1 = \frac{12 \text{ k}\Omega}{12 \text{ k}\Omega + 5 \text{ k}\Omega} 8 \text{ mA} = 5.65 \text{ mA}$$

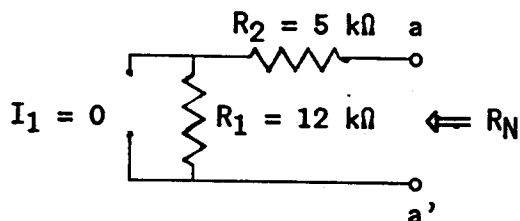The Norton resistance is found by setting I_1 to zero (open circuit) and observing the net resistance at the terminals a-a':



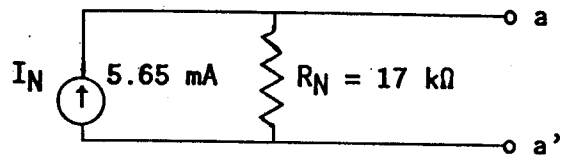$R_N = R_1 + R_2 = 5 \text{ k}\Omega + 12 \text{ k}\Omega = 17 \text{ k}\Omega$. The complete Norton equivalent of the circuit is shown below.




1.10 The open-circuit voltage of this circuit was found in Prob. 1.5:

$$v_{OC} = -\beta i_2 R_3 = V_1 \frac{-\beta R_3}{R_1 + R_2 + (\beta + 1)R_4}$$


Similarly, the Thevenin resistance, computed with V_1 set to zero, was found to be $R_{Th} = R_3$. These elements of the Thevenin equivalent circuit can be used to find the element values of the Norton equivalent circuit. Specifically, $R_N = R_3$, and

$$I_N = \frac{v_{OC}}{R_3} = \frac{-\beta V_1}{R_1 + R_2 + (\beta + 1)R_4}$$

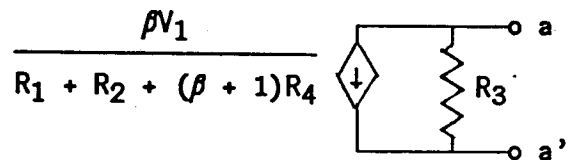The Norton equivalent of the original circuit can be represented in the following form:




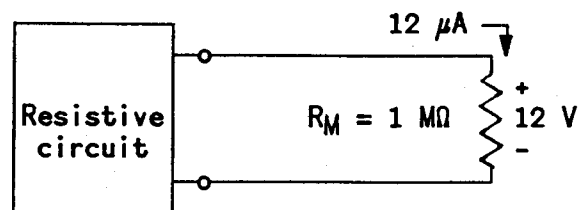1.11 Here is a summary of the measurements. With the meter alone, the current out of the resistive circuit is $(12 \text{ V})/(1 \text{ M}\Omega) = 12 \mu\text{A}$:




With an additional $1\text{ M}\Omega$ resistor connected, the current out of the resistive circuit becomes
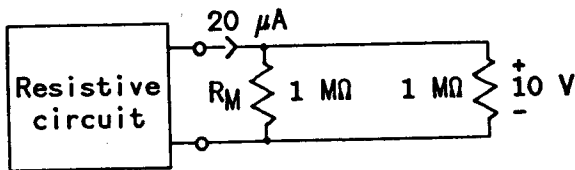
$$\frac{10\text{ V}}{(1\text{ M}\Omega) \parallel (1\text{ M}\Omega)} = 20\ \mu\text{A}$$



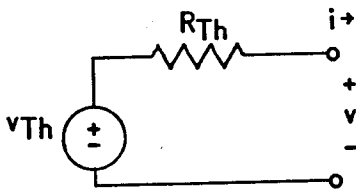For the general Thevenin equivalent shown below, $v = v_{Th} - iR_{Th}$.



Applying the known data results in:

$$12\text{ V} = v_{Th} - (12\ \mu\text{A})R_{Th}, \text{ and}$$

$$10\text{ V} = v_{Th} - (20\ \mu\text{A})R_{Th}.$$

Simultaneous solution of these equations yields $v_{Th} = 15\text{ V}$; $R_{Th} = 250\text{ k}\Omega$

1.12 The power extracted from the supply is equal to $(10\text{ V})(2\text{ mA}) = 20\text{ mW}$. The power dissipated in the load is $(5\text{ V})^2/(10\text{ k}\Omega) = 2.5\text{ mW}$. (Alternatively, $(5\text{ V})(0.5\text{ mA}) = 2.5\text{ mW}$). The power dissipated in the circuit is equal to the difference: $20\text{ mW} - 2.5\text{ mW} = 17.5\text{ mW}$