
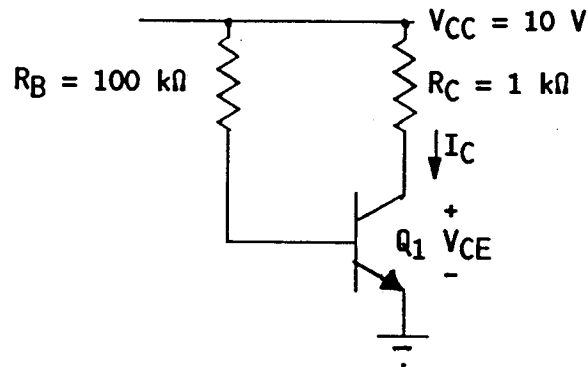


Chapter 7
Biasing

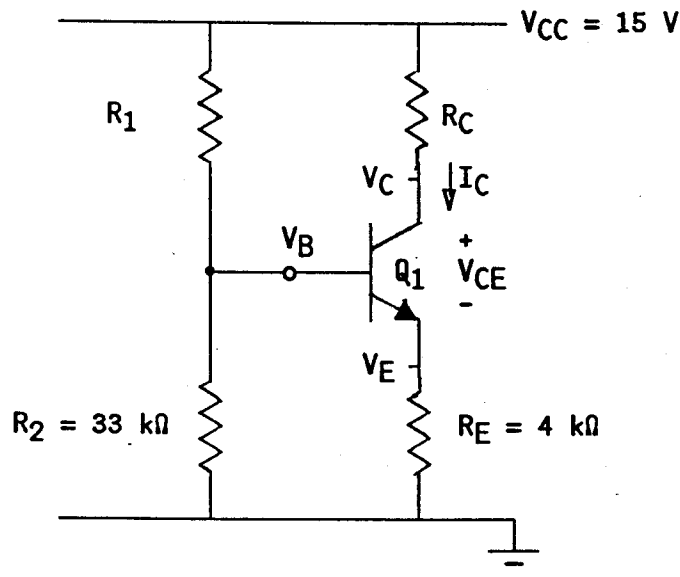- 7.1 A BJT is biased in the fixed bias configuration shown below. What is the maximum value of β_F that will still allow Q_1 to be biased in the constant-current region? For this BJT, $V_f = 0.6 \text{ V}$ and $V_{sat} = 0.2 \text{ V}$.




- 7.2 The operating point of the BJT in the feedback bias configuration shown below is to be set to $V_{CE} = 6 \text{ V}$ and $I_C = 1.7 \text{ mA}$. β_F is large, but its value is not known. Choose appropriate values of R_1 and R_C .




- 7.3 Repeat the previous problem if the BJT is replaced by an n-channel MOSFET with $K = 0.1 \text{ mA/V}^2$ and $V_{TR} = 0.5 \text{ V}$. In this case, let $R_2 = 1 \text{ M}\Omega$. The current through the device is to be set to $I_D = 1.7 \text{ mA}$ with $V_{DS} = 6 \text{ V}$.

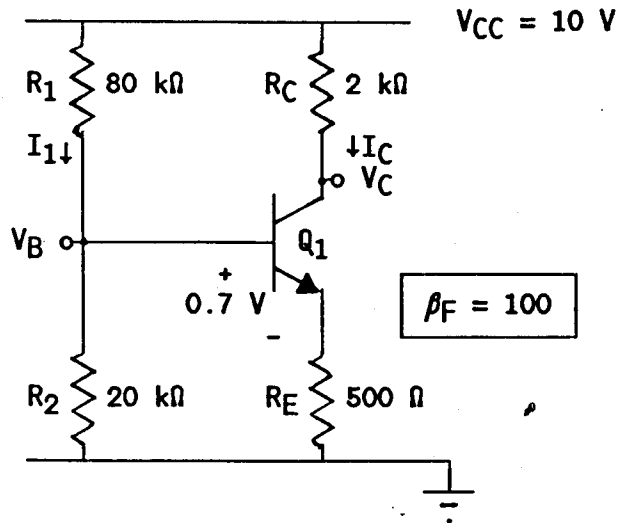
- 7.4 Consider the BJT bias circuit shown below. Find the dc values of I_C , I_1 , V_B , and V_C . For this BJT, $\beta_F = 100$ and $V_f = 0.7$ V.



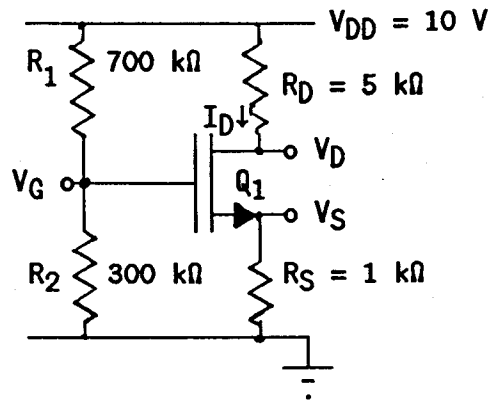
- 7.5 Repeat the previous problem for the case $\beta_F = 50$.
- 7.6 Find the dc operating point of the MOSFET circuit shown below if $K = 4$ mA/V² and $V_{TR} = 1.5$ V.



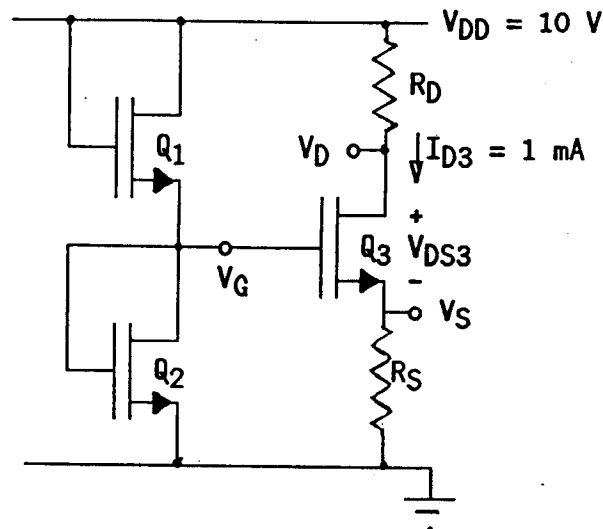
- 7.7 Consider the MOSFET circuit shown below. Choose R_D and R_S so that Q_3 operates in the constant-current region with $I_{D3} = 1$ mA. What value of V_{DS3} results from your design? The MOSFETs are all matched with $K = 2$ mA/V² and $V_{TR} = 2$ V.



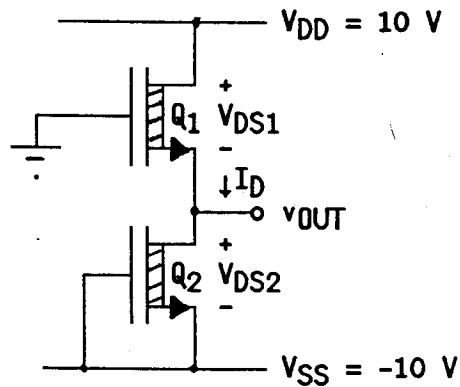- 7.8 Consider the depletion-mode MOSFET circuit shown below. Both devices have parameters $K = 0.2 \text{ mA/V}^2$ and $V_{TR} = -2 \text{ V}$. Find the bias current I_D and the voltages v_{OUT} , V_{DS1} and V_{DS2} .




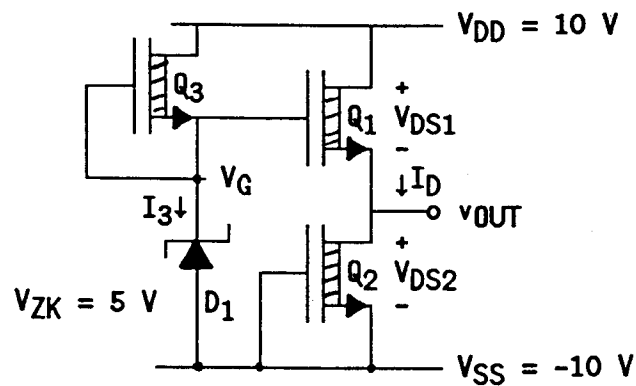- 7.9 Repeat the previous problem for the MOSFET circuit shown below.




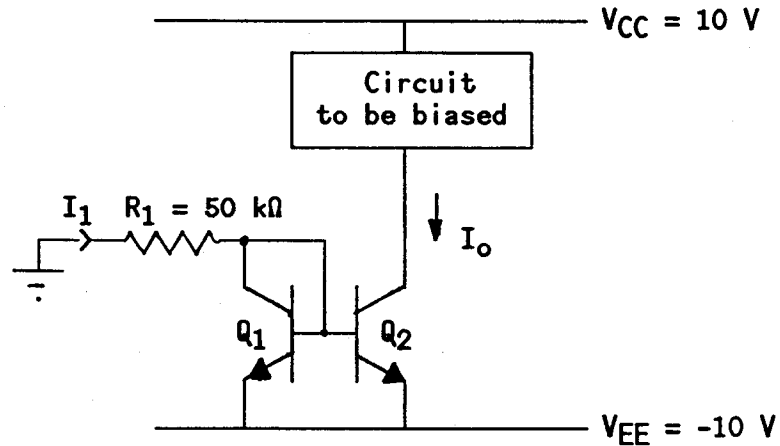7.10 Consider the BJT current mirror bias circuit shown below. Q_1 and Q_2 are perfectly matched with $V_f \approx 0.7$ V.


- Find an approximate value for I_o .
- Compute a more accurate value for I_o at room temperature ($\eta V_T = 25$ mV) if $I_{E0} = 10^{-12}$ A and $I_{B0} = 10^{-14}$ A. Do not assume a value for V_f .



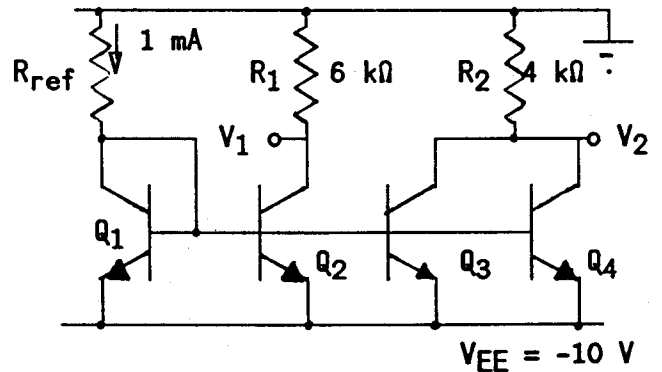
7.11 In the following current mirror all transistors are matched. Find R_{ref} , V_1 , and V_2 if $V_f \approx 0.7$ V. Neglect base currents with respect to collector currents.



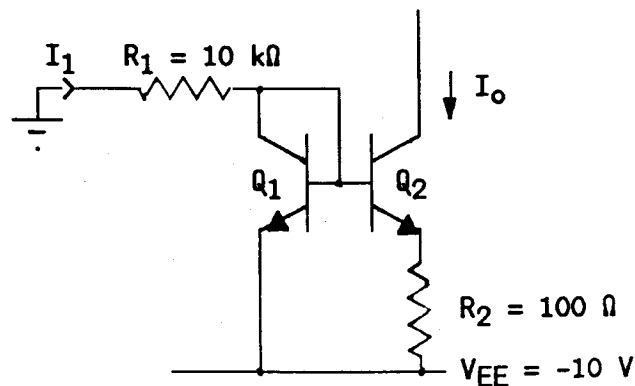
7.12 In the Widlar source shown below, find the bias current I_o at room temperature ($\eta V_T = 25$ mV) if $V_f \approx 0.7$ V



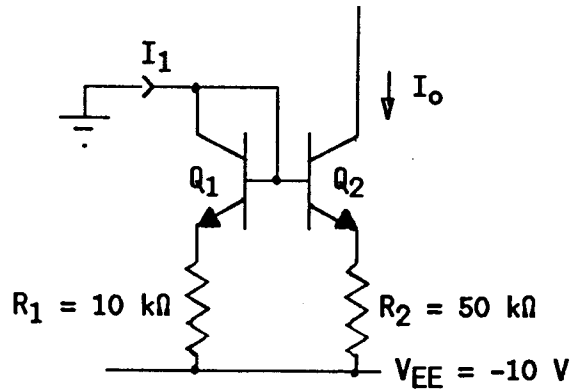
- 7.13 Find the approximate bias current I_o in the Wilson source shown below if $V_f \approx 0.7$ V.



- 7.14 The hybrid CMOS circuit shown below contains both an enhancement-mode and a depletion-mode n-channel device and a p-channel pullup load. If $K_1 = K_3 = 1$ mA/V², $K_2 = 4$ mA/V², and $|V_{TR}| = 1$ V for all transistors, find the bias current I_o and the node voltages V_A and V_B . Ignore the "body" effect.

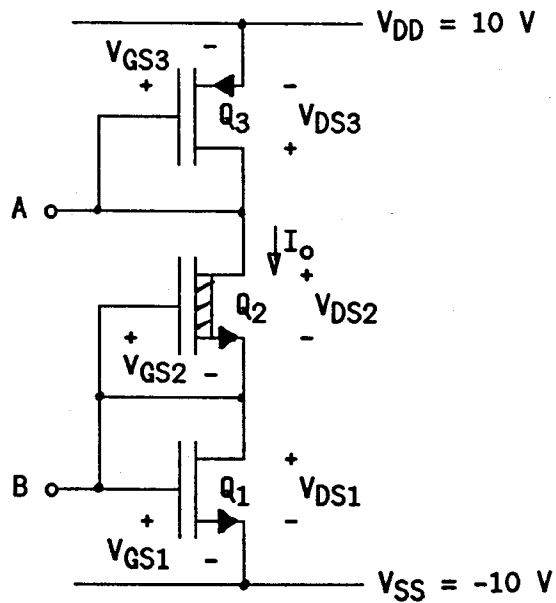

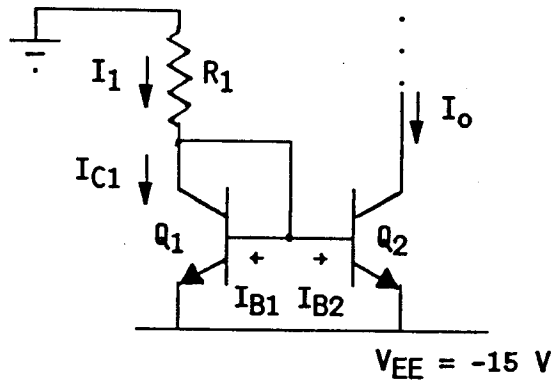- 7.15 The transistors in the following circuit are biased with $\beta_F = 10$. For the base-emitter junction of each device, $V_f = 0.7$ V.



a) Find the required value of the reference current I_1 so that the mirrored current I_o becomes 5 mA.

b) The circuit functions poorly because I_1 includes the large base current components required of Q_1 and Q_2 . Using one extra transistor, design a modified current mirror that will improve this situation.

Solutions

Chapter 7

7.1 For the bias configuration shown,

$$I_B = \frac{V_{CC} - V_f}{R_B} = \frac{10 \text{ V} - 0.6 \text{ V}}{100 \text{ k}\Omega} = 94 \mu\text{A}$$

The current I_C will be equal to $\beta_F I_B$ when the BJT operates in the constant current region. As β_F increases, I_C will increase, reducing V_{CE} . The BJT will enter saturation when V_{CE} is reduced to V_{sat} . This point will be reached when

$$I_C = \frac{V_{CC} - V_{sat}}{R_C} = \frac{10 \text{ V} - 0.2 \text{ V}}{1 \text{ k}\Omega} = 9.8 \text{ mA}$$

The β_F responsible for creating this I_C and forcing the BJT into saturation is equal to

$$\frac{I_C}{I_B} = \frac{9.8 \text{ mA}}{0.094 \text{ mA}} \approx 104$$

7.2 With β_F large, the emitter and collector currents will be approximately equal:

$$I_E = \frac{\beta_F + 1}{\beta_F} I_C \approx I_C$$

If I_C is to equal 1.7 mA, the voltage V_E (relative to ground) must be set to $I_E R_E = (1.7 \text{ mA})(4 \text{ k}\Omega) = 6.8 \text{ V}$. The voltage V_B must be set to $V_E + V_f$. For $V_f \approx 0.7 \text{ V}$, $V_B = 7.5 \text{ V}$.

If the base current is assumed negligible compared to the current through R_1 (an assumption that must be confirmed), the voltage divider can be used to approximate V_B :

$$V_B \approx \frac{R_2}{R_1 + R_2} V_{CC}$$

This equation can be rearranged to yield $\frac{R_2}{R_1 + R_2} = \frac{V_B}{V_{CC}} = \frac{7.5 \text{ V}}{15 \text{ V}} = 0.5$

This ratio will be realized for the values $R_1 = R_2 = 33 \text{ k}\Omega$. To the extent that i_B is neglected, the current through these resistors will be on the order of $(15 \text{ V})/(66 \text{ k}\Omega) = 230 \mu\text{A}$. This current will be at least five times greater than i_B for β_F greater than about 40.

With I_C set to 1.7 mA by the proper choice of R_1 , the value of V_E will be 6.8 V, as discussed above. Setting V_{CE} to 6 V thus requires that V_C be set at 12.8 V, i.e. the voltage drop across R_C must be set to

$V_{CC} - V_C = 15 \text{ V} - 12.8 \text{ V} = 2.2 \text{ V}$
With $I_C = 1.7 \text{ mA}$, this voltage drop will be realized with

$$R_C = \frac{2.2 \text{ V}}{1.7 \text{ mA}} = 1.3 \text{ k}\Omega$$

7.3 Assume the MOSFET operates in the constant-current region. This assumption must be confirmed later. If I_D is to equal 1.7 mA, the voltage V_{GS} must be set to

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TR} = \sqrt{\frac{1.7 \text{ mA}}{0.1 \text{ mA/V}^2}} + 0.5 \text{ V}$$

$\approx 4.6 \text{ V}$. If I_D is set to the desired value, the voltage across R_E will be $I_D R_E = (1.7 \text{ mA}) \times (4 \text{ k}\Omega) = 6.8 \text{ V}$. Setting V_{GS} to 4.6 V thus requires a V_G (gate voltage to ground) of $6.8 \text{ V} + 4.6 \text{ V} = 11.4 \text{ V}$.

Applying the voltage divider relationship to R_1 and R_2 results in

$$V_G = \frac{R_2}{R_1 + R_2} V_{CC}$$

For this circuit, the voltage divider can be applied without approximation, since $I_G = 0$. The above equation can be rearranged, yielding

$$\frac{R_2}{R_1 + R_2} = \frac{V_G}{V_{CC}} = \frac{11.4 \text{ V}}{15 \text{ V}} = 0.76$$

or

$$R_2 = 0.76(R_1 + R_2)$$

$$(1 - 0.76)R_2 = 0.76 R_1$$

$$R_1 = 0.316 R_2 = 316 \text{ k}\Omega$$

Setting V_{DS} to 6 V requires that V_D be biased at 12.8 V, as in the previous problem. Thus the voltage drop across R_C must again be set to


$$V_{CC} - V_D = 15 \text{ V} - 12.8 \text{ V} = 2.2 \text{ V}$$

With $I_D = 1.7 \text{ mA}$, this voltage drop is realized with

$$R_C = \frac{2.2 \text{ V}}{1.7 \text{ mA}} = 1.3 \text{ k}\Omega$$

Note that the condition $v_{DS} > v_{GS} - V_{TR} = 4.1 \text{ V}$ is satisfied in this circuit; the MOSFET is confirmed to operate in the constant current region.

7.4 First form a Thevenin equivalent of R_1 , R_2 , and V_{CC} . In this case, $R_B = R_1 || R_2 = 16 \text{ k}\Omega$ and $V_{BB} = V_{CC} R_2 / (R_1 + R_2) = 2 \text{ V}$:

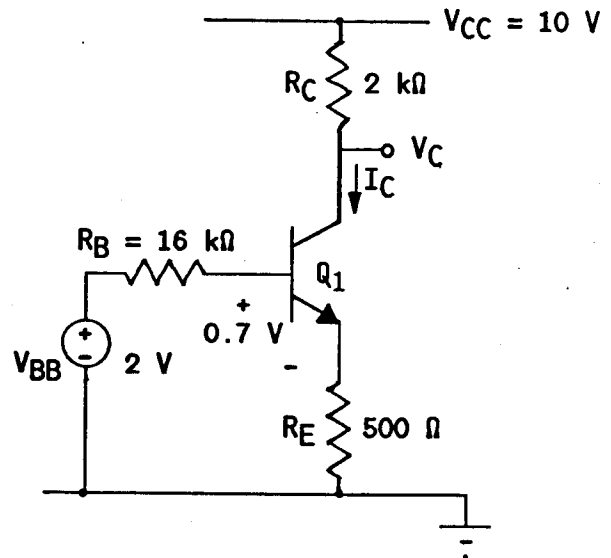

From this representation of the circuit, we note, via KVL, that

$$I_B = \frac{V_{BB} - V_f}{R_B + (\beta_F + 1)R_E} = \frac{2 \text{ V} - 0.7 \text{ V}}{16 \text{ k}\Omega + (101)(500 \Omega)} = 19.5 \mu\text{A}$$

and

$$I_C = \beta_F I_B = 100(19.5 \mu\text{A}) = 1.95 \text{ mA}$$

$$I_E = \frac{\beta_F + 1}{\beta_F} I_C = \frac{101}{100} 1.95 \text{ mA} = 1.97 \text{ mA}$$

For this value of I_E , V_E becomes $I_E R_E = (1.97 \text{ mA})(500 \Omega) = 0.99 \text{ V} \approx 1 \text{ V}$. Adding V_f to V_E yields $V_B = 1.7 \text{ V}$.

From the original circuit, it follows that

$$I_1 = \frac{V_{CC} - V_B}{R_1} = \frac{10 \text{ V} - 1.7 \text{ V}}{80 \text{ k}\Omega} \approx 104 \mu\text{A}$$

Finally, $V_C = V_{CC} - I_C R_C = 10 \text{ V} - (1.95 \text{ mA})(2 \text{ k}\Omega) = 6.1 \text{ V}$.

7.5 As before (see solution to the

previous problem)

$$I_B = \frac{V_{BB} - V_f}{R_B + (\beta_F + 1)R_E}$$

In this case $\beta_F = 50$, so that

$$I_B = \frac{2 \text{ V} - 0.7 \text{ V}}{16 \text{ k}\Omega + (51)(500\Omega)} = 31.3 \mu\text{A}$$

and

$$I_C = \beta_F I_B = 50(31.3 \mu\text{A}) = 1.57 \text{ mA}$$

$$I_E = \frac{\beta_F + 1}{\beta_F} = \frac{51}{50} 1.57 \text{ mA} = 1.6 \text{ mA}$$

For this value of I_E , V_E becomes $I_E R_E = (1.6 \text{ mA})(500\Omega) = 0.8 \text{ V}$. Adding V_f to V_E yields $V_B = 1.5 \text{ V}$.

From the original circuit, it follows that

$$I_1 = \frac{V_{CC} - V_B}{R_1} = \frac{10 \text{ V} - 1.5 \text{ V}}{80 \text{ k}\Omega} \approx 106 \mu\text{A}$$

$$\text{and } V_C = V_{CC} - I_C R_C = 10 \text{ V} - (1.6 \text{ mA})(2 \text{ k}\Omega) = 6.8 \text{ V}.$$

7.6 Here is an iterative solution method that is somewhat different from the solution methods given in the text. From the voltage divider,

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = (10 \text{ V}) \frac{300 \text{ k}\Omega}{700 \text{ k}\Omega + 300 \text{ k}\Omega} = 3 \text{ V}$$

This equation is exact because $I_G = 0$ into the gate of the MOSFET.

Assume that Q_1 operates in the constant-current region with


$$I_D = K(V_{GS} - V_{TR})^2$$

For the circuit shown, $I_D = V_S/R_S$, and $V_{GS} = V_G - V_S$, so that the constant-current region equation becomes

$$\text{or } V_S/KR_S = (V_G - V_S - V_{TR})^2$$

$$V_S = V_G - V_{TR} - \sqrt{V_S/KR_S}$$

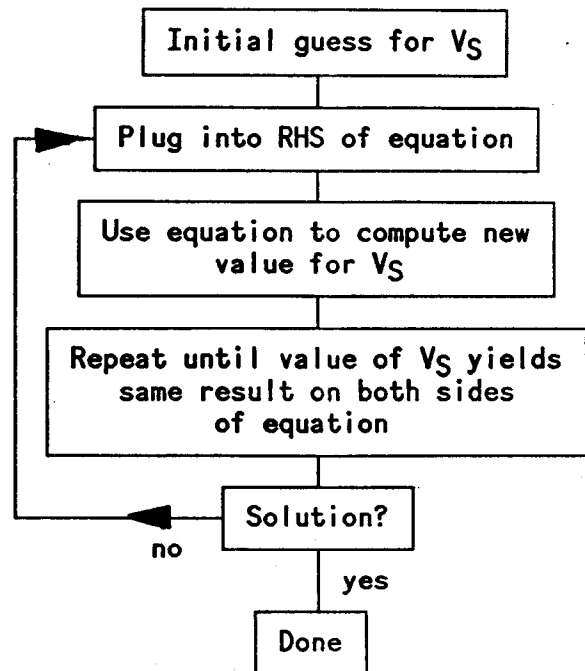This equation cannot be solved in closed form but can be solved numerically via successive iteration:



Apply the method to this problem:

- Initial guess: $V_S = 0$, with $V_G - V_{TR} = 3 \text{ V} - 1.5 \text{ V} = 1.5 \text{ V}$
 $KR_S = (4 \text{ mA/V}^2)(1 \text{ k}\Omega) = 4 \text{ V}^{-1}$
- Here are the results of the successive iterations:

$$V_G - V_{TR} - \sqrt{V_S/KR_S} = 1.5 \text{ V} - \sqrt{0} = 1.5 \text{ V}$$

$$1.5 \text{ V} - \sqrt{1.5 \text{ V}/4 \text{ V}} = 0.89 \text{ V}$$

$$1.5 \text{ V} - \sqrt{0.89 \text{ V}/4 \text{ V}} = 1.03 \text{ V}$$

$$1.5 \text{ V} - \sqrt{1.03 \text{ V}/4 \text{ V}} = 0.99 \text{ V}$$

$$1.5 \text{ V} - \sqrt{0.99 \text{ V}/4 \text{ V}} = 1.0 \text{ V}$$

$$1.5 \text{ V} - \sqrt{1.0 \text{ V}/4 \text{ V}} = 1.0 \text{ V}$$

V_S repeats itself, indicating that the iteration is complete. For this value of V_S ,

$$I_D = V_S/R_S = (1 \text{ V})/(1 \text{ k}\Omega) = 1 \text{ mA}$$

$$V_{GS} = V_G - V_S = 3 \text{ V} - 1 \text{ V} = 2 \text{ V}$$

• Check the current equation:

$$I_D = K(V_{GS} - V_{TR})^2 \\ = (4 \text{ mA/V}^2)(2 \text{ V} - 1.5 \text{ V})^2 = 1 \text{ mA}$$

This answer is consistent with the results of the iteration.

For the computed value of I_D :

$$V_D = V_{DD} - I_D R_D \\ = 10 \text{ V} - (1 \text{ mA})(5 \text{ k}\Omega) = 5 \text{ V}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S) \\ = 10 \text{ V} - (1 \text{ mA})(5 \text{ k}\Omega + 1 \text{ k}\Omega) = 4 \text{ V}$$

Note that this value of V_{DS} exceeds $V_{GS} - V_{TR} = 1.5 \text{ V}$; the initial assumption of constant-current region operation is correct.

7.7 If I_{D3} is to equal 1 mA, then V_{GS3} must be set to the value

$$\sqrt{\frac{I_{D3}}{K_3}} + V_{TR} = \sqrt{\frac{1 \text{ mA}}{2 \text{ mA/V}^2}} + 2 \text{ V} = 2.7 \text{ V}$$

The matched MOSFETs Q_1 and Q_2 will produce a voltage $V_G = V_{DD}/2 = 5 \text{ V}$ at the gate of Q_3 . The source voltage V_S of Q_3 must thus be set to 2.3 V, so that V_{GS3} will equal 2.7 V. With I_{D3} at 1 mA, V_S will be set to 2.3 V if $R_S = 2.3 \text{ k}\Omega$.

The value of R_D can be anything as long as Q_3 is not forced out of the constant-current region. The minimum value of V_{DS3} for constant-current region operation is

$V_{GS3} - V_{TR} = 2.7 \text{ V} - 2 \text{ V} = 0.7 \text{ V}$
With V_S at 2.3 V, the drain voltage V_D could be set as low as 3 V. This condition would occur if R_D were as large as

$$\frac{V_{DD} - V_D}{I_{D3}} = \frac{10 \text{ V} - 3 \text{ V}}{1 \text{ mA}} = 7 \text{ k}\Omega$$

7.8 The voltage sum $V_{DS1} + V_{DS2} =$

$= V_{DD} - V_{SS}$ is large, hence we can assume Q_1 and Q_2 to operate in the constant-current region. This assumption will be confirmed later.

With $V_{GS2} = 0$, the current I_D becomes $I_D = K_2(0 - V_{TR2})^2 = (0.2 \text{ mA/V}^2)(-2 \text{ V})^2 = 0.8 \text{ mA}$. If this current is to flow through the matched device Q_1 , then V_{GS1} must equal zero also. Hence $V_{OUT} = 0$ and $V_{DS1} = V_{DD} = 10 \text{ V}$

$$V_{DS2} = 0 - V_{SS} \\ = 0 - (-10 \text{ V}) = 10 \text{ V}$$

For both devices, the condition $V_{DS} > V_{GS} - V_{TR} = 0 - (-2 \text{ V}) = 2 \text{ V}$ is met; Q_1 and Q_2 are confirmed to operate in the constant-current region.

7.9 See the solution to the previous problem. In this circuit, $V_{GS2} = 0$ also, so that I_D is again set to $K_2(0 - V_{TR2})^2 = 0.8 \text{ mA}$ and V_{GS1} is set to zero. With $V_{GS3} = 0$, the current I_3 through Q_3 is set to 0.8 mA; I_3 flows as reverse breakdown current through D_1 .

With the zener well-established in reverse breakdown, V_G becomes

$$V_{SS} + V_{ZK} = -10 \text{ V} + 5 \text{ V} = -5 \text{ V}$$

so that $V_{OUT} = V_G - V_{GS1} = -5 \text{ V}$.

$$\text{Finally, } V_{DS1} = V_{DD} - V_{OUT} \\ = 10 \text{ V} - (-5 \text{ V}) = 15 \text{ V}$$

$$\text{and } V_{DS2} = V_{OUT} - V_{SS} \\ = -5 \text{ V} - (-10 \text{ V}) = 5 \text{ V}$$

All devices can be confirmed to operate in the constant-current region.

7.10 For $V_f = 0.7 \text{ V}$, KVL yields

$$I_1 = \frac{0 - V_f - (-V_{EE})}{R_1} = \frac{9.3 \text{ V}}{50 \text{ k}\Omega} = 186 \mu\text{A}$$

Since V_{BE1} and V_{BE2} are identical, Q_1 and Q_2 will have the same emitter current. To the extent that base currents can be neglected compared to emitter currents, the collector current of Q_1 will be equal to I_1 , so that $I_o \approx 186 \mu\text{A}$.

b) A more accurate value for I_1 can be obtained using the iterative numerical technique. In this case, I_1 is given exactly by

$$I_1 = \frac{-V_{EE} - V_{BE1}}{R_1} \quad (7.1)$$

where, via the v-i equation for Q_1 ,

$$I_{E1} = I_{E01}(e^{V_{BE1}/\eta V_T} - 1)$$

and $I_{B2} = I_{B02}(e^{V_{BE2}/\eta V_T} - 1)$

Since $V_{BE1} = V_{BE2}$, and given that that $I_1 = I_{E1} + I_{B2}$ (note that I_{E1} includes the current I_{B1}), the above becomes

$$I_1 = (I_{E01} + I_{B02})(e^{V_{BE1}/\eta V_T} - 1)$$

If the factor of -1 is neglected, this exponential equation can be inverted, yielding

$$V_{BE1} \approx \eta V_T \ln \frac{I_1}{I_{E01} + I_{B02}} \quad (7.2)$$

where $I_{E01} + I_{B02} = 10^{-12} \text{ A} + 10^{-14} \text{ A} = 1.01 \times 10^{-12} \text{ A}$. Use of the iterative technique involves substituting an initial estimate of I_1 into Eqn. (7.2) to obtain a value for V_{BE1} . This V_{BE1} value is then substituted into Eqn. (7.1) to obtain an updated value for I_1 . The procedure is repeated until the solution converges on a value for I_1 .

Here is a table that shows the results of successive iterations. An initial guess of $I_1 = 186 \mu\text{A}$ (the value of I_1 obtained in part a)

yields an initial V_{BE1} of 0.4758 V. Thereafter,

From Eqn. (7.1)	From Eqn (7.2)
$I_1 = 190.5 \mu\text{A}$	$V_{BE1} = 0.4764 \text{ V}$
$= 190.5 \mu\text{A}$	$= 0.4764 \text{ V}$

The solution is seen to converge on the value $I_1 = 190.5 \mu\text{A}$ after only two iterations.

The value of I_o can be found by noting that

$I_1 = I_{C1} + I_{B1} + I_{B2} = I_{E1} + I_{B2}$
Given $I_{E2} = I_{E1}$, this equation becomes

$$I_1 = I_{E1} \left[1 + \frac{1}{\beta_F + 1} \right] = I_{E1} \frac{\beta_F + 2}{\beta_F + 1}$$

Finally,

$$\begin{aligned} I_o = I_{C2} &= \frac{\beta_F}{\beta_F + 1} I_{E2} = \frac{\beta_F}{\beta_F + 1} I_{E1} \\ &= \frac{\beta_F}{\beta_F + 1} \frac{\beta_F + 1}{\beta_F + 2} I_1 = \frac{\beta_F}{\beta_F + 2} I_1 \end{aligned}$$

From the values of I_{E0} and I_{B0} , we note that

$$\frac{I_{E0}}{I_{B0}} = \frac{i_E}{i_B} = \beta_F + 1 \implies \beta_F = \frac{I_{E0}}{I_{B0}} - 1$$

$= 100 - 1 = 99$. For this value of β_F ,

$$I_o = \frac{99}{101} 190.5 \mu\text{A} = 186.7 \mu\text{A}$$

7.11 If base currents are neglected with respect to collector currents, an expression for the current through Q_1 can be found from KVL:

$$\begin{aligned} I_{\text{ref}} R_{\text{ref}} + V_f + V_{EE} &= 0 \\ \text{or} \quad I_{\text{ref}} &= \frac{-V_{EE} - V_f}{R_{\text{ref}}} \end{aligned}$$

Setting I_{ref} to 1 mA requires that

$$R_{\text{ref}} = \frac{-V_{EE} - V_f}{I_{\text{ref}}} = \frac{-(-10 \text{ V}) - 0.7 \text{ V}}{1 \text{ mA}}$$

= 9.3 k Ω . This current is replicated in Q₂, Q₃, and Q₄, so that

$$V_1 = 0 - I_{C2}R_1 = 0 - (1\text{mA})(6\text{k}\Omega) = -6\text{ V}$$

$$V_2 = 0 - (I_{C3} + I_{C4})R_2 \\ = 0 - (2\text{ mA})(4\text{ k}\Omega) = -8\text{ V}.$$

Note that V_{CE2} , V_{CE3} , and V_{CE4} are all greater than V_{sat} (about 0.2 V to 0.3 V). Hence Q₂, Q₃, and Q₄ operate in the constant-current region.

7.12 Neglect base currents with

respect to collector and emitter currents. The current I_1 through Q₁ is given by

$$I_1 = \frac{0 - V_f - V_{EE}}{R_1} = \frac{9.3\text{ V}}{10\text{ k}\Omega} = 0.93\text{ mA}$$

As discussed in the text, I_0 can be found by noting that

$$I_{E1} = I_{E0}(e^{V_{BE1}/\eta V_T} - 1) \approx I_{E0}e^{V_{BE1}/\eta V_T}$$

and

$$I_{E2} = I_{E0}(e^{V_{BE2}/\eta V_T} - 1) \approx I_{E0}e^{V_{BE2}/\eta V_T}$$

where $I_{E2} \approx I_0$, $I_{E1} \approx I_1$, and

$$V_{BE1} = V_{BE2} + I_0 R_2$$

Taking the logarithm of the exponential equations yields expressions for V_{BE1} and V_{BE2} . Substituting these expressions into the above equation results in

$$\eta V_T \ln \frac{I_{E1}}{I_{E0}} = \eta V_T \ln \frac{I_{E2}}{I_{E0}} + I_0 R_2$$

or

$$I_0 R_2 = \eta V_T \ln \frac{I_{E1}}{I_{E2}} = \eta V_T \ln \frac{I_1}{I_0}$$

This last equation can be solved by iteration, with $I_1 = 0.93\text{ mA}$ and $R_2 = 100\ \Omega$, yielding $I_0 = 0.29\text{ mA}$. A check shows this answer to be correct:

$$I_0 R_2 = (0.29\text{ mA})(100\ \Omega) = 29\text{ mV}$$

$$\eta V_T \ln (I_1/I_0) = 25\text{ mV} \ln (0.93/0.29) \\ = 29\text{ mV}.$$

7.13 The current I_1 is given by:

$$I_1 = \frac{0 - V_f - V_{EE}}{R_1} = \frac{9.3\text{ V}}{10\text{ k}\Omega} = 0.93\text{ mA}$$

As discussed in the text, the emitter currents in Q₁ and Q₂ are related to V_{BE1} and V_{BE2} by the equations

$$I_{E1} = I_{E0}(e^{V_{BE1}/\eta V_T} - 1) \approx I_{E0}e^{V_{BE1}/\eta V_T}$$

$$I_{E2} = I_{E0}(e^{V_{BE2}/\eta V_T} - 1) \approx I_{E0}e^{V_{BE2}/\eta V_T}$$

If base currents are neglected with respect to emitter and collector currents, then KVL yields

$$V_{BE1} + I_1 R_1 = V_{BE2} + I_0 R_2$$

where $I_{E1} \approx I_1$ and $I_{E2} \approx I_0$.

Taking the logarithm of the exponential equations yields expressions for V_{BE1} and V_{BE2} . Substituting these expressions into the above equation results in

$$\eta V_T \ln \frac{I_{E1}}{I_{E0}} + I_1 R_1 = \eta V_T \ln \frac{I_{E2}}{I_{E0}} + I_0 R_2$$

or

$$I_0 R_2 = \eta V_T \ln \frac{I_{E1}}{I_{E2}} + I_1 R_1$$

$$= \eta V_T \ln \frac{I_1}{I_0} + I_1 R_1$$

This last equation can be solved by iteration, with $I_1 = 0.93\text{ mA}$, $R_1 = 10\text{ k}\Omega$, and $R_2 = 50\text{ k}\Omega$, to yield $I_0 = 186.8\ \mu\text{A}$. A quick check shows this answer to be correct:

$$I_0 R_2 = (186.8\ \mu\text{A})(50\text{ k}\Omega) = 9.34\text{ V}$$

$$\eta V_T \ln (I_1/I_0) = (25\text{ mV}) \ln (930/186.8) \\ = 0.04\text{ V}.$$

$$I_1 R_1 = (0.93\text{ mA})(10\text{ k}\Omega) = 9.3\text{ V}$$

$$9.34\text{ V} = 0.04\text{ V} + 9.3\text{ V}$$

Note that a good approximation to this result can be obtained by assuming $V_{BE1} \approx V_{BE2}$ and equating the voltage drops across R_1 and R_2 :

$$I_1 R_1 = I_0 R_2 \implies$$

$$I_0 = \frac{R_1}{R_2} I_1 = \frac{10\text{ k}\Omega}{50\text{ k}\Omega} 0.93\text{ mA} = 186\ \mu\text{A}$$

7.14 Begin by assuming Q_2 to operate in the constant current region. This assumption must be confirmed later. Devices Q_1 and Q_3 , which are connected so that $V_{GS} = V_{DS}$, automatically operate in the constant current region. This condition follows because

$$V_{DS1} > V_{GS1} - V_{TR1}$$

is satisfied for Q_1 and

$$V_{DS3} < V_{GS3} - V_{TR3}$$

is satisfied for the p-channel device Q_3 . Note that V_{DS3} , V_{GS3} , and V_{TR3} are negative for the p-channel Q_3 .

If Q_2 operates in the constant current region, then I_o will be given by $I_o = K_2(V_{GS2} - V_{TR2})^2 = K_2(-V_{TR2})^2$ where $V_{GS2} = 0$. For the parameter values given, ($V_{TR2} = -1$ V for an n-channel depletion-mode device):

$$I_o = (4 \text{ mA/V}^2)(1 \text{ V})^2 = 4 \text{ mA}$$

The current I_o also flows through Q_1 :

$$I_o = K_1(V_{GS1} - V_{TR1})^2 \\ \equiv K_1(V_{DS1} - V_{TR1})^2$$

Solving this equation for V_{DS1} yields

$$V_{DS1} = (I_o/K_1)^{1/2} + V_{TR1}$$

$$= \sqrt{4\text{mA}/(1 \text{ mA/V}^2)} + 1 \text{ V} = 3 \text{ V}$$

so that

$$V_B = V_{SS} + V_{DS1} = -10 \text{ V} + 3 \text{ V} = -7 \text{ V}$$

Similarly, the current I_o also flows through Q_3 . The current I_o is equivalent to $-i_{D3}$; the latter is defined as positive into the drain of Q_3 , so that

$$-I_o = -K_3(V_{GS3} - V_{TR3})^2 \\ \equiv -K_3(V_{DS3} - V_{TR3})^2 \implies$$

$$V_{DS3} = (I_o/K_3)^{1/2} + V_{TR3}$$

$$= -\sqrt{4\text{mA}/(1 \text{ mA/V}^2)} - 1 \text{ V} = -3 \text{ V}$$

Note that the negative root has been chosen to compute V_{DS3} . Choosing the positive root would yield $V_{DS3} = V_{GS3} = 1$ V which would place the p-channel device Q_3 in cutoff.

For the above value of V_{DS3} , $V_A = V_{DD} + V_{DS3} = 10 \text{ V} - 3 \text{ V} = 7 \text{ V}$. Finally, we note that

$$V_{DS2} = V_A - V_B = 7 \text{ V} - (-7 \text{ V}) = 14 \text{ V}$$


The condition $V_{DS2} > V_{GS2} - V_{TR2} = 1$ V is satisfied; Q_2 is confirmed to operate in the constant-current region.

7.15 a) For $I_{C2} = I_o = 5$ mA, $I_{B2} = I_{C2}/\beta_F = (5 \text{ mA})/10 = 0.5$ mA. The two transistors have the same V_{BE} , hence they will have the same I_B , I_C , and I_E . It thus follows that


$$I_1 = I_{C1} + I_{B1} + I_{B2} \\ = 5 \text{ mA} + 0.5 \text{ mA} + 0.5 \text{ mA} = 6 \text{ mA}$$

This current can be set by choosing
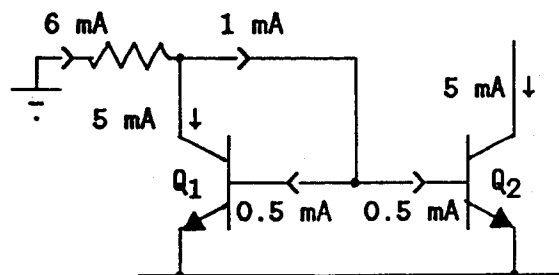
$$R_1 = \frac{0 - V_f - V_{EE}}{I_1} = \frac{14.3 \text{ V}}{6 \text{ mA}} \approx 2.4 \text{ k}\Omega$$



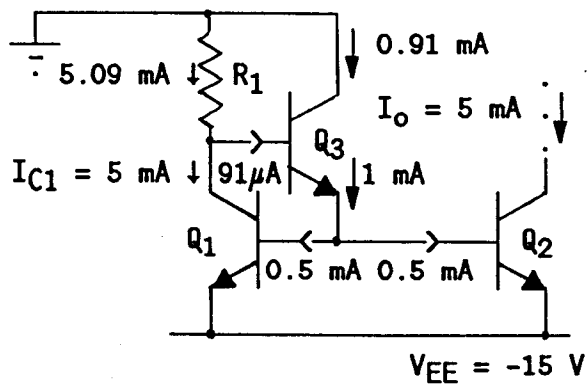b) The following circuit configuration provides a buffer to the bases of Q_1 and Q_2 .



For this configuration,

$$R_1 = \frac{0 - 2V_f - (-15\text{ V})}{5.09\text{ mA}} = 2.67\text{ k}\Omega$$

One V_f drop each is contributed by Q_1 and Q_3 to the above equation.