

EK 307: Electric Circuits

Fall 2017

Lecture 6

Sep 21, 2017

Prof. Miloš Popović

Department of Electrical and Computer Engineering

Boston University

Administrivia

- You should have read Ch 1-3 and should be reading Ch 4!
- HW 1 is in, 2 is due next Tuesday, 3 is out Friday.
- First midterm exam is 3.5 weeks away.

Lecture 6: What you should know at end of this lecture


- ✓ 1. Complete supernodes
- ✓ 2. Review circuits in context of lab: measuring voltage and current
- ✓ 3. Linear and nonlinear circuits: LED
- ✓ 4. Physics of the resistor (revisit Ohm's law)
5. Equivalent resistance
6. Mesh current analysis
7. Linearity, superposition
8. Dependent sources
9. Transistor model circuits

Supernodes

(for practice see Fig. 3.7 in book and explanation, and practice prob 3.3 and around there)

A:

Supernodes

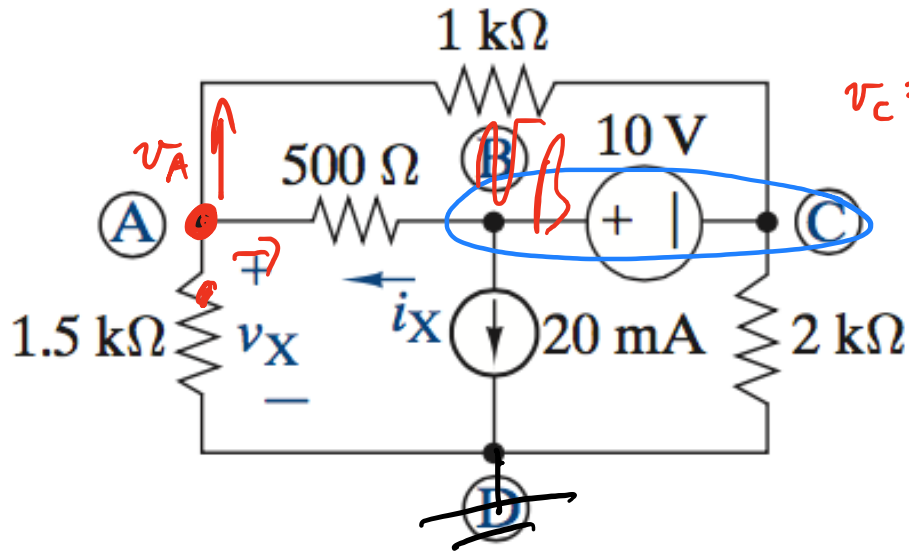


$$v_C \equiv v_B - 10V$$

$$\begin{bmatrix} | \\ | \\ | \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} 0 \\ \cdot \end{bmatrix}$$

$$A: \left(\frac{1}{1.5k} + \frac{1}{0.5k} + \frac{1}{1k} \right) v_A + \left(\frac{-1}{0.5k} \right) v_B \quad \left(\frac{-1}{1k} \right)$$

$$B: 20mA + \frac{v_B - v_A}{0.5k}$$


Supernodes

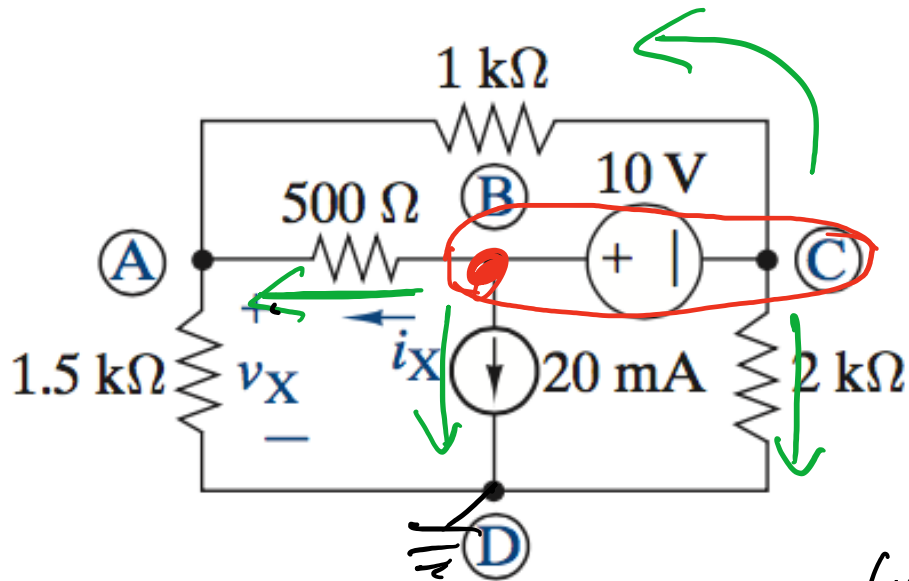


$$\textcircled{A}: \frac{v_A - 0}{1.5 \text{ k}\Omega} + \frac{v_A - v_B}{500 \Omega} + \frac{v_A - (v_B - 10 \text{ V})}{1 \text{ k}\Omega} = 0$$

$$\textcircled{B}: \frac{v_B - v_A}{500 \Omega} + 20 \text{ mA} + \frac{(v_B - 10 \text{ V}) - v_A}{1 \text{ k}\Omega} + \frac{(v_B - 10 \text{ V})}{2 \text{ k}\Omega} = 0$$

Supernodes

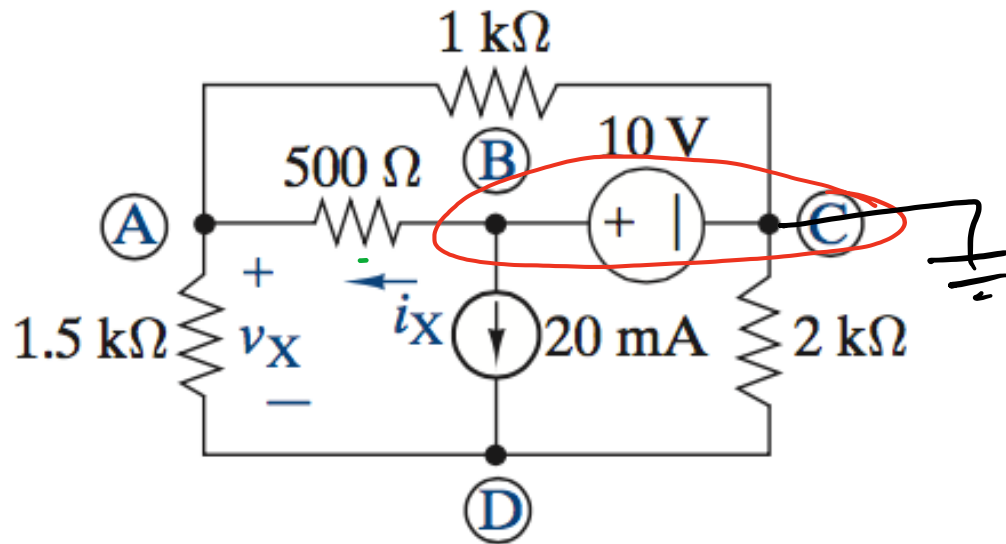


Supernodes

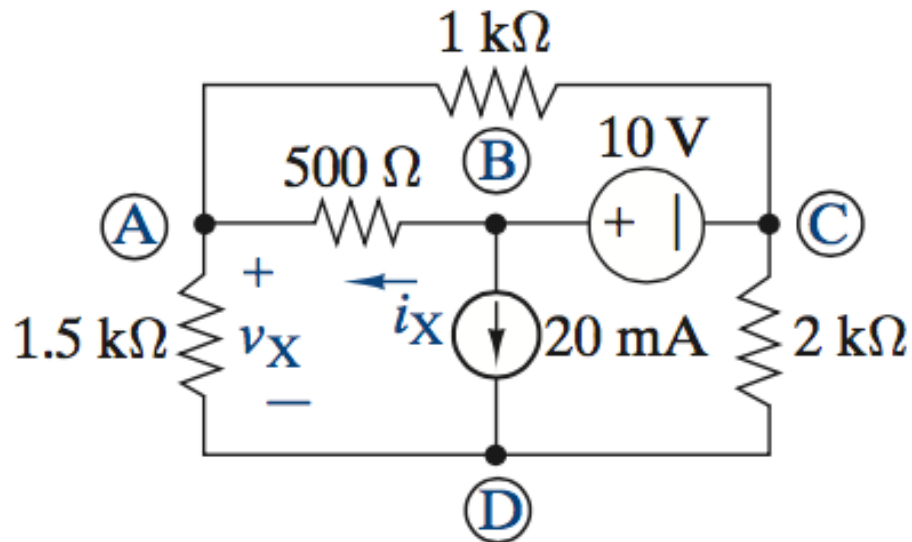

Node A:
$$\frac{V_A - 10}{0.5k} + \frac{V_A - V_D}{1.5k} + \frac{V_A}{1k} = 0$$




Node D:
$$\frac{V_D - V_A}{1.5k} - 0.020 + \frac{V_D}{2k} = 0$$

Another supernode problem

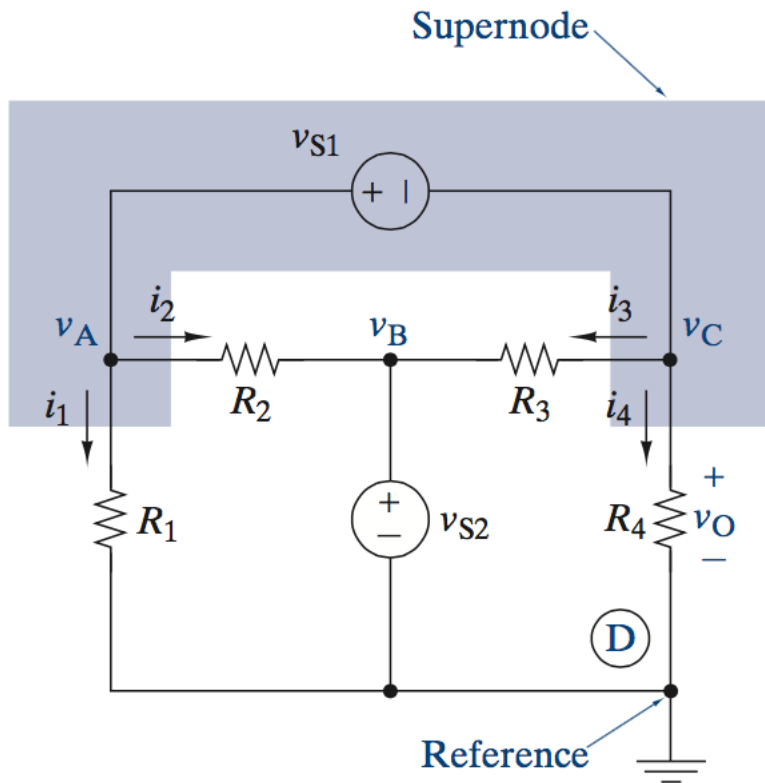

Review circuits in context of lab:
measuring voltage and current


Measuring voltage and current in the lab

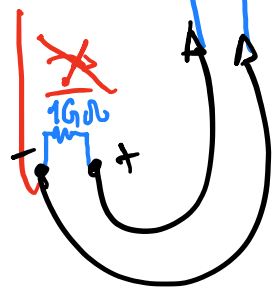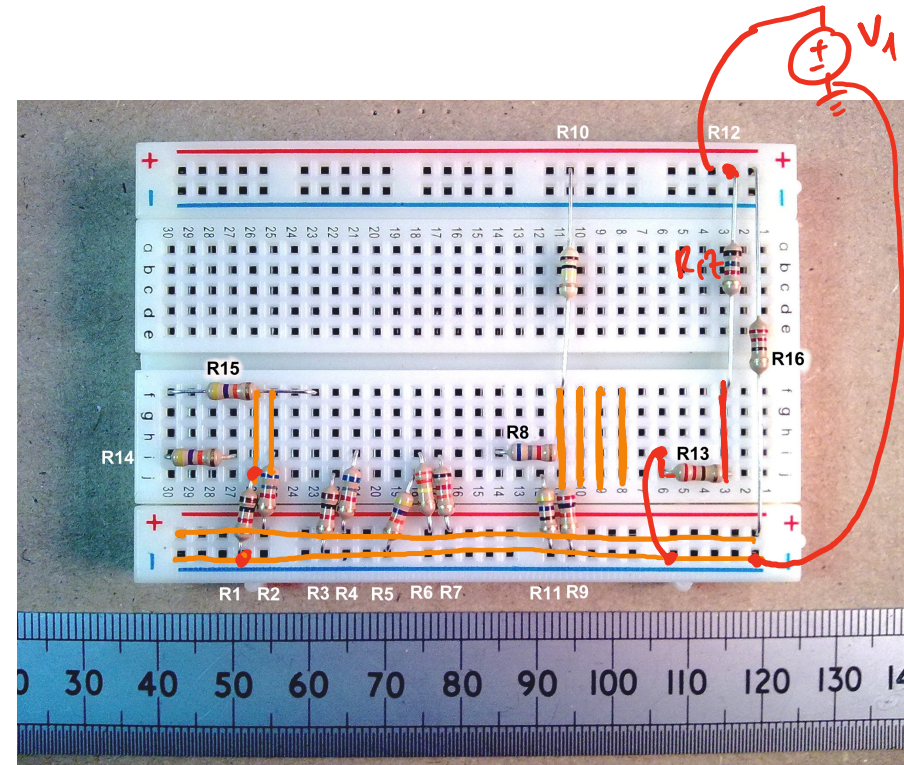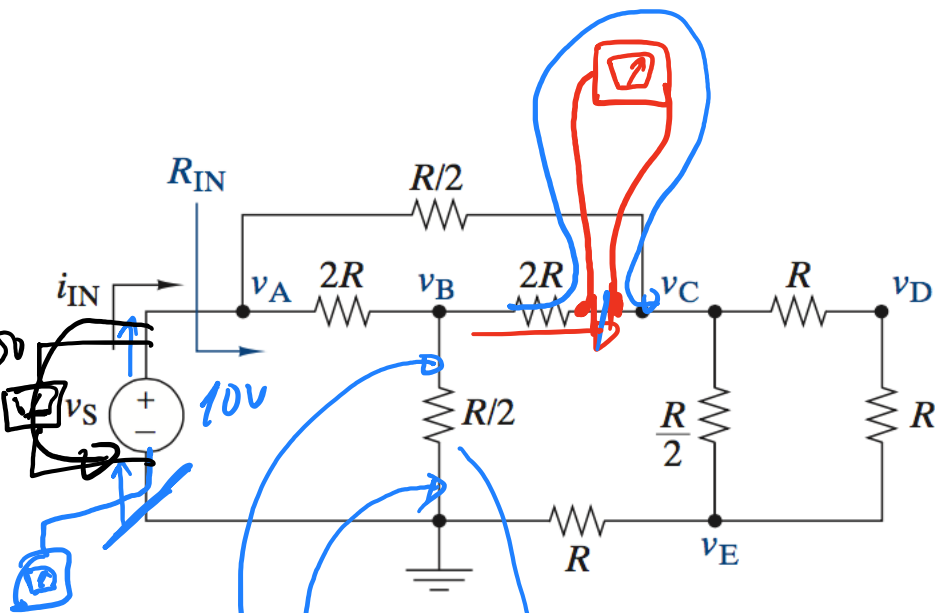




16Ω
 $1k\Omega$
res.

$$\frac{1}{R_{eq}} = \frac{1}{16\Omega} + \frac{1}{1k\Omega} = \frac{1}{10^{-9}} + \frac{1}{10^{-3}} = 10^{-9} + 10^{-3} = 10^{-3} \frac{1}{\Omega}$$





$R_{eq} = 1k\Omega$

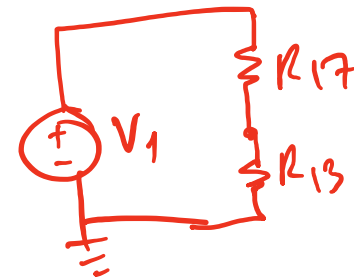


Measuring voltage and current in the lab

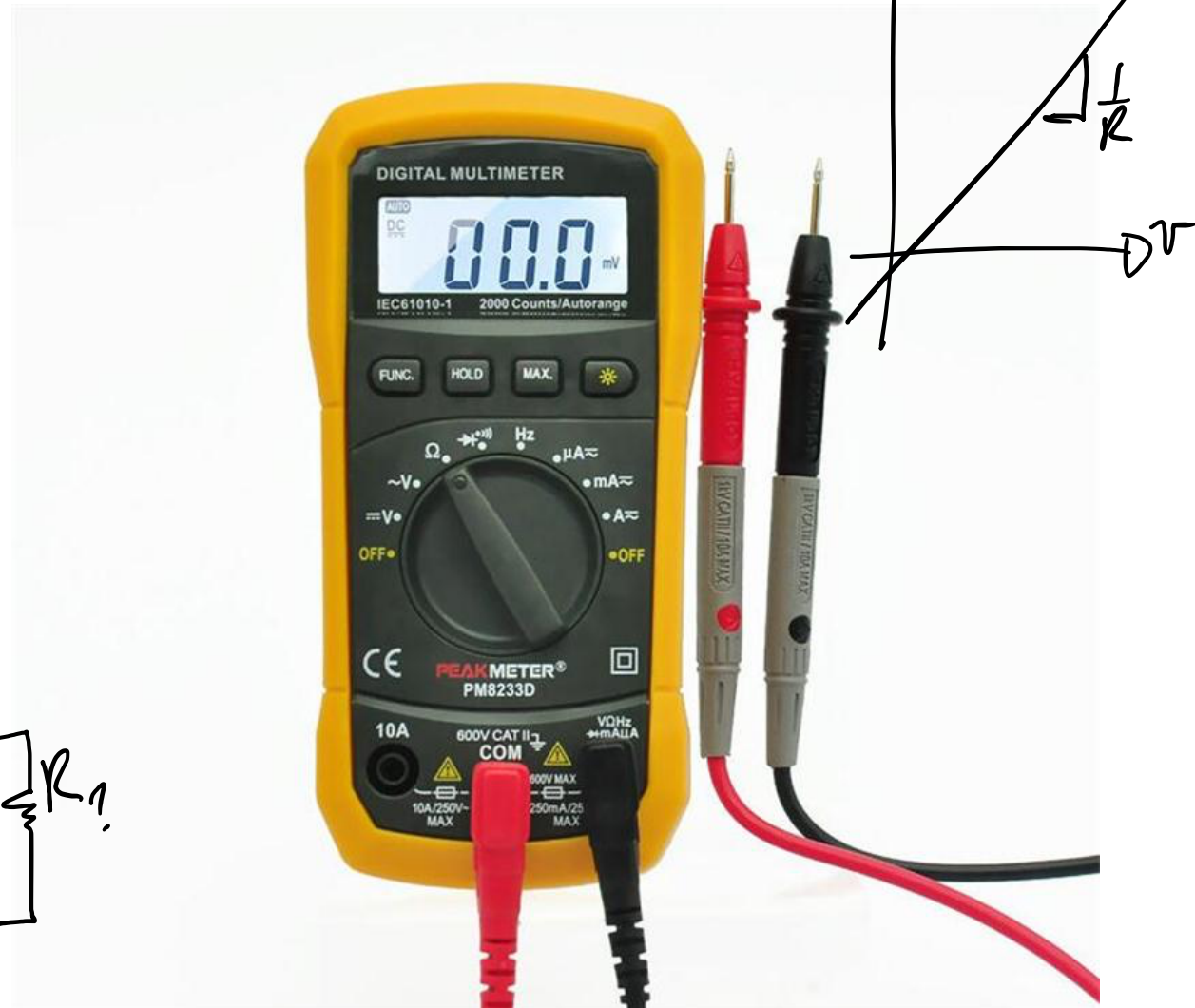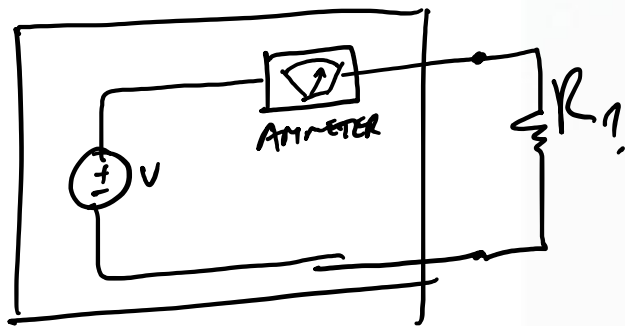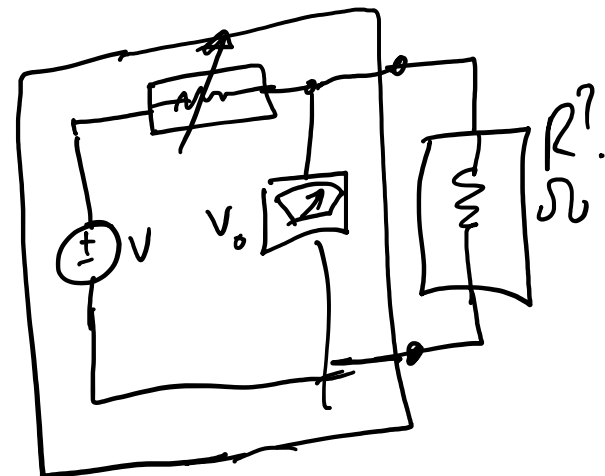

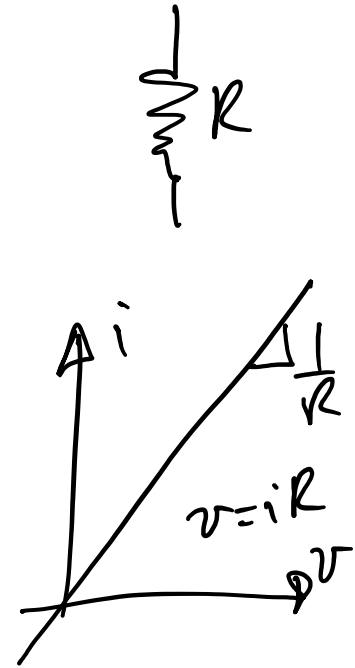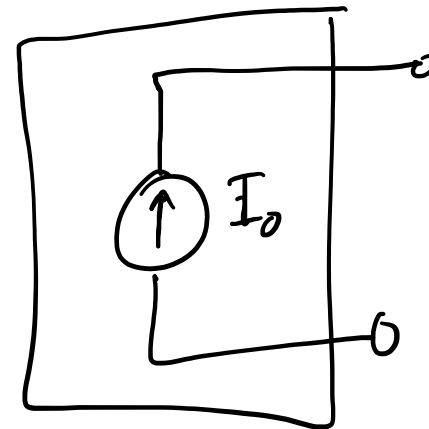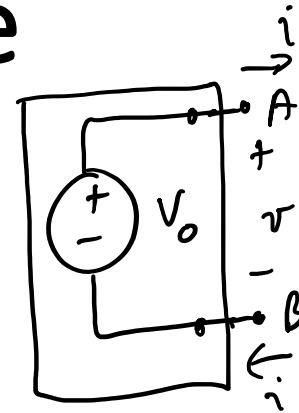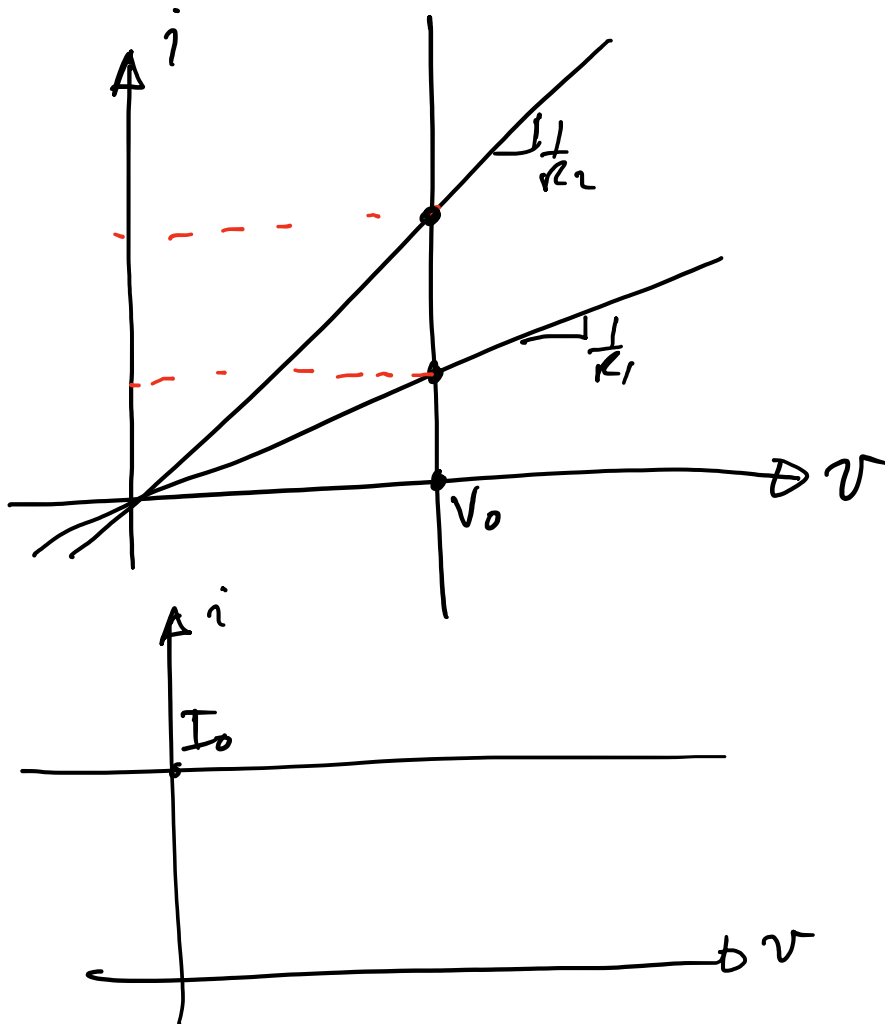
Linear and nonlinear circuits: the Light Emitting Diode



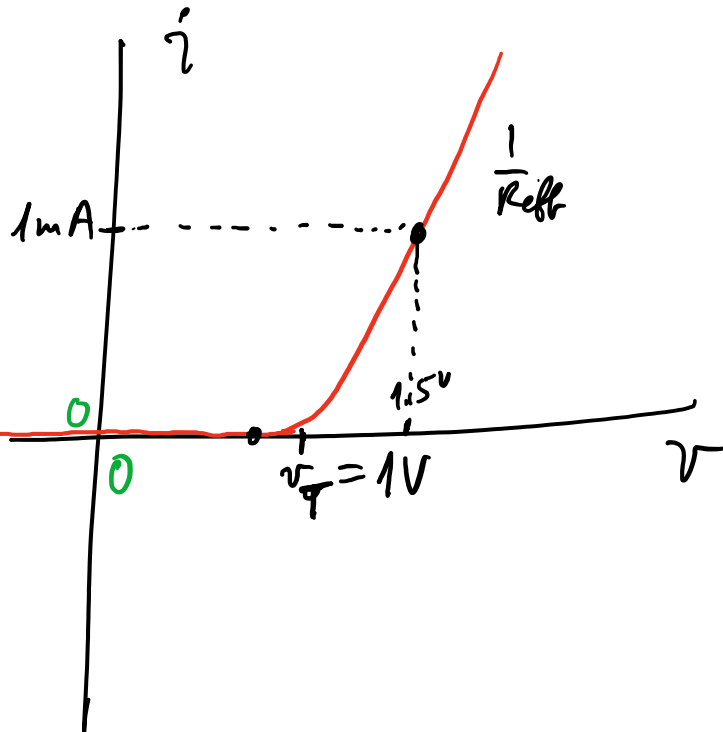Linear and nonlinear circuits: the Light Emitting Diode






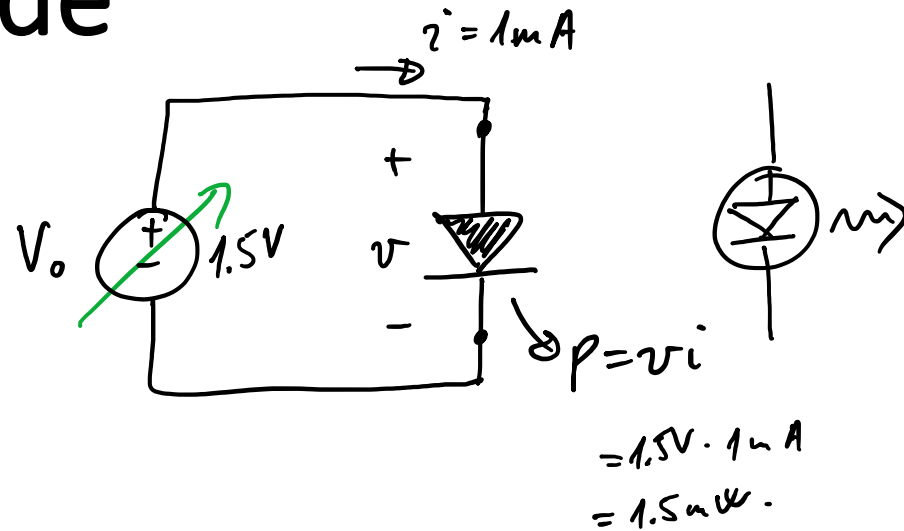Resistor symbol: $i = \frac{1}{R} v$
 $\frac{di}{dv} = \frac{1}{R}$





$$i_D = I_S (e^{v_D/V_T} - 1)$$

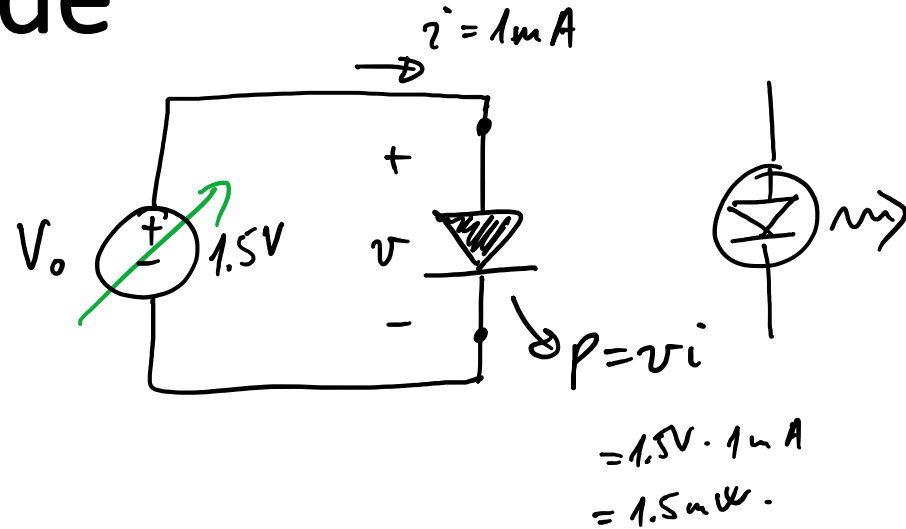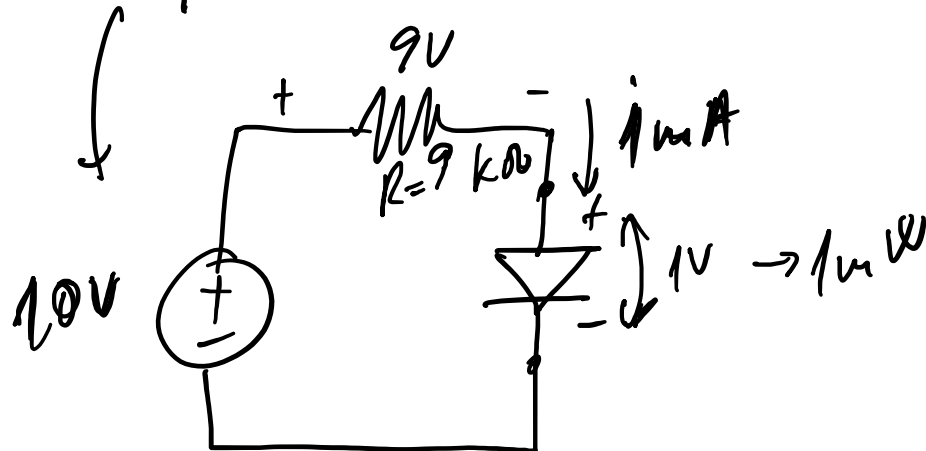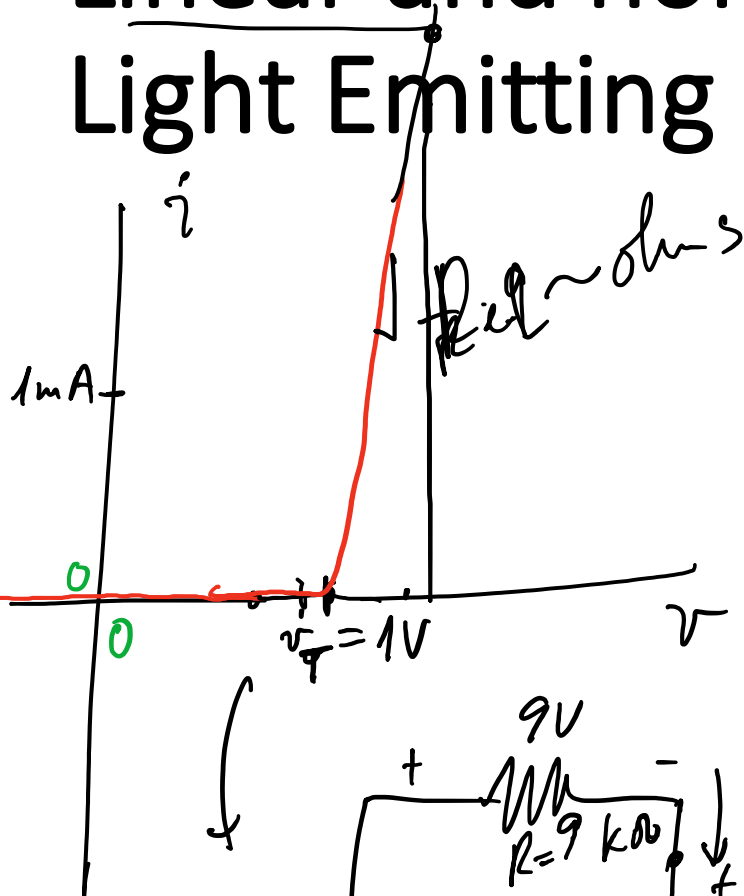Linear and nonlinear circuits: the Light Emitting Diode



$$i_D = I_S (e^{v_D/V_T} - 1)$$

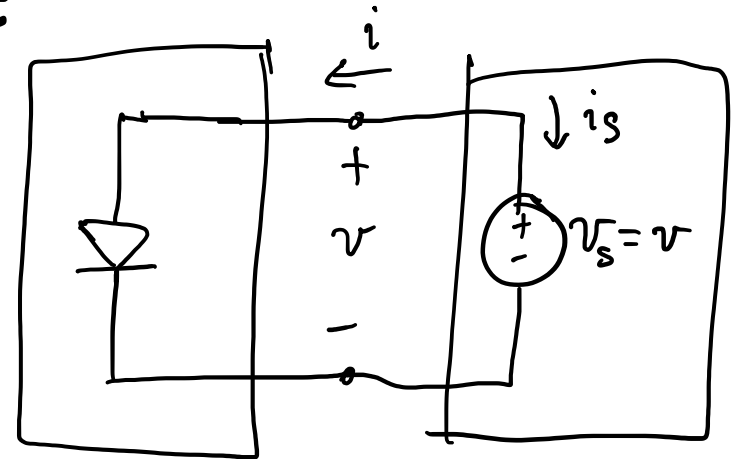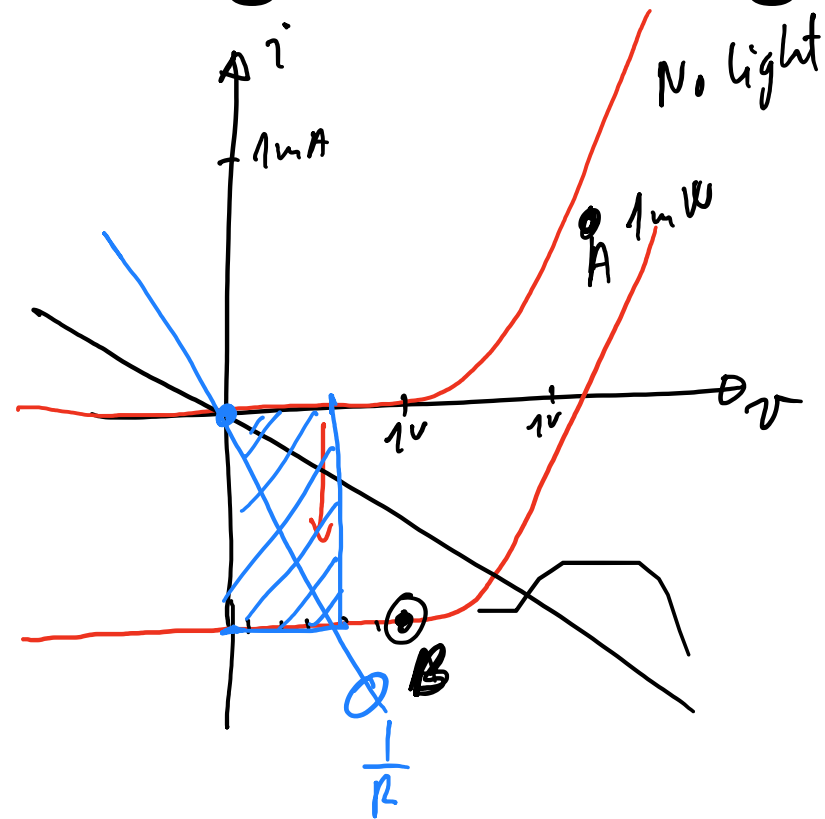Linear and nonlinear circuits: the Light Emitting Diode




$$\begin{aligned} p &= v_s i_s \\ &= v(-i) \\ &= (1V)(-(-1mA)) \\ &= 1mW \end{aligned}$$



$$p = v i$$

$$= (1V)(-1mA) = -1mW$$

$$i_D = I_S (e^{v_D/V_T} - 1)$$

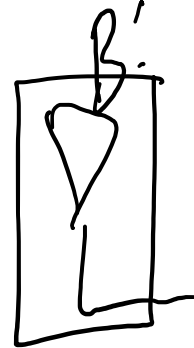


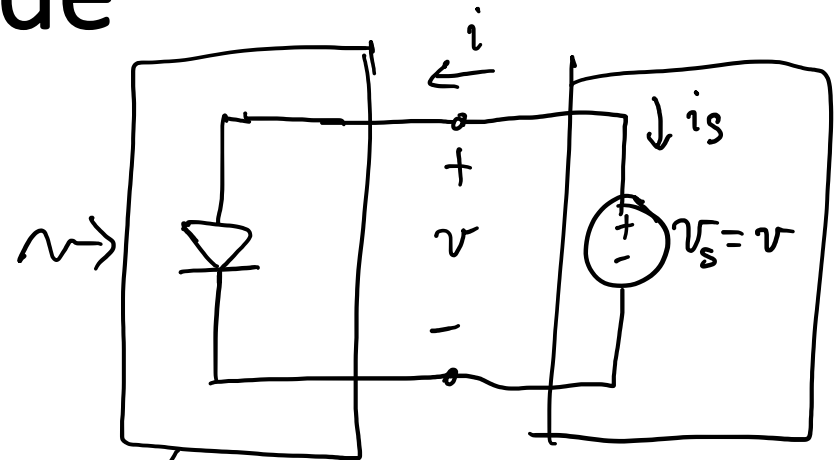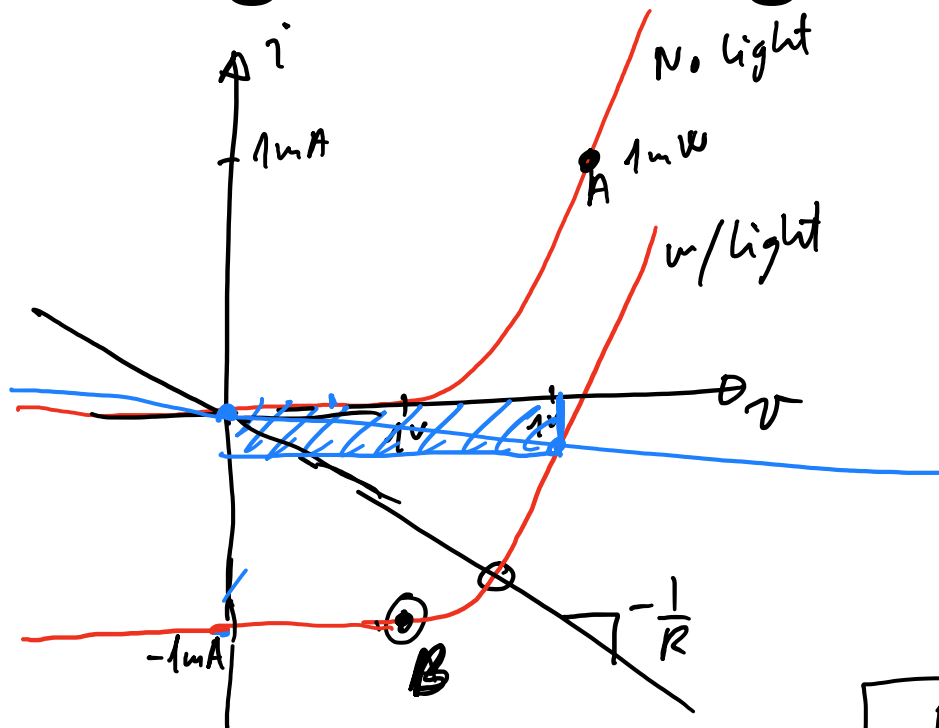Linear and nonlinear circuits: the Light Emitting Diode





B: $p = vi$
 $= (1V)(-1mA) = -1mW$

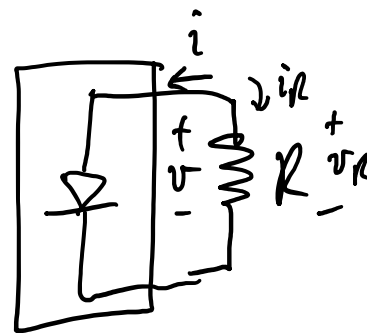$p = v_s i_s$
 $= v(-i)$
 $= (1V)(-(-1mA))$
 $= 1mW$




$$i_D = I_S (e^{v_D/V_T} - 1)$$

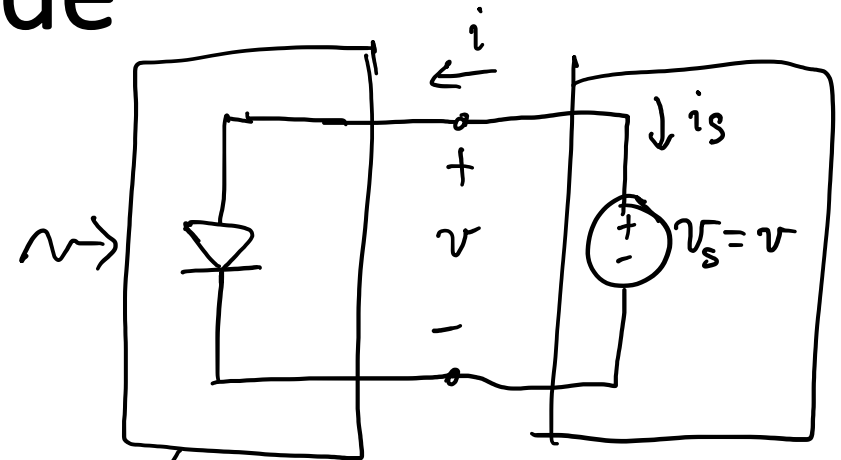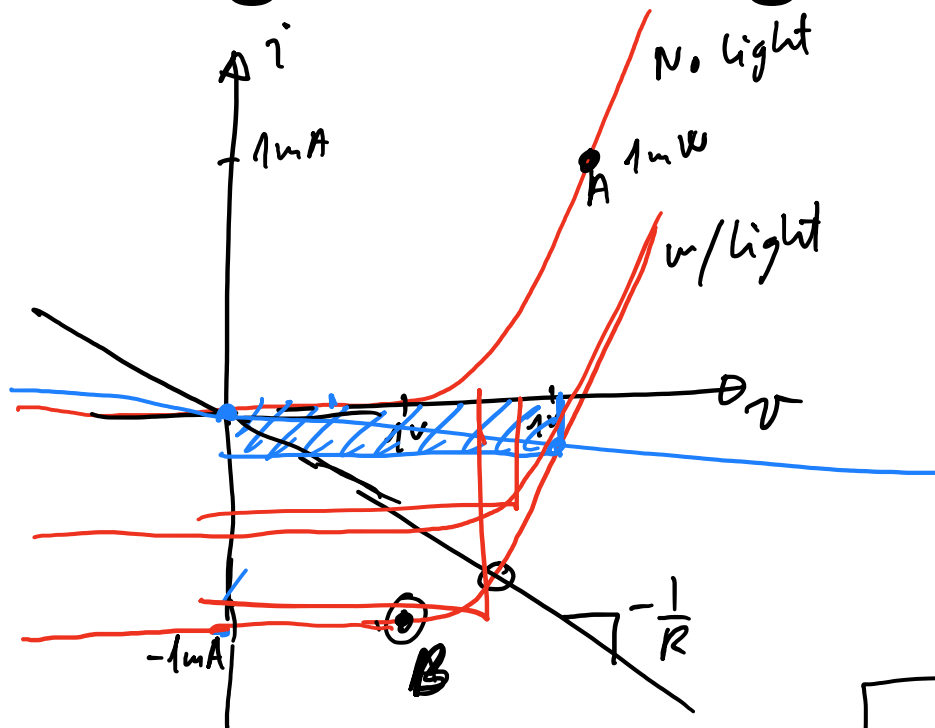Linear and nonlinear circuits: the Light Emitting Diode




B: $p = vi$
 $= (1V)(-1mA) = -1mW$

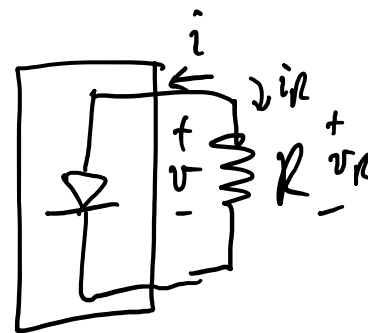$p = v_s i_s$
 $= v(-i)$
 $= (1V)(-(-1mA))$
 $= 1mW$





$$i_D = I_S (e^{v_D/V_T} - 1)$$

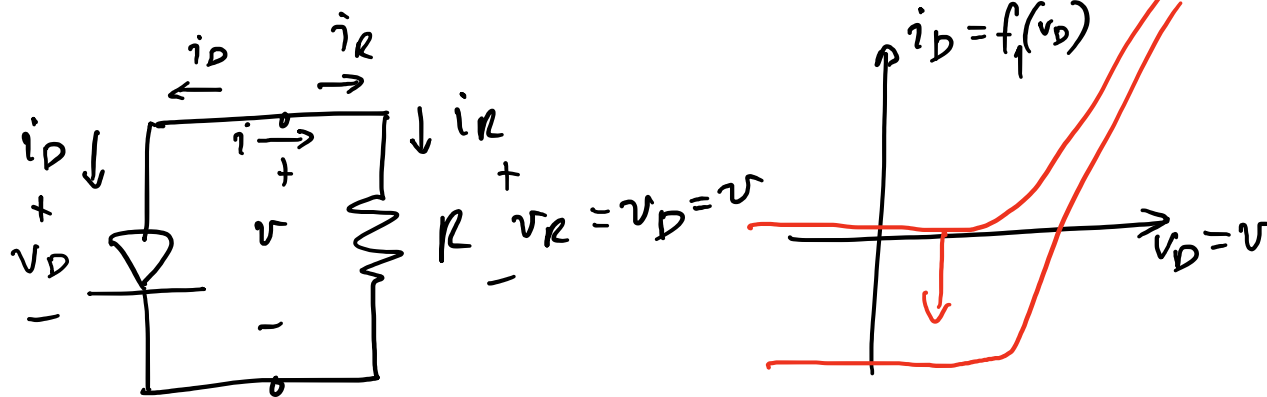Linear and nonlinear circuits: the Light Emitting Diode




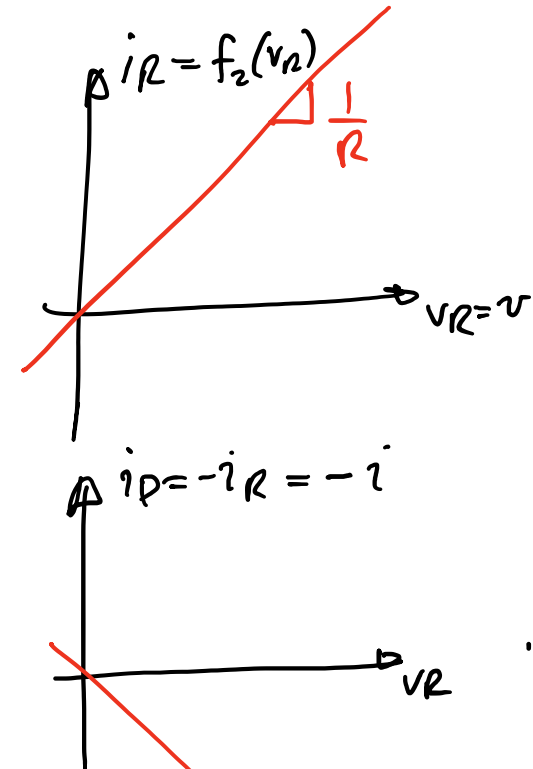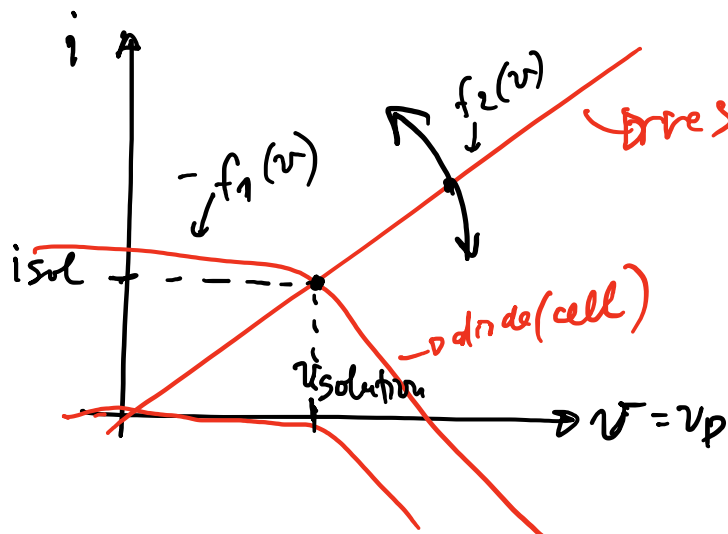
$$i_R = -i_D = i \rightarrow f_2(v_D) = -f_1(v_D)$$




$$i_D = I_S (e^{v_D/V_T} - 1)$$

Ohm's law

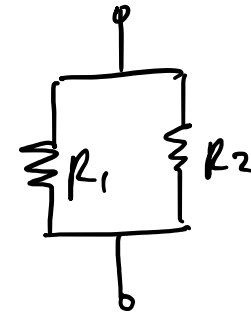
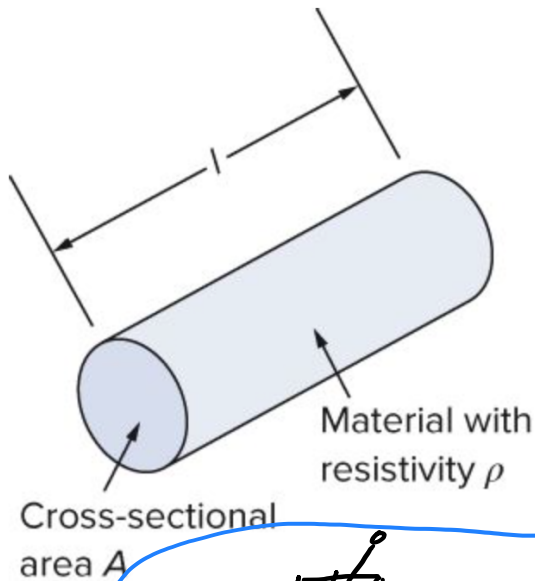


$$R_{eq} = R_1 + R_2$$
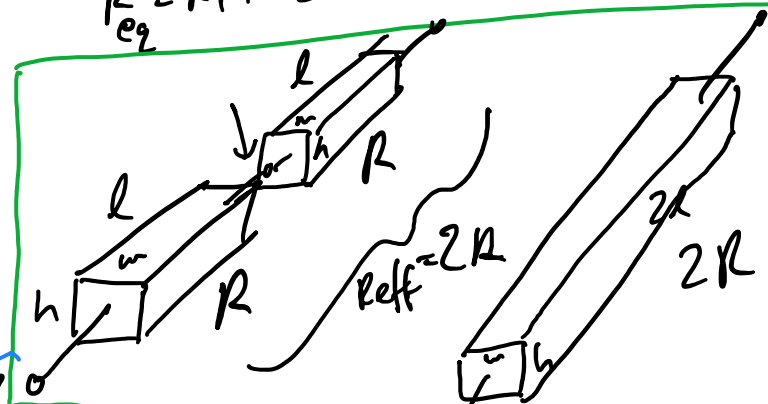
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$





$$R \propto l$$

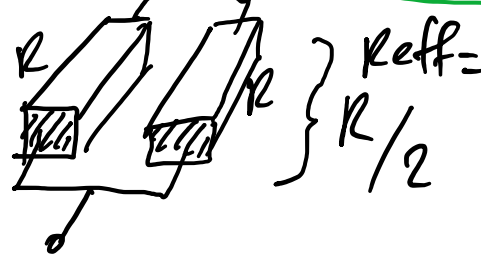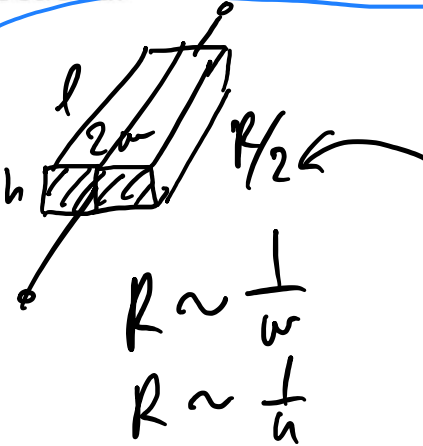

$$R \propto \frac{l}{wh} = \frac{l}{A}$$

Ohm's law

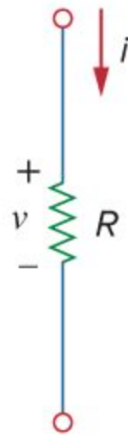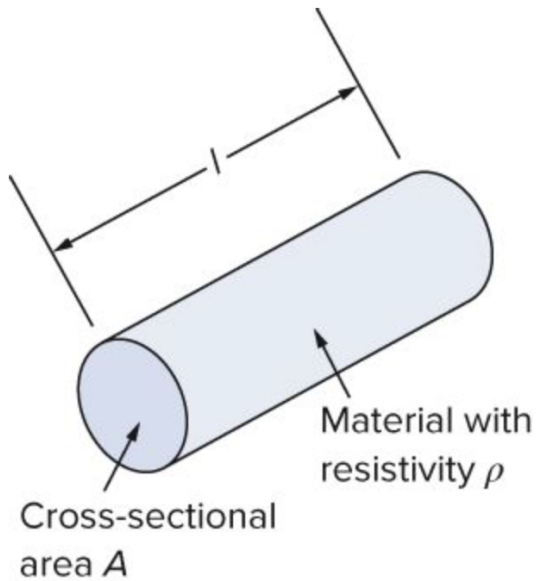

$$R = \rho \frac{l}{A}$$


Handwritten annotations for the formula $R = \rho \frac{l}{A}$:

- ρ is labeled "resistivity" with an arrow pointing to it.
- l is labeled with an arrow pointing to it.
- A is labeled with an arrow pointing to it.
- Units are indicated below the variables: Ω for ρ , Ωm for l , and m^2 for A .

conductivity

$$\sigma = \frac{1}{\rho}$$

Design a carbon resistor

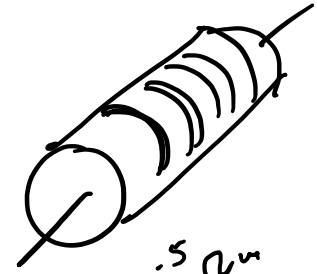

$$R = 1k\Omega$$

$$R = 1k\Omega = \rho \frac{l}{A}$$

$$4 \cdot 10^{-5} \Omega \cdot m$$

TABLE 2.1

Resistivities of common materials.

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	$\rho = 4 \times 10^{-5} \Omega \cdot m$	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

$$A = \pi r^2 = \pi (0.5 \text{ mm})^2$$

$$= 3.14 (5e-4)^2$$



$$= 75e-8 \text{ m}^2$$

$$1e3 \Omega = (4e-5 \text{ } \cancel{\Omega \cdot m}) \frac{l}{75e-8 \text{ m}^2}$$


$$l = \frac{1e3 \cdot 75e-8}{4e-5} = \frac{75e-5}{4e-5}$$

$$l = 20 \text{ m}$$

Sheet resistance

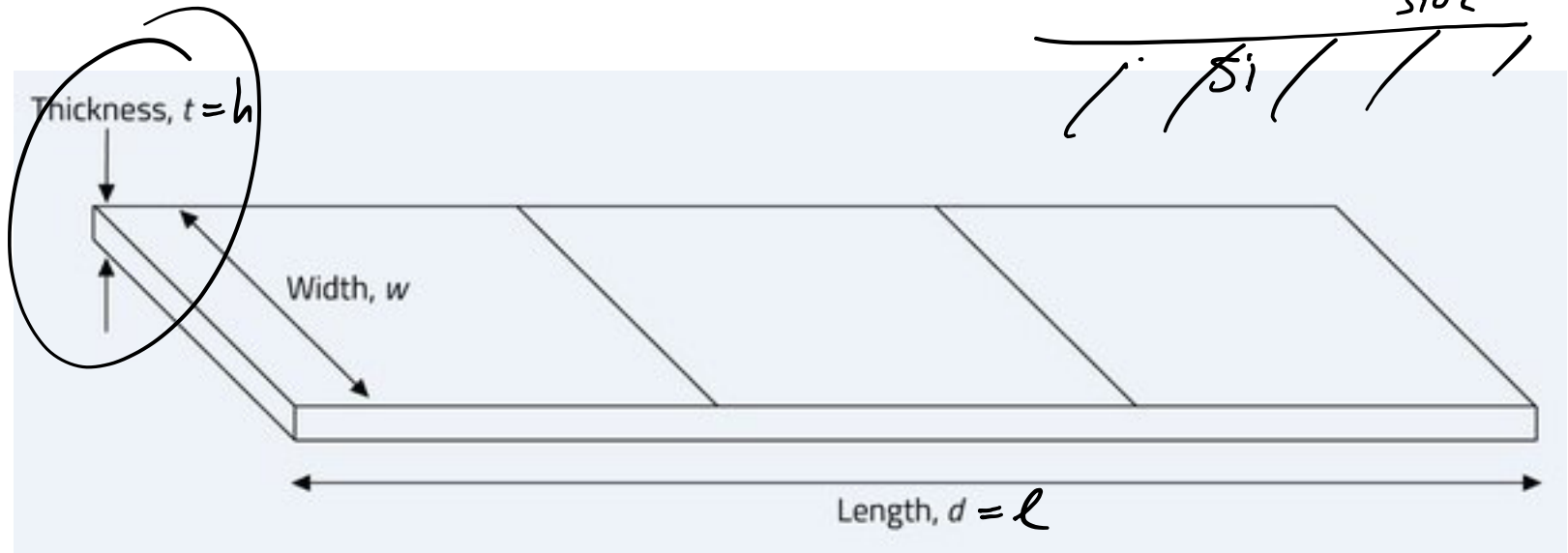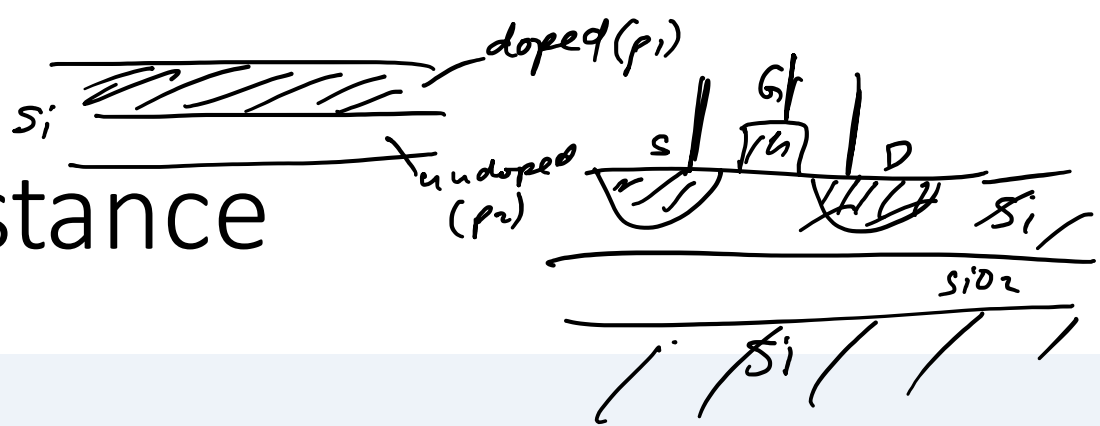

$$R = \rho \frac{l}{wh}$$

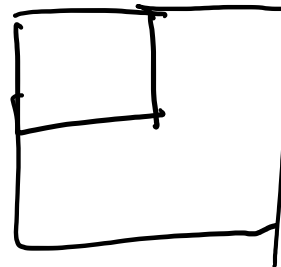


Resistance per square



$$R_{\square} = 10 \Omega$$

20Ω : 




Input resistance

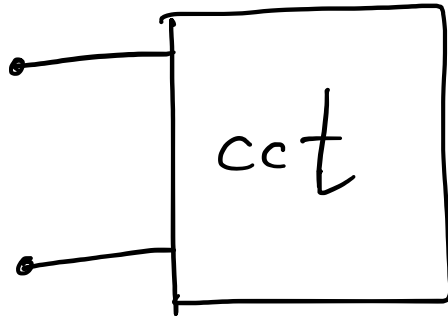


Find input resistance:

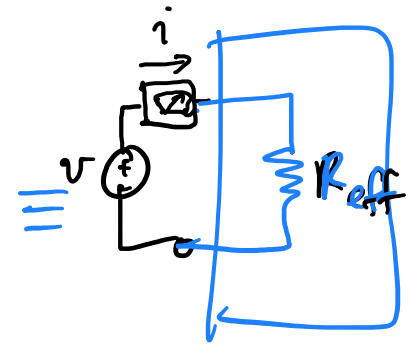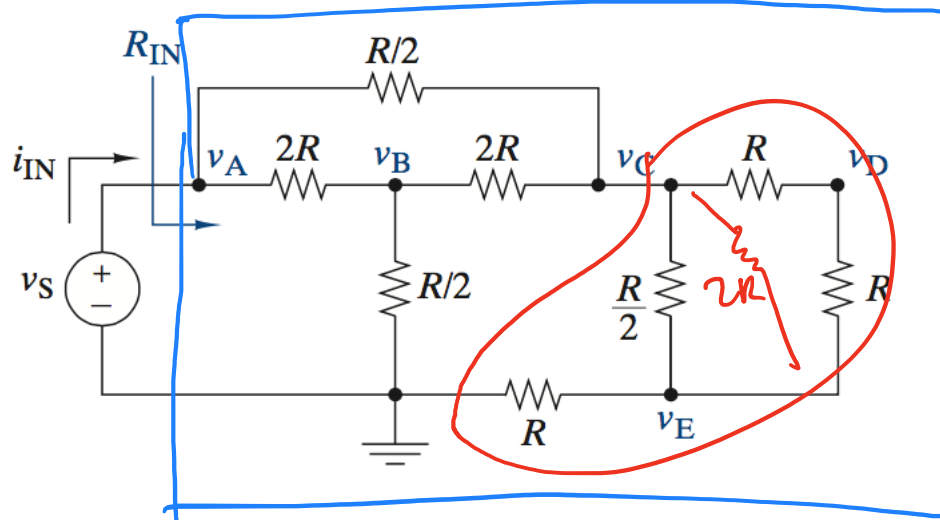

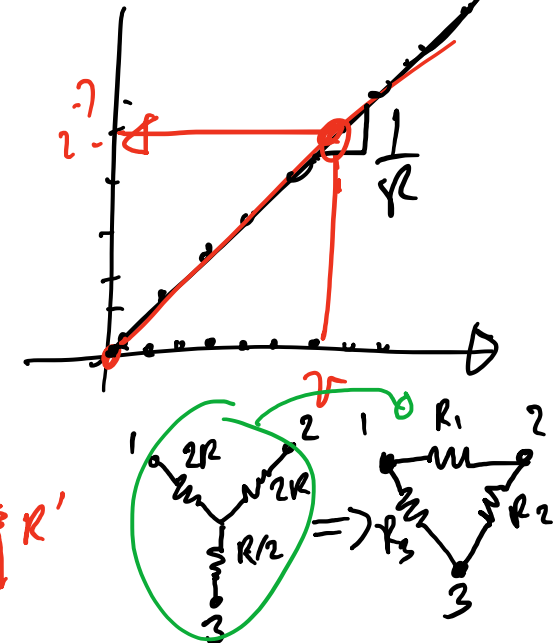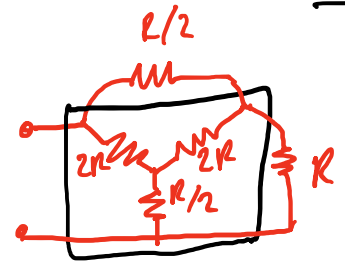
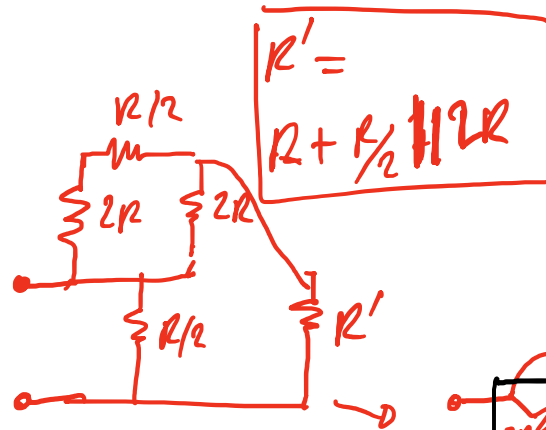
- Apply v_S
 - Solve i_{IN}
- So $R_{IN} = \frac{v_S}{i_{IN}}$





Find input resistance:

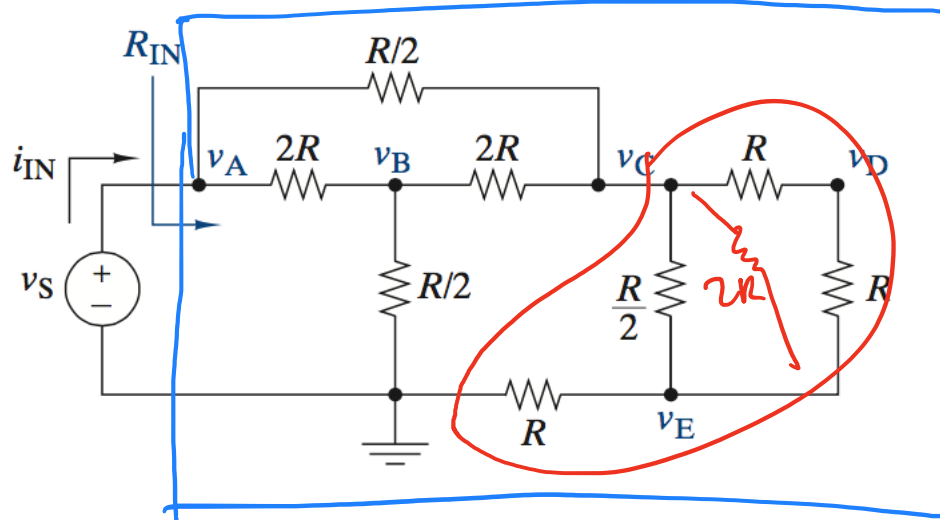

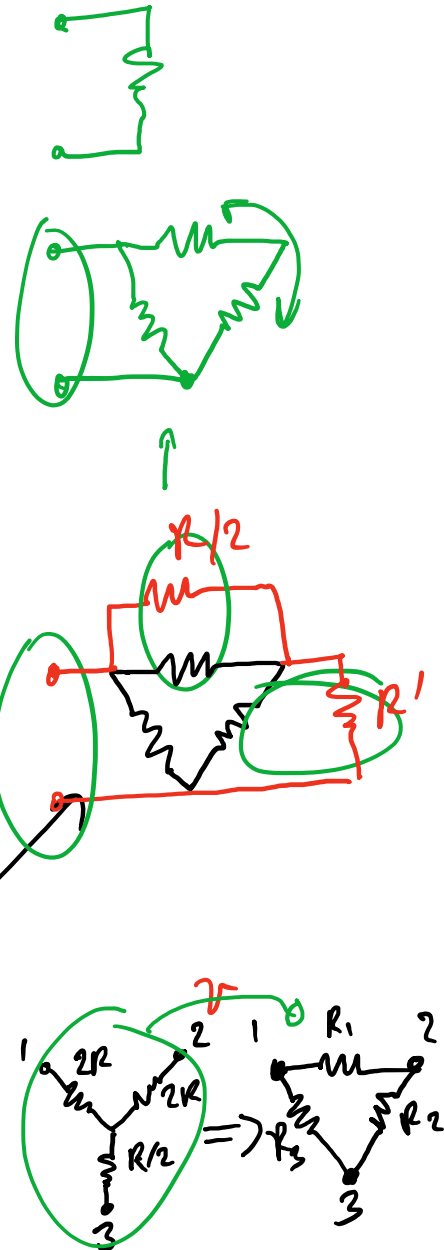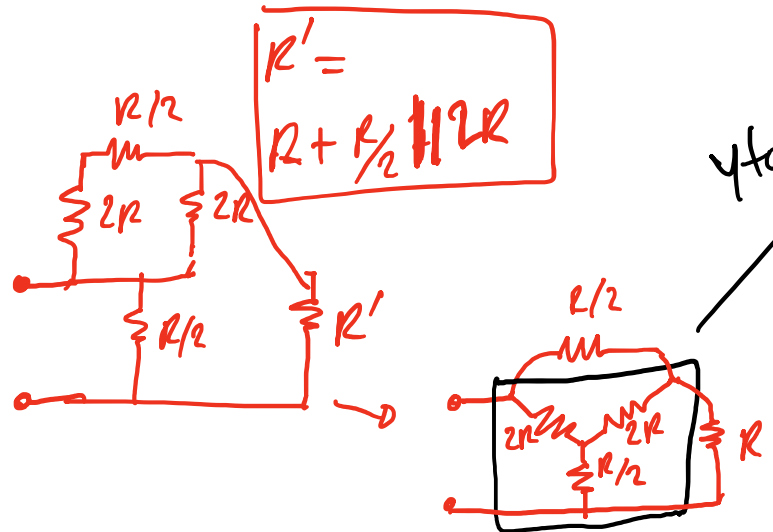- Apply v_S
 - Solve i_{IN}
- So $R_{IN} = \frac{v_S}{i_{IN}}$



Find input resistance:

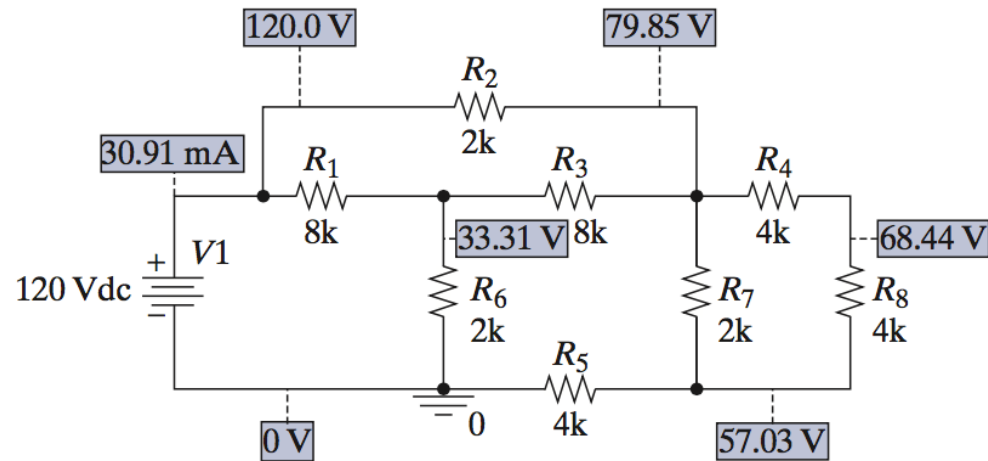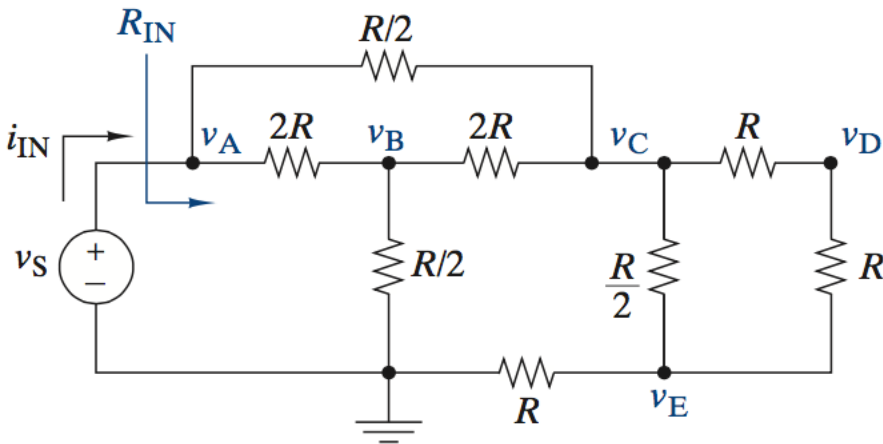



$$\text{Node B: } -v_A \left(\frac{1}{2R} \right) + v_B \left(\frac{1}{2R} + \frac{2}{R} + \frac{1}{2R} \right) - v_C \left(\frac{1}{2R} \right) = 0$$

$$\text{Node C: } -v_A \left(\frac{2}{R} \right) - v_B \left(\frac{1}{2R} \right) + v_C \left(\frac{2}{R} + \frac{1}{2R} + \frac{2}{R} + \frac{1}{R} \right) - v_D \left(\frac{1}{R} \right) - v_E \left(\frac{2}{R} \right) = 0$$

$$\text{Node D: } -v_C \left(\frac{1}{R} \right) + v_D \left(\frac{1}{R} + \frac{1}{R} \right) - v_E \left(\frac{1}{R} \right) = 0$$

$$\text{Node E: } -v_C \left(\frac{2}{R} \right) - v_D \left(\frac{1}{R} \right) + v_E \left(\frac{1}{R} + \frac{1}{R} + \frac{2}{R} \right) = 0$$

Find input resistance:

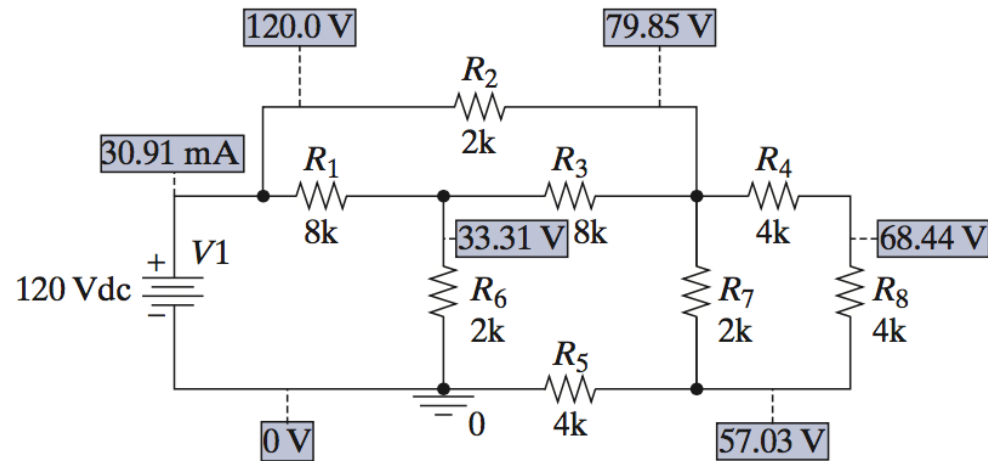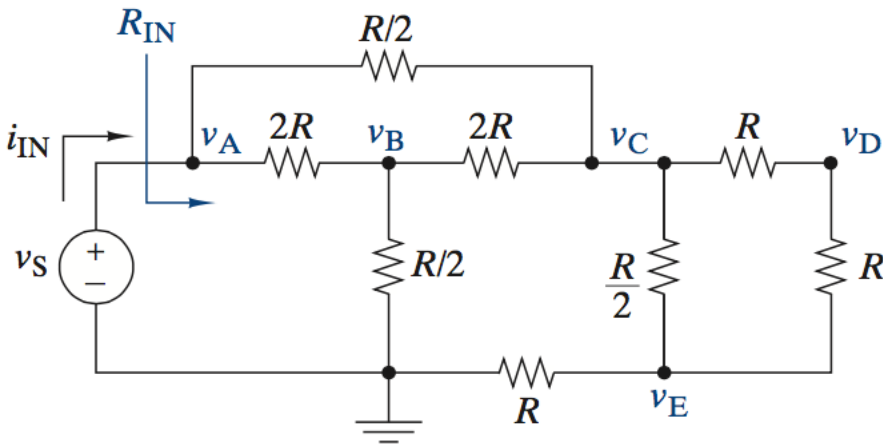

$$\text{Node B: } -v_A \left(\frac{1}{2R} \right) + v_B \left(\frac{1}{2R} + \frac{2}{R} + \frac{1}{2R} \right) - v_C \left(\frac{1}{2R} \right) = 0$$

$$\text{Node C: } -v_A \left(\frac{2}{R} \right) - v_B \left(\frac{1}{2R} \right) + v_C \left(\frac{2}{R} + \frac{1}{2R} + \frac{2}{R} + \frac{1}{R} \right) - v_D \left(\frac{1}{R} \right) - v_E \left(\frac{2}{R} \right) = 0$$

$$\text{Node D: } -v_C \left(\frac{1}{R} \right) + v_D \left(\frac{1}{R} + \frac{1}{R} \right) - v_E \left(\frac{1}{R} \right) = 0$$

$$\text{Node E: } -v_C \left(\frac{2}{R} \right) - v_D \left(\frac{1}{R} \right) + v_E \left(\frac{1}{R} + \frac{1}{R} + \frac{2}{R} \right) = 0$$

$$\begin{bmatrix} \frac{3}{R} & -\frac{1}{2R} & 0 & 0 \\ -\frac{1}{2R} & \frac{11}{2R} & -\frac{1}{R} & -\frac{2}{R} \\ 0 & -\frac{1}{R} & \frac{2}{R} & -\frac{1}{R} \\ 0 & -\frac{2}{R} & -\frac{1}{R} & \frac{4}{R} \end{bmatrix} \begin{bmatrix} v_B \\ v_C \\ v_D \\ v_E \end{bmatrix} = \begin{bmatrix} \frac{v_S}{2R} \\ \frac{2v_S}{R} \\ 0 \\ 0 \end{bmatrix}$$

Matlab code


```
syms vS vB vC vD vE R
A = [3/R -1/2/R 0 0;...
-1/2/R 11/2/R -1/R -2/R; ... 0 -1/R 2/R -1/R;...
0 -2/R -1/R 4/R];
B = [vS/2/R; 2*vS/R; 0; 0]; x = A\B;
vB = x(1)
vC = x(2)
vD = x(3) vE = x(4)
```

$$i_{\text{IN}} = \frac{v_{\text{S}} - v_{\text{C}}}{R/2} + \frac{v_{\text{S}} - v_{\text{B}}}{2R}$$

$$R_{\text{IN}} = \frac{v_{\text{IN}}}{i_{\text{IN}}} = \frac{263R}{271}$$

Mesh current analysis

Mesh current analysis

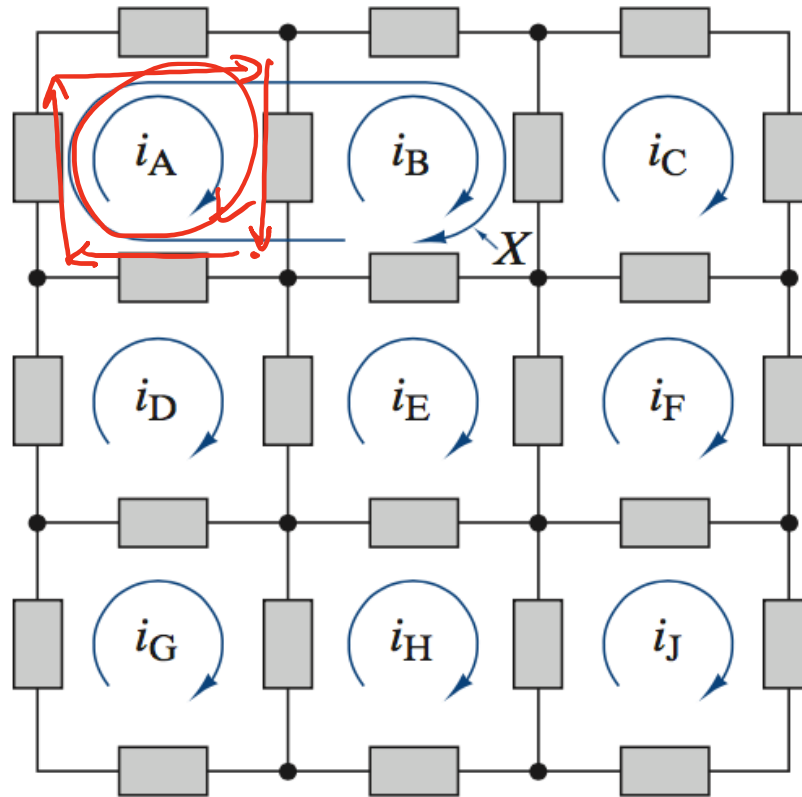

$$\bar{X} = \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \\ \vdots \\ i_J \end{bmatrix}$$

$$\bar{A} \cdot \bar{X} = \bar{b}$$

$$\bar{X} = \bar{A}^{-1} \cdot \bar{b}$$

To be continued...