

EK 307: Electric Circuits

Fall 2017

Lecture 7

Sep 26, 2017

Prof. Miloš Popović

Department of Electrical and Computer Engineering

Boston University

Administrivia

- HW 2 due today
- Should be reading Ch. 4

Lecture 6: Reminder

- 1. Complete supernodes**
- 2. Review circuits in context of lab: measuring voltage and current**
- 3. Linear and nonlinear circuits: LED**
- 4. Physics of the resistor (revisit Ohm's law)**
- 5. Equivalent resistance**

Lecture 7 (today): What you should know at end of this lecture

1. Mesh current analysis (2 examples)

→ **2. Linearity, superposition**


3. Dependent sources, transistor model circuits

→ **4. Thevenin and Norton theorems**

5. Equivalent resistance (max power transfer)

Mesh current analysis

Mesh current analysis

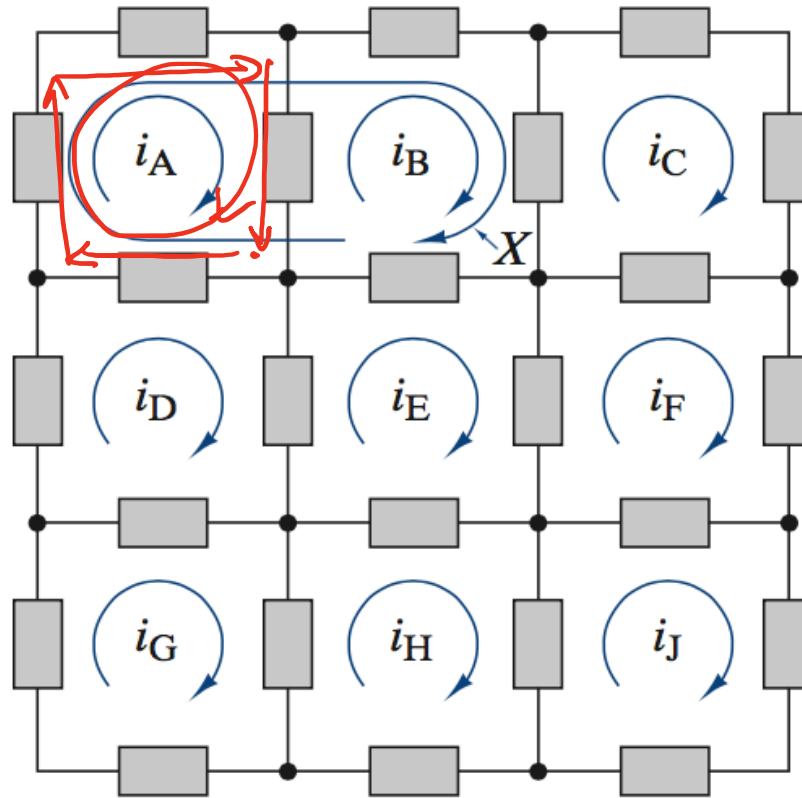

$$\bar{X} = \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \\ \vdots \\ i_J \end{bmatrix}$$




$$\bar{A} \cdot \bar{X} = \bar{b}$$

$$\bar{X} = \bar{A}^{-1} \cdot \bar{b}$$

Mesh current analysis

- STEP 1 Identify a mesh current with every mesh and a voltage across every circuit element.
- STEP 2 Write KVL connection constraints in terms of the element voltages around every mesh.
- STEP 3 Use KCL and the i – v relationships of the elements to express the element voltages in terms of the mesh currents.
- STEP 4 Substitute the element constraints from step 3 into the connection constraints from step 2 and arrange the resulting equations in standard form.


Planar meshes

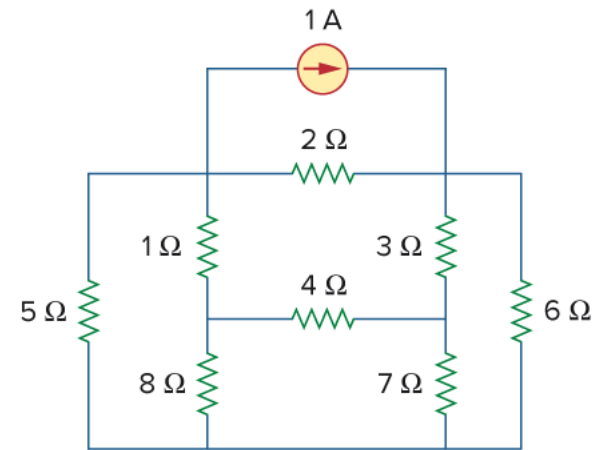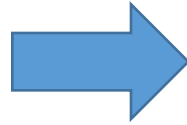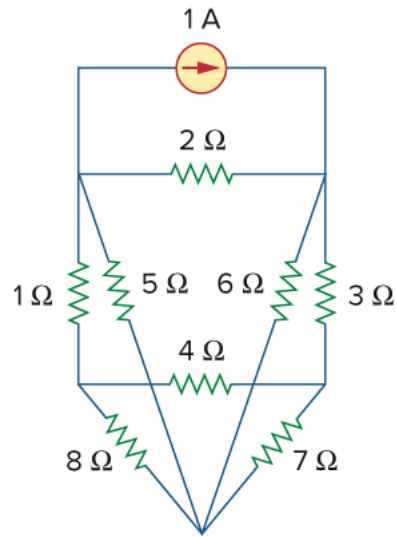

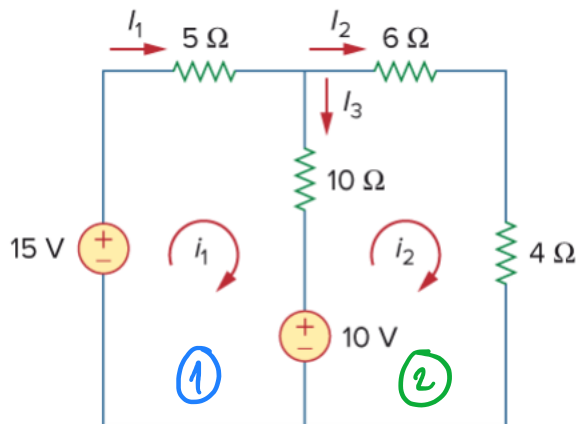Example

(Ex 3.5 in book, 6th ed)

Find the branch currents I_1 , I_2 , and I_3 using mesh analysis.



$$\textcircled{1} \quad -15\text{V} + I_1 \cdot 5\Omega + (I_3 \cdot 10\Omega + 10\text{V}) = 0$$






$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$\hookrightarrow 15i_1 - 10i_2 - 5 = 0$$

$$-10 + (i_2 - i_1)10 + 6i_2 + 4i_2 = 0$$


$$\textcircled{2} \quad \hookrightarrow -10i_1 + 20i_2 - 10 = 0$$
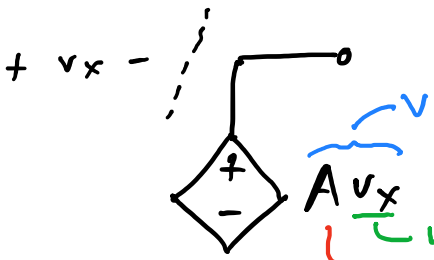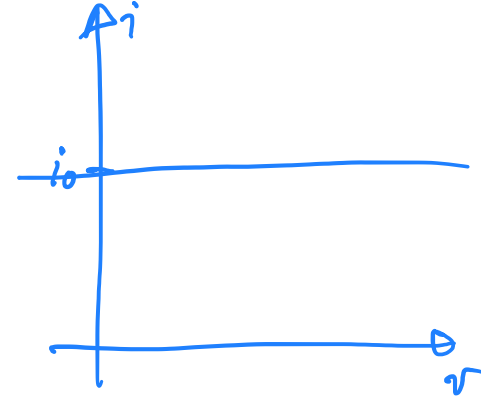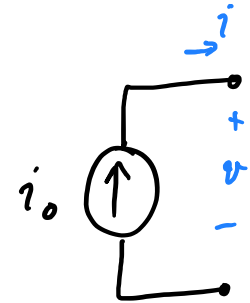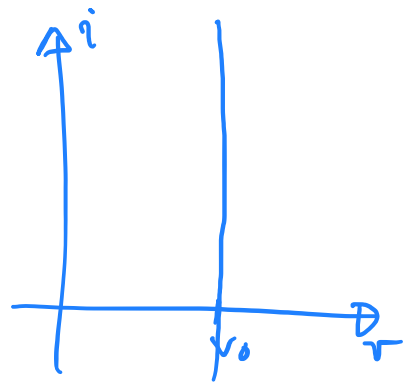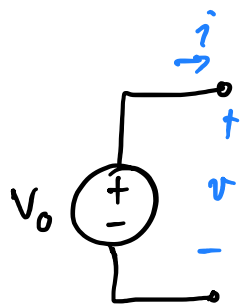
$$\begin{bmatrix} 15 & -10 \\ -10 & 20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$




VCVS

unitless, voltage gain

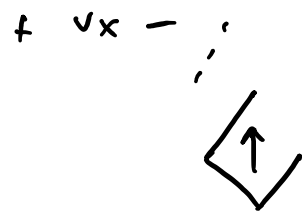


$A/V = 1/\Omega$, transconductance

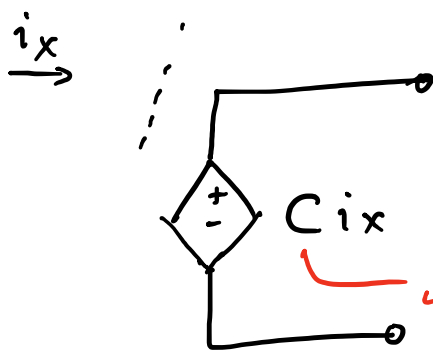


CCVS

Ω , transresistance

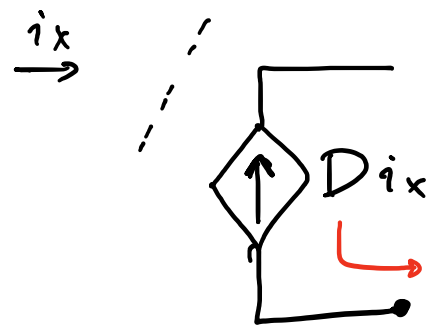


unitless, current gain

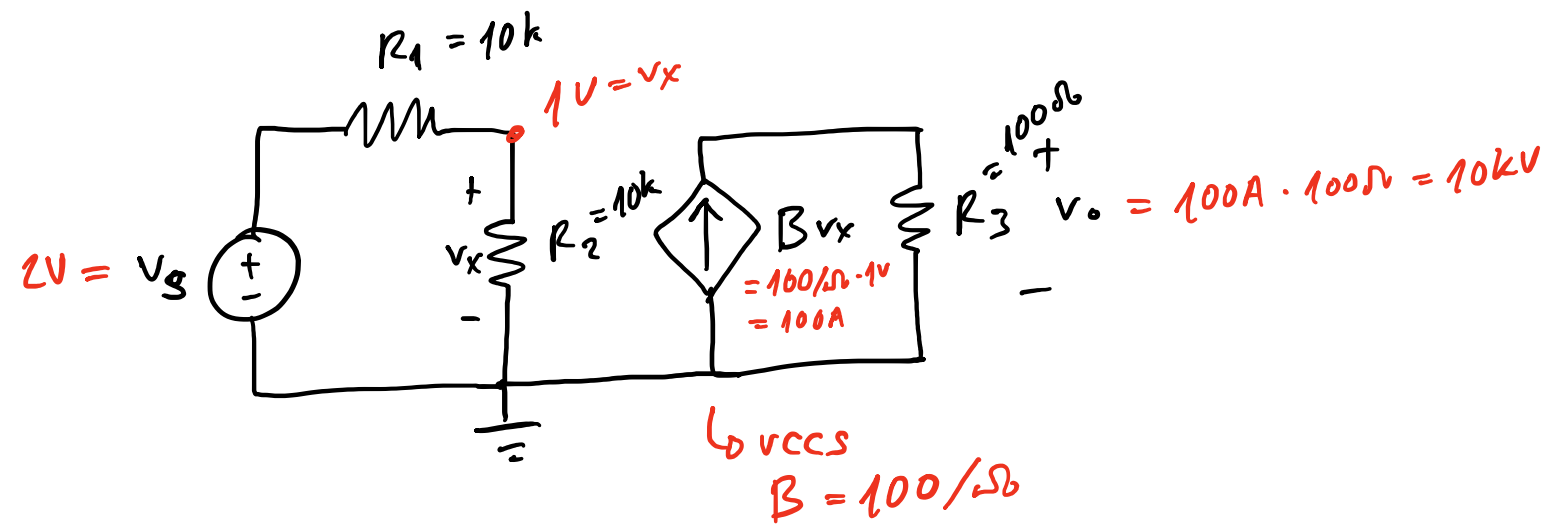

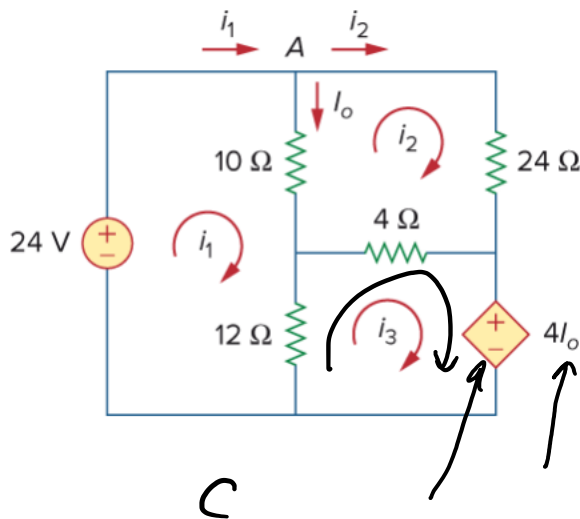Example

Use mesh analysis to find the current I_o in the circuit



$$\textcircled{1} \quad -24 + 10(i_1 - i_2)$$

$$\textcircled{2} \quad 24i_2 + 4(i_2 - i_3) + 1$$

$$\textcircled{3} \quad 12(i_3 - i_1) + 4(i_3 - i_2) + 1$$


$$I_o = i_1 - i_2$$

$$12(i_3 - i_1) + 4(i_3 - i_2) + 4(i_1 - i_2) = 0$$

$$= 0$$

Example



Mesh analysis with a current source...?

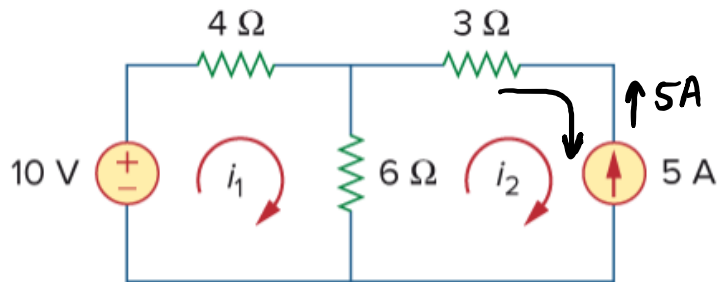

$$i_2 = -5A$$

$$\textcircled{1} -10 + 4i_1 + 6(i_1 - i_2) = 0$$

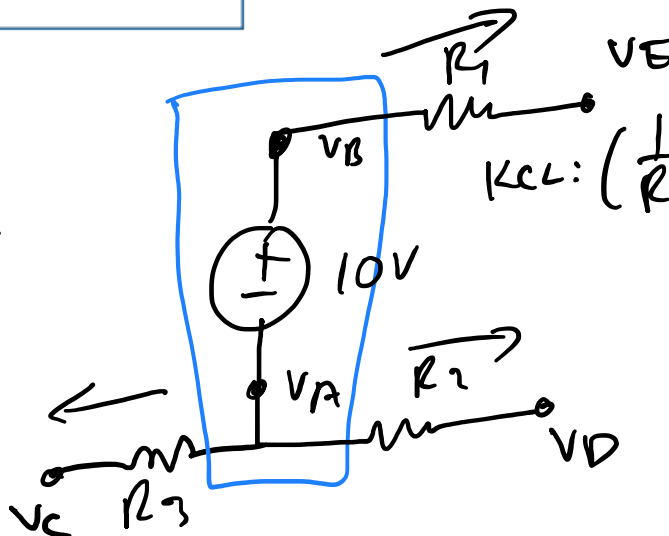
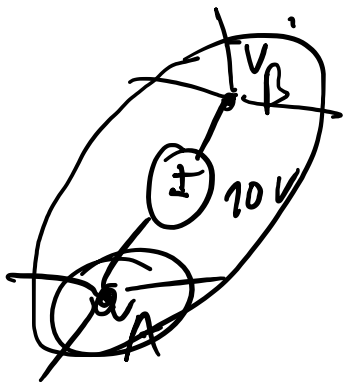
$$\textcircled{2} 6(i_2 - i_1) + 3i_2 + ? = 0$$



$$\text{KCL: } \left(\frac{1}{R_2} + \frac{1}{R_3} \right) V_A - \frac{1}{R_2} V_C - \frac{1}{R_3} V_D + \frac{1}{R_1} (V_A + 10V) - \frac{1}{R_1} V_E = 0$$

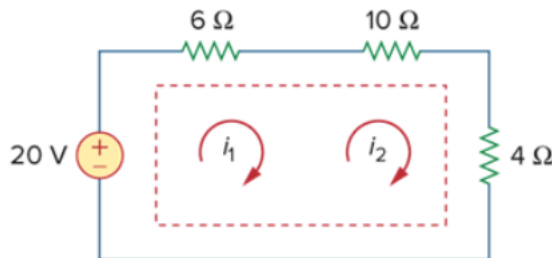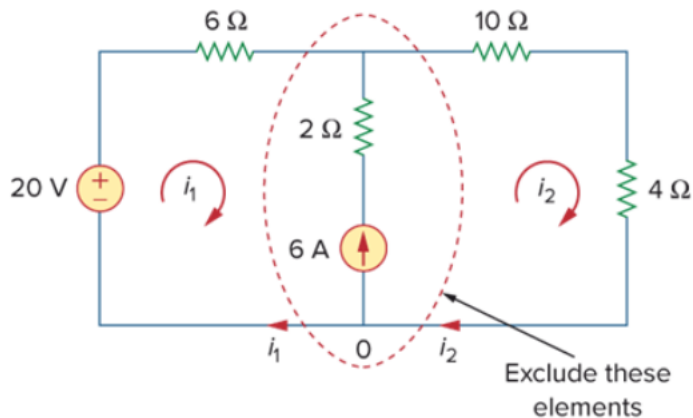Example

Mesh analysis with a current source between two mesh panels.



$$i_1 + 6A = i_2 \quad \rightarrow \quad i_1 = i_2 - 6A$$

$$\text{KVL: } -20 + 6i_1 + 10i_2 + 4i_2 = 0$$

$\downarrow \qquad \qquad \downarrow$
 $(i_1 + 6) \quad (i_1 + 6)$

$$(6 + 10 + 4)i_1 - 20 + 60 + 24 = 0$$




$$20i_1 + 44 = 0$$

$$i_1 = \frac{-44}{20} = -2.2A$$



Dependent sources and DC Transistor Circuits

Transistors

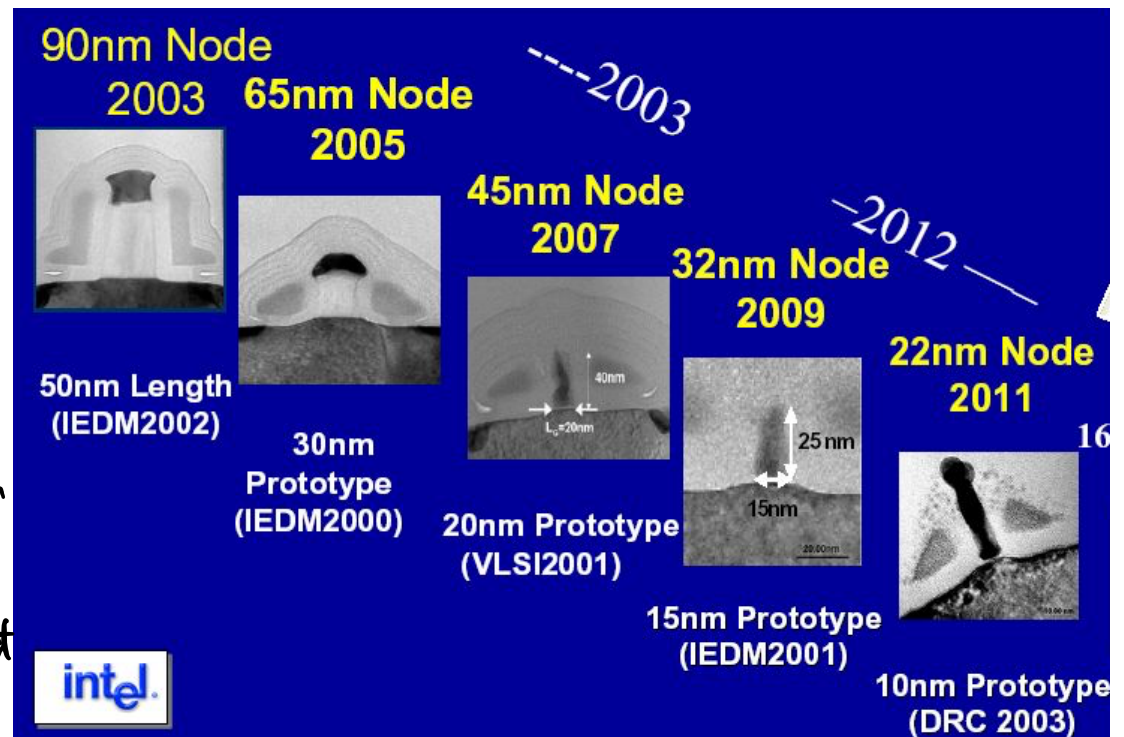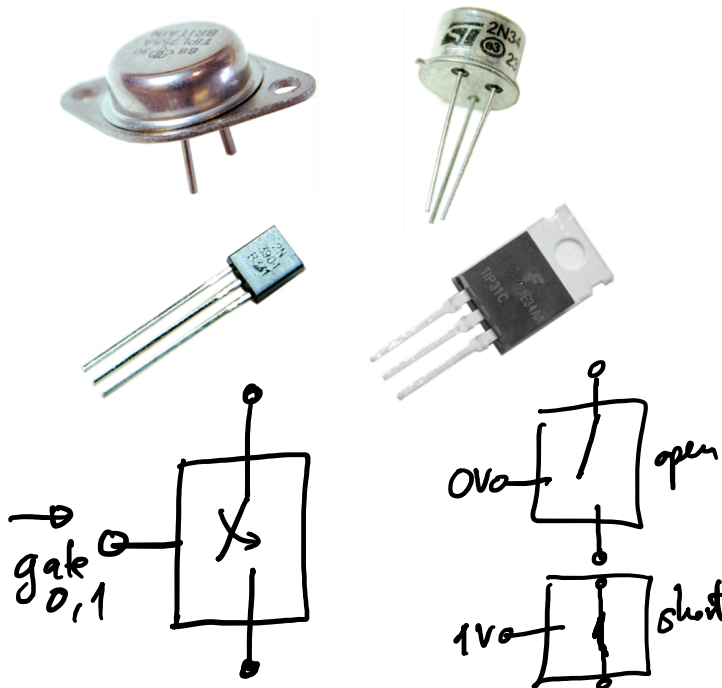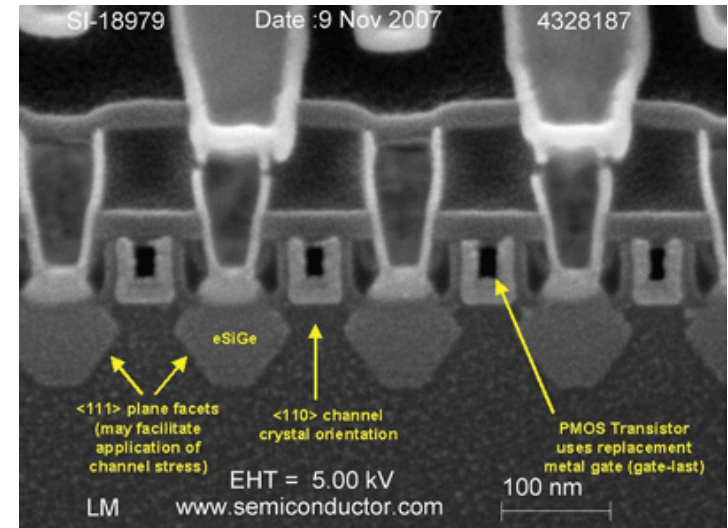
- Bipolar junction transistor (BJT)
- Field effect transistor (FET)



Examples

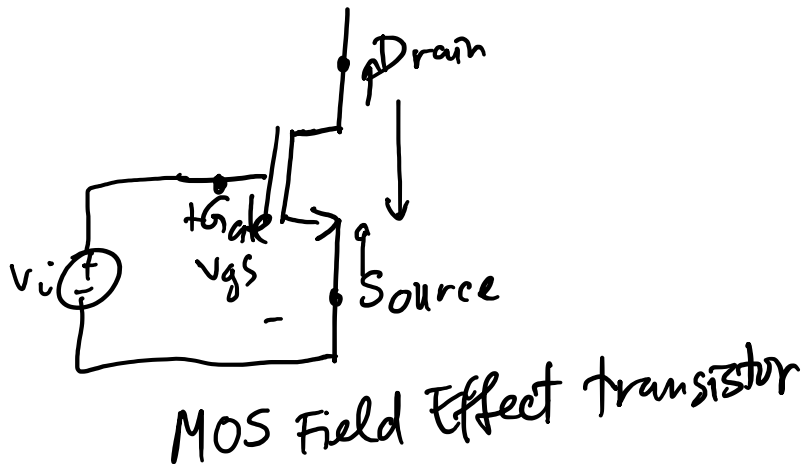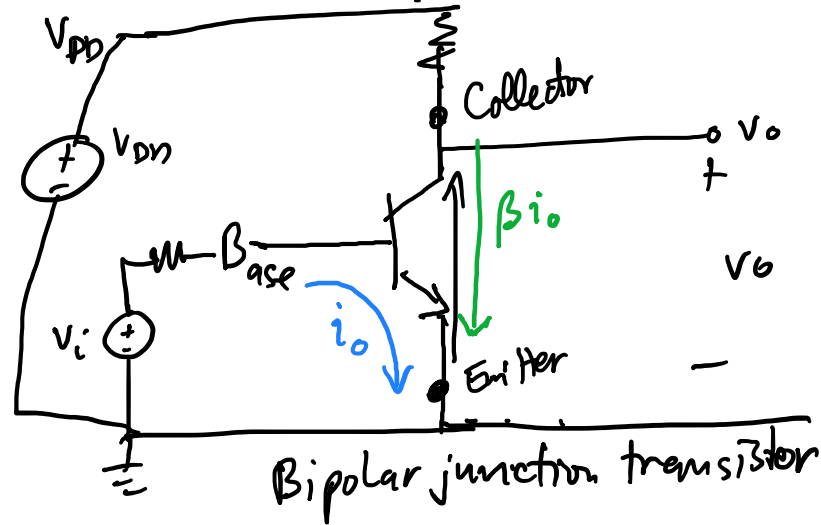

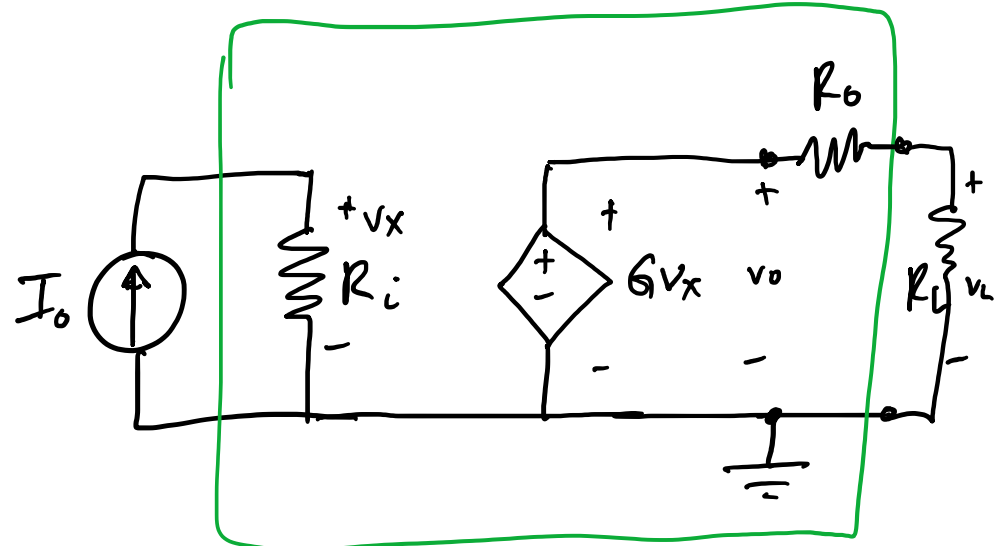Typical ect with dependent source
(we will revisit similar ones when modeling transistors)




$$v_x = I_o R_i$$

$$v_o = G v_x = G I_o R_i$$

$$v_L = \frac{R_L}{R_o + R_L} v_o$$

Transistor Model

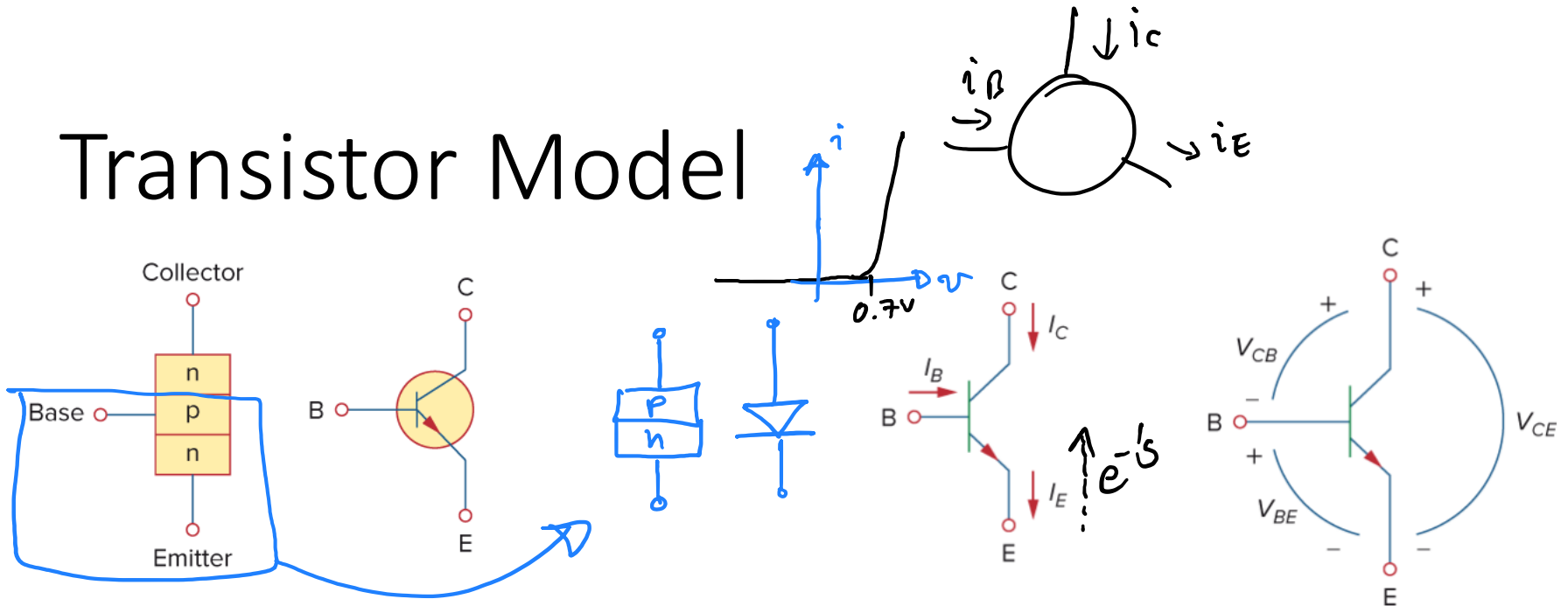

KCL: $I_E = I_B + I_C$

- Modes:

- Active
- Cutoff
- Saturation


=>

$I_C = \beta I_B$

current gain



- Active mode: $v_{BE} \sim 0.7V$, $I_C = \beta I_B$, β is current gain

Transistor Model

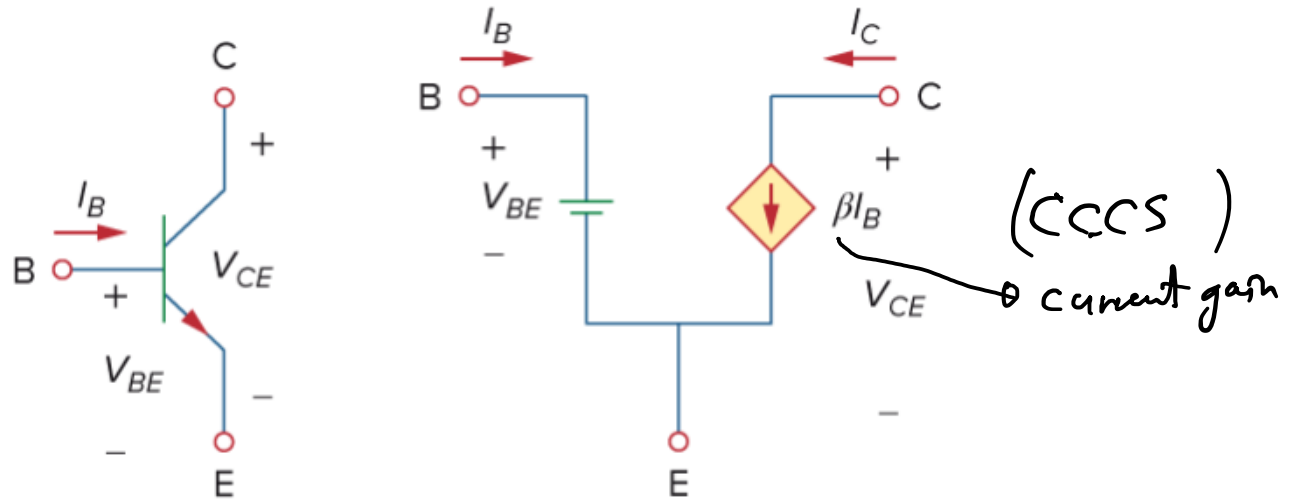

Transistor Example

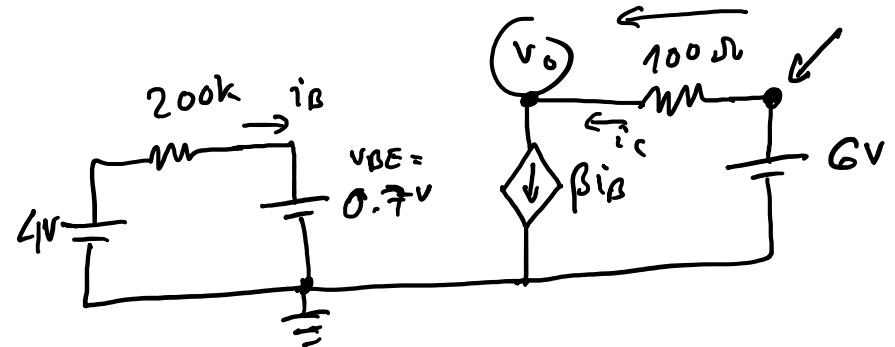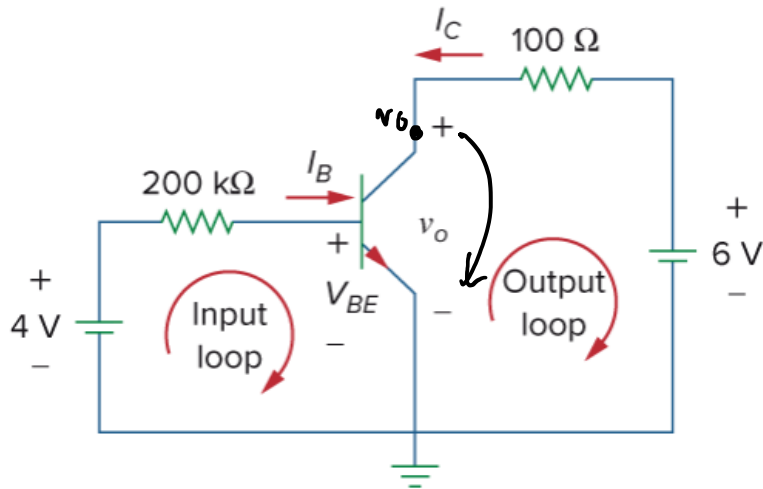
Find I_B , I_C and v_o . Assume active mode and $\beta = 50$.



$$i_B = \frac{4V - 0.7V}{200k} = \frac{3.3V}{200k} = \frac{16.7}{1000} \text{ mA} = 16.7 \mu A$$






$$i_C = \beta i_B = \frac{1670}{2} \mu A = 835 \mu A$$
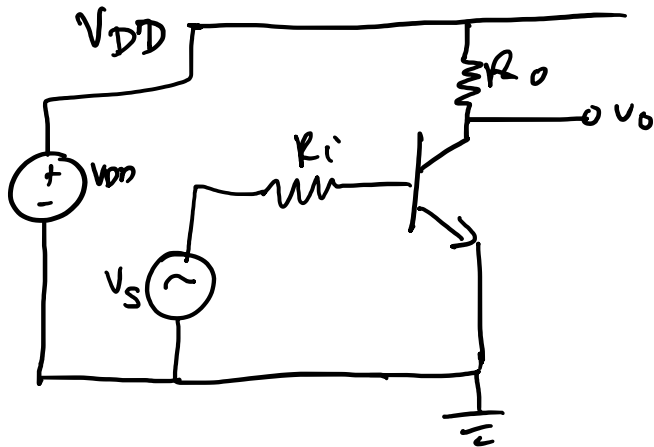
$$\begin{aligned} v_o &= 6V - 100i_C = 6V - 100\Omega \cdot 835 \mu A \\ &= 6V - 83.5 \text{ mV} = 6V - 0.0835V \\ &= \underline{5.9165V} \end{aligned}$$



Transistor Example

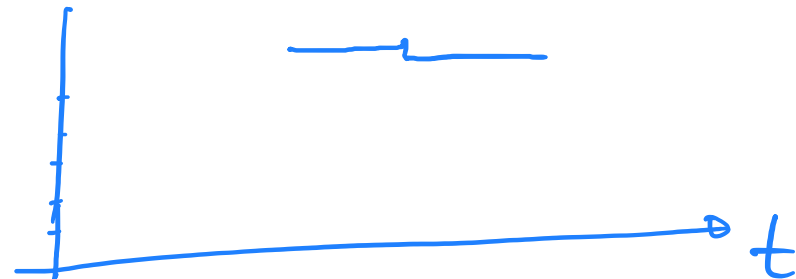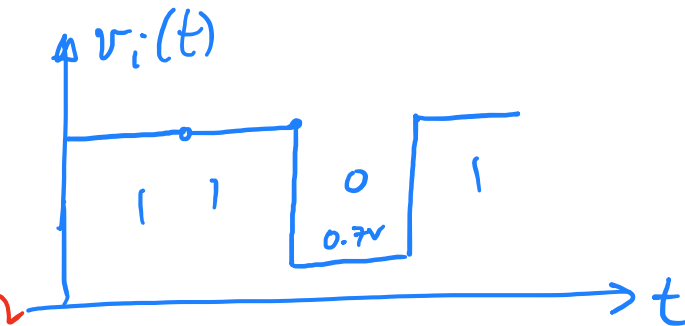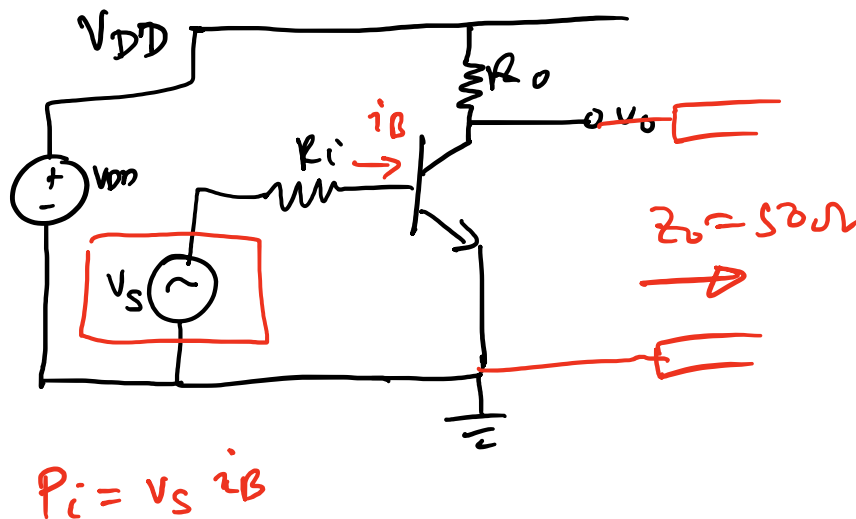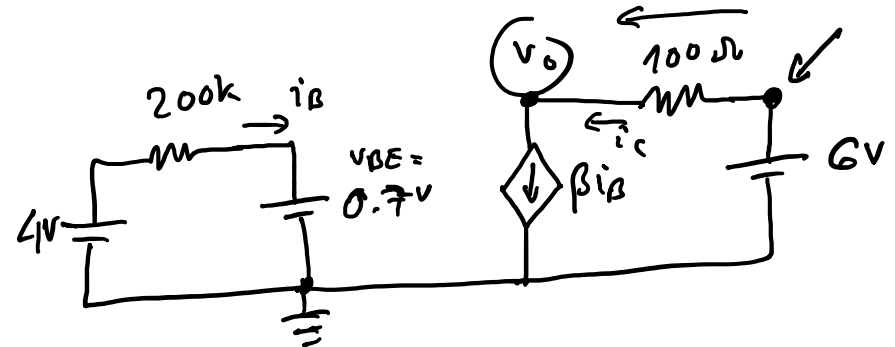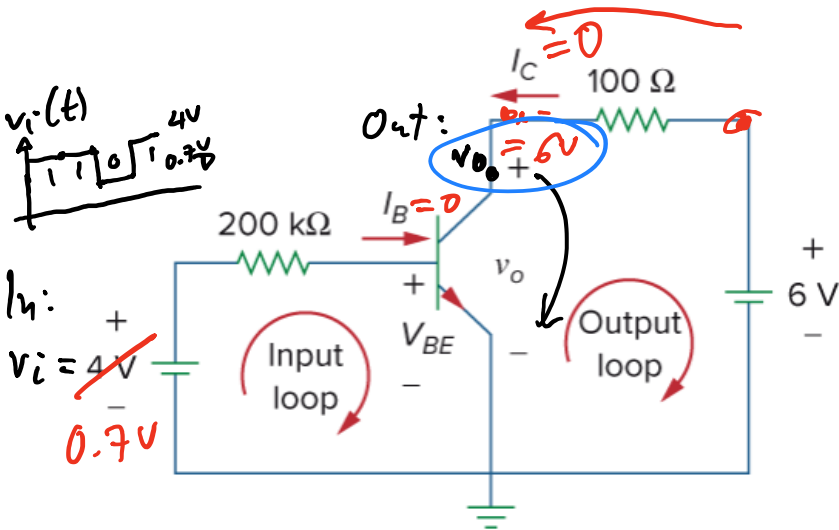
Find I_B , I_C and v_o . Assume active mode and $\beta = 50$.



Linearity, superposition, source transformation



Linearity

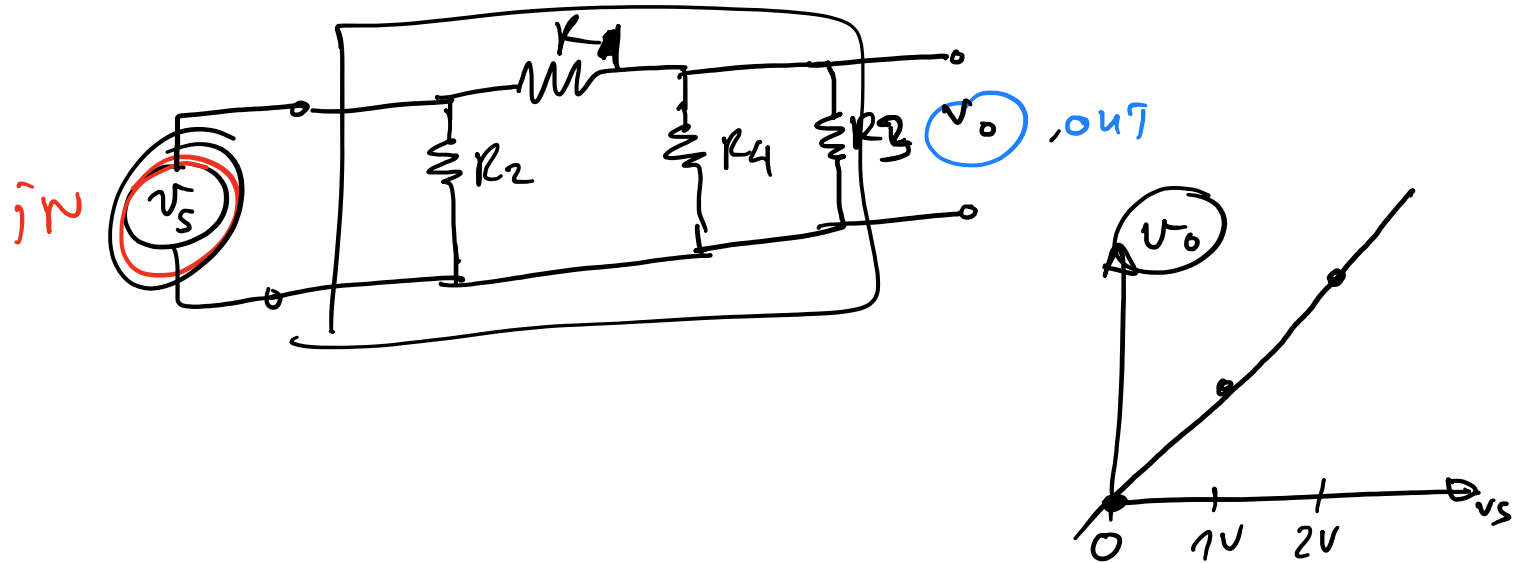- Any output is proportional to any input




Linearity: example

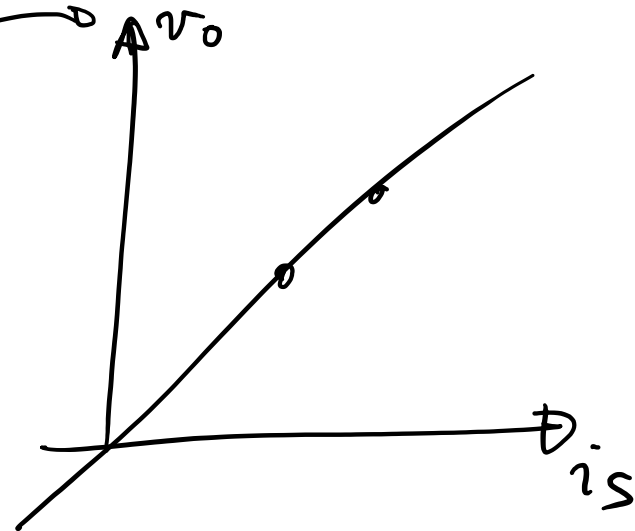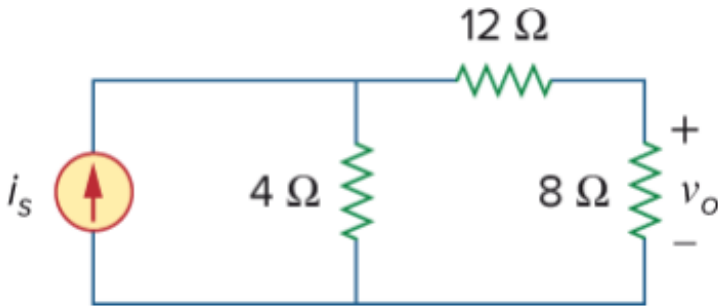Plot v_o vs. i_s . Try $i_s = 30\text{A}$, 45A




Superposition

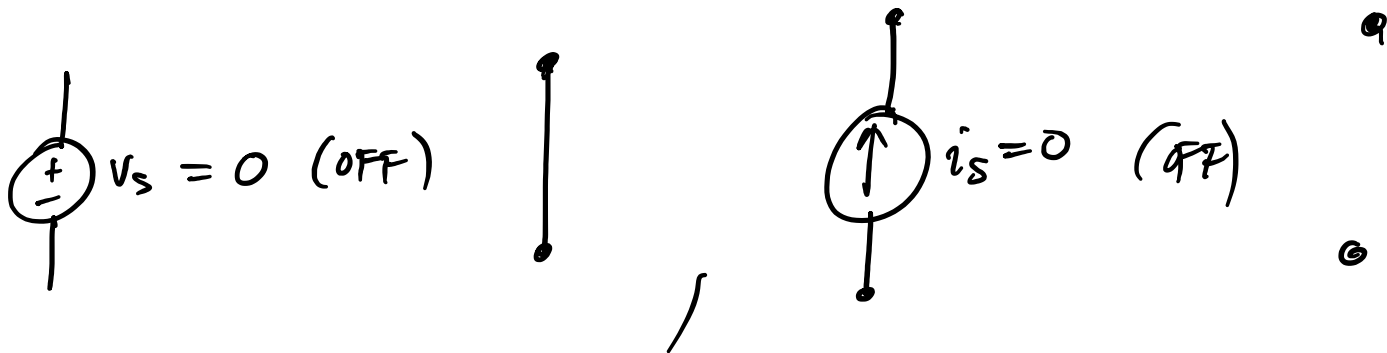- For multiple inputs (e.g. sources):
 - Any output is the sum of outputs due to each input turned on separately
 - “Turned off input” means $V=0$ for voltage sources, $I=0$ for current sources.
 - Dependent sources stay.




Superposition: example 1


- Use superposition to find v .

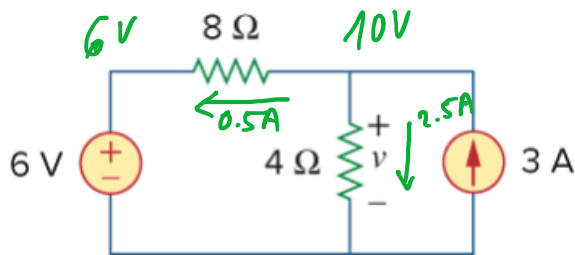

—

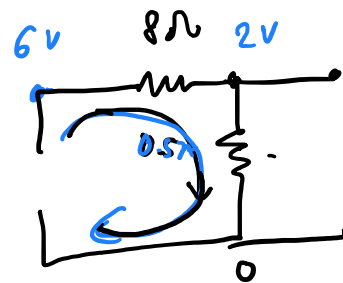

4Ω

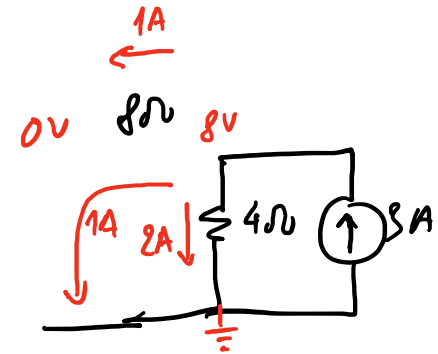

Superposition: example 2

Use superposition to find v_x in the circuit of **Fig. 4.11**.

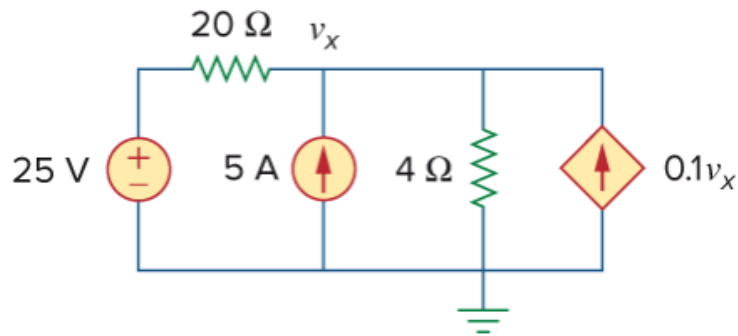


Figure 4.11 For **Practice Prob. 4.4**.