

EK 307: Electric Circuits

Fall 2017

Lecture 19

Nov 14, 2017

Milos Popovic

Department of Electrical and Computer Engineering

Boston University

Administrivia

- Homework 8 due
- Midterm #2: Thu Nov 16

Last time (Lecture 18):

1. First-order op-amp circuits
2. Second-order circuits & resonators





(Chapter 8)

Lecture 18: Chapter 8 – 2nd order ccts

Second-order circuits

- 1st-order circuits $\Rightarrow$ 1st order diff eq. $\Rightarrow$ 1 energy storage element
- 2nd-order circuits $\Rightarrow$ 2nd order diff eq. $\Rightarrow$ 2 energy storage elements

Examples

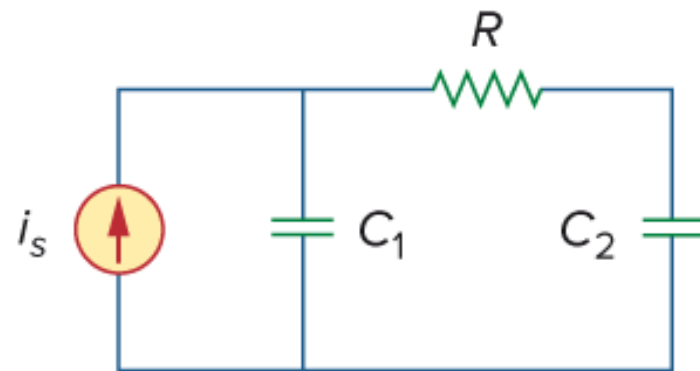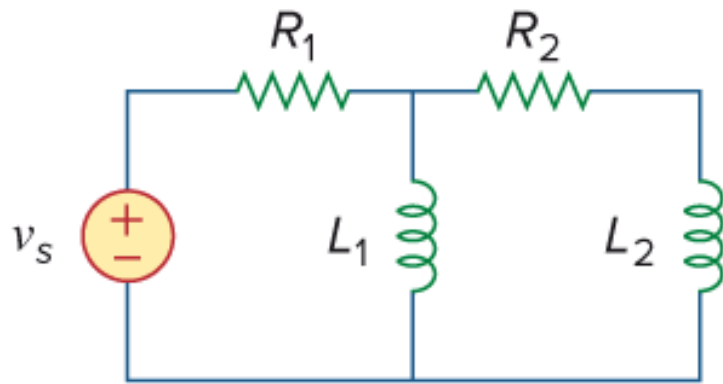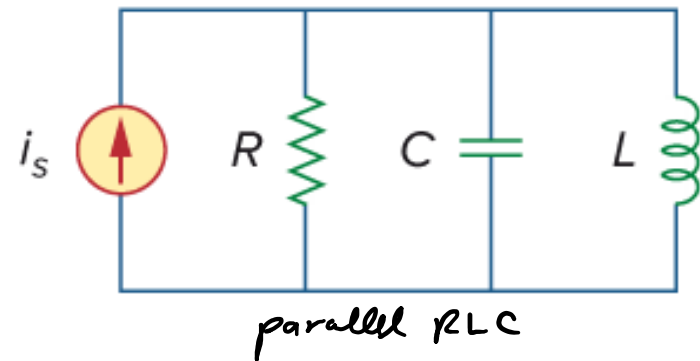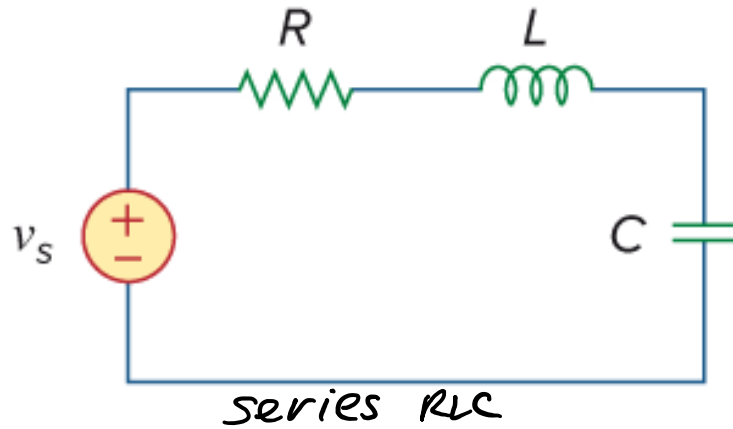


Initial conditions

- We will need: $v(0)$, $i(0)$, $dv(0)/dt$, $di(0)/dt$, $i(\infty)$, and $v(\infty)$.
- Remember: use passive sign convention
- For capacitor: $v(0^-) = v(0^+)$
- For inductor: $i(0^-) = i(0^+)$

Source-free Series RLC Circuit

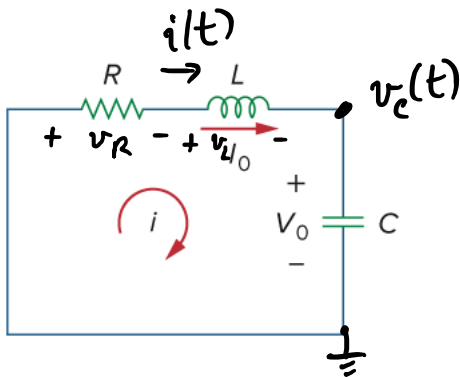Give: $v(0), i(0)$ at $t=0$. Find: $v(t), i(t), t > 0$.



$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$i = C \frac{dv_C}{dt} \rightarrow \frac{dv_C(t)}{dt} = \frac{i(t)}{C} \Rightarrow v_C(t) = \int_0^t \frac{1}{C} i(t') dt'$$

$$\begin{aligned} v_R(t) + v_L(t) + v_C(t) &= 0 \\ iR + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t') dt' &= 0 \end{aligned}$$

$$\frac{d}{dt} \left(iR + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t') dt' \right) = 0$$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

we need $i(0)$
 $i'(0) = \frac{v_L(0)}{L} \Rightarrow v_C \dots$

$$\frac{d^2}{dt^2} i + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$\frac{1}{LC} \rightarrow s^{-2} \rightarrow \frac{1}{\sqrt{LC}} \rightarrow s^{-1}$

$$L \frac{d}{dt} i + iR = 0$$




$$\frac{d}{dt} i + \frac{R}{L} i = 0$$

$$\frac{1}{i} \frac{d}{dt} i = -\frac{R}{L}$$

$$\frac{d}{dt} \ln i = -\frac{R}{L}$$

$$\ln i = -\frac{R}{L} \int dt = -\frac{R}{L} t$$

$$i(t) = e^{-\frac{R}{L} t}$$

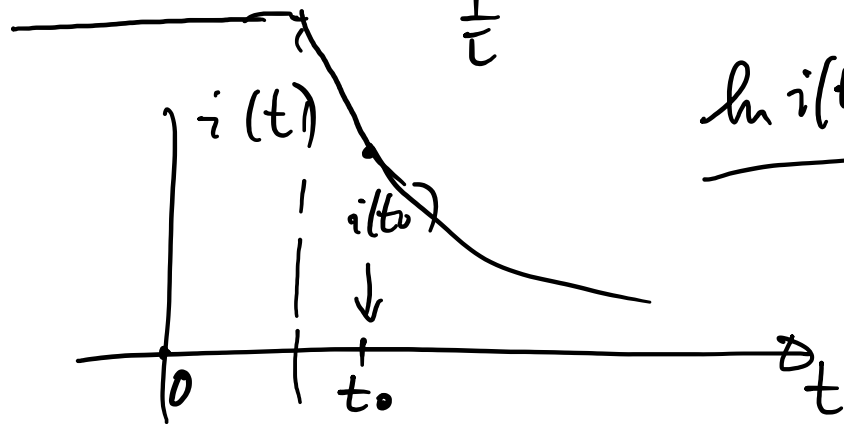

$$\int_0^t \frac{d}{dt'} \ln i(t') dt' =$$


$$\ln i(t') \Big|_{t'=0}^{t'=t} = - \frac{t'=t}{t'=0} = -\frac{R}{L} (t-0)$$

$$\ln i(t) - \ln i(0) = -\frac{R}{L} t \Rightarrow \frac{i(t)}{i(0)} = e^{-\frac{R}{L} t}$$

$$\ln i(t) - \ln i(t_0) = -\frac{R}{L} (t-t_0)$$

$$\boxed{\frac{i(t)}{i(t_0)} = e^{-\frac{R}{L} (t-t_0)}}$$

Source-free Series RLC Circuit

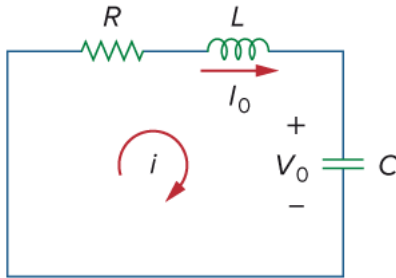

$$\frac{d^2}{dt^2} i + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$s^2 \cancel{Ae^{st}} + \frac{R}{L} s \cancel{Ae^{st}} + \frac{1}{LC} \cancel{Ae^{st}} = 0$$

$$\boxed{s^2 + \frac{R}{L}s + \frac{1}{LC} = 0}$$

$$s = -\frac{1}{\tau}$$

$$e^{-\frac{1}{\tau}t}$$

$$s = j\omega_0$$

$$(j\omega_0)t$$

$$= \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2}$$

freq (rad/s)



$$\cos(\omega_0 t)$$

s_1 and s_2 : natural frequencies, measured in nepers per second (Np/s).

ω_0 : resonant frequency or strictly as the undamped natural frequency, expressed in radians per second (rad/s)

$$\boxed{i = Ae^{st}} \rightarrow \frac{di}{dt} = sAe^{st}$$

$$\frac{d^2 i}{dt^2} = s^2 Ae^{st}$$

$$\boxed{s^2 + \frac{R}{L}s + \frac{1}{LC} = 0}$$

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



$$s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$Ax^2 + Bx + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\frac{1}{LC}}}{2}$$
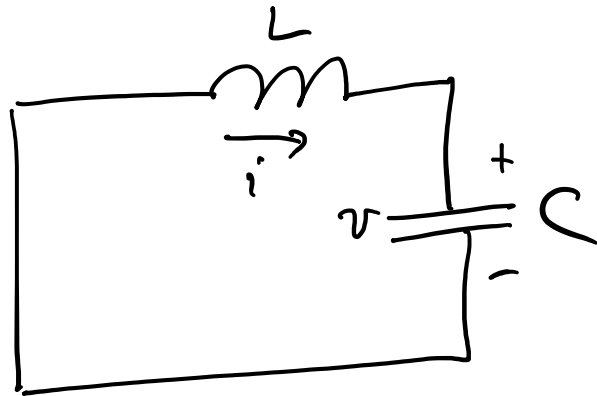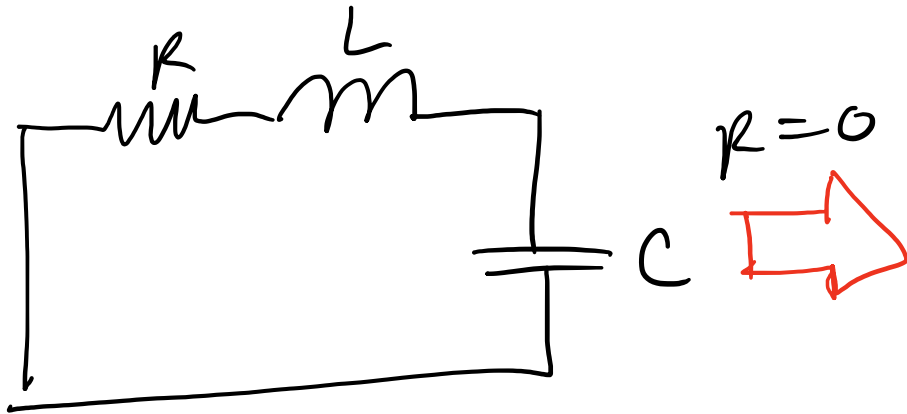
$$\boxed{s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}$$



$$s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$


$$s = 0 \pm \sqrt{0 - \frac{1}{LC}}$$


$$s_{1,2} = \pm j \frac{1}{\sqrt{LC}} = \pm j\omega_0$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t}$$





$$= A_1 (e^{j\omega_0 t} + e^{-j\omega_0 t}) = \underline{A_1 \cos(\omega_0 t)}$$

$$T = \frac{2\pi}{\omega_0}$$

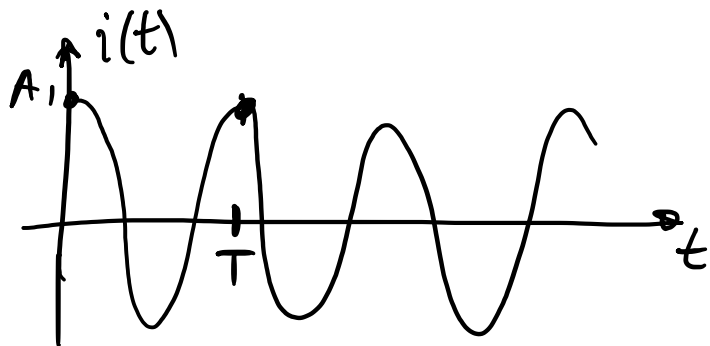

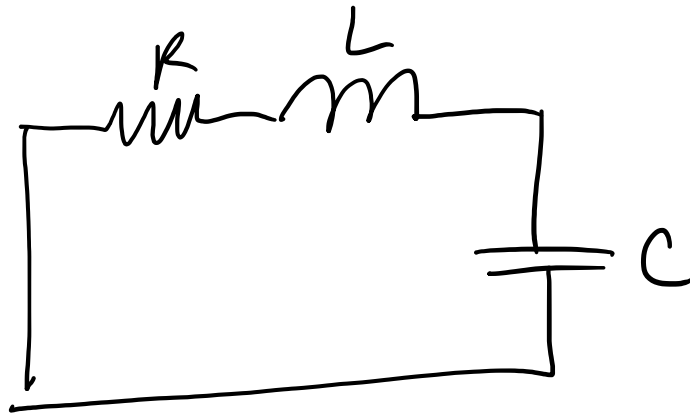

$$R=0$$

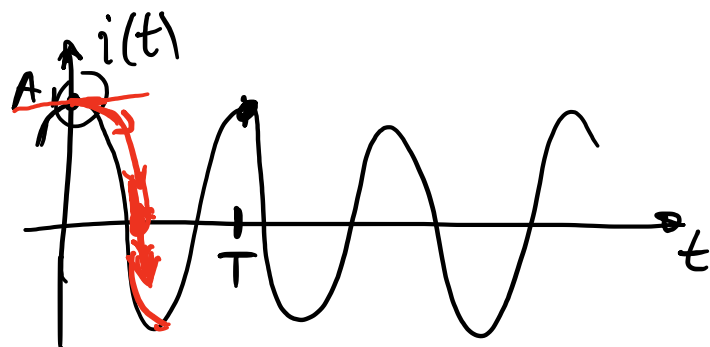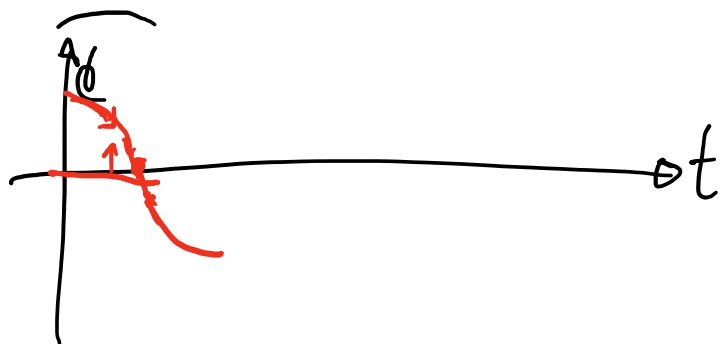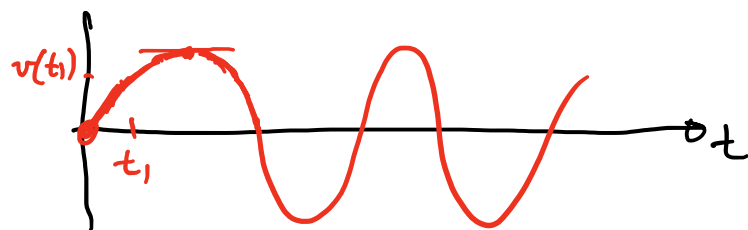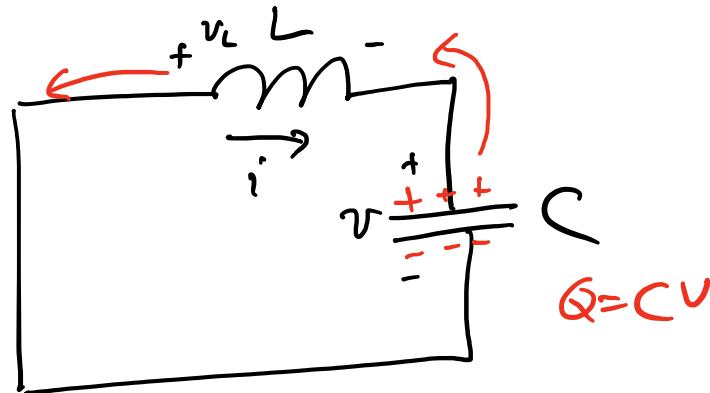



$$-v = +v_L = L \frac{di}{dt} \quad i = C \frac{dv}{dt}$$

$$\frac{di}{dt} = -\frac{v}{L}$$






$$= 0 \text{ at } t=0$$

$$\left. \frac{di}{dt} \right|_{t=t_1} = -\frac{v(t_1)}{L} < 0$$

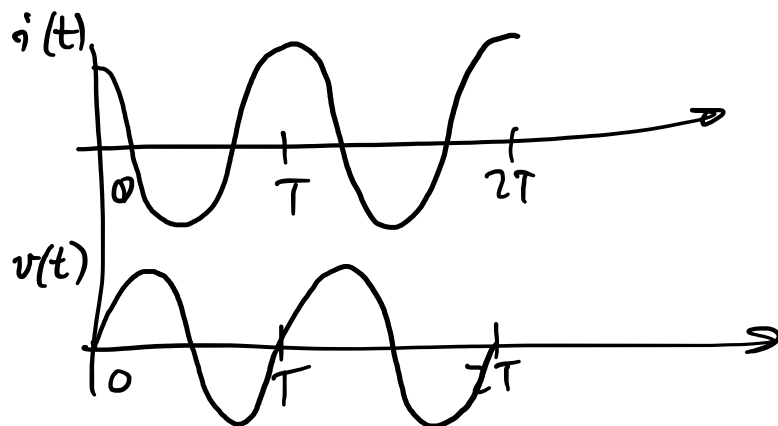








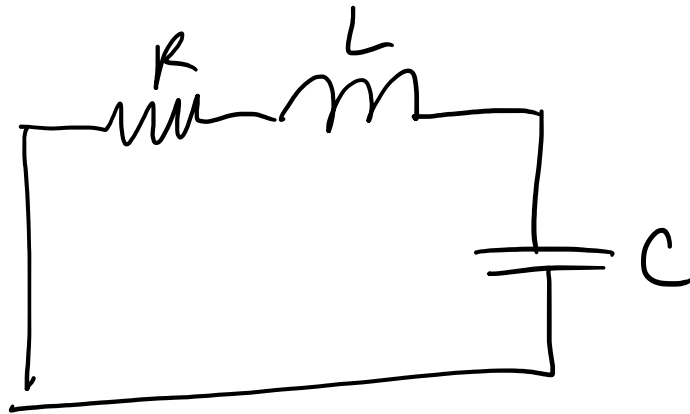



$$R=0$$

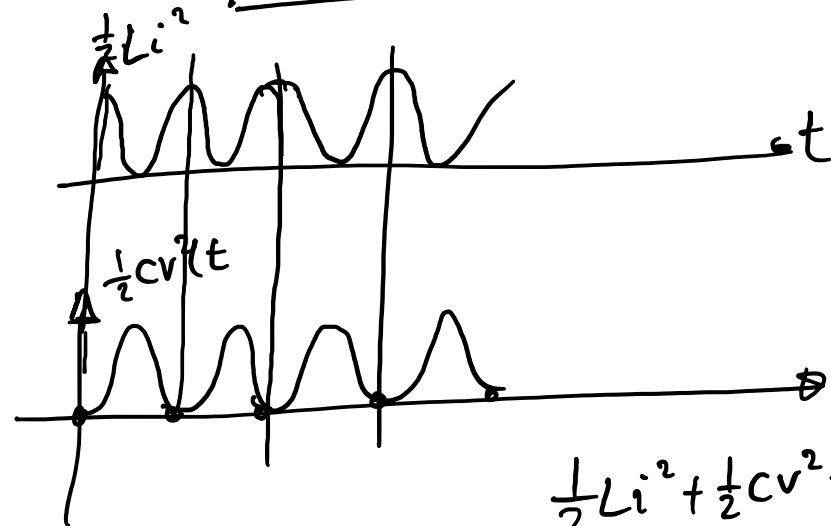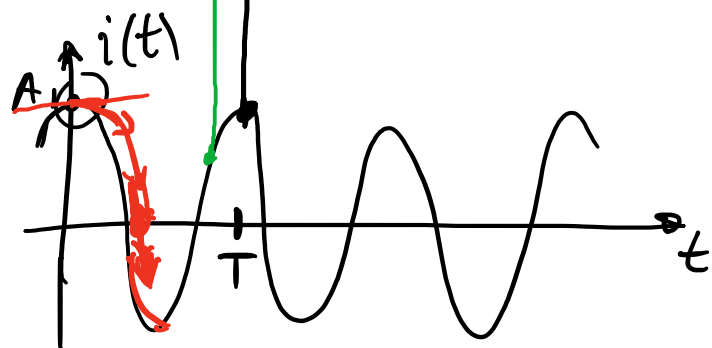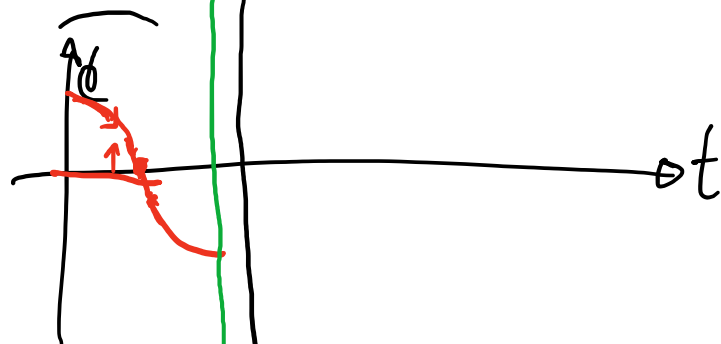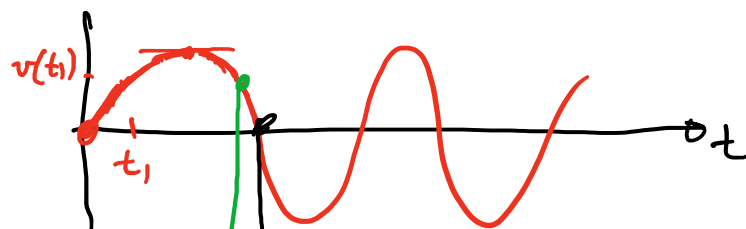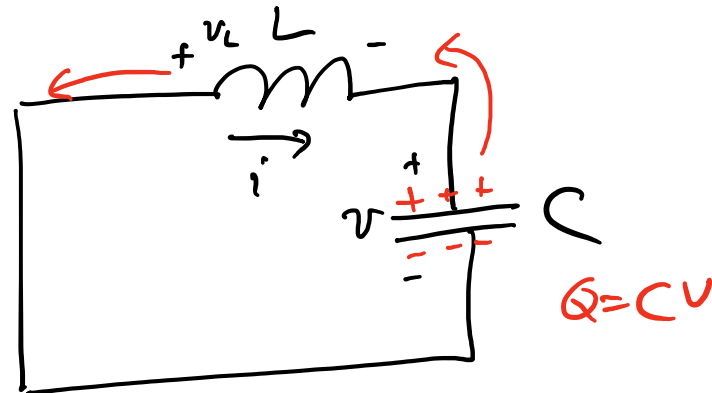






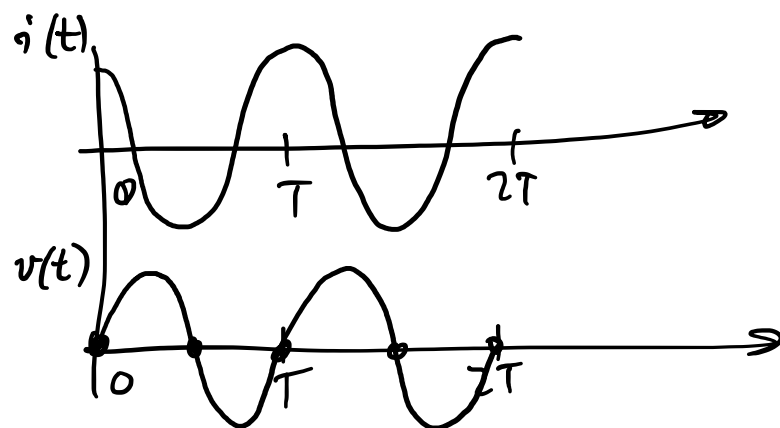
$$\frac{1}{2}Li^2 + \frac{1}{2}Cv^2 = \text{const.}$$



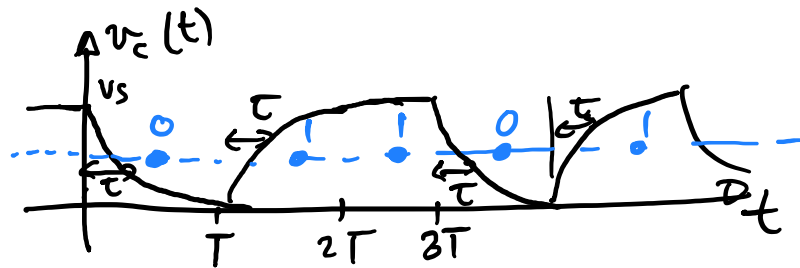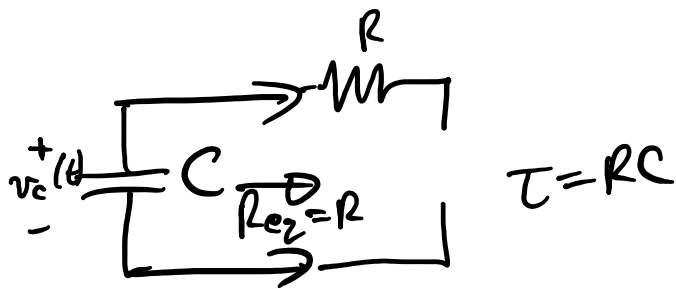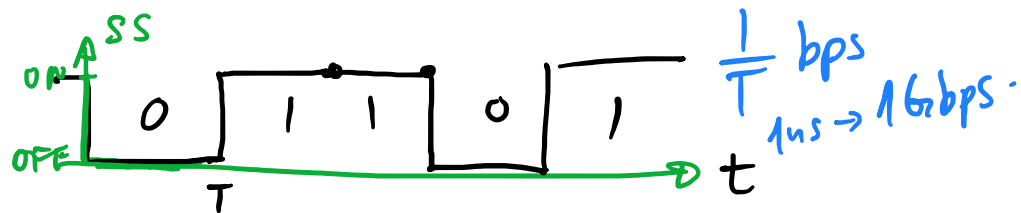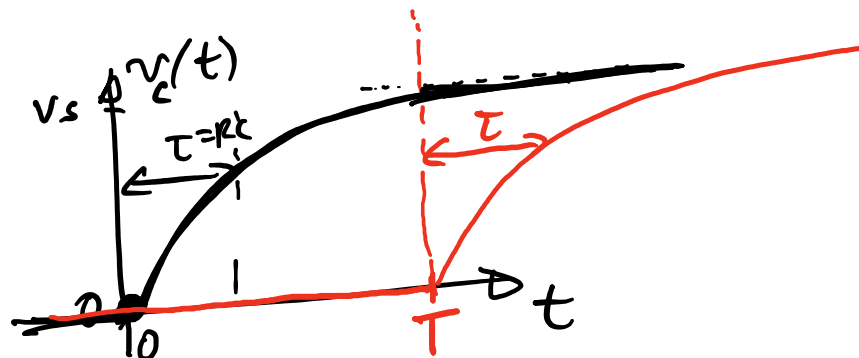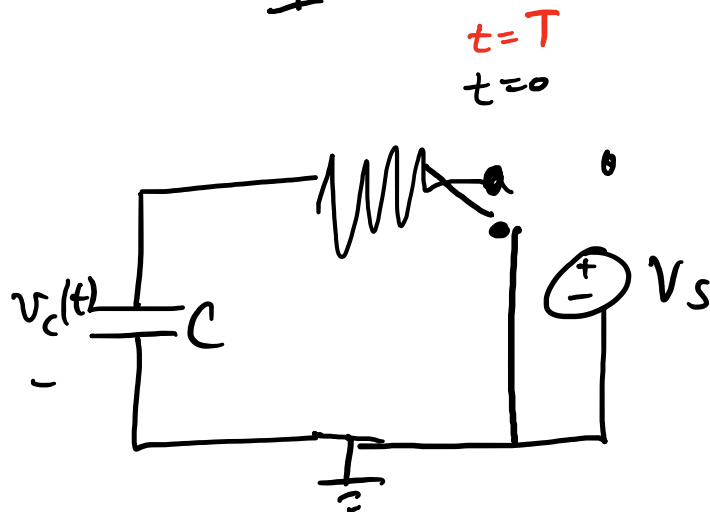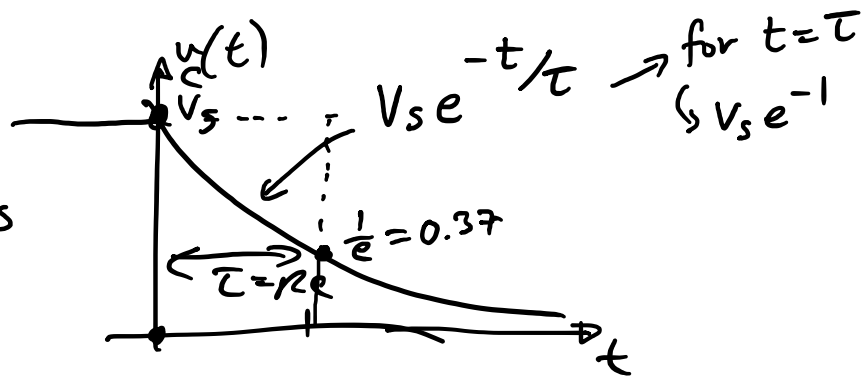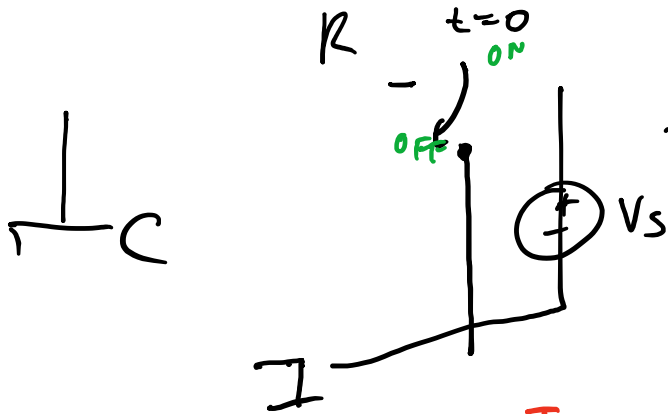

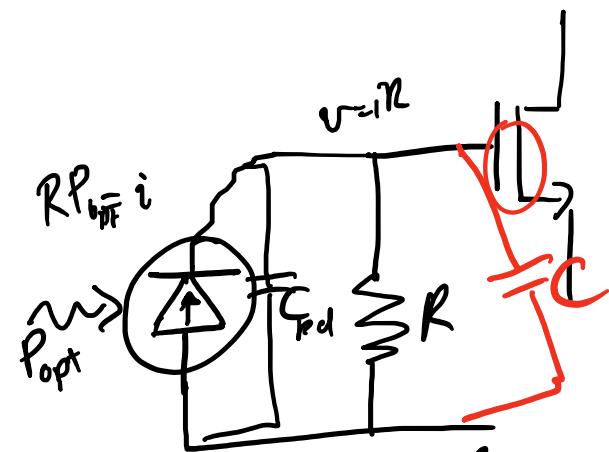


$$\tau = RC$$

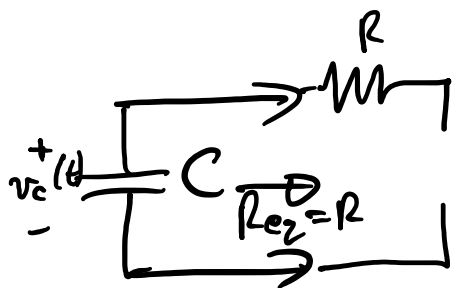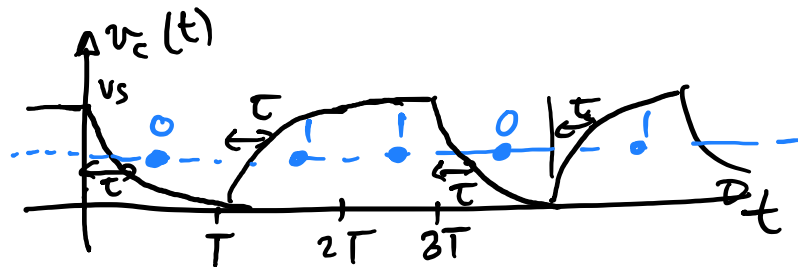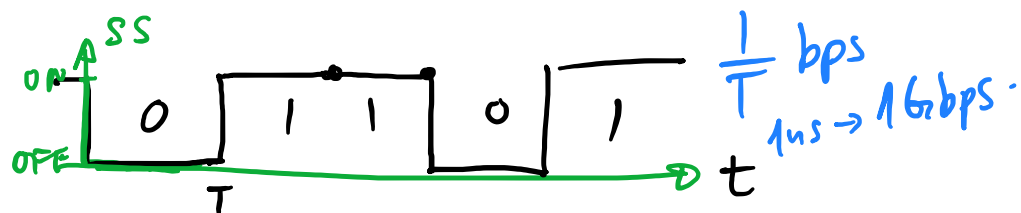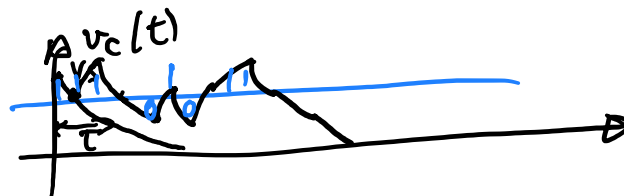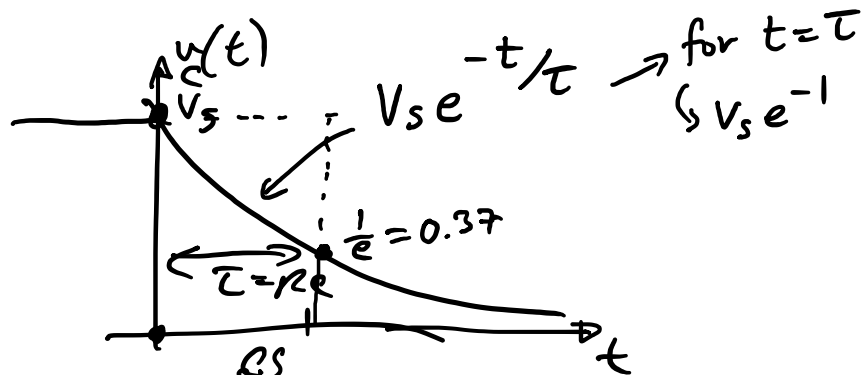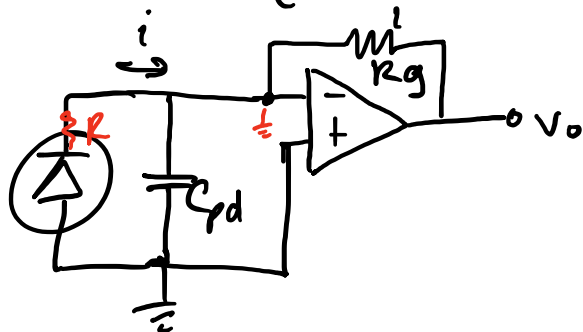

$$\tau = RC$$

Source-free Series RLC Circuit

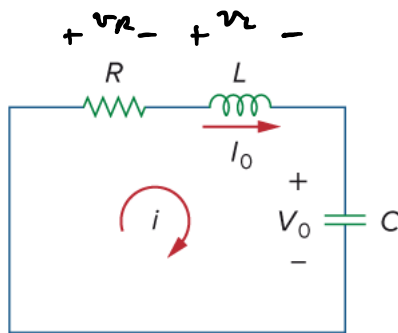

$$iR + L \frac{di}{dt} + \int \frac{1}{C} i dt = 0$$

$$L i'' + R i' + \frac{1}{C} i = 0$$

$$L C i'' + R C i' + i = 0$$

$$i'' + \frac{R}{L} i' + \frac{1}{LC} i = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$A s^2 + B s + C = 0$$

$$1 s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

where $s = \frac{-B}{2A} \pm \sqrt{\frac{B^2 - 4AC}{4A^2}}$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


resonant freq.

$$i = \underline{A} \underline{e^{st}} \quad \frac{d}{dt} i = \underline{A s e^{st}} = s i$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$i_1 = A_1 e^{s_1 t}, \quad i_2 = A_2 e^{s_2 t}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

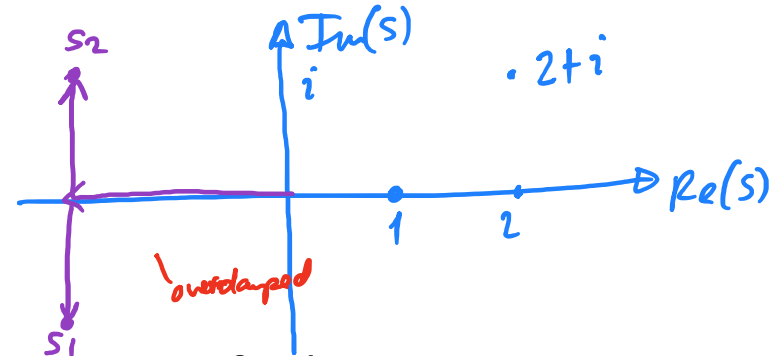

We can infer 3 types of soln:

- 1) If $\alpha > \omega_0$ we have the *overdamped* case.
- 2) If $\alpha = \omega_0$ we have the *critically damped* case.
- 3) If $\alpha < \omega_0$ we have the *underdamped* case.

Source-free Series RLC Circuit


We can infer 3 types of soln:

- 1) If $\alpha > \omega_0$, we have the *overdamped* case.
- 2) If $\alpha = \omega_0$, we have the *critically damped* case.
- 3) If $\alpha < \omega_0$, we have the *underdamped* case.

$$s = -\alpha \pm \Delta\alpha$$

$$i(t) = e^{-\alpha_1 t} - e^{-\alpha_2 t}$$


$$= e^{-t/\tau_1} - e^{-t/\tau_2}$$

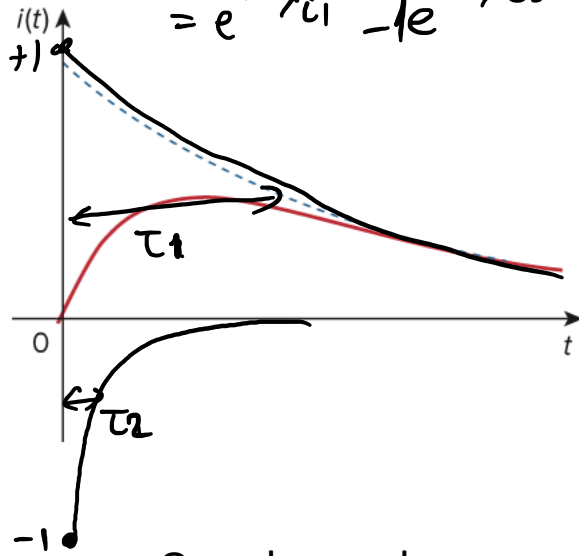

Overdamped

$$s = -\alpha \pm 0$$
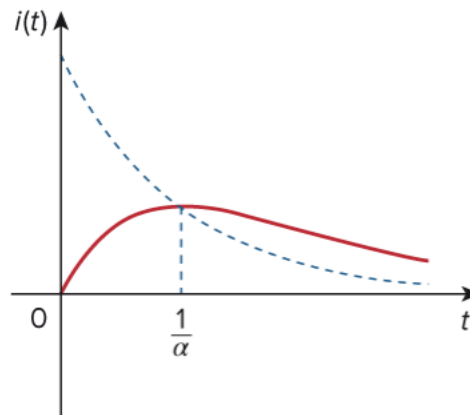
$$i(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$




Critically damped

$$s = -\alpha \pm j\omega_0$$

$$i(t) = A_1 e^{(-\alpha + j\omega_0)t} + A_2 e^{(-\alpha - j\omega_0)t}$$

$$= A_1 2 \cos(\omega_0 t) e^{-\alpha t}$$

if $A_1 = A_2$

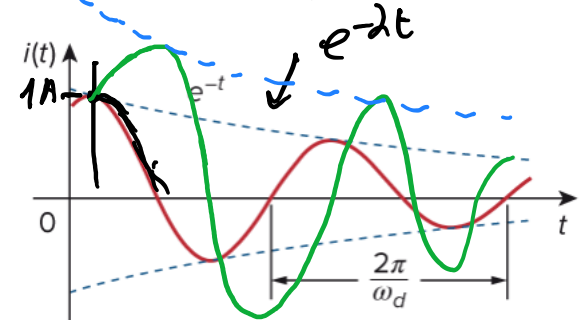


$$i(0) = 1A, v(0) = 0$$

$$i(0) = 1A, v(0) = 1V$$

Underdamped


Overdamped case
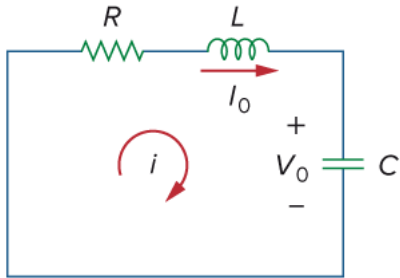
$$\alpha > \omega_0 \rightarrow C > 4L/R^2$$




$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$
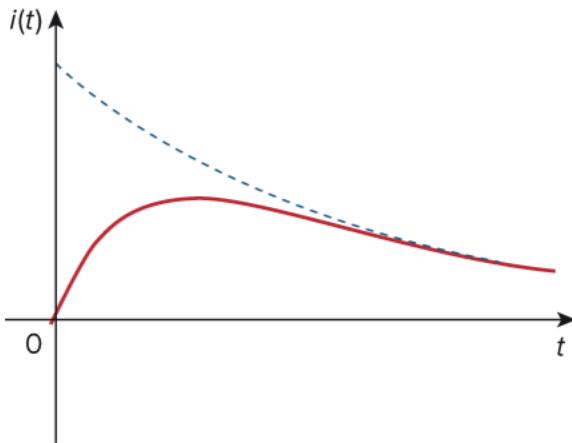
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$



Overdamped case
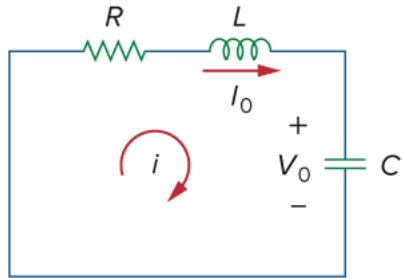
$$\alpha > \omega_0 \quad \Rightarrow \quad C > 4L/R^2$$




$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

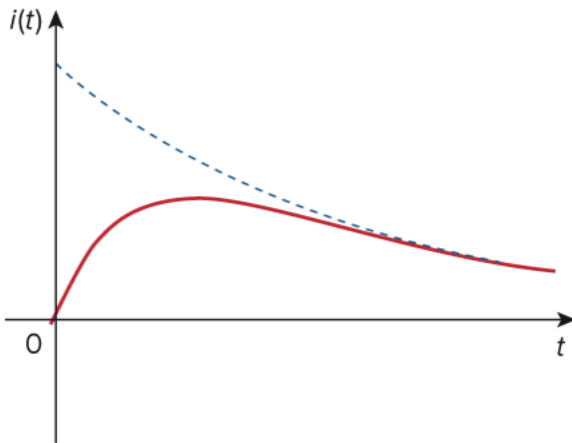

Critically damped case

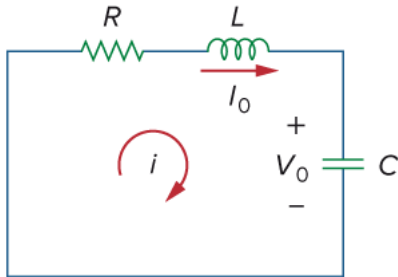

$$\boxed{\alpha = \omega_0} \Rightarrow C = 4L/R^2$$

$$s_1 = s_2 = -\alpha = -\frac{R}{2L}$$

$$i(t) = A_1 e^{-\alpha t} + A_2 e^{-\alpha t} = A_3 e^{-\alpha t}$$

Assumption of exponential solution
wrong for critical damping case!


$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \Rightarrow \frac{d^2 i}{dt^2} + 2\alpha \frac{di}{dt} + \alpha^2 i = 0$$

$\uparrow$ $\uparrow$
 2α ω_0^2
 $\hookrightarrow \alpha^2$

Critically damped case
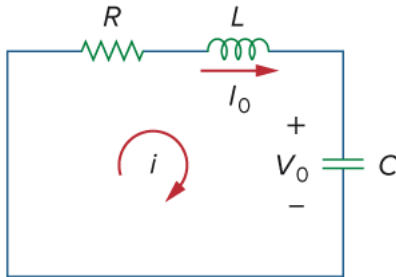
$$\alpha = \omega_0 \rightarrow C = 4L/R^2$$



$$\frac{d^2 i}{dt^2} + 2\alpha \frac{di}{dt} + \alpha^2 i = 0$$

$$\begin{aligned} (A+B)^2 &= A^2 + 2AB + B^2 \\ \left(\frac{d}{dt} + \alpha\right)^2 i &= \left(\frac{d^2}{dt^2} + \frac{d}{dt}\alpha + \alpha\frac{d}{dt} + \alpha^2\right)i \\ &= \left(\frac{d^2}{dt^2} + 2\alpha\frac{d}{dt} + \alpha^2\right)i \end{aligned}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\left(\frac{d}{dt} + \alpha\right)\left(\frac{d}{dt} + \alpha\right)i = \frac{d}{dt}\left(\frac{di}{dt} + \alpha i\right) + \alpha\left(\frac{di}{dt} + \alpha i\right) = 0$$

$$f(t) \equiv f = \frac{di}{dt} + \alpha i$$


$$\boxed{\frac{df}{dt} + \alpha f = 0}$$

$$\rightarrow \frac{df}{dt} = -\alpha f$$


$$f(t) = A e^{-\alpha t} = \frac{di}{dt} + \alpha i$$

Critically damped case
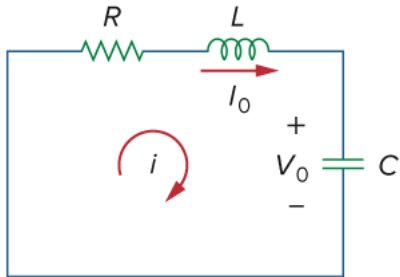
$$\alpha = \omega_0 \rightarrow C = 4L/R^2$$


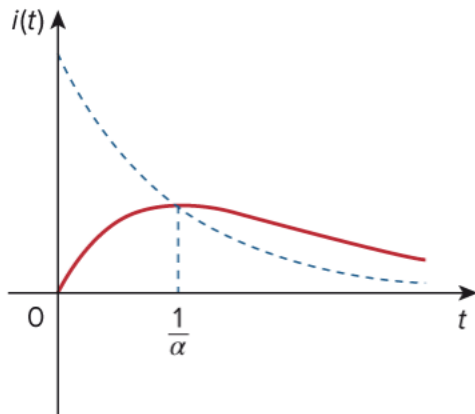
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$



$$\frac{df}{dt} + \alpha f = 0$$

$$-\frac{di}{dt} + \alpha i = \boxed{A_1 e^{-\alpha t}} \rightarrow e^{\alpha t} \left(\frac{di}{dt} + \alpha i \right) = A_1$$

$$\frac{d}{dt}(\underbrace{e^{\alpha t} i}_g) = A_1$$


$$e^{\alpha t} i = A_1 t + A_2$$

$$i = (A_1 t + A_2) e^{-\alpha t}$$

$$\begin{aligned} & \downarrow \\ & \frac{d}{dt}(e^{\alpha t} i) = A_1 \\ & \frac{d}{dt}(e^{\alpha t} i) = A_1 \end{aligned}$$

Critically damped case

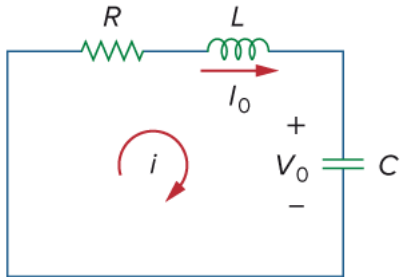
$$\alpha = \omega_0 \rightarrow C = 4L/R^2$$



$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$
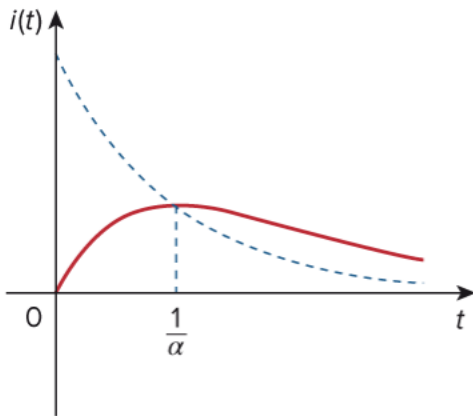
$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$




$$i(t) = (A_2 + A_1 t)e^{-\alpha t}$$

Under damped Case

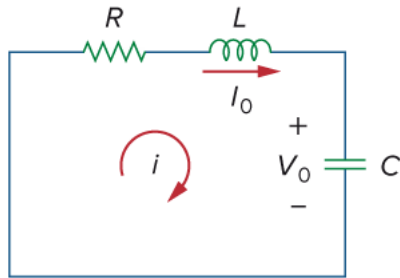
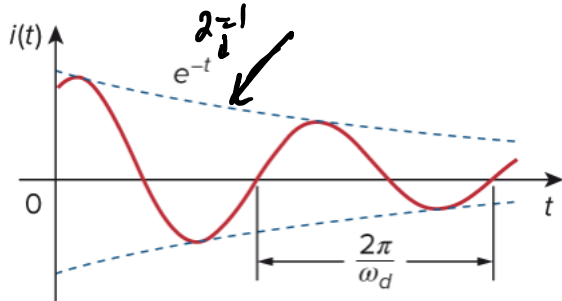
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$



$$\alpha < \omega_0 \Rightarrow$$

$$C < 4L/R^2$$

$$i(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$= e^{-\alpha t} (A_1 e^{+j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$e^{j\omega_0 t} = \cos \omega_0 t + j \sin \omega_0 t$$


$$i(t) = e^{-\alpha t} \left[A_1 (\cos \omega_0 t + j \sin \omega_0 t) + A_2 (\cos \omega_0 t - j \sin \omega_0 t) \right]$$

$$= e^{-\alpha t} \left[\underbrace{(A_1 + A_2)}_{B_1} \cos \omega_0 t + j \underbrace{(A_1 - A_2)}_{B_2} \sin \omega_0 t \right]$$


$$A_1 = A_2^*$$

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

Under damped Case

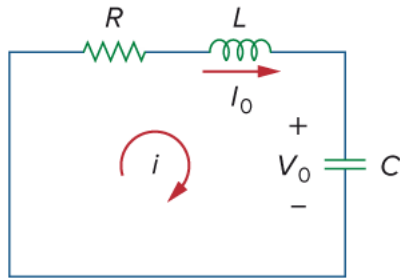
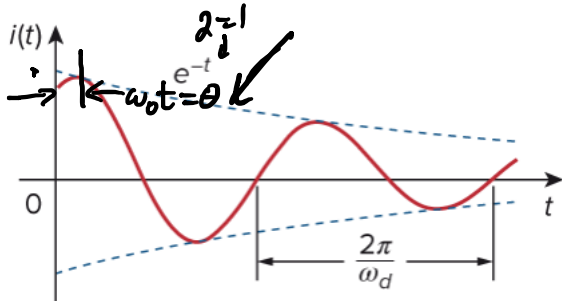
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$



$$\alpha < \omega_0 \Rightarrow$$

$$C < 4L/R^2$$

$$i(t) = A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t}$$

$$= e^{-\alpha t} (A_1 e^{+j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$i(t) = e^{-\lambda t} (A_1 e^{j\omega_0 t} + A_2 e^{-j\omega_0 t})$$

$\uparrow$ real
 $\uparrow$ real


$$A_1 = A e^{j\theta}$$

$$A_2 = A e^{-j\theta}$$

$$= e^{-\lambda t} (A e^{j\theta} e^{j\omega_0 t} + A e^{-j\theta} e^{-j\omega_0 t})$$


$$= e^{-\lambda t} (A e^{j(\omega_0 t + \theta)} + A e^{-j(\omega_0 t + \theta)})$$
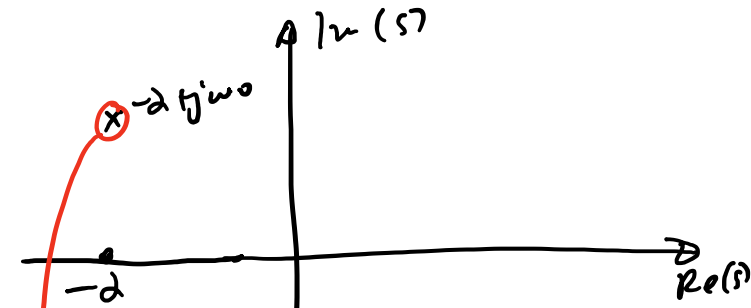
$$i(t) = e^{-\lambda t} A \cos(\omega_0 t + \theta)$$



Summary
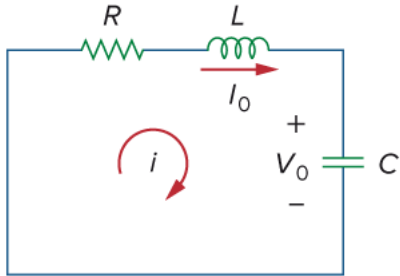
$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$




$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$


Overdamped

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

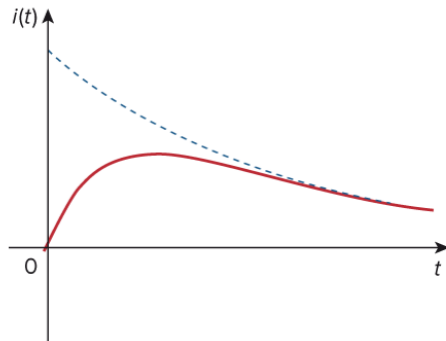


Critically damped

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

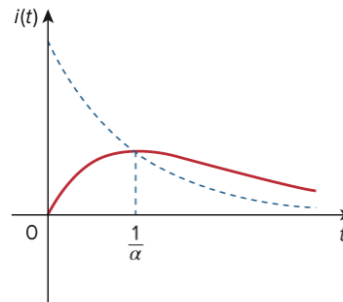



Underdamped

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

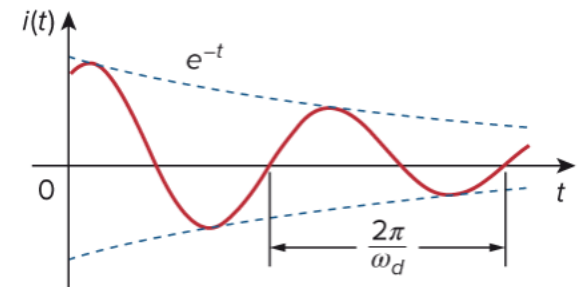

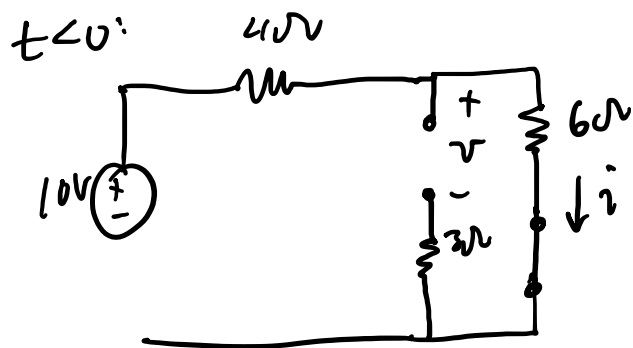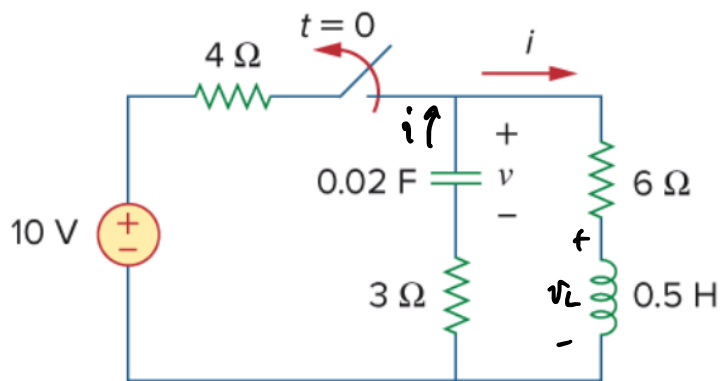Example 8.4




Find $i(t)$ in the circuit of Fig. 8.10. Assume that the circuit has reached steady state at $t = 0^-$.



$$i(0^+) = i = 1A$$

$$v(0^+) = v = 6V$$

$t > 0$:

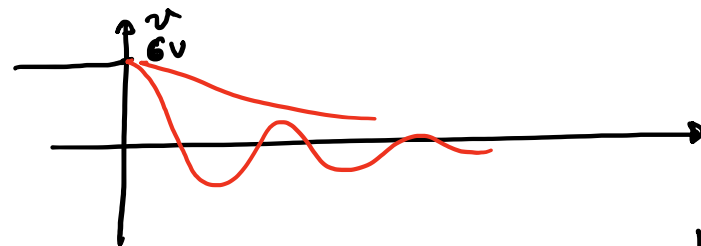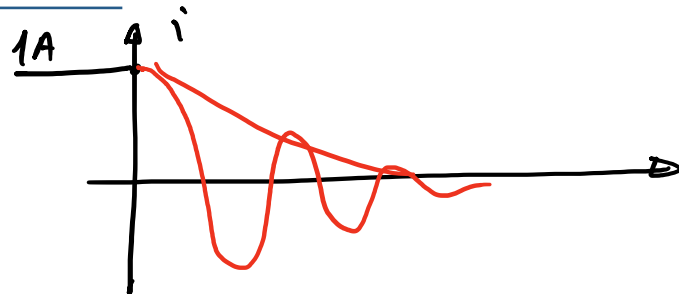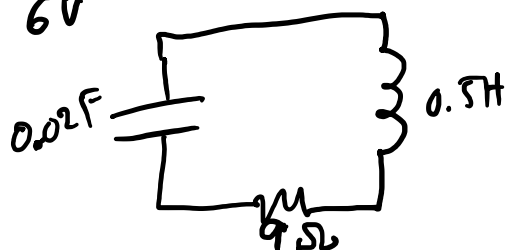

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \rightarrow \alpha = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$i'' + \frac{R}{L}i' + \frac{1}{LC}i = 0$$

$$= \frac{9\Omega}{2 \times 0.5H} = 9 \text{ Np/s}$$

$$= \frac{1}{\sqrt{0.01}} = 10 \text{ rad/s}$$

$$i(t) = e^{-\alpha t} [B_1 \cos(\omega_0 t) + B_2 \sin(\omega_0 t)]$$

$$i(0) = 1A = B_1$$

$$v_L(0) = v(0) - i(0)6 - i(0)3 = v(0) - 9i(0)$$

$$= 6V - 9 \cdot 1A = -3V$$

$$v_L(t) = L \frac{di}{dt} = L \left[2e^{-\alpha t} (B_1 \cos \omega_0 t + B_2 \sin \omega_0 t) + e^{-\alpha t} (-B_1 \omega_0 \sin \omega_0 t + B_2 \omega_0 \cos \omega_0 t) \right]$$

$$v_L(0) = L [-\alpha (B_1) + (B_2 \omega_0)]$$


$$= L (B_2 \omega_0 - B_1 \alpha) = 3V$$

$$\alpha < \omega_0$$

underdamped

Practice Problem 8.4

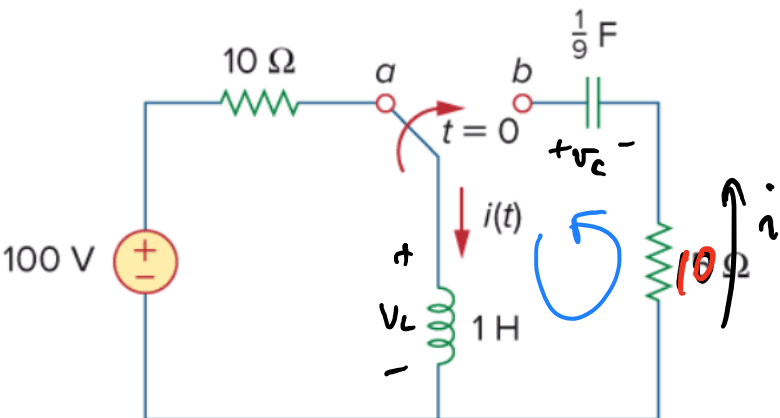The circuit in Fig. 8.12 has reached steady state at $t = 0^-$. If the make-before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.



$$i(0^-) = 10A$$

$$i(0^+) = 10A$$

$$v_c(0^-) = 0 = v_c(0^+)$$

$$\alpha = \frac{R}{2L} = \frac{10}{2} = 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1/9}} = 3 \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{5^2 - 3^2}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i(0) = 10A$$

$$= A_1 + A_2$$

$$v_L = L \frac{di}{dt} = L[(-9)A_1 e^{-9t} - A_2 e^{-t}]$$

At $t=0^+$:

$$v_L(0^+) + i(0^+)10 + (-v_c) = 0$$

$$v_L(0^+) = -i(0^+)10 + v_c(0^+)$$

$$= -100 + 0$$

$\rightarrow$ At $t=0^+ \Rightarrow -100$

$$1H(-9A_1 - (A_1 + A_2)) = -100$$

$$-8A_1 = -90$$

$$A_1 = \frac{90}{8} \sim 11$$

$$A_2 = 10 - 90/8 \sim -1$$





$$i(t) = 11e^{-9t} - 1e^{-t}$$

↓

$$e^{-t/(1/9)}_s \quad e^{-t/(1)}_s$$
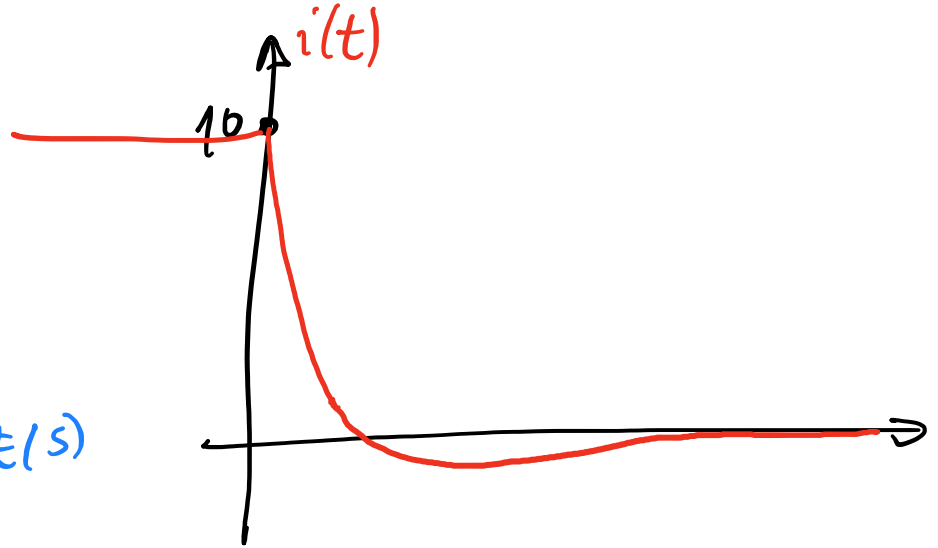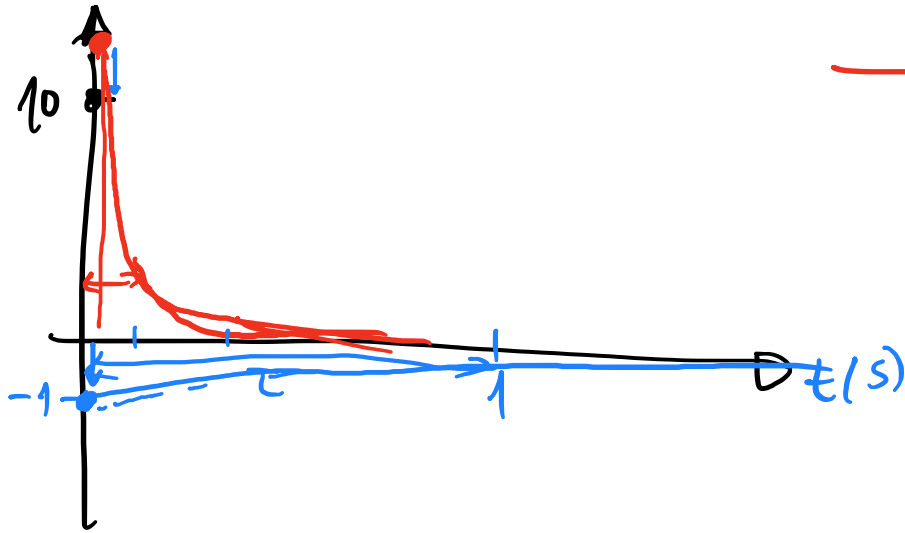
$$\tau_{1,2} = \frac{1}{9}, 1 \quad e^{-t/\tau}$$



Step Response


$$v(0^-) = 0, i(0^-) = 0$$

$$\text{At } t=0^+: \underline{v(0^+) = 0}, \underline{i(0^+) = 0}$$

$$\text{KVL} \rightarrow L \frac{di}{dt} + Ri + v = V_s$$

$$\frac{di}{dt} = \frac{V_s}{L}$$

$$i = C \frac{dv}{dt}$$




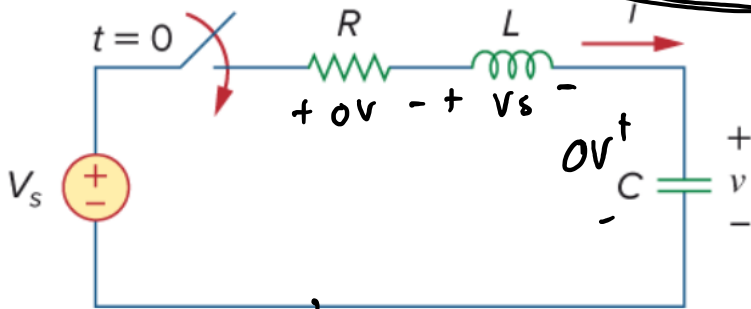


$$LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v = V_s$$

$$\boxed{\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}}$$


$$s^2 + \frac{R}{L}s + \frac{1}{LC} = \frac{V_s}{LC}$$

$$\boxed{V(\infty) = V_s}$$

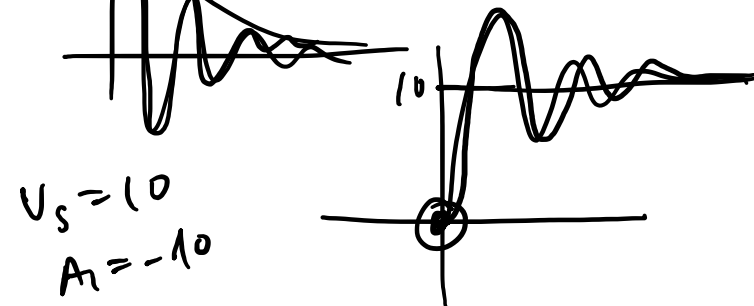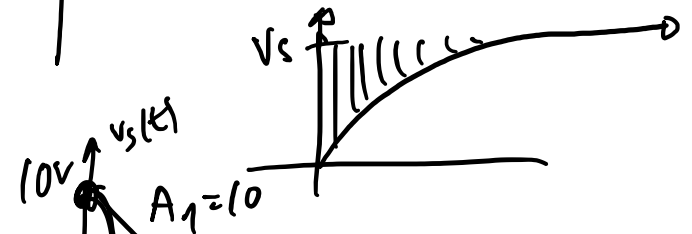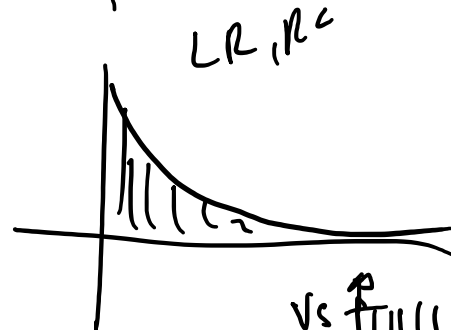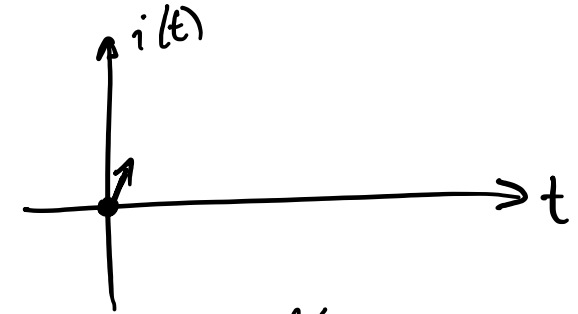

Step Response

$$L \frac{di}{dt} + Ri + v = V_s$$

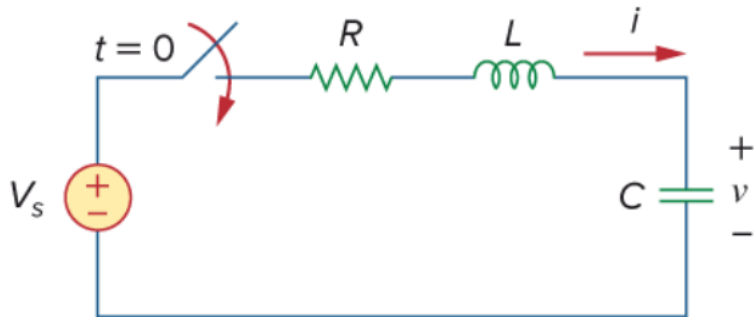

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

$$v(t) = v_t(t) + v_{ss}(t)$$

$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v_t(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$


$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

Example 8.7

For the circuit in Fig. 8.19, find $v(t)$ and $i(t)$ for $t > 0$. Consider these cases:
 $R = 5\ \Omega$, $R = 4\ \Omega$, and $R = 1\ \Omega$.

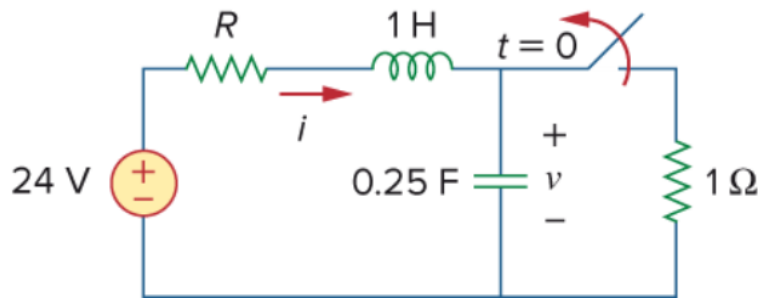

Example 8.11

In the op amp circuit of **Fig. 8.33**, find $v_o(t)$ for $t > 0$ when $v_s = 10u(t)$ mV. Let $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$, and $C_2 = 100 \text{ }\mu\text{F}$.

