

Practice Problem 8.7

Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $i(t)$ for $t > 0$.


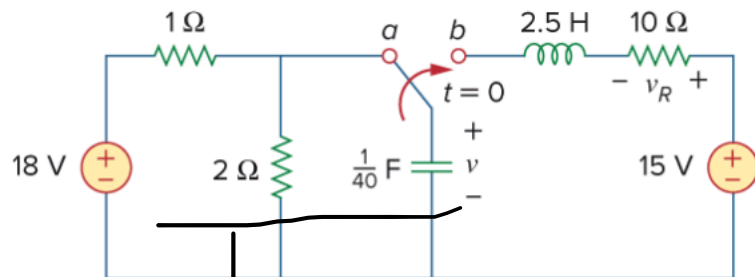


Figure 8.21 For Practice Prob. 8.7.

Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$ V, $3.464e^{-2t} \sin 3.464t$ V.

①


$v(0^-), i(0^-)$.

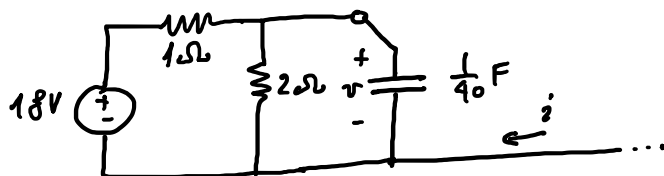

$$v(0^-) = \frac{2}{3} 18V = 12V$$

$$i(0^-) = 0$$

② Find response of ckt.

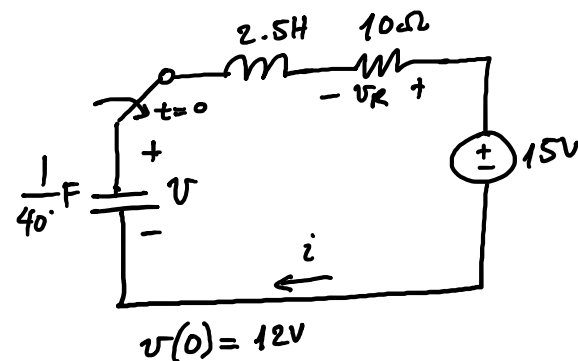

KVL: $v - L \frac{di}{dt} + v_R - 15V = 0$

$$v - L \frac{di}{dt} - iR - 15V = 0$$

$$-i = C \frac{dv}{dt}$$

We can replace either i or v . In class we replaced v with i , and the resulting math was complicated. Here, we replace i with v :

$$v + L \frac{d}{dt} + RC \frac{d}{dt} v - 15V = 0$$

$$LCv'' + RCv' + v = 15V$$

$$v'' + \frac{R}{L}v' + \frac{1}{LC}v = \frac{15V}{LC}$$

Has solutions

$$v(t) = v_{\text{transient}}(t) + v_{\text{steady-state}}(t)$$

$$= v_t(t) + 15V$$

Practice Problem 8.7

Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $v_R(t)$ for $t > 0$.

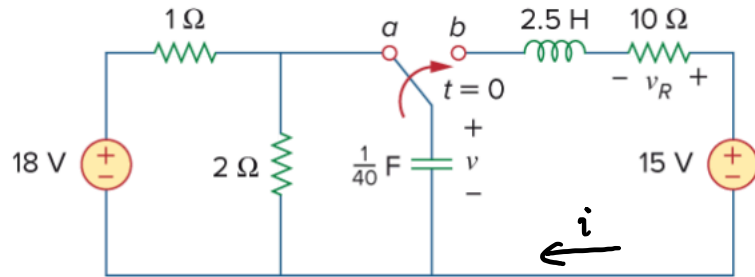


Figure 8.21 For Practice Prob. 8.7.

Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$ V, $3.464e^{-2t} \sin 3.464t$ V.

③ Now, $\alpha = \frac{R}{2L} = \frac{10\Omega}{2 \cdot 2.5H} = 2 \text{ Np/s}$, $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2.5 \cdot \frac{1}{40}}} = \sqrt{16} = 4 \text{ rad/s}$

$\alpha < \omega_0 \Rightarrow \text{underdamped.}$

Now, this means a solution with roots:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2 \pm j\sqrt{\omega_0^2 - \alpha^2} \equiv -2 \pm j\omega_d$$

Note that this has a frequency $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

∴ The solution is

$$\begin{aligned} v_t(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t} \end{aligned}$$

$$v_t(t) = e^{-\alpha t} \left[A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t) \right]$$

$$= e^{-\alpha t} \left[B_1 \cos \omega_d t + B_2 \sin \omega_d t \right]$$

where

$$\omega_d \equiv \sqrt{\omega_0^2 - \alpha^2}$$

$$= \sqrt{4^2 - 2^2}$$

$$\omega_d = \sqrt{12} \approx 3.464 \text{ rad/s}$$

Practice Problem 8.7

Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $v_R(t)$ for $t > 0$.

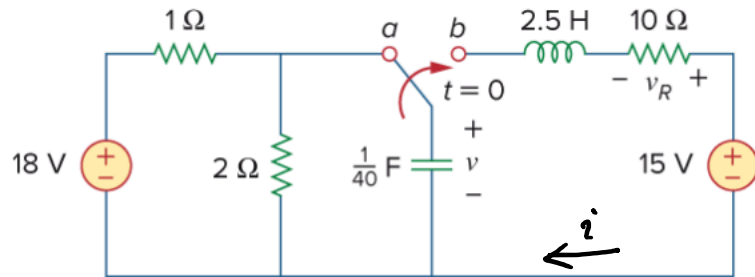


Figure 8.21 For Practice Prob. 8.7.

Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$ V, $3.464e^{-2t} \sin 3.464t$ V.

④ Now, match initial conditions at $t=0$ ($v(0) = 12$ V, $i(0) = 0$).

$$v_t(t) = e^{-2t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\lambda = 2, \quad \omega_d = \sqrt{12}$$

$$v(t) = v_t(t) + v_{ss} = v_t(t) + 15$$

THEN: $v(0) = B_1 + 15 \text{ V} = 12 \text{ V} \rightarrow B_1 = -3 \text{ V}$

$$-i = C \frac{dv}{dt} = C \left[-2e^{-2t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) + e^{-2t} (-B_1 \omega_d \sin \omega_d t + B_2 \omega_d \cos \omega_d t) \right]$$

$$i(0) = 0 = -C [-2B_1 + B_2 \omega_d]$$

$$\therefore B_2 = \frac{2B_1}{\omega_d} = \frac{2 \times -3}{\sqrt{12}} = \frac{-6}{\sqrt{12}} = \frac{-3}{\sqrt{3}} = -\sqrt{3} \approx -1.732$$

⑤ FINAL SOLUTION:

$$v(t) = v_t(t) + v_{ss}$$

$$= v_t(t) + 15 \text{ V}$$

$$= e^{-2t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) + 15 \text{ V}$$

$$= e^{-2t} (-3 \cos \omega_d t - 1.732 \sin \omega_d t) + 15 \text{ V}$$

$$v(t) = 15 - e^{-2t} (3 \cos \omega_d t + 1.732 \sin \omega_d t)$$

(Same as answer key)

$$\omega_d = \sqrt{12} = 3.464$$

Now for v_R :

$$v_R(t) = -iR, \quad -i = C \frac{dv}{dt}$$

$$\therefore v_R(t) = RCe^{-2t} \left[-2(B_1 \cos \omega_d t + B_2 \sin \omega_d t) + B_2 \omega_d \cos \omega_d t - B_1 \omega_d \sin \omega_d t \right]$$

$$= -RCe^{-2t} (2B_2 + \omega_d B_1) \sin \omega_d t$$


$$\begin{aligned} & RC(2B_2 + \omega_d B_1) \\ &= 10 \frac{1}{40} [2(-\sqrt{3}) + \sqrt{12}(-3)] \\ &= \frac{1}{4} [2\sqrt{3} + 3 \cdot 2\sqrt{3}] \\ &= -2\sqrt{3} \\ &= -3.464 \end{aligned}$$

$$\therefore v_R(t) = 3.464 e^{-2t} \sin \omega_d t$$

DONE!

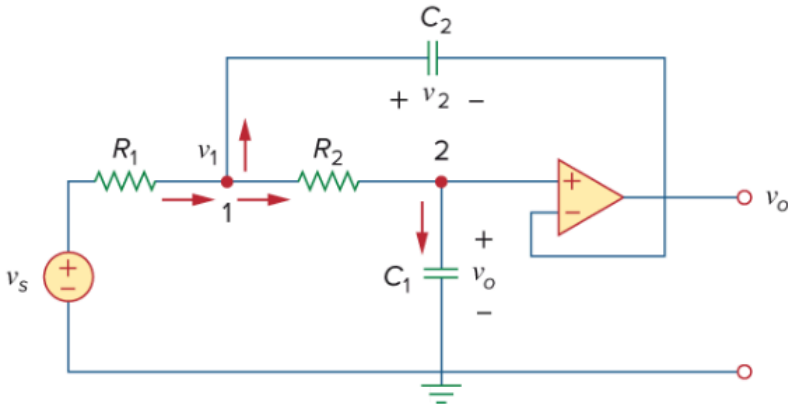Example 8.11

In the op amp circuit of **Fig. 8.33**, find $v_o(t)$ for $t > 0$ when $v_s = 10u(t)$ mV. Let $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$, and $C_2 = 100 \text{ }\mu\text{F}$.



Please study example 8.11 in Section 8.8 (6th edition of book).
pages 342-344.