

EK 307: Electric Circuits

Fall 2017

Lecture 20

Nov 21, 2017

Milos Popovic


Department of Electrical and Computer Engineering

Boston University

Administrivia

- Homework backlog cleared, hopefully all resolved
 - HW5,7,8 cleanup, back next Tues
- HW9 due next Tuesday
- Midterm #2: results
- Calibration: I will email out grade summary to date before Thanksgiving.


Midterm 2

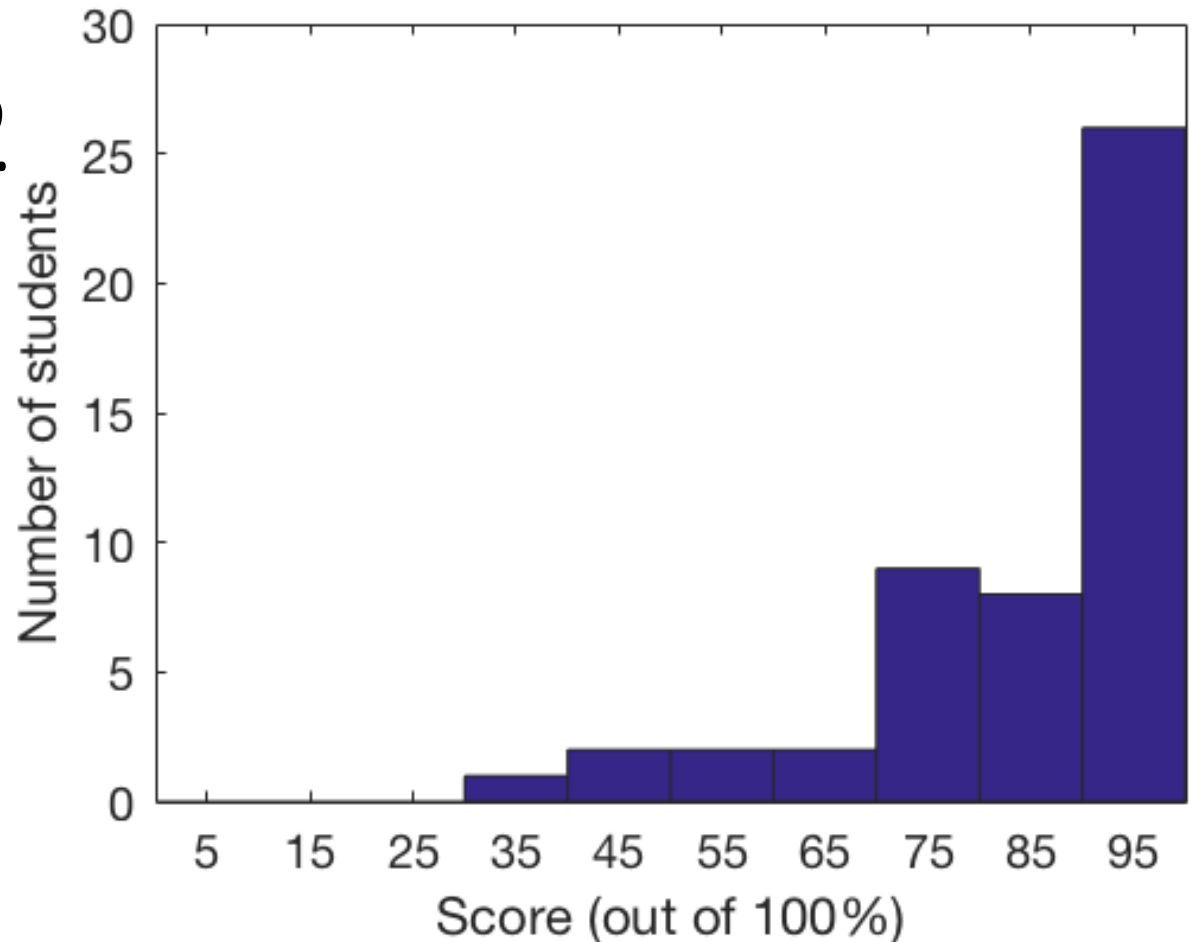

Midterm 2

Average: 85%
Standard deviation: 15%
Max score: 100%
Min score: 38% (3 of 50 students below 50%)

Midterm 2

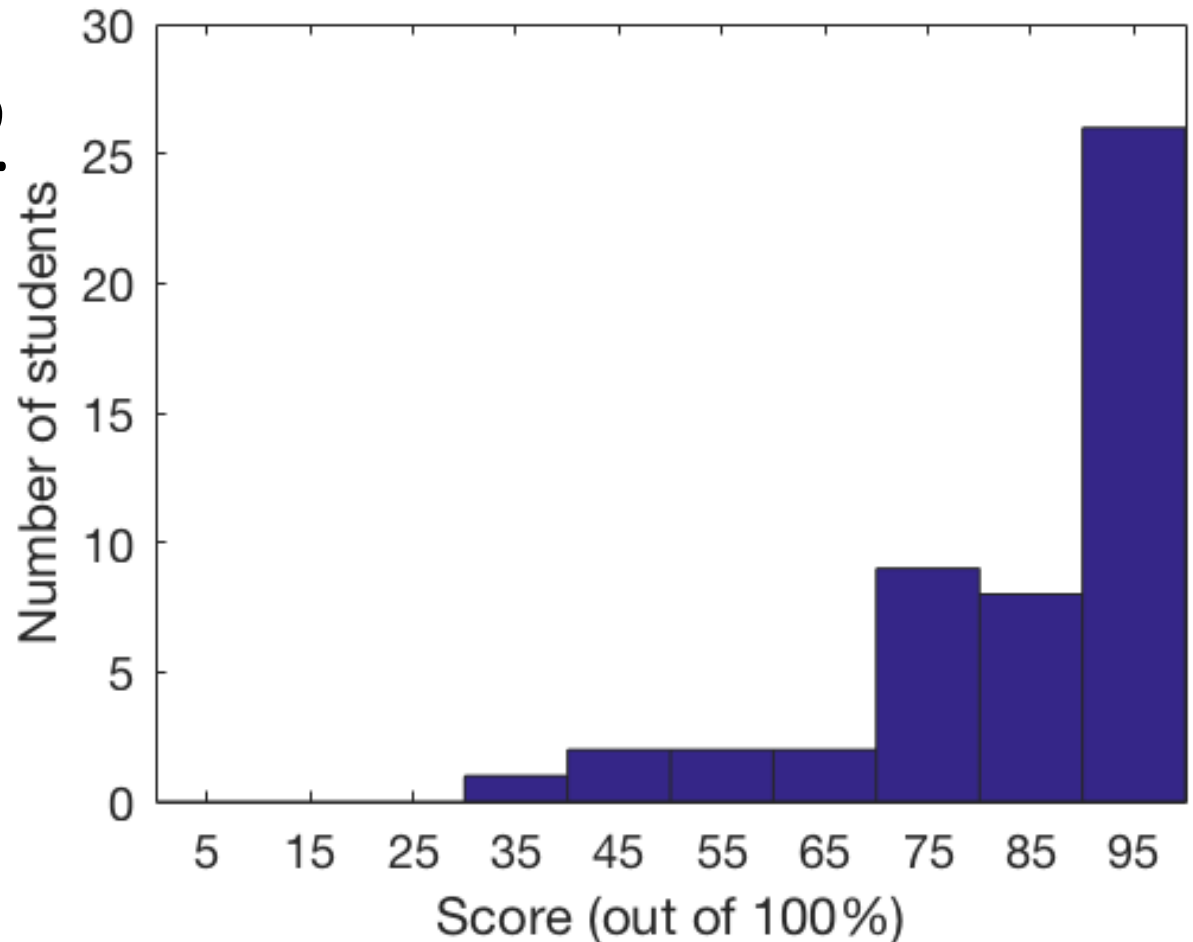

Midterm 2

Midterm 1

Average:

85% (B+)

72% (B-/C+)

Standard deviation:

15%

20%

Max score:

100%

98%


Min score:

38% (3 of 50 students below 50%)


26%

Midterm 2

Multiple Choice

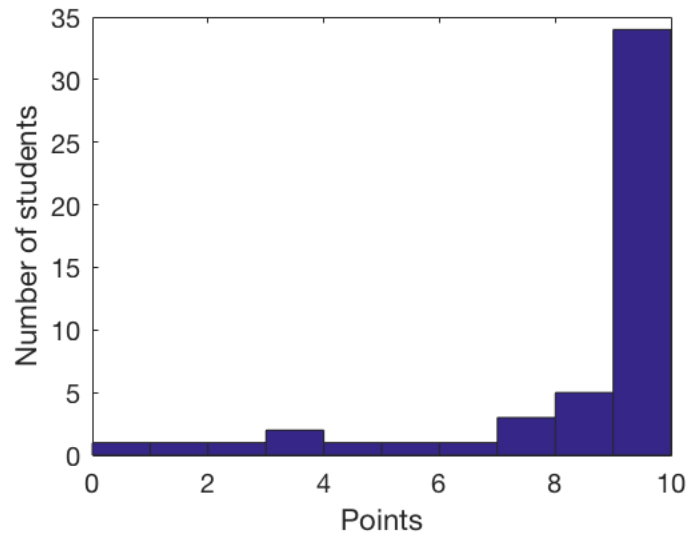


Problem 1

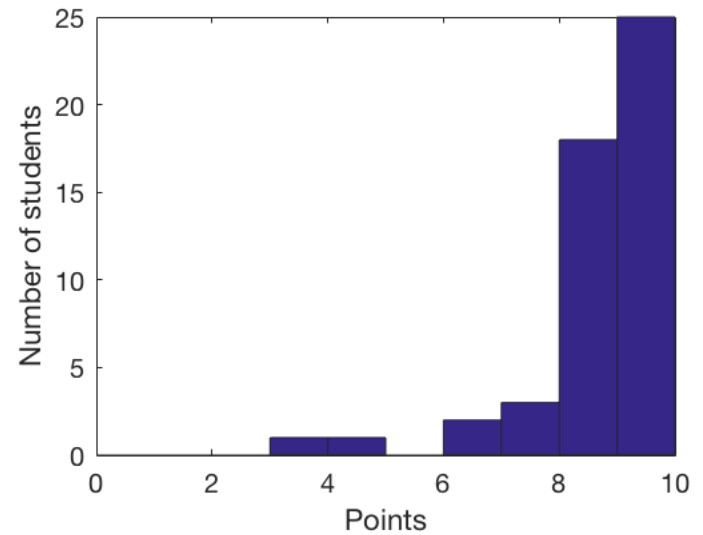


Midterm 2


Problem 2

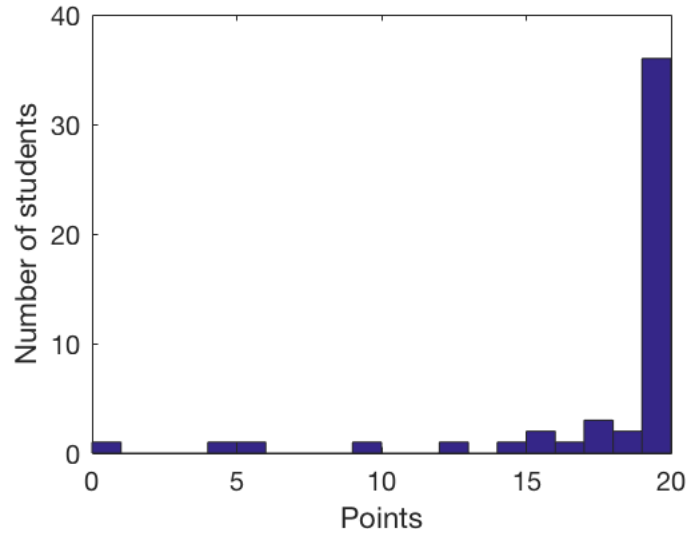


Problem 3

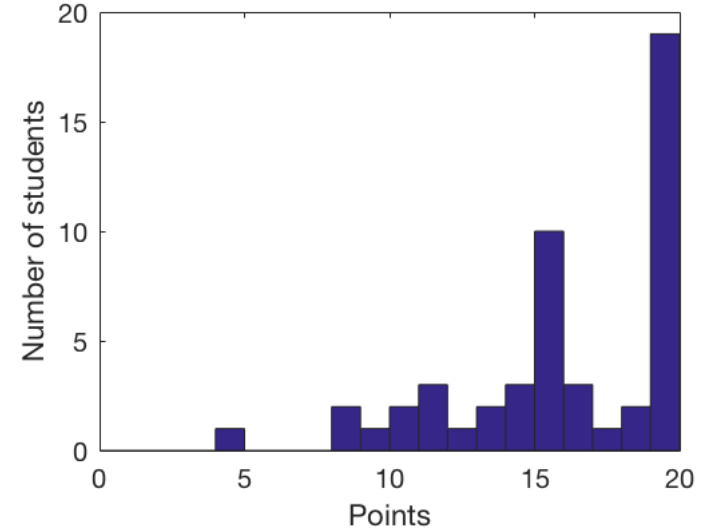

Problem 4

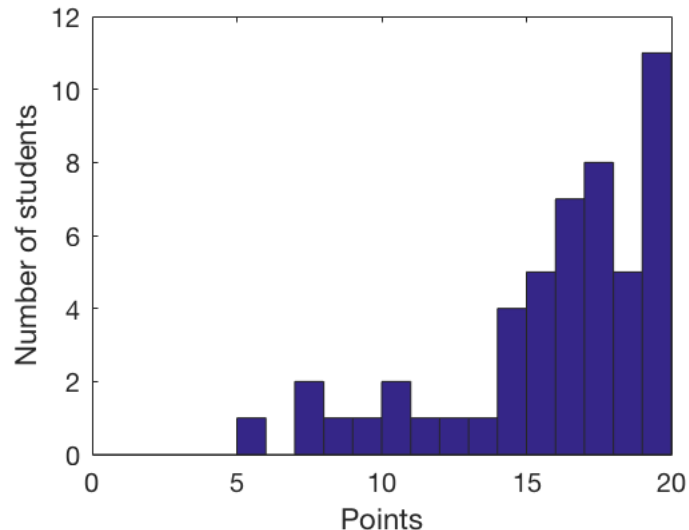


Problem 5

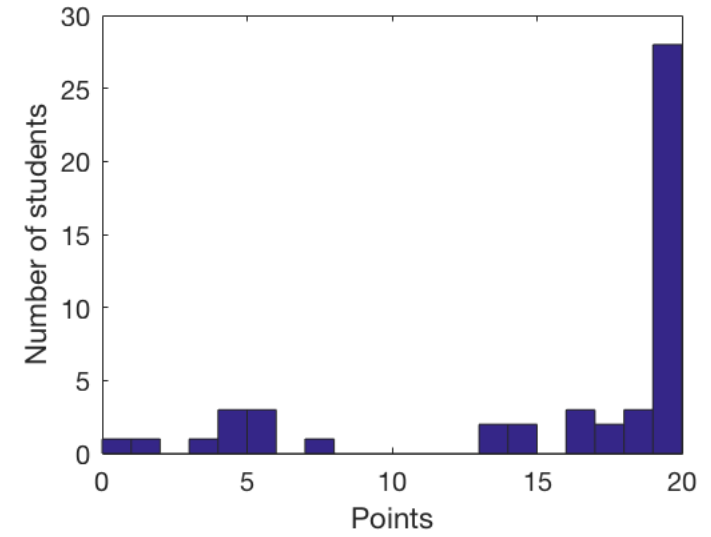

Last time (Lecture 19):

1. Second-order circuits & resonators

(Chapter 8)

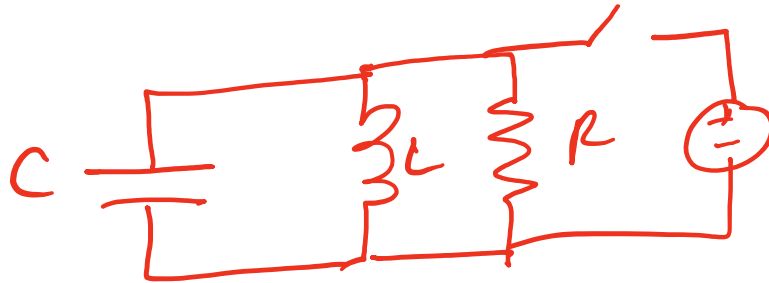


Lecture 20: Chapter 8 – 2nd order ccts

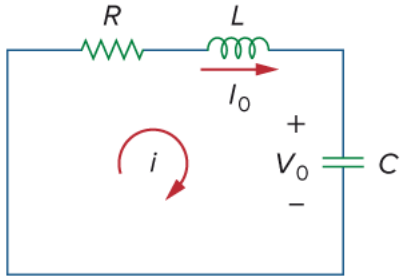1. Solving 2nd order ccts – Sec 8.5-8.8
2. Chapter 9 – Phasors & Sinusoidal Steady State

Summary

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$




$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$


Overdamped
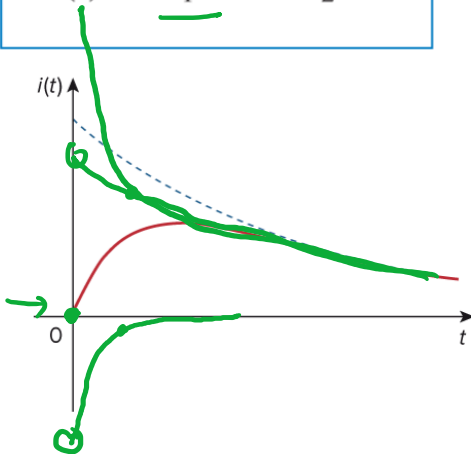
$$i(t) = \underbrace{A_1}_{-1} e^{s_1 t} + \underbrace{A_2}_{+1} e^{s_2 t}$$




Critically damped

$$i(t) = (A_2 + A_1 t) e^{-\alpha t}$$

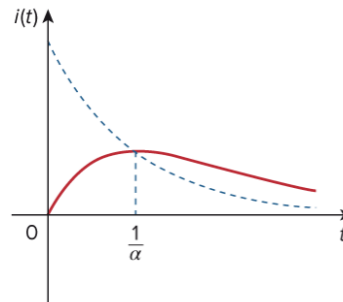




Underdamped

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

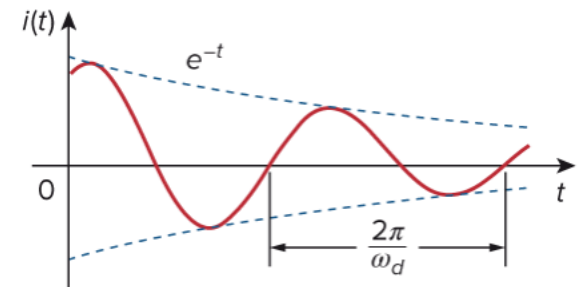

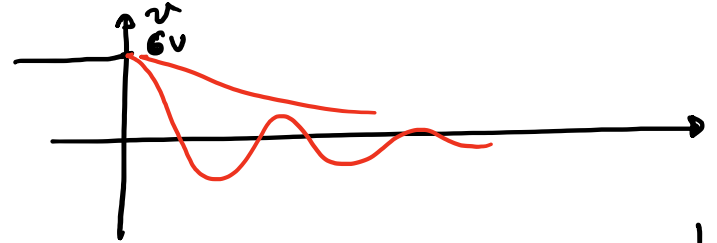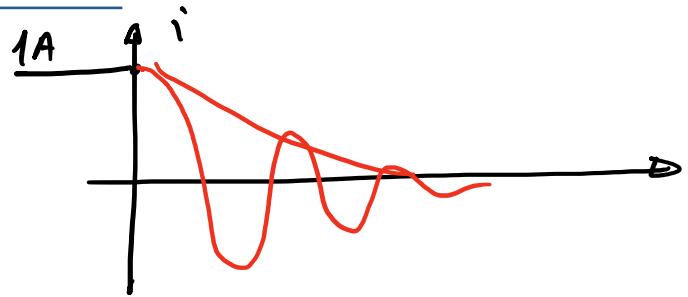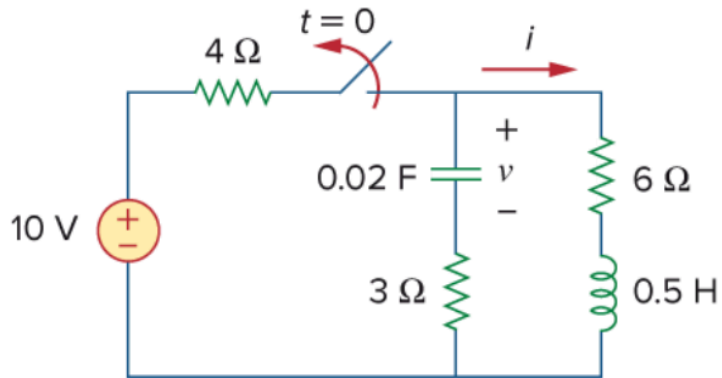Example 8.4

Find $i(t)$ in the circuit of Fig. 8.10. Assume that the circuit has reached steady state at $t = 0^-$.



$$Z_L, \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= \frac{9\Omega}{2 \times 0.5H} = \frac{1}{\sqrt{0.01}}$$

$$= 9 \text{ Np/s} = 10 \text{ rad/s}$$


$$\boxed{2 < \omega_0}$$

underdamped

$$i(0^+) = i = 1A$$

$$v(0^+) = v = 6V$$

$t > 0$:

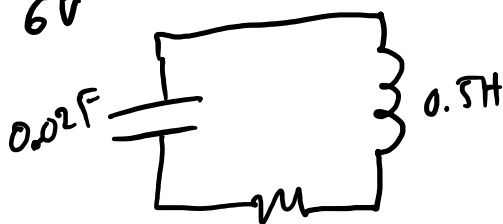

$$v_L(t) = L \frac{di}{dt}$$


$$= L(\beta_2 \omega_0 - \beta_1 2) = 3V$$

$$\cos \omega_0 t + \beta_2 \sin \omega_0 t$$

$$\left[\beta_1 \omega_0 \sin \omega_0 t + \beta_2 \omega_0 \cos \omega_0 t \right]$$

Practice Problem 8.4

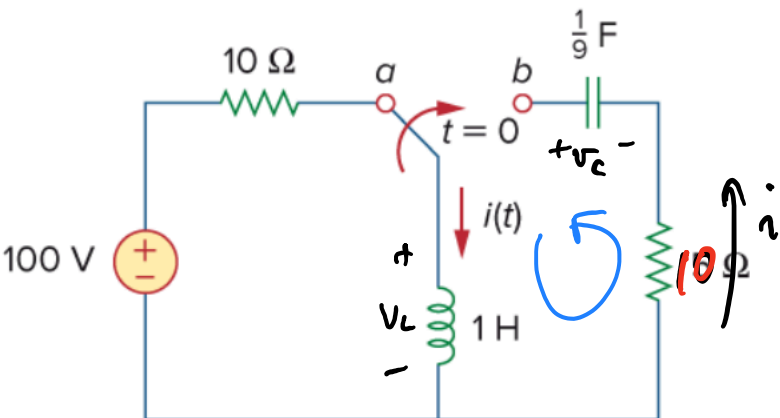The circuit in Fig. 8.12 has reached steady state at $t = 0^-$. If the make-before-break switch moves to position b at $t = 0$, calculate $i(t)$ for $t > 0$.



$$i(0^-) = 10A$$

$$i(0^+) = 10A$$

$$v_c(0^-) = 0 = v_c(0^+)$$

$$\alpha = \frac{R}{2L} = \frac{10}{2} = 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \cdot \frac{1}{9}}} = 3 \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{5^2 - 3^2}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i(0) = 10A$$

$$= A_1 + A_2$$

$$v_L = L \frac{di}{dt} = L[(-9)A_1 e^{-9t} - A_2 e^{-t}]$$

At $t=0^+$:

$$v_L(0^+) + i(0^+)10 + (-v_c) = 0$$

$$v_L(0^+) = -i(0^+)10 + v_c(0^+)$$

$$= -100 + 0$$

$\rightarrow$ At $t=0^+ \Rightarrow -100$

$$1H(-9A_1 - (A_1 + A_2)) = -100$$

$$-8A_1 = -90$$

$$A_1 = \frac{90}{8} \sim 11$$

$$A_2 = 10 - 90/8 \sim -1$$





$$i(t) = 11e^{-9t} - 1e^{-t}$$

$$\downarrow$$


$$e^{-t/\tau_1} \quad e^{-t/\tau_2}$$

$$\tau_{1,2} = \frac{1}{9}, 1 \quad e^{-t/\tau}$$

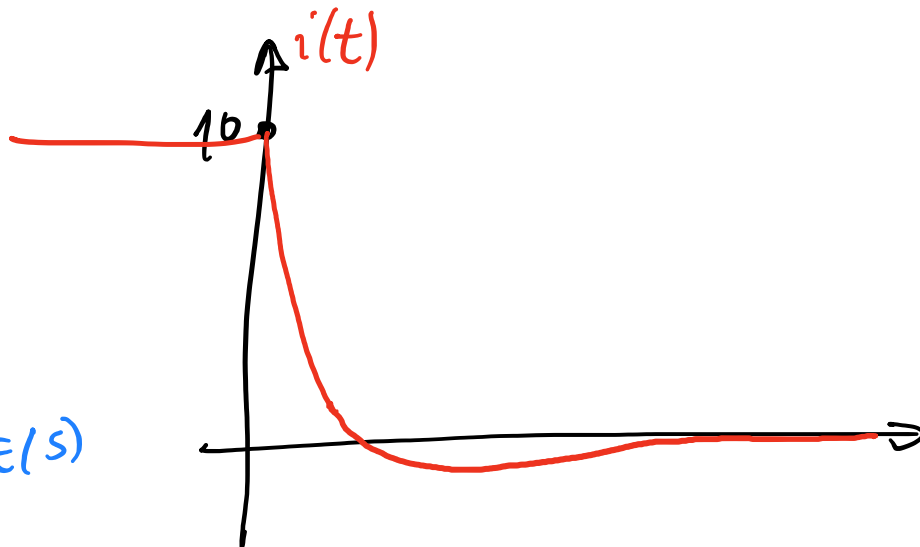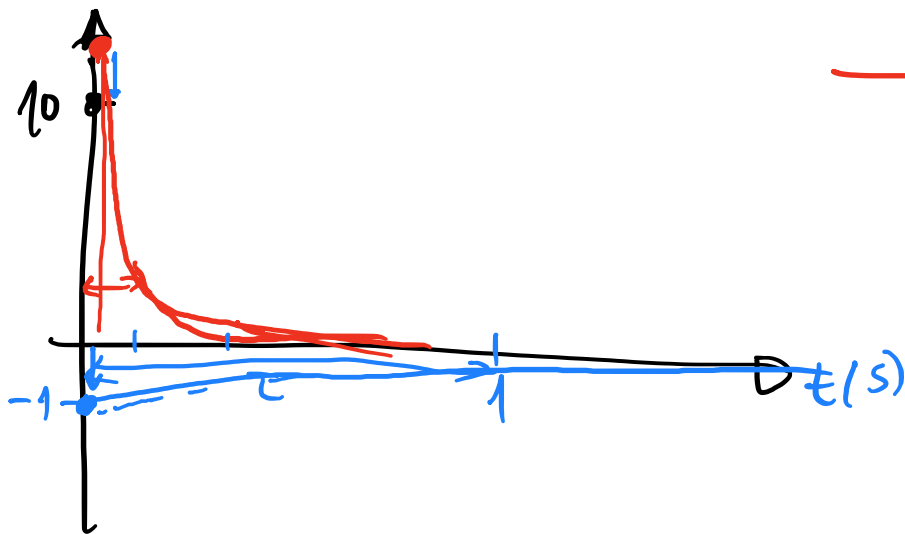


Example 8.7

For the circuit in Fig. 8.19, find $v(t)$ and $i(t)$ for $t > 0$. Consider these cases:
 $R = 5\ \Omega$, $R = 4\ \Omega$, and $R = 1\ \Omega$.

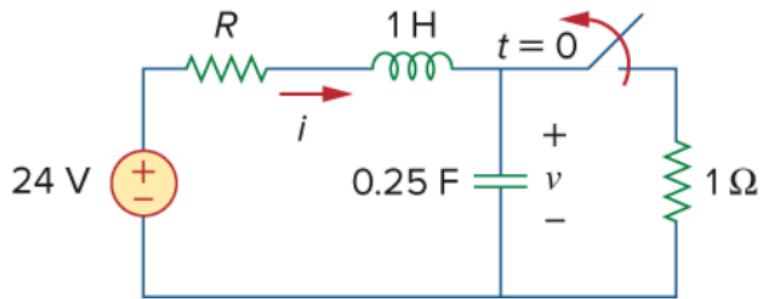


Example 8.6

Find $v(t)$ for $t > 0$ in the RLC circuit of **Fig. 8.15**.

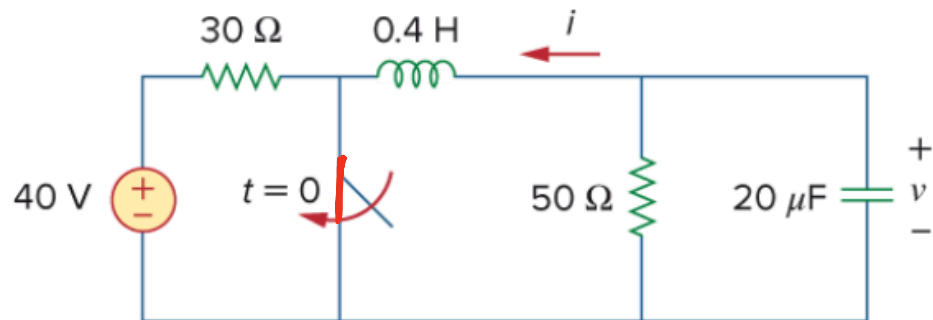

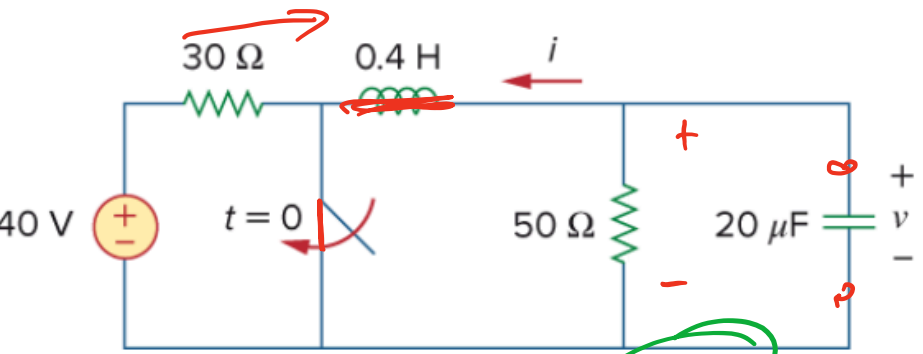
Example 8.6

Find $v(t)$ for $t > 0$ in the RLC circuit of Fig. 8.15.



At $t=0^-$, $v = \frac{50}{80} \cdot 40 = 25V$.

$i(0^-) = i_- = -0.5A \equiv i(0^+)$

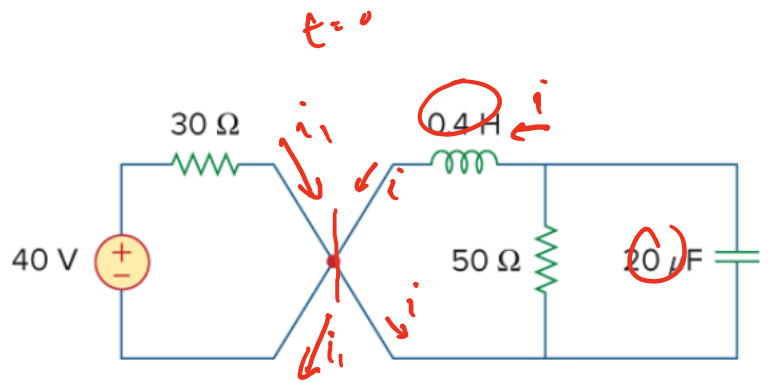

$\lambda = \frac{R}{2L}, \omega_0 = \frac{1}{\sqrt{LC}}$
 $= \frac{50\Omega}{2 \cdot 0.4H}$

$2 \leq \omega_0?$

$i(t) = -0.5A, t < 0$

For $t \geq 0$: $i(t) = e^{-\lambda t} (B_1 \cos \omega_0 t + B_2 \sin \omega_0 t)$

$\frac{di}{dt} = -\lambda e^{-\lambda t} (B_1 \cos \omega_0 t + B_2 \sin \omega_0 t) + e^{-\lambda t} (-B_1 \omega_0 \sin \omega_0 t + B_2 \omega_0 \cos \omega_0 t)$

At $t=0$: $\frac{di}{dt} = -\lambda B_1 + B_2$

$i(0^+) = -0.5A = B_1$

$v = L \frac{di}{dt}$

$v(0^+) = 25$

Step response of RLC circuits

Step Response


$$v(0^-) = 0, i(0^-) = 0$$

$$\text{At } t=0^+: \underline{v(0^+) = 0}, \underline{i(0^+) = 0}$$

$$\text{KVL} \rightarrow L \frac{di}{dt} + Ri + v = V_s$$

$$\frac{di}{dt} = \frac{V_s}{L}$$

$$i = C \frac{dv}{dt}$$



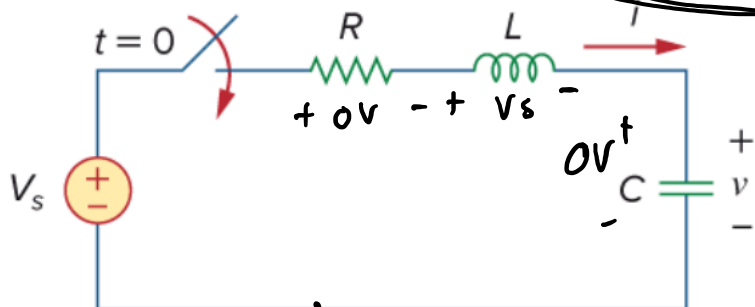


$$LC \frac{d^2v}{dt^2} + RC \frac{dv}{dt} + v = V_s$$


$$\boxed{\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = \frac{V_s}{LC}$$

$$\boxed{V(\infty) = V_s}$$

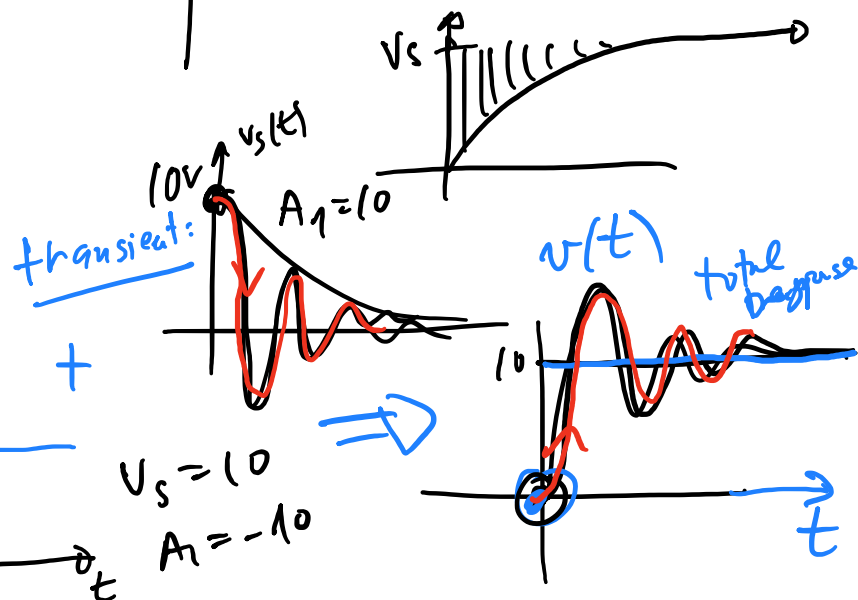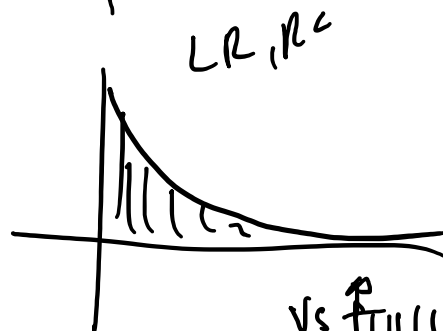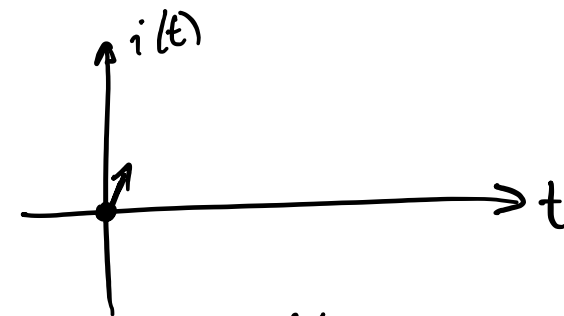


Step Response

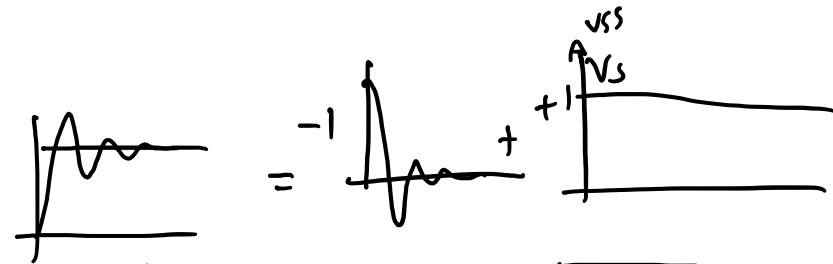

$$v(t) = v_t(t) + \boxed{v_{ss}(t)}$$

$$L \frac{di}{dt} + Ri + v = V_s$$

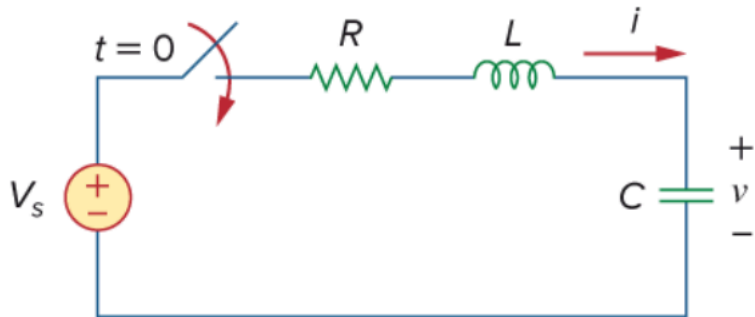

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{v}{LC} = \frac{V_s}{LC}$$

$$v_t(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v_t(t) = (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v_t(t) = (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$




$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{Overdamped})$$

$$v(t) = V_s + (A_1 + A_2 t) e^{-\alpha t} \quad (\text{Critically damped})$$

$$v(t) = V_s + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-\alpha t} \quad (\text{Underdamped})$$

Practice Problem 8.7

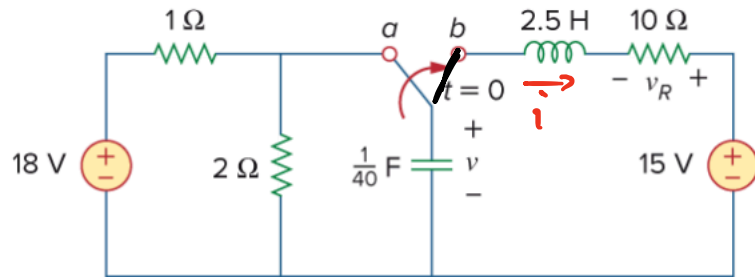Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $i(t)$ for $t > 0$.



$$\rightarrow v(0^-) = 12V = v(0^+)$$


$$i(0^-) = 0 = i(0^+)$$

$$v(\infty) = 15V$$

$$i(\infty) = 0$$

Figure 8.21 For Practice Prob. 8.7.

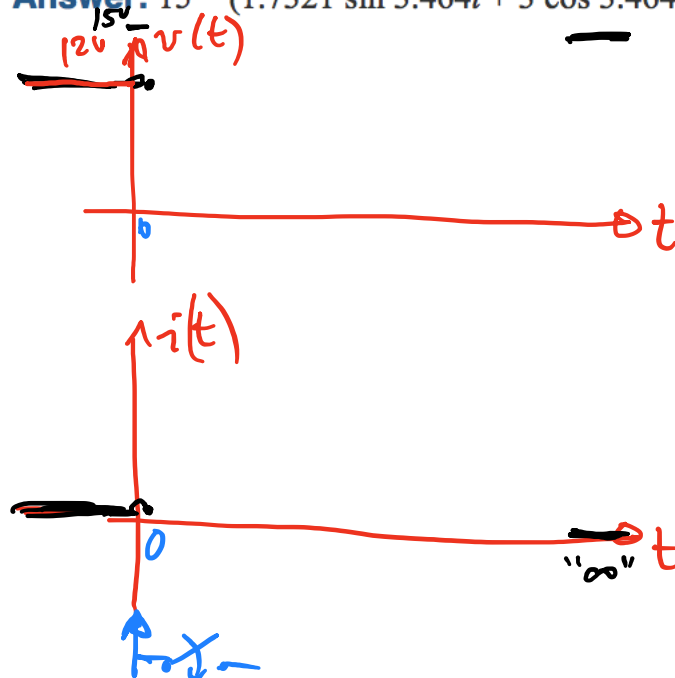
Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$ V, $3.464e^{-2t} \sin 3.464t$ V.



$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$L \frac{di}{dt} + iR + \frac{1}{C} \int i dt' = 15$$

$$v(t) e^{-2t} \cos \omega_0 t$$

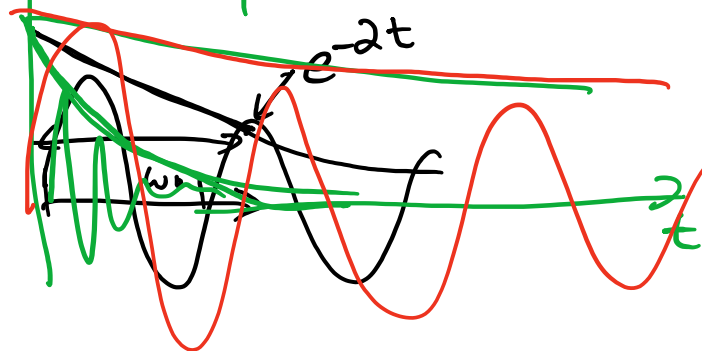

$$\alpha = \frac{R}{2L} = \frac{10}{2 \cdot 2.5} = 2$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{40} \cdot 2.5}}$$

$$= \sqrt{\frac{40}{2.5}}$$

$$\omega_0 = 4$$

Practice Problem 8.7

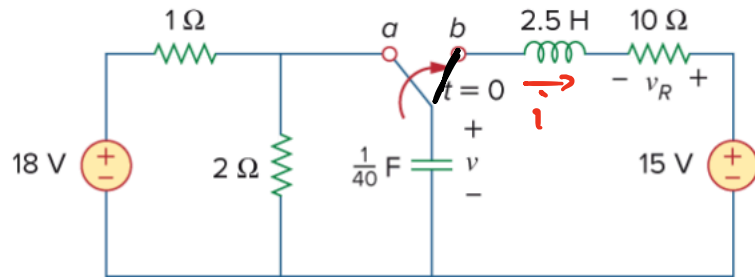Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $i(t)$ for $t > 0$.



$$\rightarrow v(0^-) = 12V = v(0^+)$$


$$i(0^-) = 0 = i(0^+)$$

$$v(\infty) = 15V$$

$$i(\infty) = 0$$

Figure 8.21 For Practice Prob. 8.7.

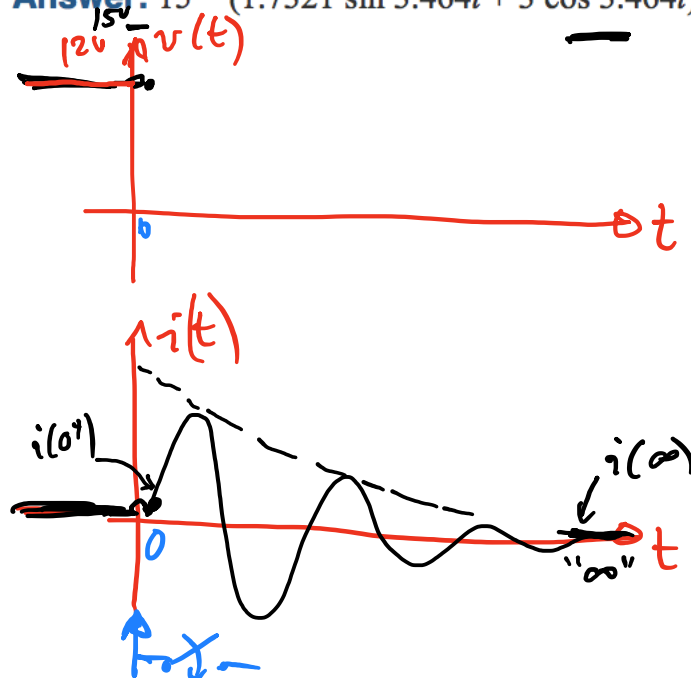Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t} \text{ V}, 3.464e^{-2t} \sin 3.464t \text{ V}.$



$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$L \frac{di}{dt} + iR +$$

$$i(t) = e^{-\lambda t} \left(B_1 \cos \omega_0 t + B_2 \sin \omega_0 t \right)$$

$$i(t) = e^{-\lambda t} B_2 \sin \omega_0 t$$

$$= e^{-\lambda t} B_2 \frac{e^{j\omega_0 t} - e^{-j\omega_0 t}}{2j}$$

$$= \frac{B_2}{2j} e^{(-\lambda + j\omega_0)t} - \frac{B_2}{2j} e^{(-\lambda - j\omega_0)t}$$

$$i = -C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_0^t i dt' = \frac{1}{C} \frac{B_2}{2j} \left[\frac{e^{(-\lambda + j\omega_0)t'}}{-\lambda + j\omega_0} - \frac{e^{(-\lambda - j\omega_0)t'}}{-\lambda - j\omega_0} \right]_0^t$$

$$2 \frac{1}{2L} = \frac{10}{2 \cdot 2.5}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{40} \cdot 2.5}} = \frac{1}{\sqrt{0.0625}} = \frac{1}{0.25} = 4$$

Practice Problem 8.7

Having been in position *a* for a long time, the switch in Fig. 8.21 is moved to position *b* at $t = 0$. Find $v(t)$ and $i(t)$ for $t > 0$.


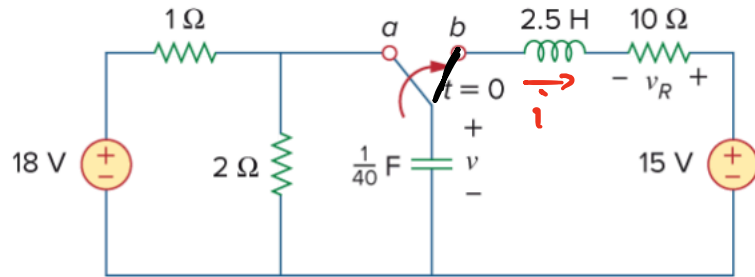


Figure 8.21 For Practice Prob. 8.7.

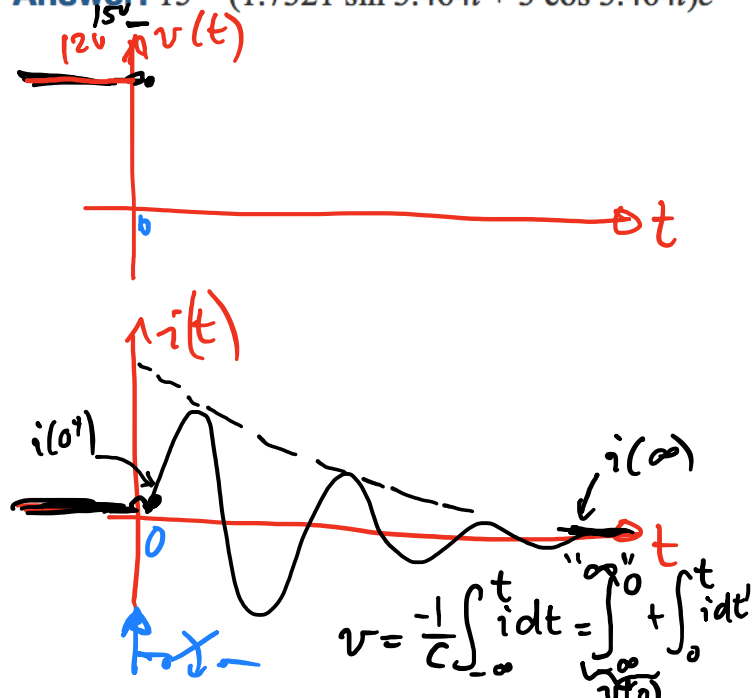Answer: $15 - (1.7321 \sin 3.464t + 3 \cos 3.464t)e^{-2t}$ V, $3.464e^{-2t} \sin 3.464t$ V.



$$v(0^+) = 12 \text{ V} = \frac{\beta_2}{C(2^2 + \omega_0^2)} [\omega_0 - \omega_0] = \frac{\beta_2}{C(2^2 + \omega_0^2)} (-2 + j\omega_0)(-2 - j\omega_0) = \frac{\beta_2}{C(2^2 + \omega_0^2)} (-4 + \omega_0^2)$$

$$v(\infty) = \frac{\beta_2}{C(2^2 + \omega_0^2)} (-\omega_0) + v(0^+) = 15 \text{ V}$$

$$v(t) = \frac{\beta_2}{C(2^2 + \omega_0^2)} \left[\frac{e^{-2t}}{2} \sin \omega_0 t - 0 + \omega_0 \frac{(\cos \omega_0 t - 1)}{2^2 + \omega_0^2} \right]$$

$$v = \frac{\beta_2}{C} \left[\frac{+2e^{-2t} \sin \omega_0 t}{2^2 + \omega_0^2} + \frac{\omega_0 (e^{(-2+j\omega_0)t} - e^{(-2-j\omega_0)t})}{(-2+j\omega_0)(-2-j\omega_0)} - j\omega_0 \right]$$

$$v = \frac{-\beta_2}{2jC} \left[\frac{-2(e^{(-2+j\omega_0)t} - e^{(-2-j\omega_0)t})}{2^2 + \omega_0^2} \right]$$

$$v = \frac{-\beta_2}{2jC} \left[\frac{e^{(-2+j\omega_0)t}}{(-2+j\omega_0)} - \frac{e^{(-2-j\omega_0)t}}{(-2-j\omega_0)} \right] + v(0^+)$$

$$i = -C \frac{dv}{dt}$$

$$v = \frac{1}{C} \int_0^t i dt' = \frac{1}{C} \left[\frac{e^{(-2+j\omega_0)t'}}{-2+j\omega_0} - \frac{e^{(-2-j\omega_0)t'}}{-2-j\omega_0} \right] + v(0^+)$$

Step Response of Parallel RLC

- Section 8.6
- Similar to series
- Please review on own

General 2nd order circuits

1. We first determine the initial conditions $x(0)$ and $dx(0)/dt$ and the final value $x(\infty)$, as discussed in [Section 8.2](#).
2. We turn off the independent sources and find the form of the transient response $x_t(t)$ by applying KCL and KVL. Once a second-order differential equation is obtained, we determine its characteristic roots. Depending on whether the response is overdamped, critically damped, or underdamped, we obtain $x_t(t)$ with two unknown constants as we did in the previous sections.

3. We obtain the steady-state response as

$$x_{ss}(t) = x(\infty) \quad (8.51)$$

where $x(\infty)$ is the final value of x , obtained in step 1.


4. The total response is now found as the sum of the transient response and steady-state response

$$x(t) = x_t(t) + x_{ss}(t) \quad (8.52)$$

We finally determine the constants associated with the transient response by imposing the initial conditions $x(0)$ and $dx(0)/dt$, determined in step 1.

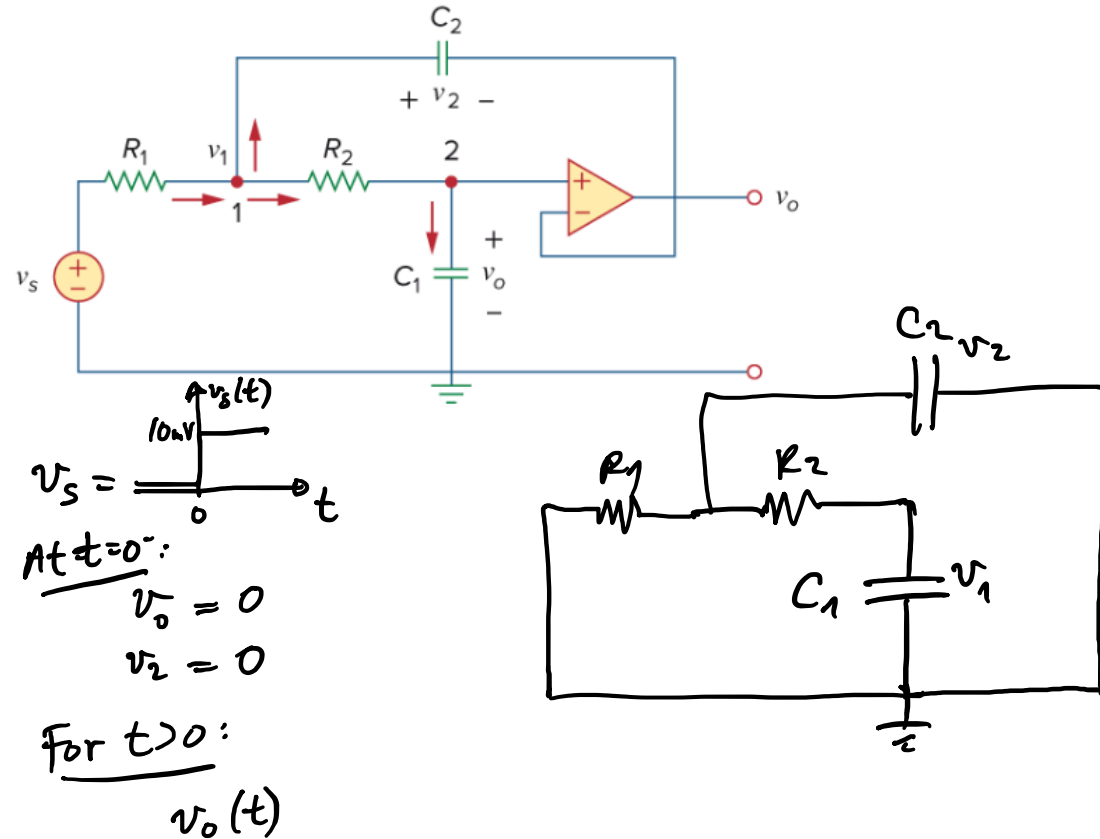Example 8.11


In the op amp circuit of **Fig. 8.33**, find $v_o(t)$ for $t > 0$ when $v_s = 10u(t)$ mV. Let $R_1 = R_2 = 10 \text{ k}\Omega$, $C_1 = 20 \text{ }\mu\text{F}$, and $C_2 = 100 \text{ }\mu\text{F}$.



Sinusoids and Phasors

Chapter 9



AC circuits

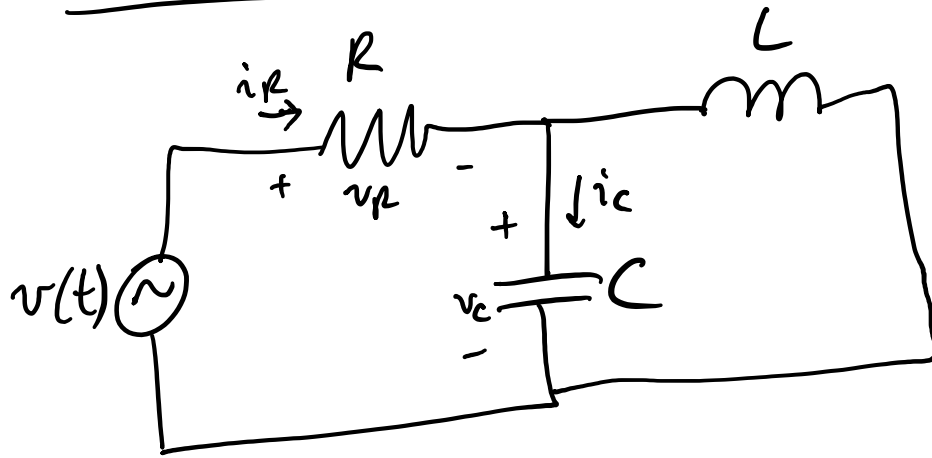

DC $v_R = i_R R$

$$i_C = C \frac{dv}{dt}$$

$$v_L = L \frac{di}{dt}$$

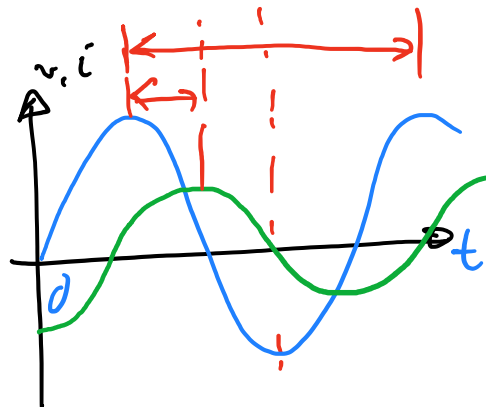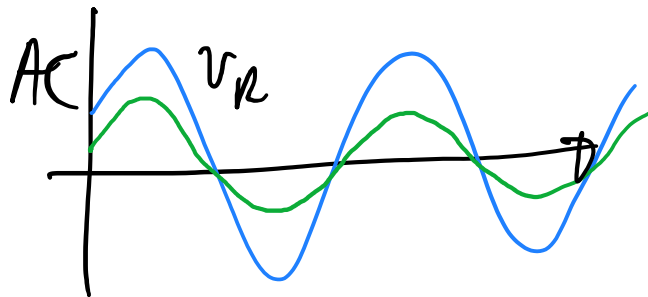

$$\begin{aligned}
 v(t) &= \operatorname{Re}\{e^{j\omega_0 t}\} = \operatorname{Re}\{\tilde{v}(t)\} = \cos \omega_0 t \\
 &= \operatorname{Re}\{\cos \omega_0 t + j \sin \omega_0 t\} \\
 &= \cos \omega_0 t
 \end{aligned}$$

$$\begin{aligned}
 \tilde{i}(t) &= C \frac{d\tilde{v}}{dt} \\
 &= C \frac{d}{dt} e^{j\omega_0 t} \\
 &= C j \omega_0 e^{j\omega_0 t} \\
 &= C j \omega_0 \tilde{v}
 \end{aligned}$$

$$\begin{aligned}
 i(t) &= C \frac{dv}{dt} \\
 &= C \frac{d}{dt} V_0 \cos \omega_0 t \\
 &= C \omega_0 V_0 \sin \omega_0 t
 \end{aligned}$$

$$\begin{aligned}
 i(t) &= \operatorname{Re}\{\tilde{i}(t)\} = \operatorname{Re}\{C j \omega_0 e^{j\omega_0 t}\} \\
 &= C \omega_0 \operatorname{Re}\{j(\cos \omega_0 t + j \sin \omega_0 t)\} \\
 &= -C \omega_0 \sin \omega_0 t
 \end{aligned}$$

Sinusoids and Phasors

A **sinusoid** is a signal that has the form of the sine or cosine function.



- aka AC

A **periodic function** is one that satisfies $f(t) = f(t + nT)$, for all t and for all integers n .

$$v(t) = V_m \sin \omega t$$

↑
rad/s

$$T = \frac{2\pi}{\omega}$$

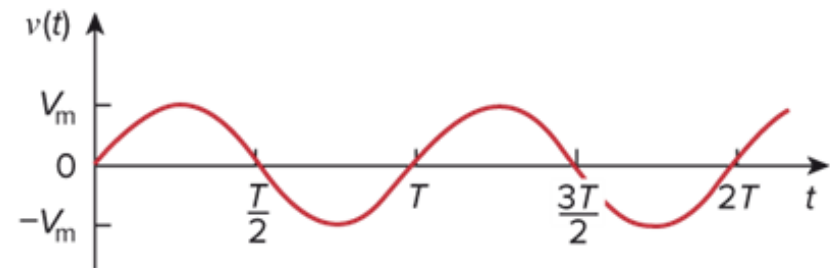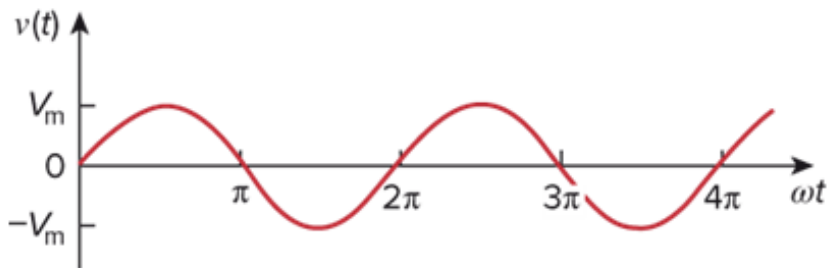

Sinusoids and Phasors

A **sinusoid** is a signal that has the form of the sine or cosine function.

- aka AC



A **periodic function** is one that satisfies $f(t) = f(t + nT)$, for all t and for all integers n .

$$v(t) = V_m \sin \omega t$$

$$T = \frac{2\pi}{\omega}$$



$$f = \frac{1}{T}$$

$$\omega = 2\pi f$$

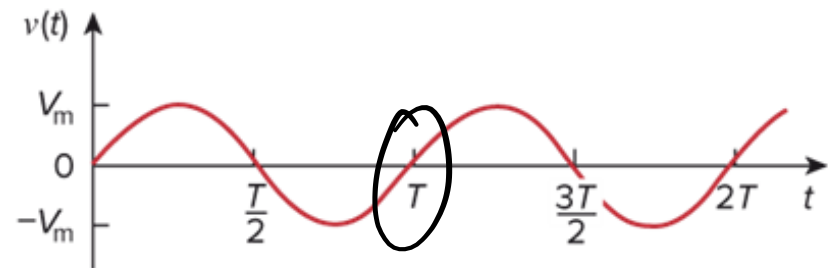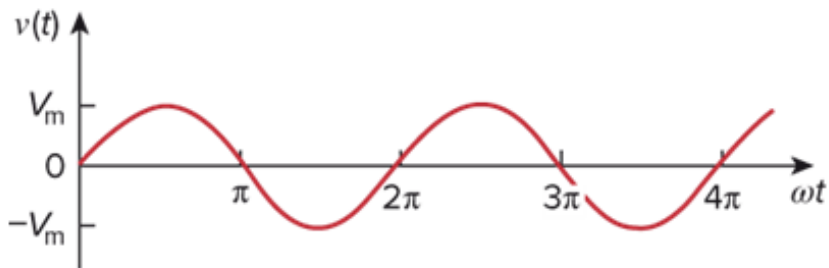

Sinusoids and Phasors

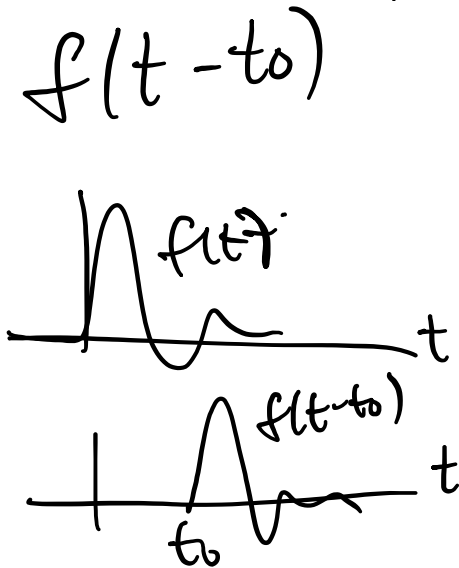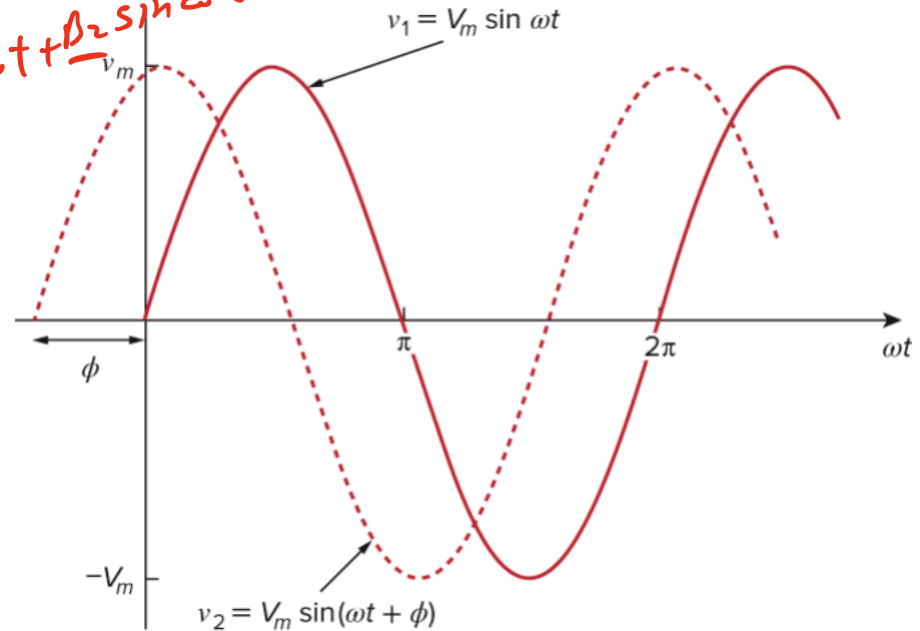
$$v(t) = V_m \sin(\omega t + \phi) = B_1 \cos \omega t + B_2 \sin \omega t$$



$$\begin{aligned} \sin(A+B) &= \sin A \cos B + \cos A \sin B \\ &= \sin \omega t \underbrace{\cos \phi}_{B_1} + \cos \omega t \underbrace{\sin \phi}_{B_2} \end{aligned}$$


Sinusoids and Phasors

$$v(t) = V_m \sin(\omega t + \phi)$$

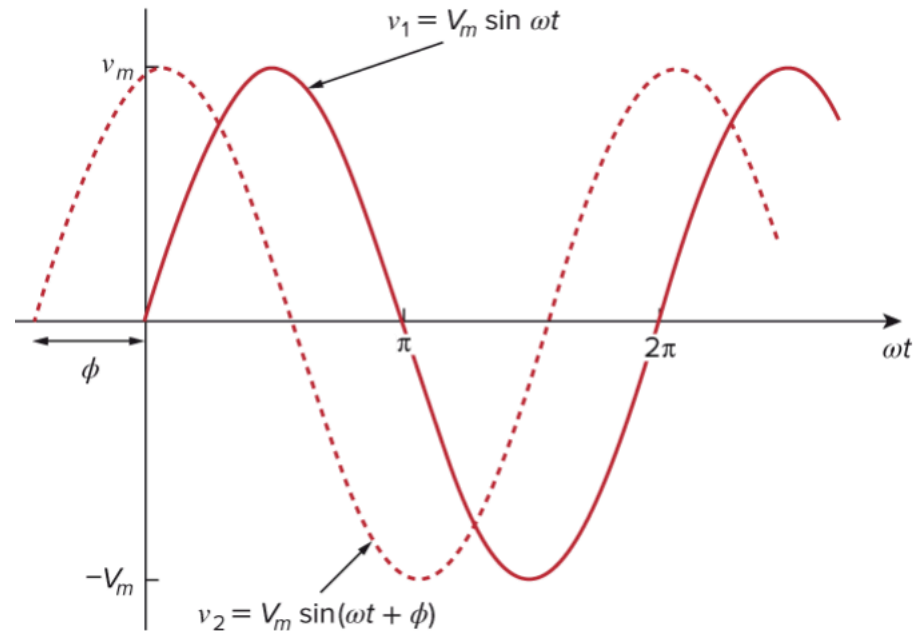

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

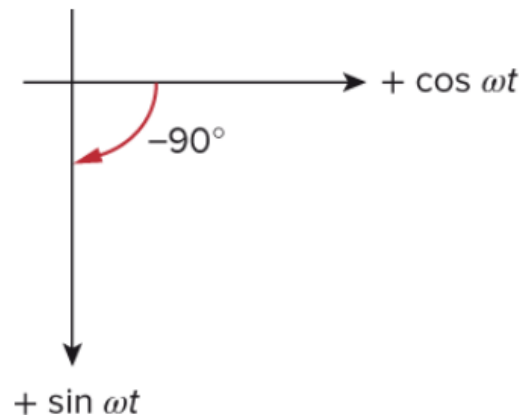

Example 9.1

Find the amplitude, phase, period, and frequency of the sinusoid

$$v(t) = 12 \cos(50t + 10^\circ) \text{ V.}$$

Phasors

A **phasor** is a complex number that represents the amplitude and phase of a sinusoid.

$$z = x + jy$$

$$z = r \angle \phi = re^{j\phi}$$

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

$$\cos \phi = \operatorname{Re}(e^{j\phi})$$

$$\sin \phi = \operatorname{Im}(e^{j\phi})$$

$$\tilde{v}(t) = \underline{V} e^{j\omega_0 t}$$



$$= (\underbrace{V e^{j\theta}}_{\substack{\uparrow \\ V e^{j\theta}}}) e^{j\omega_0 t}$$

$$v(t) = \operatorname{Re}\{\tilde{v}(t)\} = \operatorname{Re}\{\underline{V} e^{j\omega_0 t}\}$$

$$= \operatorname{Re}\{V e^{j\theta} e^{j\omega_0 t}\} = \operatorname{Re}\{V e^{j(\omega_0 t + \theta)}\}$$

$$= \operatorname{Re}\{\cos(\omega_0 t + \theta) + j \sin(\omega_0 t + \theta)\}$$

$$= V \cos(\omega_0 t + \theta)$$

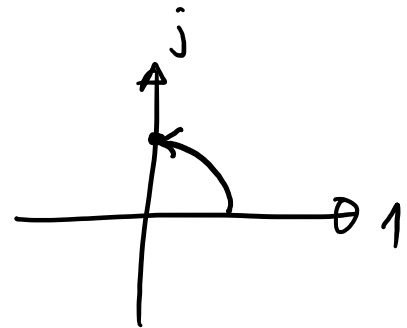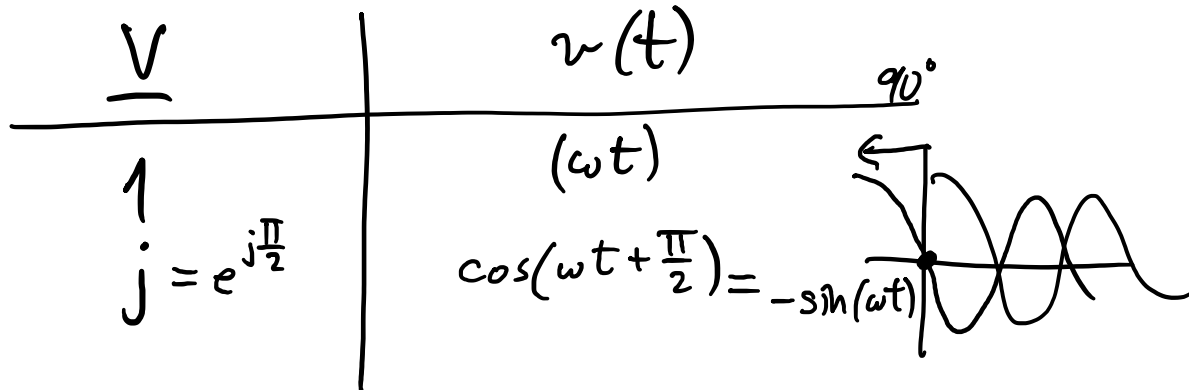

Phasors

$$v(t) = \text{Re}(\mathbf{V}e^{j\omega t})$$

$$z = x + jy$$


$$z = r/\phi = re^{j\phi}$$

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$


$$\cos \phi = \text{Re}(e^{j\phi})$$

$$\sin \phi = \text{Im}(e^{j\phi})$$
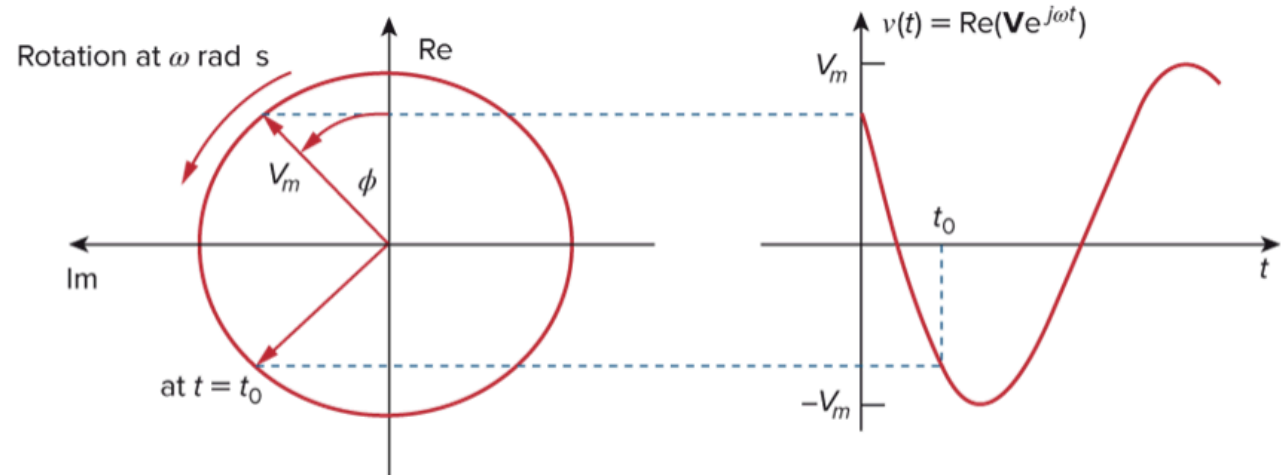
$$\mathbf{V} = V_m e^{j\phi} = V_m/\phi$$



Phase

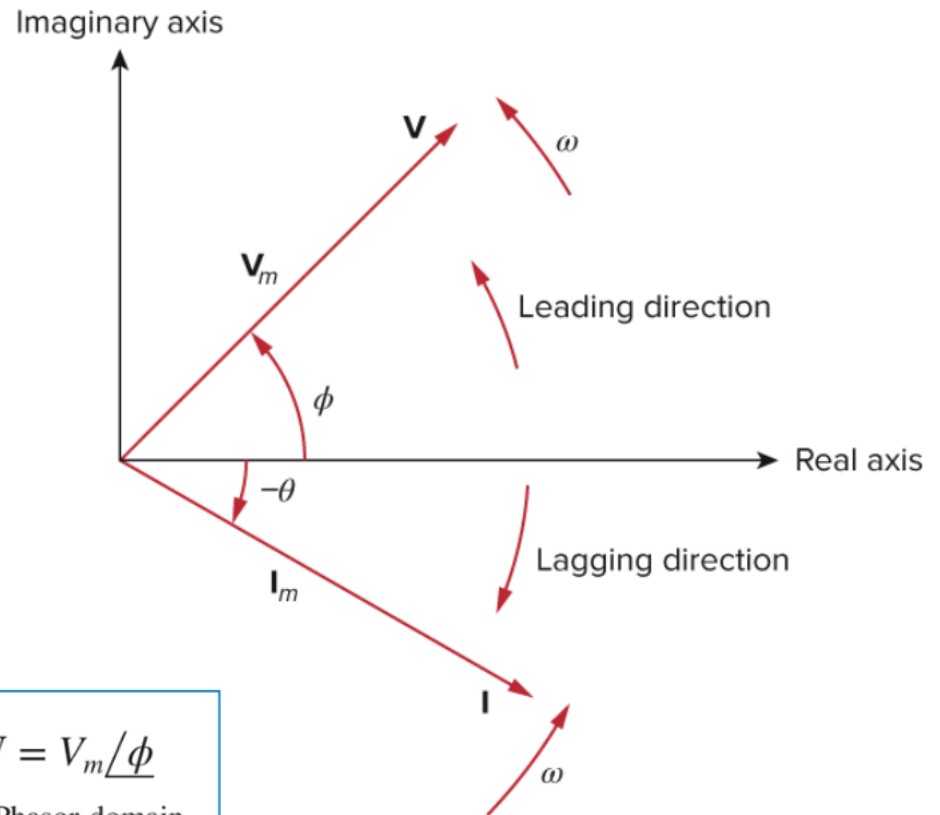

$$v(t) = V_m \cos(\omega t + \phi)$$

(Time-domain
representation)

$\Leftrightarrow$

$$\mathbf{V} = V_m \angle \phi$$

(Phasor-domain
representation)

Phase

TABLE 9.1

Sinusoid-phasor transformation.

Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

Circuit equations

$$\begin{array}{ccc} \frac{dv}{dt} & \Leftrightarrow & j\omega \mathbf{V} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$

$$\begin{array}{ccc} \int v \, dt & \Leftrightarrow & \frac{\mathbf{V}}{j\omega} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$

Sinusoids and Phasors