

EK 307: Electric Circuits

Fall 2017

Lecture 22

Nov 30, 2017

Milos Popovic

Department of Electrical and Computer Engineering

Boston University

Administrivia

- HW9 due today

Last Lecture (21): Chapter 9

- 1. Started Chapter 9 – Phasors & Sinusoidal Steady State; Impedance/Admittance**

Phasors

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

$$z = x + jy = r \angle \phi, \quad z_1 = x_1 + jy_1 = r_1 \angle \phi_1 \\ z_2 = x_2 + jy_2 = r_2 \angle \phi_2$$

Add in component form.

Multiply in polar form.

Addition:

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction:

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication:

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

Division:

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

Reciprocal:

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

Square Root:

$$\sqrt{z} = \sqrt{r} \angle \phi/2$$

Complex Conjugate:

$$z^* = x - jy = r \angle -\phi = re^{-j\phi}$$

Time and frequency domains

$$\begin{array}{ccc} \frac{dv}{dt} & \Leftrightarrow & j\omega \mathbf{V} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$

$$\begin{array}{ccc} \int v \, dt & \Leftrightarrow & \frac{\mathbf{V}}{j\omega} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$

$v(t)$

$\mathbf{V}$

Instantaneous/time domain

phasor/frequency domain

Time dependent

Time independent


Always real valued

Complex number in general

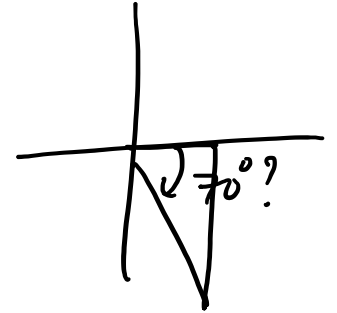Example 9.7

Using the phasor approach, determine the current $i(t)$ in a circuit described by the integrodifferential equation

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$




$$4\underline{I} + 8 \frac{1}{j\omega} \underline{I} - 3j\omega \underline{I} = 50 \angle 75^\circ, \omega = 2$$

$$4\underline{I} + 8 \frac{1}{j2} \underline{I} - 3j2 \underline{I} = 50 \angle 75^\circ$$

$$(4 - j4 - j6) \underline{I} = 50 \angle 75^\circ \rightarrow \underline{I} = \frac{50 \angle 75^\circ}{4 - j10} = \frac{50 \angle 75^\circ}{12 \angle -70^\circ}$$
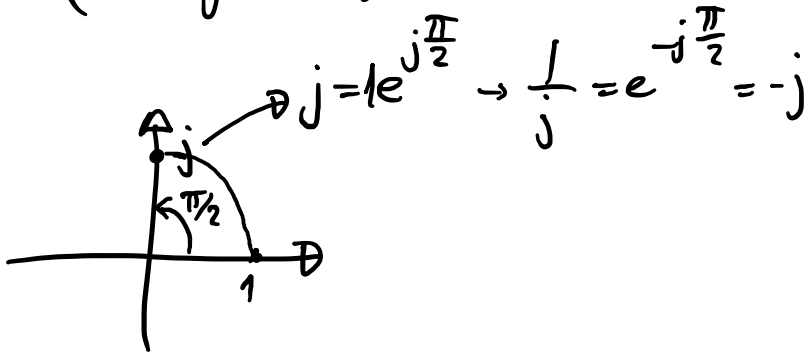
$$\underline{I} \approx 4 \angle 145^\circ$$




$$i(t) = 4 \cos(2t + 145^\circ)$$

Phasor Circuit Laws

TABLE 9.2

Summary of voltage-current relationships.

Element	Time domain	Frequency domain
R	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
L	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$
C	$i = C \frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

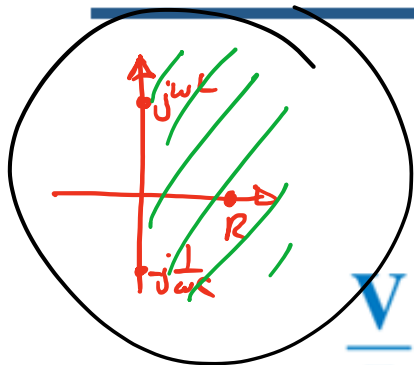

$$\frac{\mathbf{V}}{\mathbf{I}} = R,$$

$$= z_R$$

$$\frac{\mathbf{V}}{\mathbf{I}} = j\omega L,$$

$$= z_L$$

$$\frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C} = -j\frac{1}{\omega C}$$

$$= z_C$$

Concept of impedance

$$\frac{\mathbf{V}}{\mathbf{I}} = R, \quad \frac{\mathbf{V}}{\mathbf{I}} = j\omega L, \quad \frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C}$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} \quad \text{or} \quad \mathbf{V} = \mathbf{Z}\mathbf{I}$$

The **impedance** $\mathbf{Z}$ of a circuit is the ratio of the phasor voltage $\mathbf{V}$ to the phasor current $\mathbf{I}$, measured in ohms (Ω).

$$Y = \frac{\mathbf{I}}{\mathbf{V}}$$

TABLE 9.3

Impedances and admittances of passive elements.




Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R} = G$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$


$$Z = R + jX$$

resistance *reactance*


$$Y = G + jB$$

cond *susceptance*

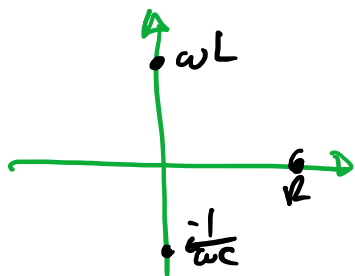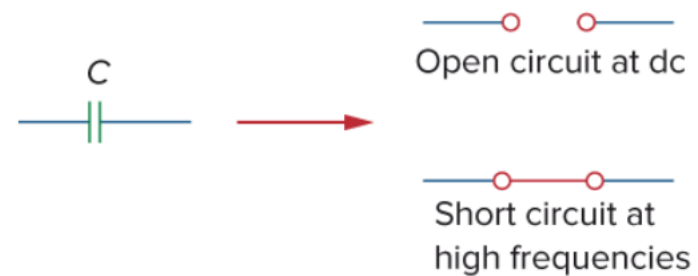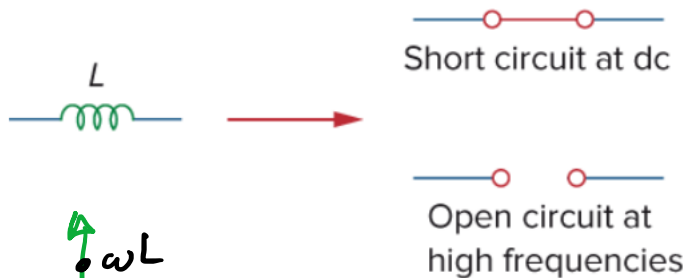

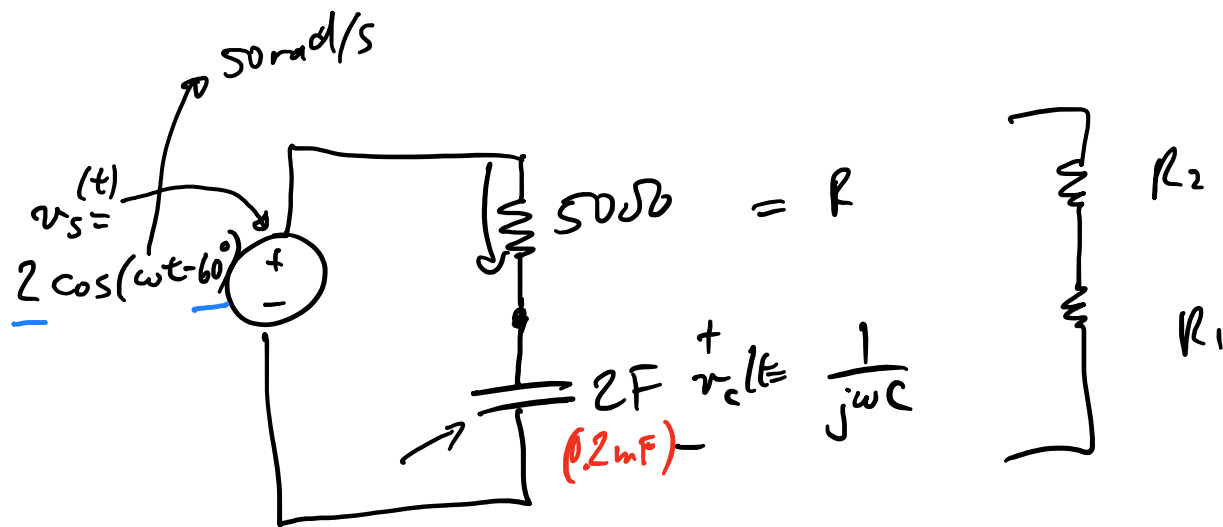
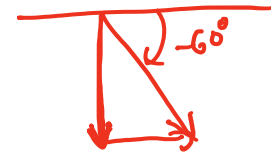
$$v_s \longrightarrow \underline{V_s} = 2 \angle -60^\circ \text{ [V]}$$



$$\underline{V_c} = \frac{\cancel{R_1}}{\cancel{R_2} + \cancel{R_1}} \underline{V_s} = \frac{Z_c}{Z_c + Z_R} \underline{V_s}$$

$$\underline{V_c} = \left| \frac{2}{3} \right| \angle -30^\circ \underline{V_s} = \frac{2}{3} \angle -30^\circ \cdot 2 \angle -60^\circ$$

$$\underline{V_c} = \frac{4}{3} \angle -90^\circ \quad \omega = 50 \text{ rad/s}$$

$$v_c(t) = \frac{4}{3} \cos(\omega t - 90^\circ) \text{ [V]}$$

$$= \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \underline{V_s} = \frac{-j \frac{1}{(50)(2)}}{-j \frac{1}{50 \cdot 2} + 50} \underline{V_s} = \frac{-j 0.01}{-j 0.01 + 50} \underline{V_s}$$

$$= \frac{0.01 \angle -90^\circ}{50 \angle 0^\circ} \underline{V_s}$$

$$\approx 0.0002 \angle -90^\circ \underline{V_s}$$

APPROXIMATELY !!!


$$\left| \frac{2}{3} \right| \angle -30^\circ \underline{V_s} =$$

$$\underline{V_s} \approx \frac{1}{j100 + 50} \underline{V_s}$$

$$\underline{V_s}$$

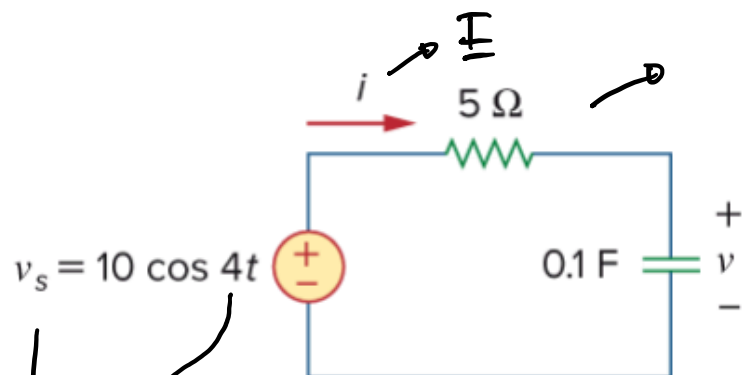Example 9.9

Find $v(t)$ and $i(t)$ in the circuit shown in Fig. 9.16.



$$Z = 5 \Omega + \frac{1}{j4(0.1)} = 5 - j2.5$$

$\omega = 4$

$$\underline{V}_s = 10 \angle 0^\circ$$


$$10 \angle 0^\circ = \underline{V}_s = \underline{V}_R + \underline{V}_C = \underline{I}R + \frac{1}{j\omega C} \underline{I}$$

$$\underline{I} = \frac{10 \angle 0^\circ}{(5 - j2.5)} = \frac{10}{5 - j2.5} = \frac{10 \angle 0^\circ}{6 \angle -30^\circ}$$

$$\underline{I} \sim 1.8 \angle 30^\circ$$

$$i(t) = 1.8 \cos(4t + 30^\circ) \text{ A}$$

KVL and KCL in Phasor Domain

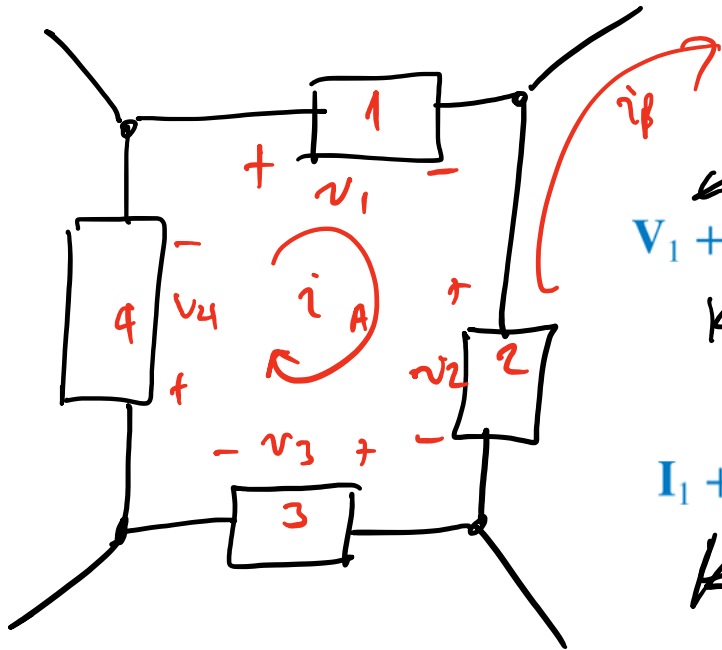

$$v_1^{(t)} + v_2^{(t)} + v_3^{(t)} + v_4^{(t)} = 0$$

$$\underline{V}_1 + \underline{V}_2 + \dots + \underline{V}_n = 0$$

KVL


$$\underline{\text{Re}}\{\underline{V}_1 e^{j\omega t}\} + \underline{\text{Re}}\{\underline{V}_2 e^{j\omega t}\} + \dots = 0$$

$$\underline{I}_1 + \underline{I}_2 + \dots + \underline{I}_n = 0$$

KCL


$$\underbrace{(\dots)}_{\underline{V}_{\text{total}} = 0} e^{j\omega t} = 0$$

Series elements

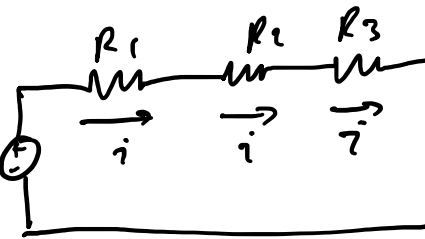



$$iR_1 + iR_2 + iR_3 - v_s = 0$$

$$i(R_{eq}) - v_s = 0$$

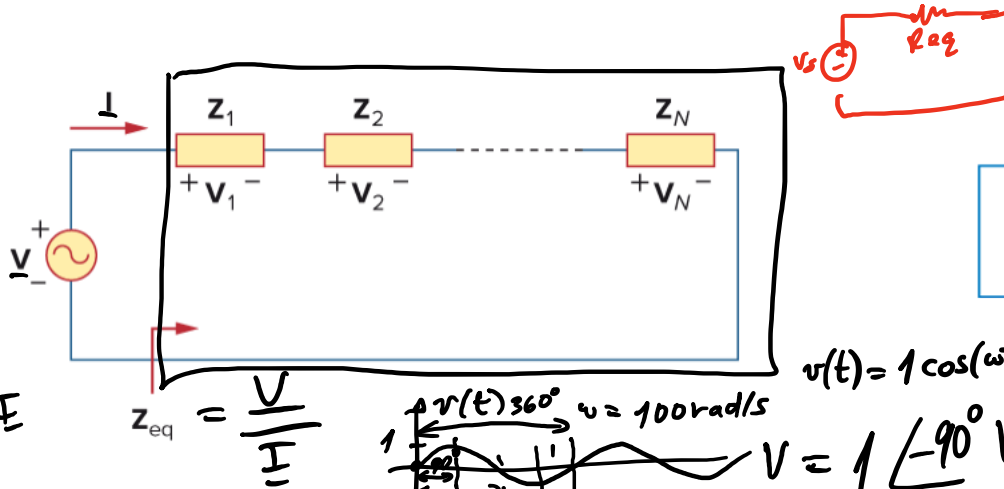


$$Z_{eq} = Z_1 + Z_2 + \dots + Z_N$$

$$v(t) = 1 \cos(\omega t - 90^\circ)$$

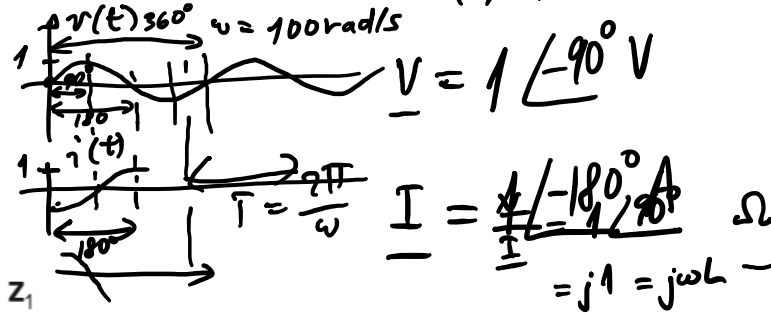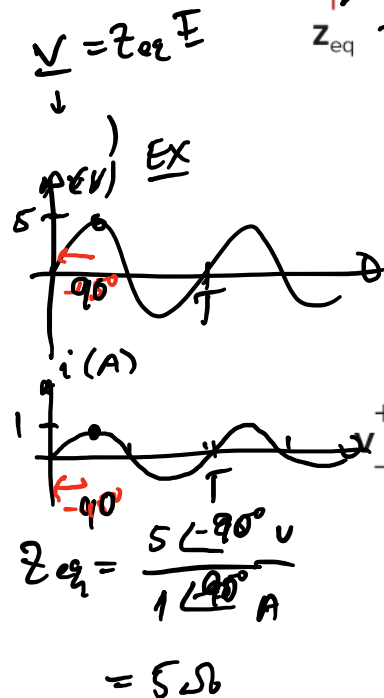


$$\omega L = 1 \Omega$$

$$L = 0.01 \text{ H} = 10 \text{ mH}$$

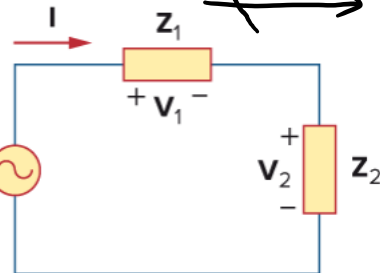
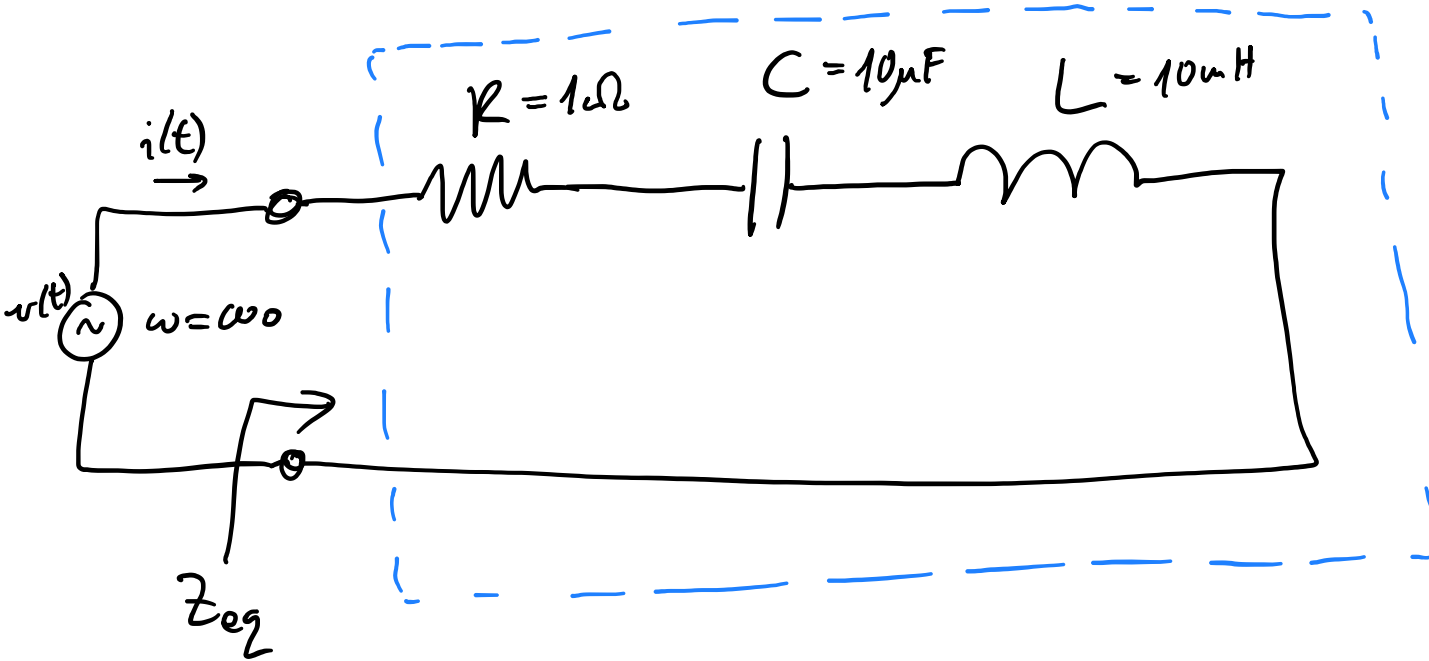
$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$



$$\begin{aligned}
 Z_{eq} &= Z_R + Z_C + Z_L \\
 &= R - j\frac{1}{\omega C} + j\omega L = R + j\left(\omega L - \frac{1}{\omega C}\right) \\
 &= 1\Omega - j\frac{1}{\omega 10\mu F} + j\omega 10mH = 1\Omega + j\left(\omega 10mH - \frac{1}{\omega 10\mu F}\right)
 \end{aligned}$$



$$\begin{aligned}
 \omega L &= \frac{1}{\omega C} \Rightarrow \omega^2 = \frac{1}{LC} \\
 \omega &= \frac{1}{\sqrt{LC}}
 \end{aligned}$$

0!




$$\rightarrow R = R_1 + R_2$$

$$\frac{Z}{R}$$




$$\rightarrow L = L_1 + L_2$$

$$j\omega L$$

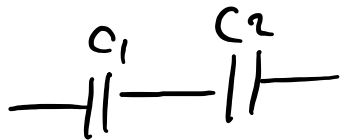

$$\rightarrow \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$\frac{1}{j\omega C}$$

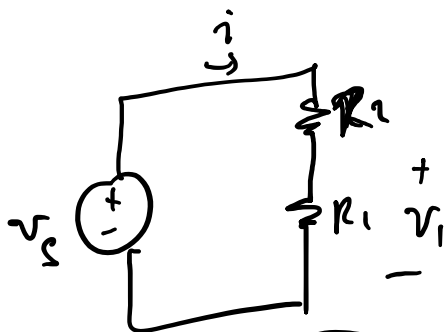

$$i = \frac{v_s}{R_1 + R_2}$$


$$v_1 = i R_1$$

$$v_1 = \frac{R_1}{R_1 + R_2} v_s$$

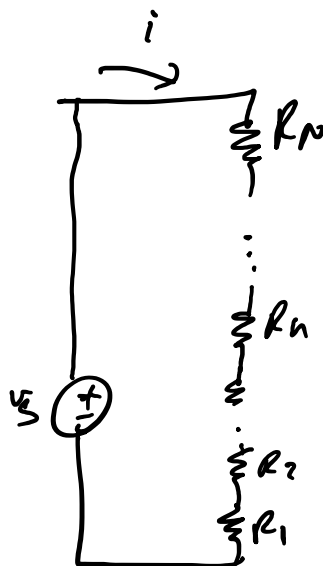

$$i = \frac{v_s}{\sum_n R_n}$$
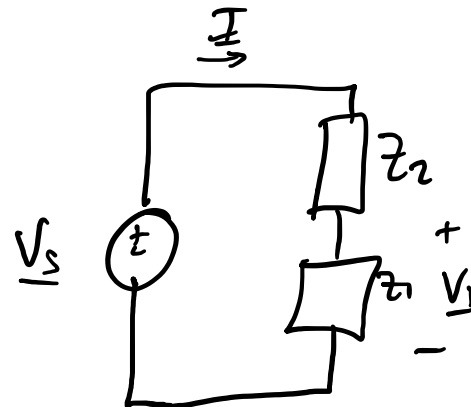
$$v_n = i R_n \rightarrow v_n = \frac{R_n}{\sum_{m=1}^n R_m} v_s$$




$$I = \frac{v_s}{z_1 + z_2}$$


$$v_1 = I \cdot z_1$$

$$v_1 = \frac{z_1}{z_1 + z_2} v_s$$

Series elements

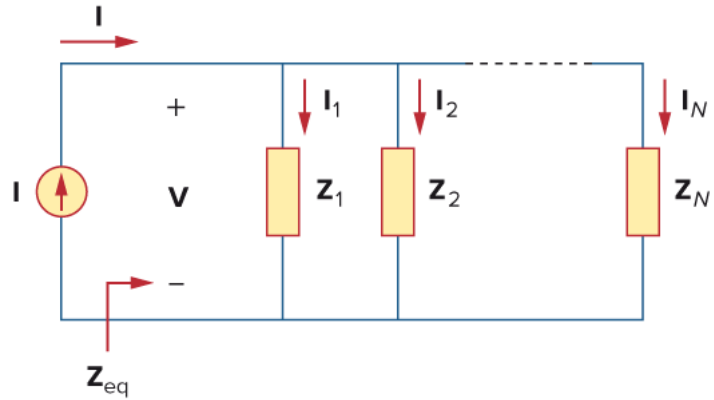


$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

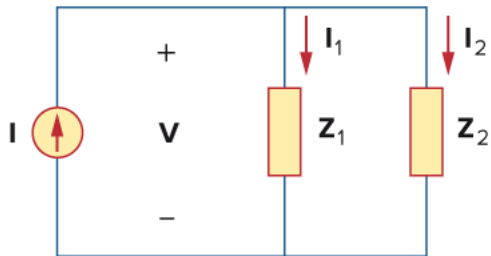

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

Series elements

$$Y \equiv \frac{1}{Z}$$

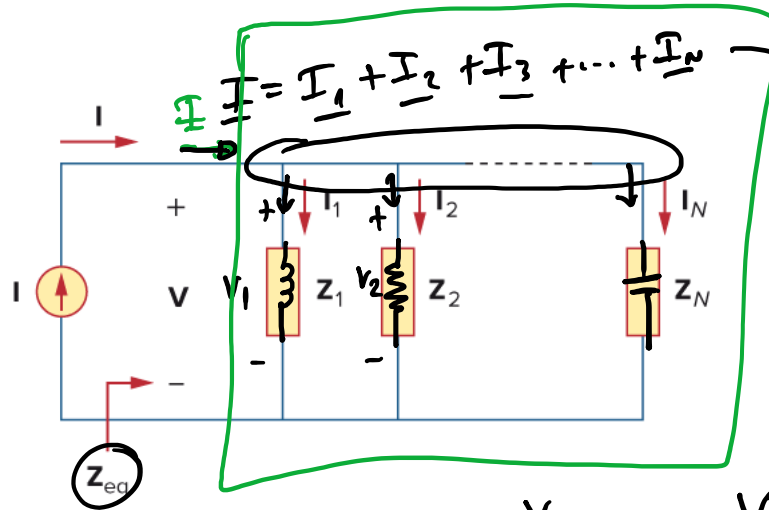

$$I = I_1 + I_2 + I_3 + \dots + I_N$$

$$Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$

$$\rightarrow V_1 = Z_1 I_1 \rightarrow I_1 = \frac{V}{Z_1}$$

$$\rightarrow V_2 = Z_2 I_2 \rightarrow I_2 = \frac{V}{Z_2}$$

$$V_3 = Z_3 I_3$$

$$V_1 = V_2 = V_3 = \dots = V$$

$$V = Z_{eq} I$$

$$= Z_{eq} (I_1 + I_2 + \dots + I_N)$$

$$Y = \frac{1}{Z_{eq}} = \frac{1}{Z} \left(\frac{V}{Z_1} + \frac{V}{Z_2} + \dots + \frac{V}{Z_N} \right) = \frac{1}{Z} \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$


$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = \sum_{k=1}^N Y_k$$

$$\left[R_1 \right] \left[R_2 \right] \rightarrow \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$G = G_1 + G_2$$

Series elements

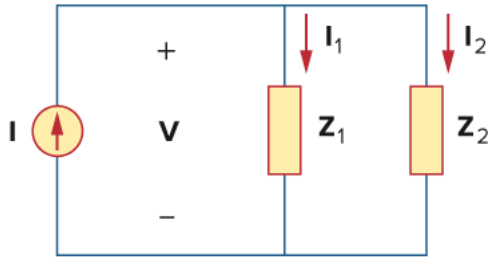


$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$

$$= \frac{Y_1}{Y_1 + Y_2} I = \frac{\frac{1}{z_1}}{\frac{1}{z_1} + \frac{1}{z_2}} I = \frac{z_2}{z_2 + z_1} I$$

$$I_1 = \frac{R_2}{R_1 + R_2} I_s =$$

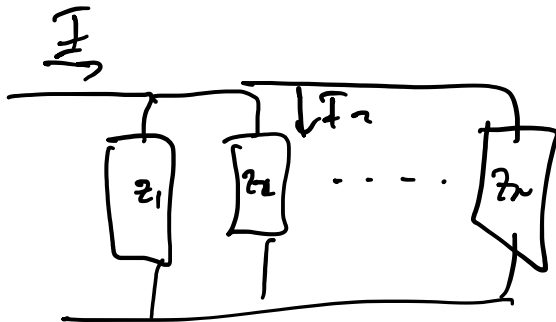
$$\left(V_1 = \frac{R_1}{R_1 + R_2} V_s \right)$$



$$I_2 = \frac{Y_2}{Y_1 + Y_2 + \dots + Y_n} I$$


Practice Problem 9.10

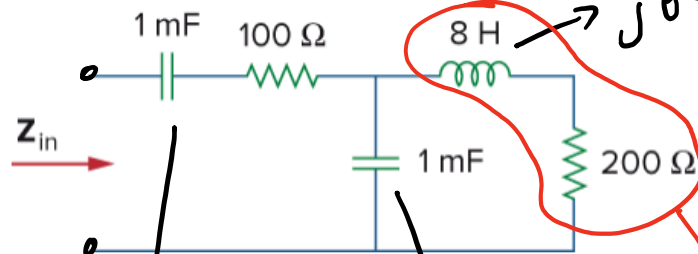Determine the input impedance of the circuit in Fig. 9.24 at $\omega = 20$ rad/s.




$$Z_{C1} = \frac{1}{j 1 \text{ mF} \cdot 20 \text{ rad/s}} = \frac{1}{j 0.02} = -j 50 \Omega$$

$$0.02 \angle 0^\circ = -j 50$$

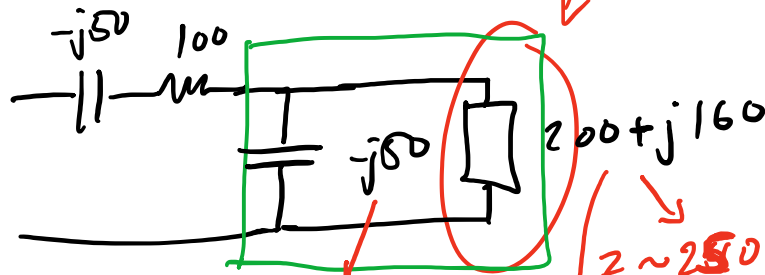

$$Y = j \frac{1}{50} = j 0.02$$


$$Y = 0.003049 - j 0.002439$$

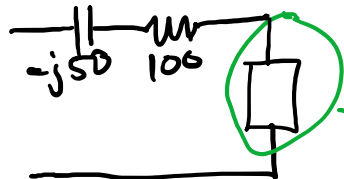

$$Y = j 0.020 + 0.003 - j 0.002 = 0.003 + j 0.018$$

$$Z = \frac{1}{Y} = 52 \angle -80^\circ = 9.60 - j 55.3$$

$$j 8 \cdot 20 = j 160 \Omega$$

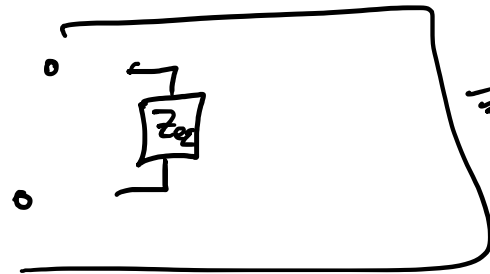

$$Z_{eq} = -j 50 + 100 + 9.60 - j 55.3$$

$$= 109.6 - j 105.3$$


$$= R - j \frac{1}{\omega C} + j \omega L$$

$$R = 109.6 \Omega$$

$$\frac{1}{\omega C} = 105.3 \Omega$$

$$C = \frac{1}{20 \cdot 105.3} = 0.0005 \text{ F}$$

$$C = 500 \mu\text{F}$$

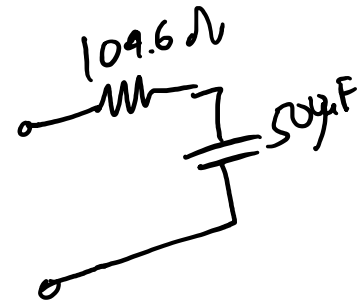

Practice Problem 9.10

Determine the input impedance of the circuit in **Fig. 9.24** at $\omega = 20$ rad/s.

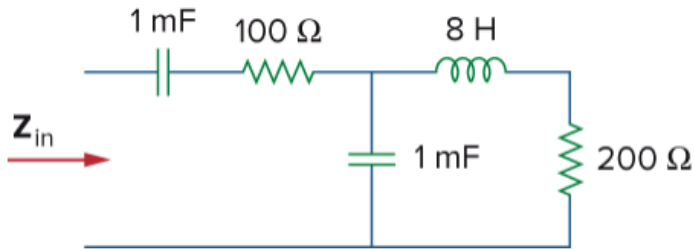



Figure 9.24 For Practice Prob. 9.10.

Answer: $(109.53 - j105.29)\ \Omega$.

$$\begin{aligned} Z &= 200 + j\omega 8 \\ Y &= \frac{1}{Z} = \frac{200 - j\omega 8}{(200 + j\omega 8)(200 - j\omega 8)} = \frac{200 - j\omega 8}{200^2 + (\omega 8)^2} \\ &= \frac{200}{200^2 + (\omega 8)^2} - j \frac{\omega 8}{200^2 + (\omega 8)^2} \end{aligned}$$

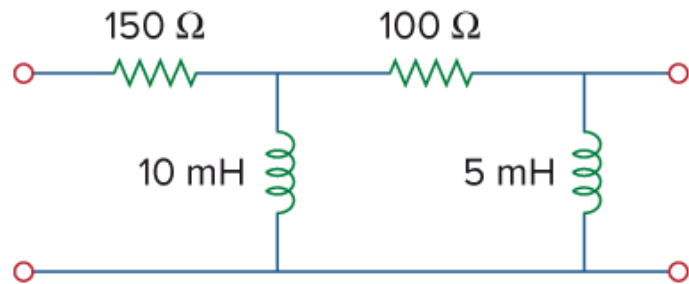Example 9.14

For the RL circuit shown in **Fig. 9.35(a)**, calculate the amount of phase shift produced at 2 kHz.



Solving AC Circuits

(Chapter 10)


Steps to Analyze AC Circuits:

1. Transform the circuit to the phasor or frequency domain.
2. Solve the problem using circuit techniques (nodal analysis, mesh analysis, superposition, etc.).
3. Transform the resulting phasor to the time domain.

Node voltage method

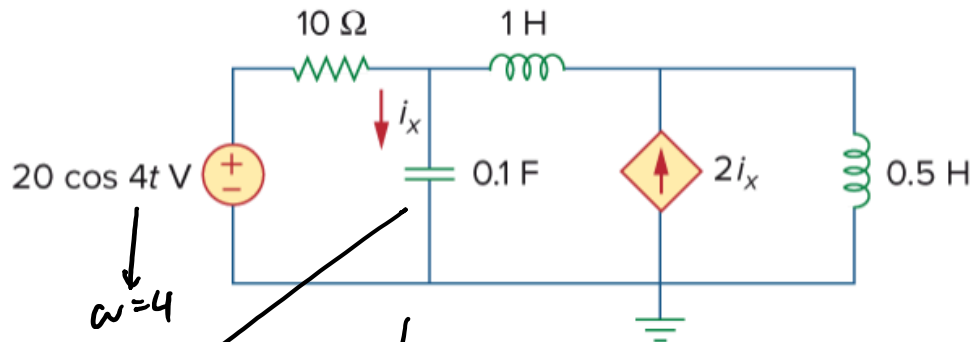
Example 10.1

Find i_x in the circuit of **Fig. 10.1** using nodal analysis.



$\omega = 4$
 $Z_C = \frac{1}{j\omega C}$
 $= \frac{1}{j4 \cdot 0.1} = -j2.5$
 $= -j2.5 \Omega$

Find impedances

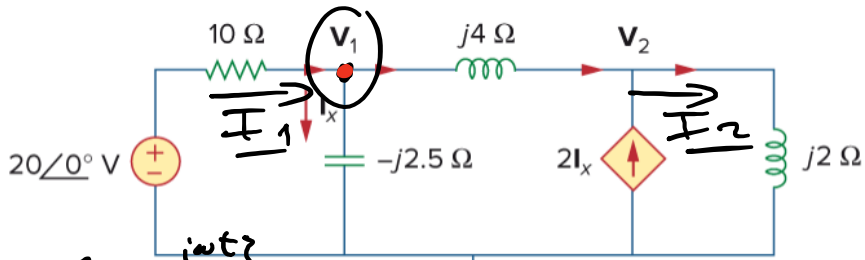

$i_x(t) = \text{Re}\{ \underline{I}_x e^{j\omega t} \}$
 $= \text{Re}\{ 10 e^{j(\omega t - 45^\circ)} \}$ say $= 10 \cos(\omega t - 45^\circ)$
 $i_x(t) = 10 \cos(\omega t - 45^\circ)$
 $\underline{I}_x = \frac{V_1}{-j2.5}$

$$\textcircled{1}: \frac{20\angle 0^\circ - V_1}{10} = \frac{V_1 - V_2}{j4} + \frac{V_1}{-j2.5}$$

$$\textcircled{2}: \frac{V_1 - V_2}{j4} + 2 \frac{V_1}{-j2.5} = \frac{V_2}{j2}$$

$$\underline{I}_x = \frac{V_1}{-j2.5}$$


$$\frac{20\angle 0^\circ - V_1}{10} = \frac{V_1 - V_2}{j4} + \frac{V_1}{-j2.5}$$

$$\frac{V_1 - V_2}{j4} + 2 \frac{V_1}{-j2.5} = \frac{V_2}{j2}$$

$$\begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

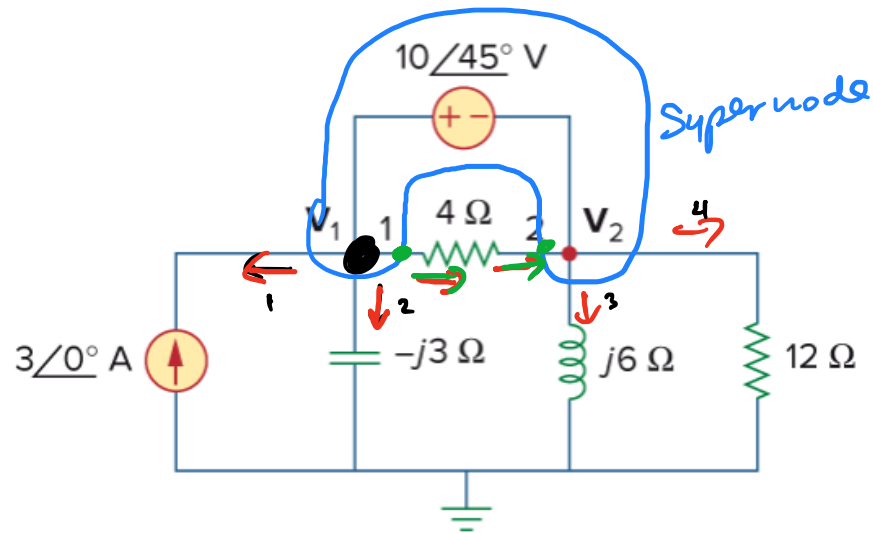Example 10.2

Compute V_1 and V_2 in the circuit of Fig. 10.4.



$$\underline{V_2} = \underline{V_1} - 10 \angle 45^\circ$$


$$-3 \angle 0^\circ + \frac{\underline{V_1}}{-j3} + \frac{\underline{V_1} - 10 \angle 45^\circ}{j6} + \frac{\underline{V_1} - 10 \angle 45^\circ}{12} = 0$$

$\begin{matrix} 1 & 2 & 3 & 4 \end{matrix}$

$$\underline{V_2} = \underline{V_1} - 10 \angle 45^\circ$$

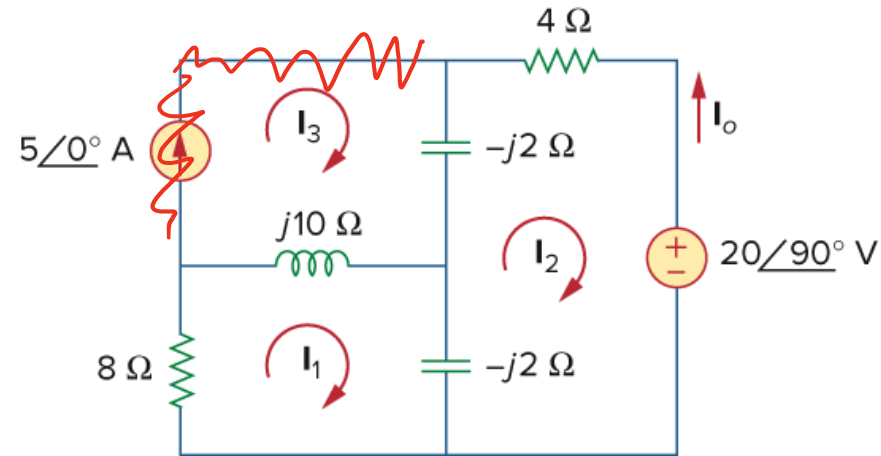Example 10.3

Determine current $\mathbf{I}_o$ in the circuit of **Fig. 10.7** using mesh analysis.




2 eqns bc $\underline{I}_3 = 5 \angle 0^\circ \text{ A}$, $i_3(t) = 5 \cos(\omega t) \text{ A}$

$\Rightarrow \begin{bmatrix} + \end{bmatrix} \begin{bmatrix} \underline{I}_2' \end{bmatrix} = \begin{bmatrix} 0 \end{bmatrix}$

$\hookrightarrow \underline{I}_o = -\underline{I}_2$

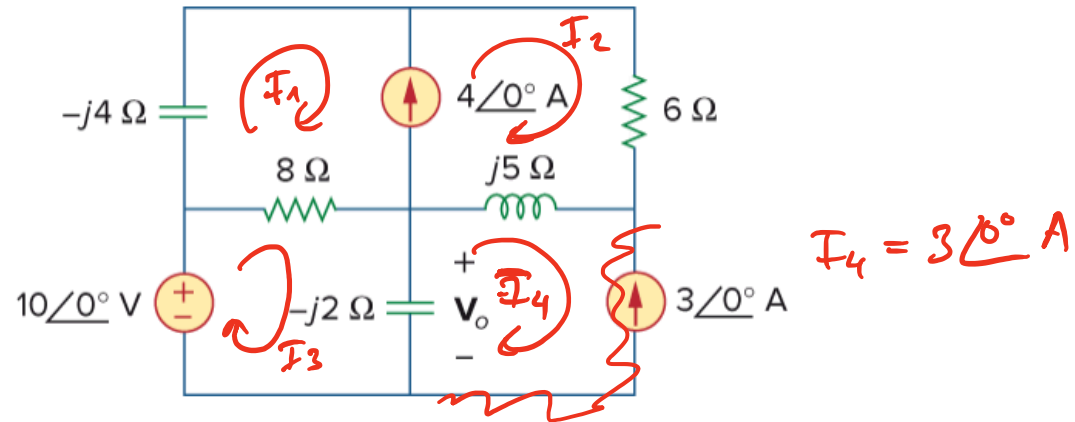
Example 10.4

Solve for V_o in the circuit of Fig. 10.9 using mesh analysis.




Source transformations

$$\mathbf{V}_s = \mathbf{Z}_s \mathbf{I}_s \quad \Leftrightarrow \quad \mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}_s}$$


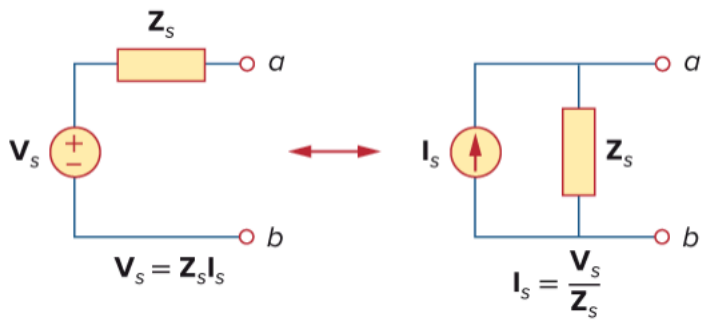


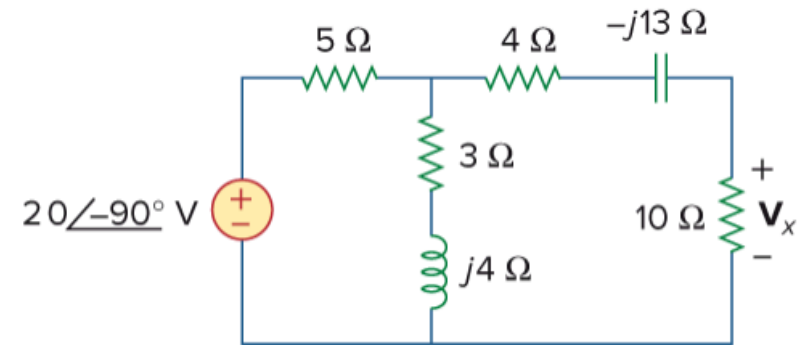Example 10.7

Calculate V_x in the circuit of **Fig. 10.17** using the method of source transformation.




Thevenin and Norton equivalents

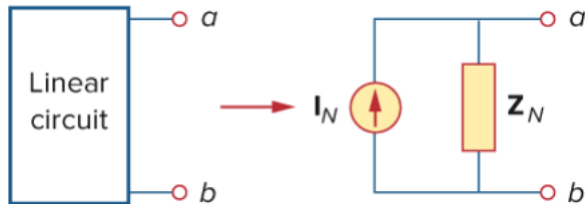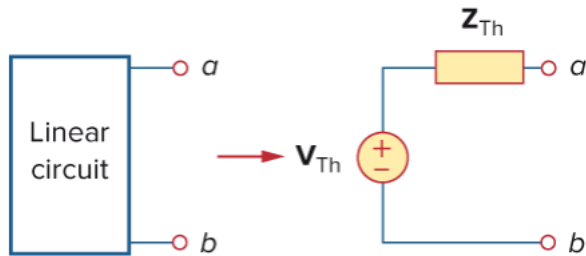

$$V_{Th} = Z_N I_N, \quad Z_{Th} = Z_N$$



Example 10.8

Obtain the Thevenin equivalent at terminals a - b of the circuit in **Fig. 10.22**.

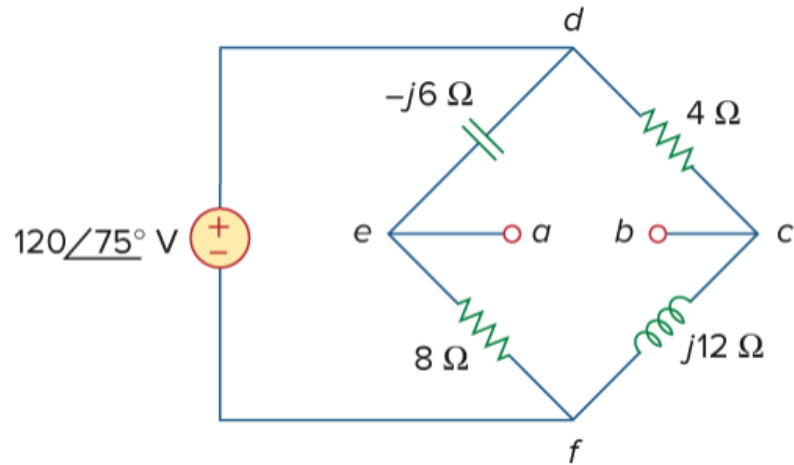



Example 10.11

Determine $v_o(t)$ for the op amp circuit in **Fig. 10.31(a)** if $v_s = 3 \cos 1000t$ V.

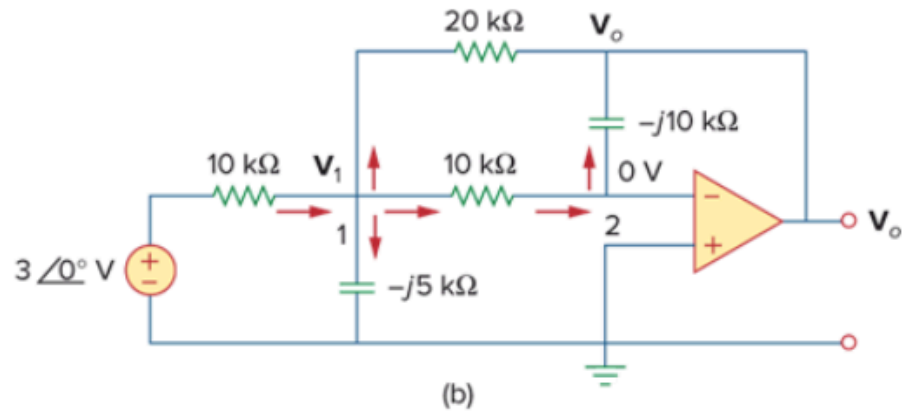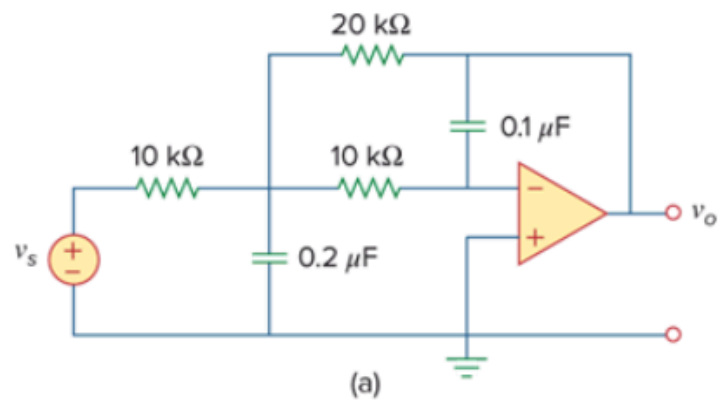

Example 10.11


Determine $v_o(t)$ for the op amp circuit in **Fig. 10.31(a)** if $v_s = 3 \cos 1000t$ V.

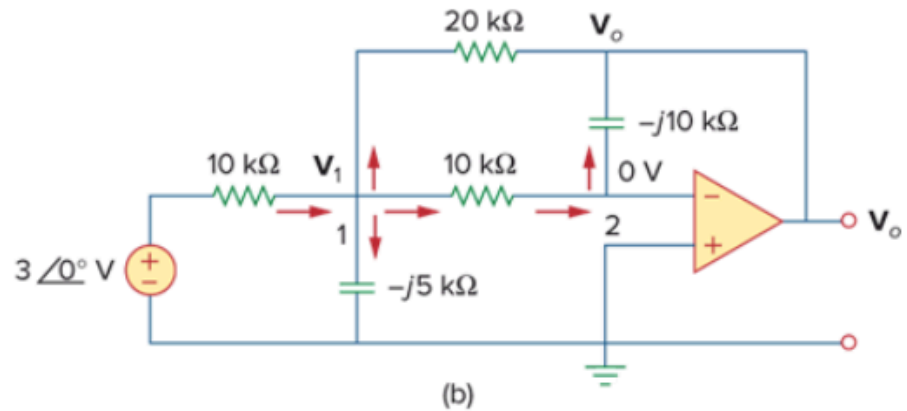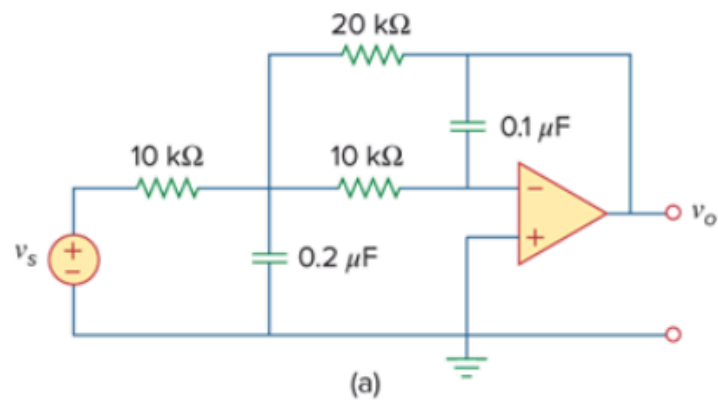

Example 10.12

Compute the closed-loop gain and phase shift for the circuit in **Fig. 10.33**.


Assume that $R_1 = R_2 = 10\text{ k}\Omega$, $C_1 = 2\text{ }\mu\text{F}$, $C_2 = 1\text{ }\mu\text{F}$, and $\omega = 200\text{ rad/s}$.

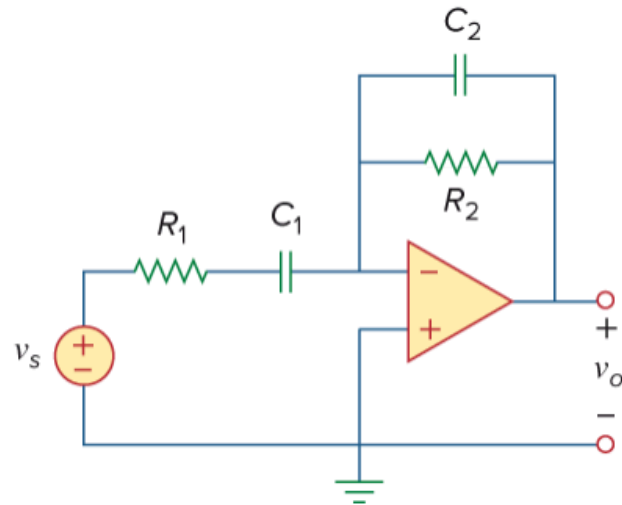

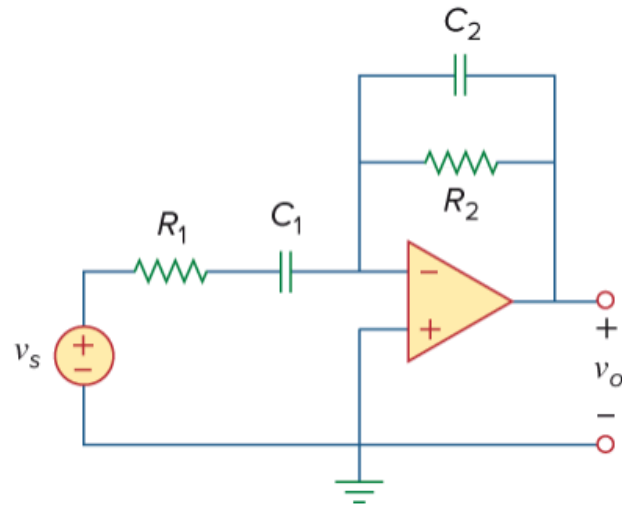Example 10.12


Compute the closed-loop gain and phase shift for the circuit in **Fig. 10.33**.

Assume that $R_1 = R_2 = 10\text{ k}\Omega$, $C_1 = 2\text{ }\mu\text{F}$, $C_2 = 1\text{ }\mu\text{F}$, and $\omega = 200\text{ rad/s}$.



Oscillators

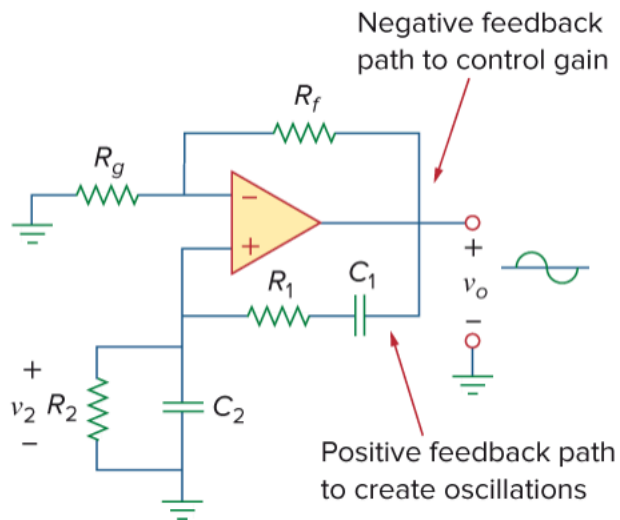An **oscillator** is a circuit that produces an ac waveform as output when powered by a dc input.




In order for sine wave oscillators to sustain oscillations, they must meet the *Barkhausen criteria*:

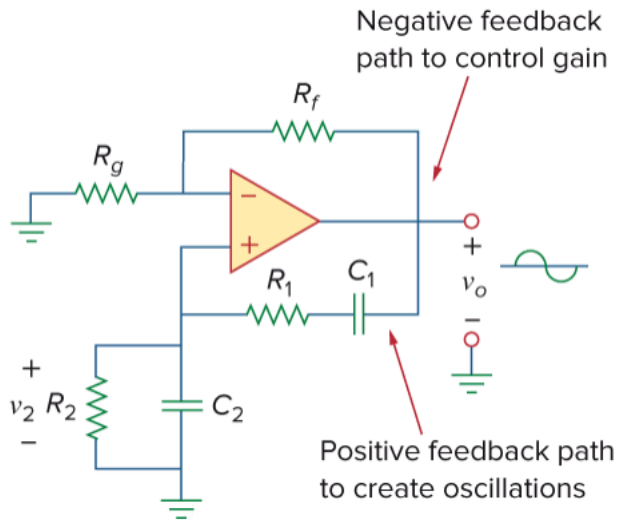1. The overall gain of the oscillator must be unity or greater. Therefore, losses must be compensated for by an amplifying device.
2. The overall phase shift (from input to output and back to the input) must be zero.

Oscillators

An **oscillator** is a circuit that produces an ac waveform as output when powered by a dc input.




$$\mathbf{Z}_s = R_1 + \frac{1}{j\omega C_1} = R_1 - \frac{j}{\omega C_1}$$

$$\mathbf{Z}_p = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

Oscillators

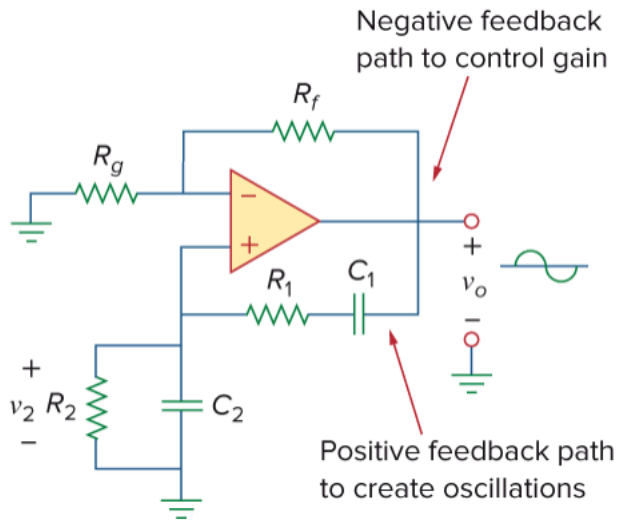An **oscillator** is a circuit that produces an ac waveform as output when powered by a dc input.



$$Z_s = R_1 + \frac{1}{j\omega C_1} = R_1 - \frac{j}{\omega C_1}$$


$$Z_p = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$\frac{V_2}{V_o} = \frac{Z_p}{Z_s + Z_p}$$

$$\begin{aligned} \frac{V_2}{V_o} &= \frac{R_2}{R_2 + \left(R_1 - \frac{j}{\omega C_1}\right)(1 + j\omega R_2 C_2)} \\ &= \frac{\omega R_2 C_1}{\omega(R_2 C_1 + R_1 C_1 + R_2 C_2) + j(\omega^2 R_1 C_1 R_2 C_2 - 1)} \end{aligned}$$

Oscillators

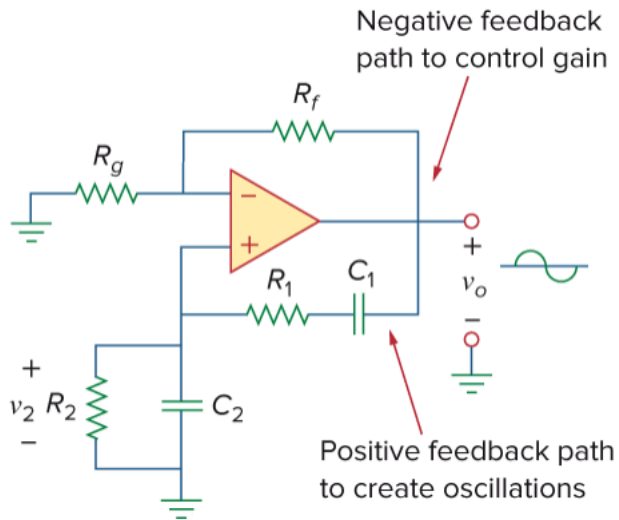An **oscillator** is a circuit that produces an ac waveform as output when powered by a dc input.



$$\frac{V_2}{V_o} = \frac{R_2}{R_2 + \left(R_1 - \frac{j}{\omega C_1}\right)(1 + j\omega R_2 C_2)}$$

$$= \frac{\omega R_2 C_1}{\omega(R_2 C_1 + R_1 C_1 + R_2 C_2) + j(\omega^2 R_1 C_1 R_2 C_2 - 1)}$$


$$\omega_o^2 R_1 C_1 R_2 C_2 - 1 = 0$$

$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\omega_o = \frac{1}{RC} = 2\pi f_o$$

Oscillators

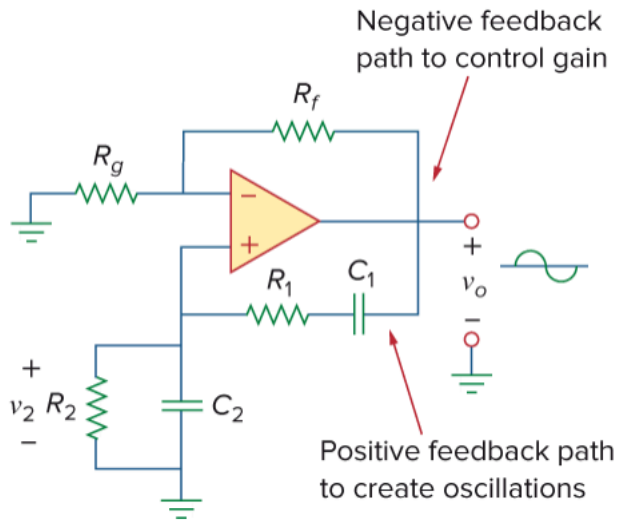An **oscillator** is a circuit that produces an ac waveform as output when powered by a dc input.



$$\omega_o = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\omega_o = \frac{1}{RC} = 2\pi f_o$$

$$\frac{V_2}{V_o} = \frac{1}{3}$$

$$\frac{V_o}{V_2} = 1 + \frac{R_f}{R_g} = 3$$

$$R_f = 2R_g$$