

EK 307: Electric Circuits

Fall 2017

Lecture 11

Oct 12, 2017

Prof. Miloš Popović

Department of Electrical and Computer Engineering





Boston University

Administrivia

- Homework 3 back today (also HW1,2)
- Regrade HW2 after midterm
 - Posting corrected Problem Set and Solution online
- Midterm Exam #1: in class, Tuesday, Oct 17
 - Covers Ch 1 to 4, Chap 5.1-5.5, 5.7-5.8
 - Closed book, closed notes.
 - Single page of notes (1 side), handheld calculator

Lecture 10: Last time


1. Review op-amp (non-ideal, ideal)
2. Inverting amplifier
 - a. Trans-resistance amp
3. Non-inverting amplifier
4. Equivalent ccts
5. Voltage follower
6. Cascaded op-amp circuits

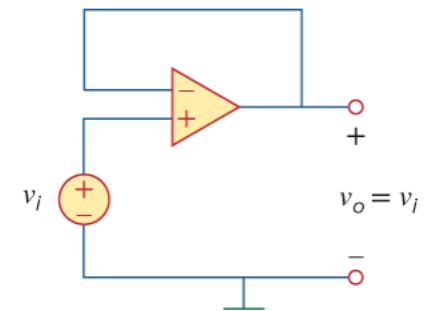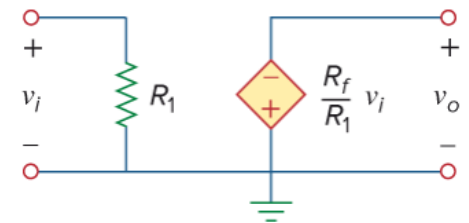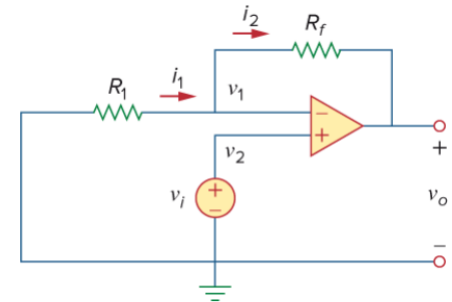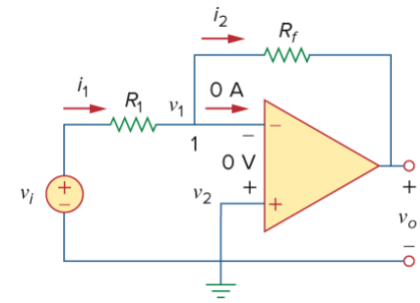

Lecture 10: Today

- 1. Review opamp**
- 2. DAC on the homework**
- 3. Cascading Op Amps (continued)**
- 4. Summing amplifiers**
- 5. Differencing amplifiers**
- 6. Applications: DAC, instrumentation amp**

Review of the op-amps


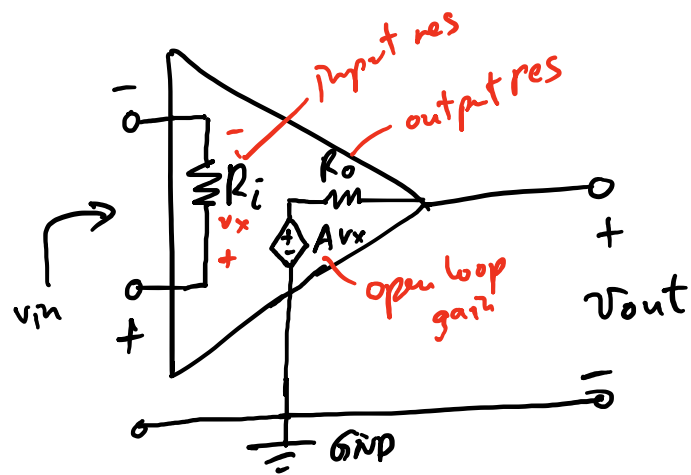


non-ideal opamp


$$A = \infty$$

$$R_i = \infty$$




$$R_o = 0$$

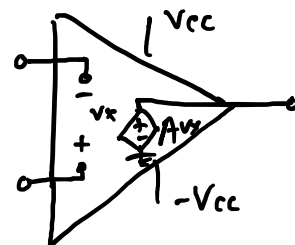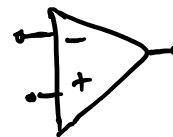

ideal



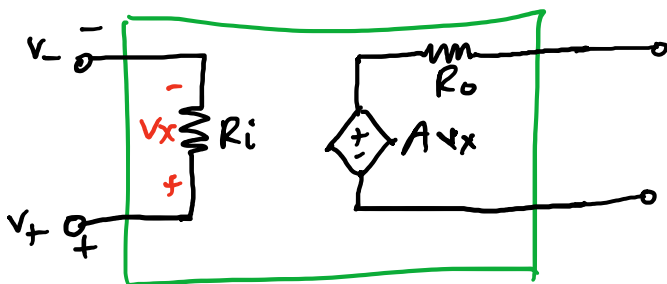


$$v_x = v_+ - v_-$$

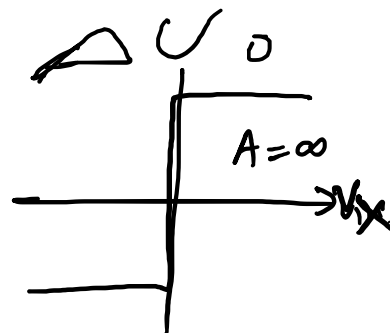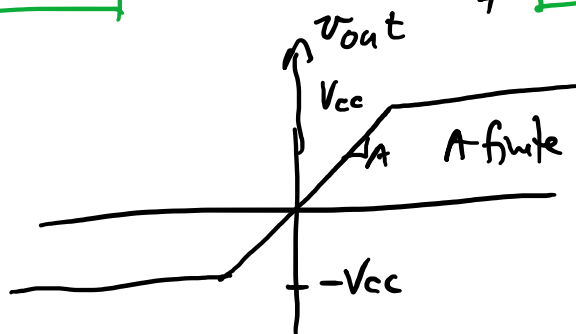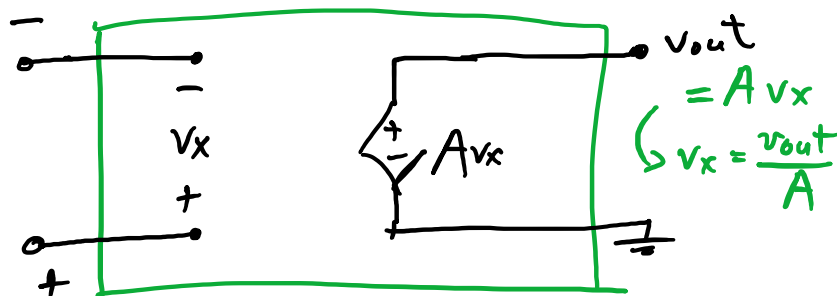

Review

Examples

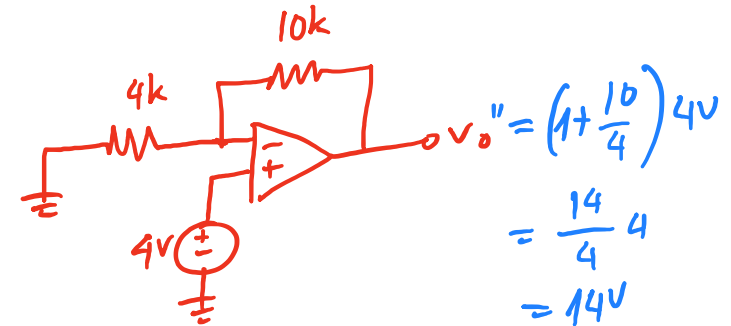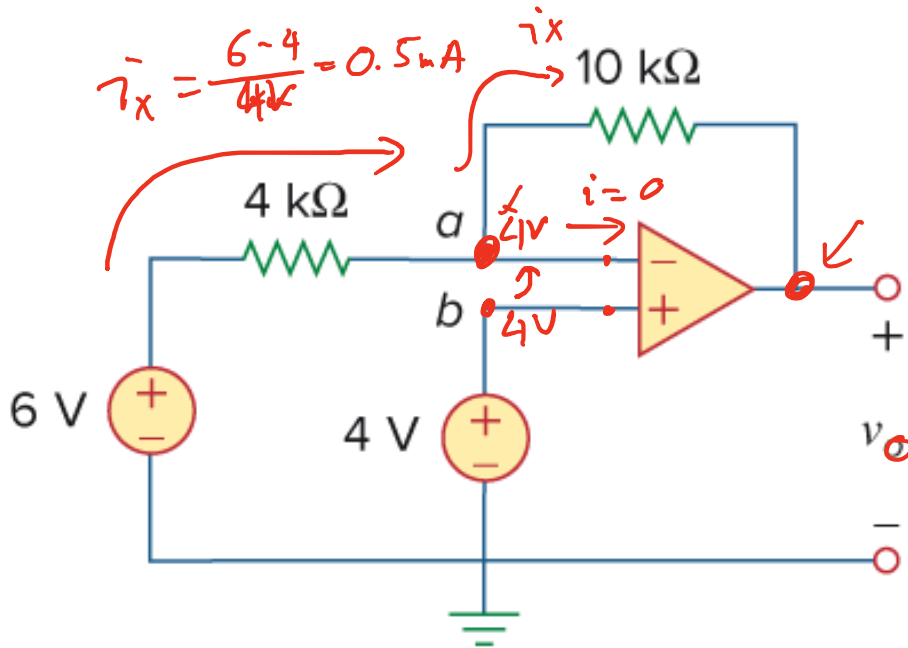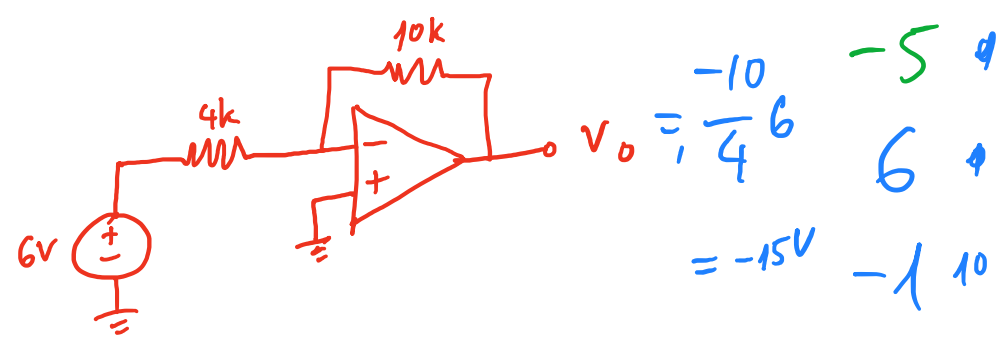

$$V_o = V_{b'} + V_{b''} = -1V$$

$$i_x = \frac{4V - V_o}{10k} = 0.5 \mu A$$


$$\Rightarrow 4V - V_o = 5V$$

$$-1V = V_o$$

Example (design 2)

 ~~$R_1 = 10 \text{ k}\Omega$ and $R_3 = 20 \text{ k}\Omega$ or $R_1 = R_3 = 10 \text{ k}\Omega$.~~


What does this do?

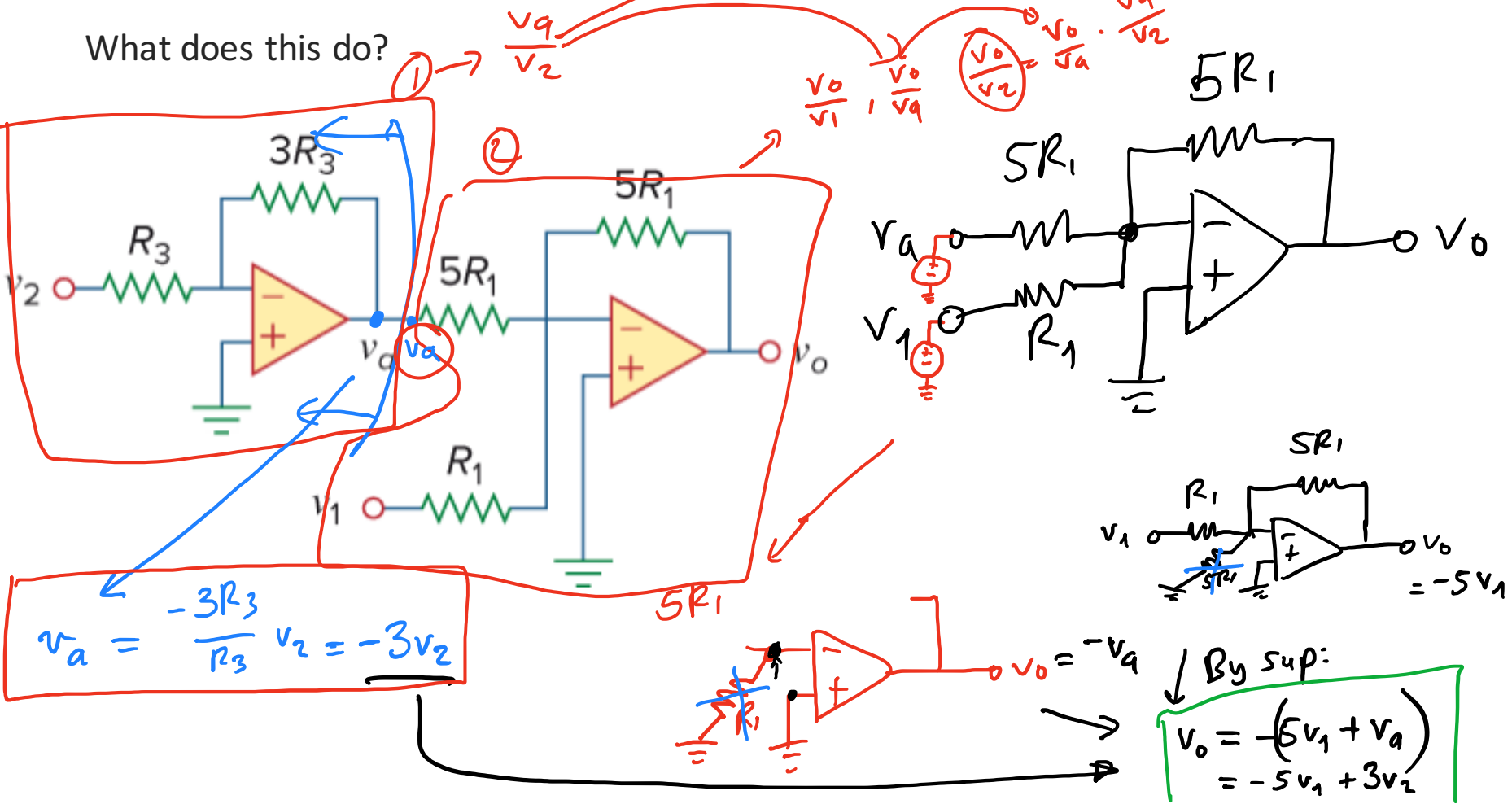

Example (design 2)


$R_1 = 10 \text{ k}\Omega$ and $R_3 = 20 \text{ k}\Omega$ or $R_1 = R_3 = 10 \text{ k}\Omega$.

What does this do?

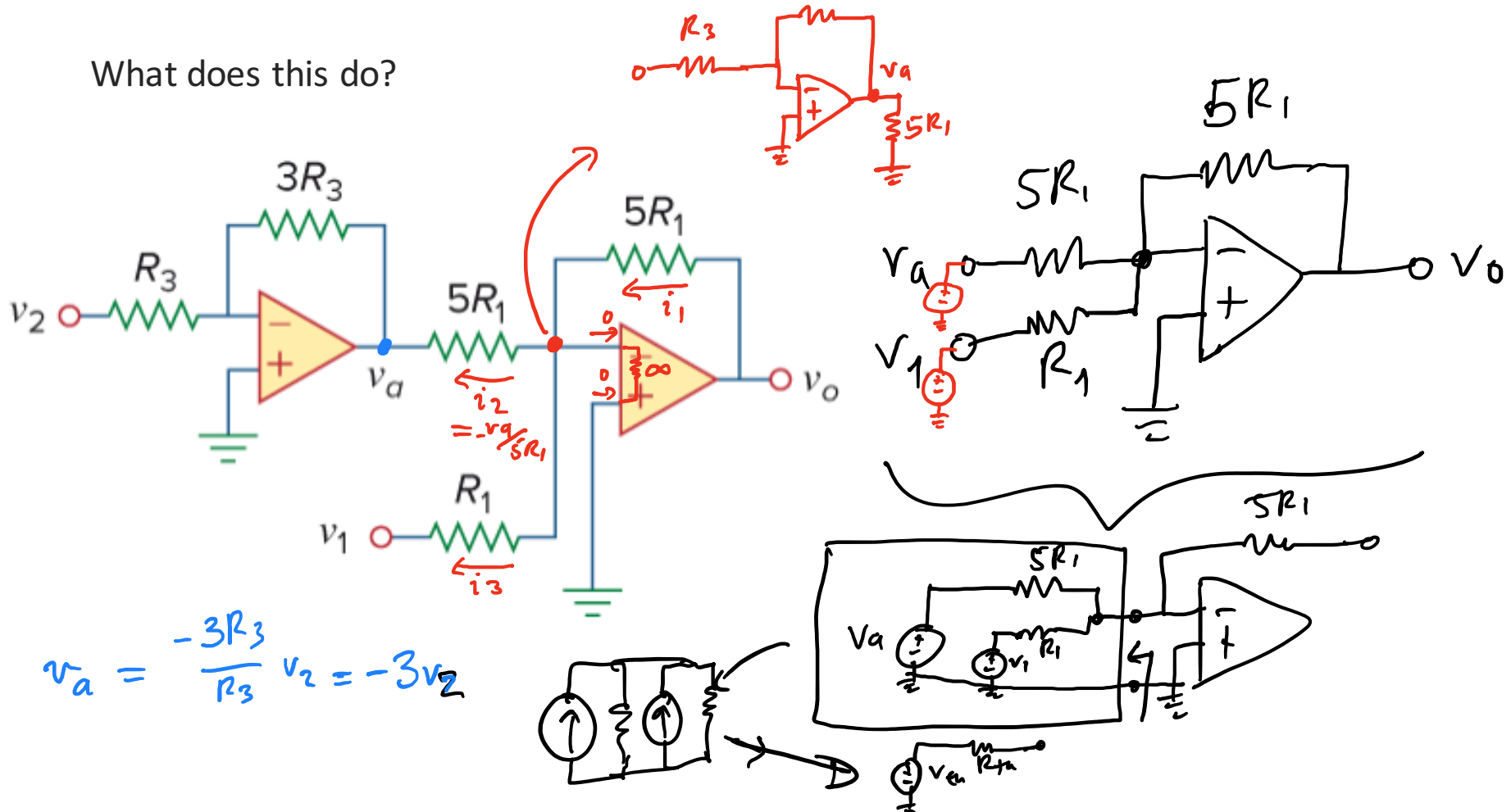

$$v_a = -\frac{3R_3}{R_3} v_2 = -3v_2$$

Cascading Op-Amp Circuits



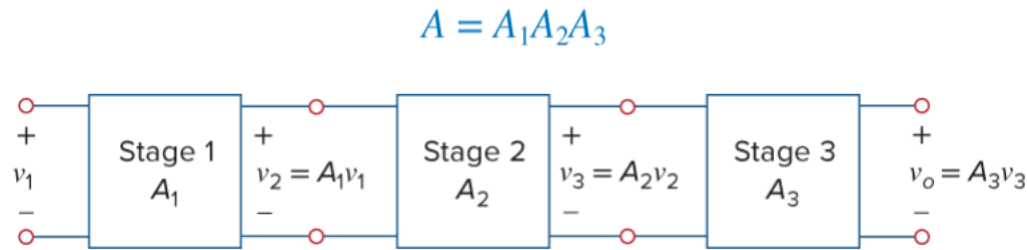


Op amp circuits have the advantage that they can be cascaded without changing their input-output relationships.

This is due to the fact that each (ideal) op amp circuit has infinite input resistance and zero output resistance.

Cascading Op-Amp Circuits

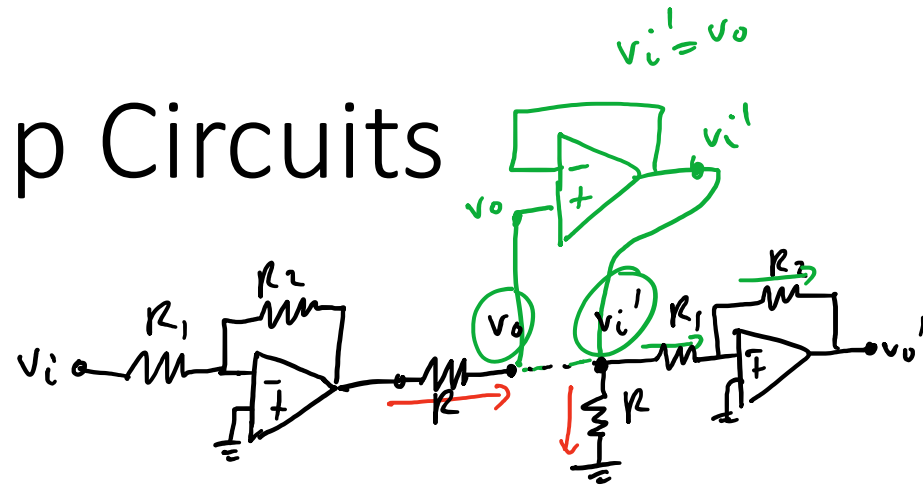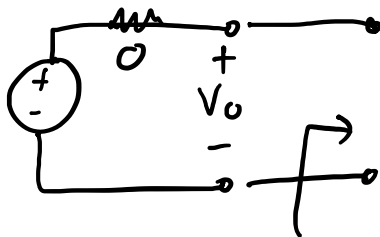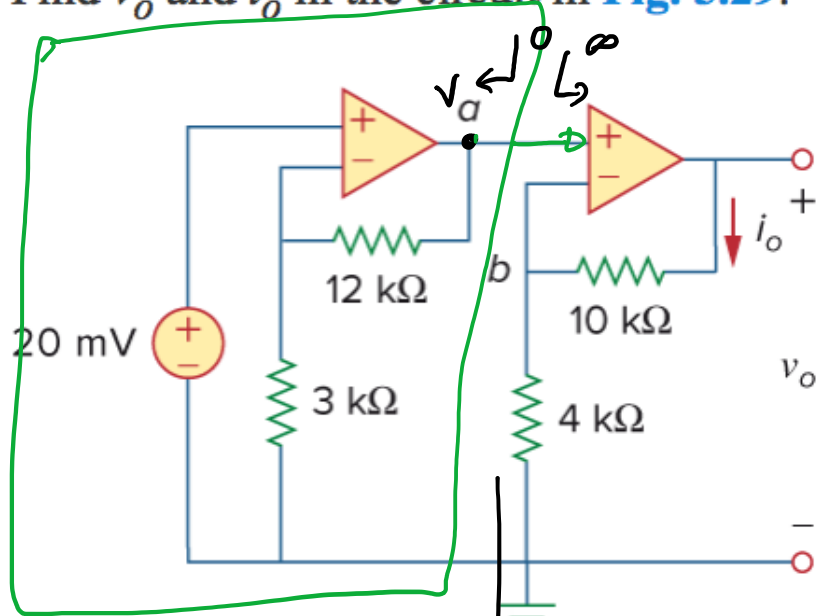Find v_o and i_o in the circuit in Fig. 5.29.



$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

$$\frac{v_o'}{v_i'} = \frac{-R_2}{R_1}$$

$$v_a = \left(1 + \frac{12k}{3k}\right) 20mV$$


$$v_o = \left(1 + \frac{10k}{4k}\right) v_a = \left(1 + \frac{10}{4}\right) \left(1 + \frac{12}{3}\right) 20mV$$

$$= 3.5 (5) 20mV$$

$$= 0.35V$$

Summing Amplifier

Summing Amplifier

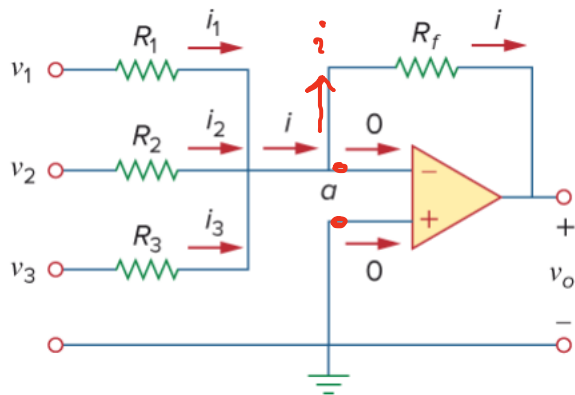

$$i = i_1 + i_2 + i_3$$

$$i_3 = \frac{v_3}{R_3}$$

$$i_2 = \frac{v_2}{R_2}$$

$$i_1 = \frac{v_1}{R_1}$$


$$i = i_1 + i_2 + i_3$$
$$= \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3}$$

$$(0 - v_o) = i R_f$$

$$-v_o = \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right) R_f$$

$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right)$$

Summing Amplifier

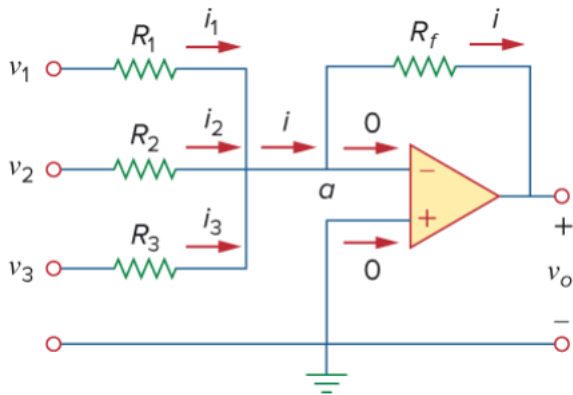

$$i = i_1 + i_2 + i_3$$

$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3\right)$$

$$R_1 = R_2 = R_3 = R$$

$$v_o = -\frac{R_f}{R} (v_1 + v_2 + v_3)$$

Example

Calculate v_o and i_o in the op amp circuit in Fig. 5.22.

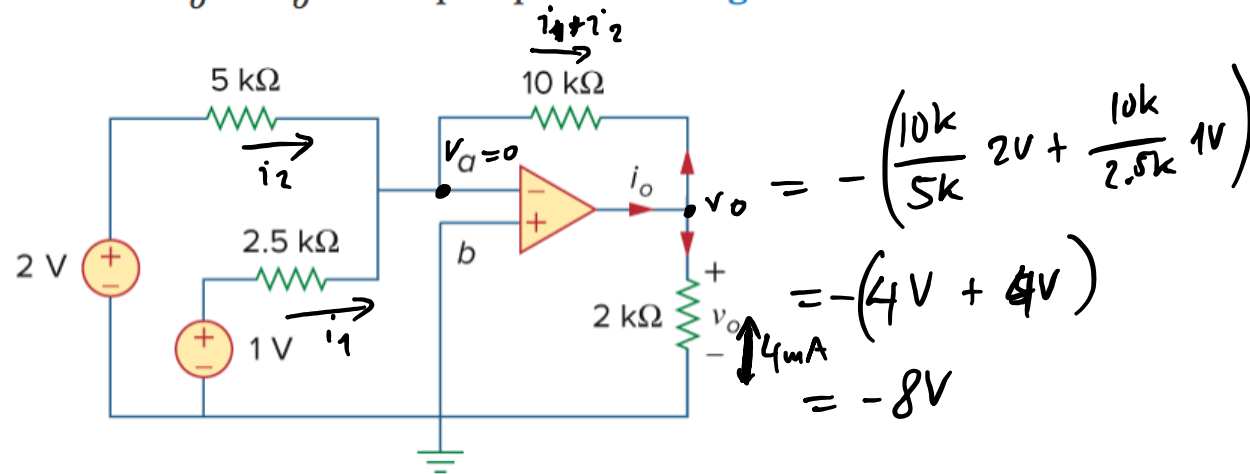


Figure 5.22 For Example 5.6.

Example (students)

Find v_o and i_o in the op amp circuit shown in **Fig. 5.23**.


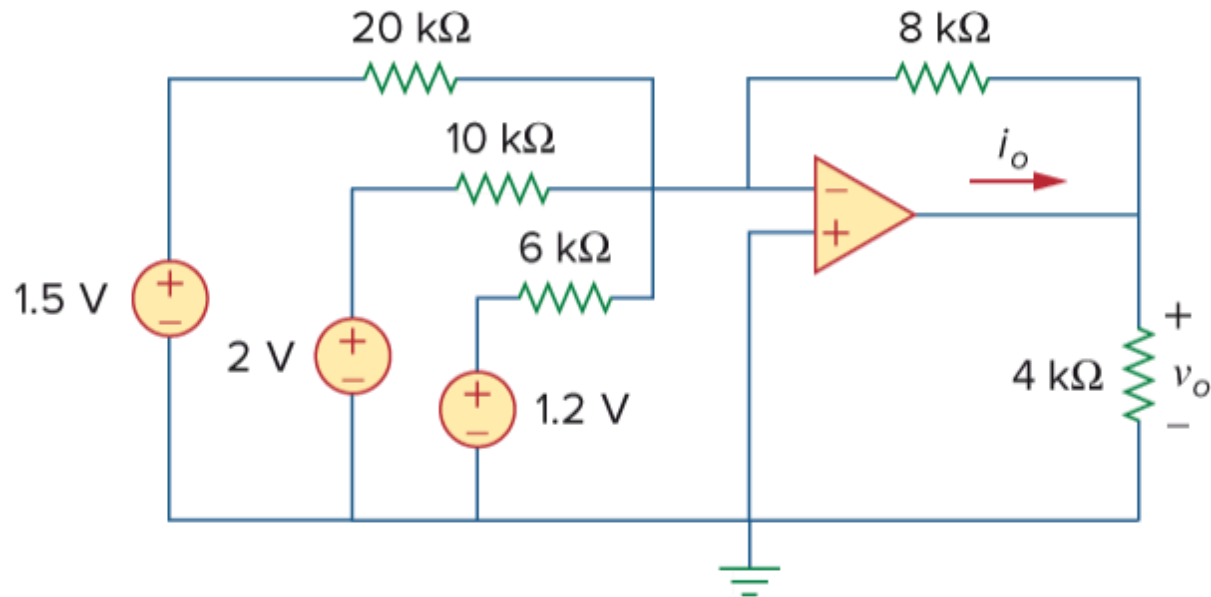


Figure 5.23 For **Practice Prob. 5.6**.

$$v_o = \frac{-3.8 \text{ V} - 19 \text{ V}}{5} \checkmark$$

Difference amplifier





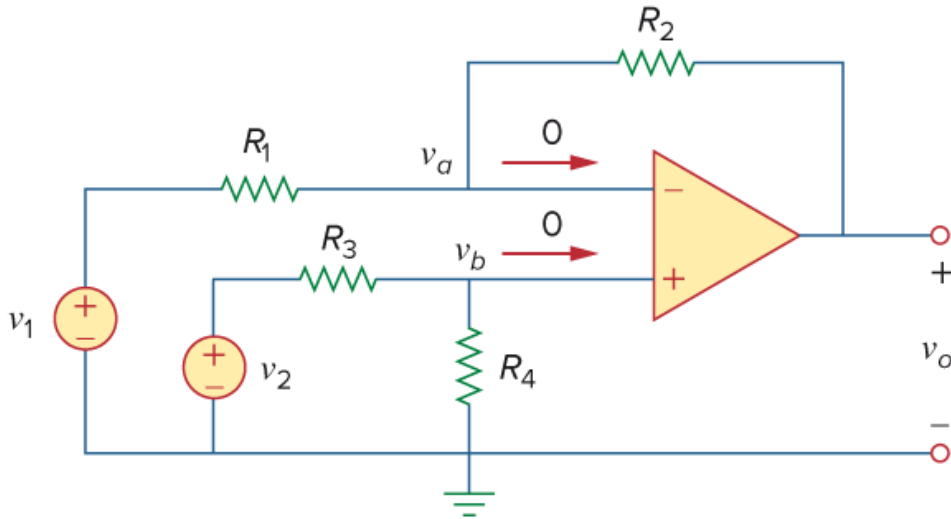


Goal: $v_o = \frac{R_2}{R_1}(v_2 - v_1)$

Together:

$$v_o = -\frac{R_2}{R_1} v_1 + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2$$
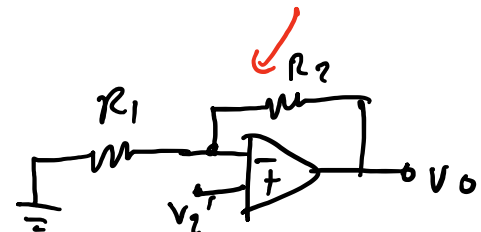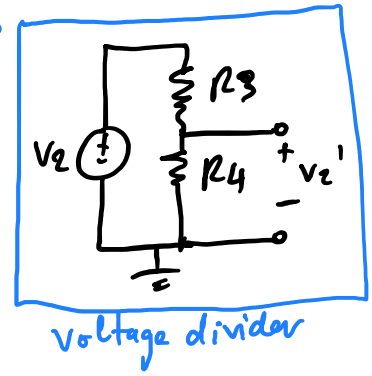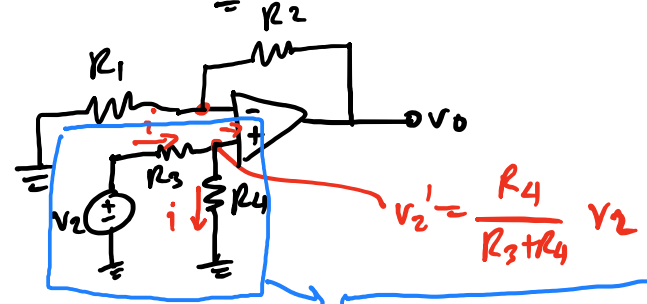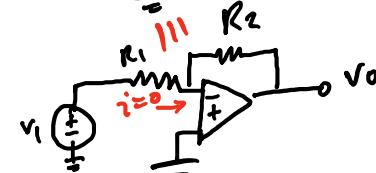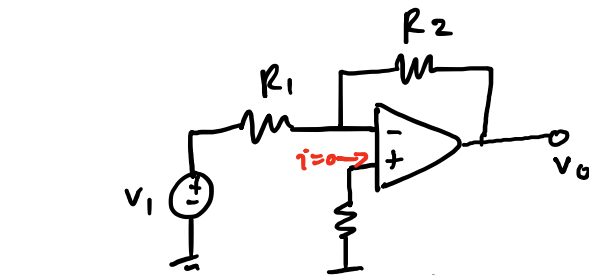
$$= -\frac{R_2}{R_1} v_1 + \left(\frac{R_2}{R_1}\right) v_2$$



$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_2'$$


$$= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2$$

$$\frac{R_1 + R_2}{R_1} \frac{R_4}{R_3 + R_4} = \frac{R_2}{R_1} \rightarrow (R_1 + R_2) R_4 = (R_3 + R_4) R_2$$

$$R_3 = R_1$$

$$R_4 = R_2$$

Difference amplifier

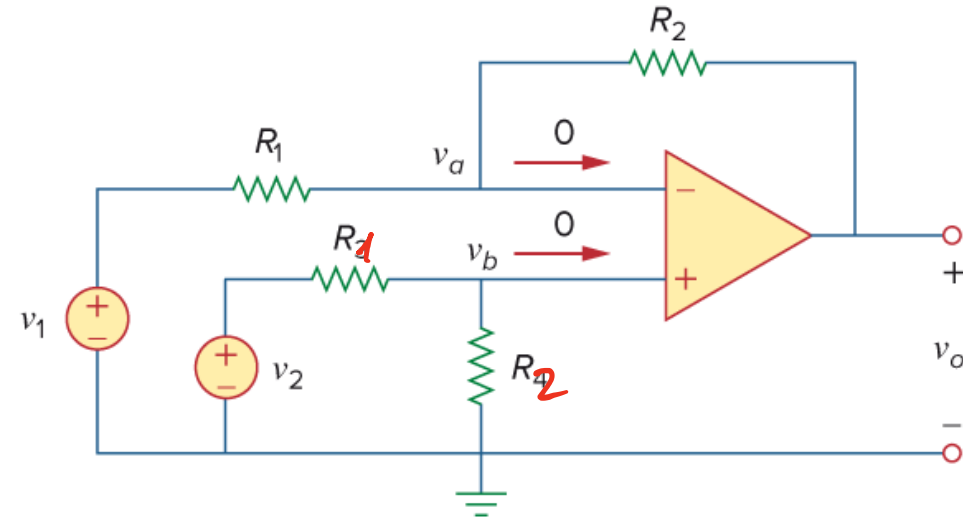

Goal: $v_o = \frac{R_2}{R_1}(v_2 - v_1)$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$v_o = \left(\frac{R_2}{R_1} + 1 \right) \frac{R_4}{R_3 + R_4} v_2 - \frac{R_2}{R_1} v_1$$


Example (students)

Design a differencing amplifier with a gain of 20.

Instrumentation Amplifier

Show that:
$$v_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4} \right) (v_2 - v_1)$$

Discussion: what does this do?

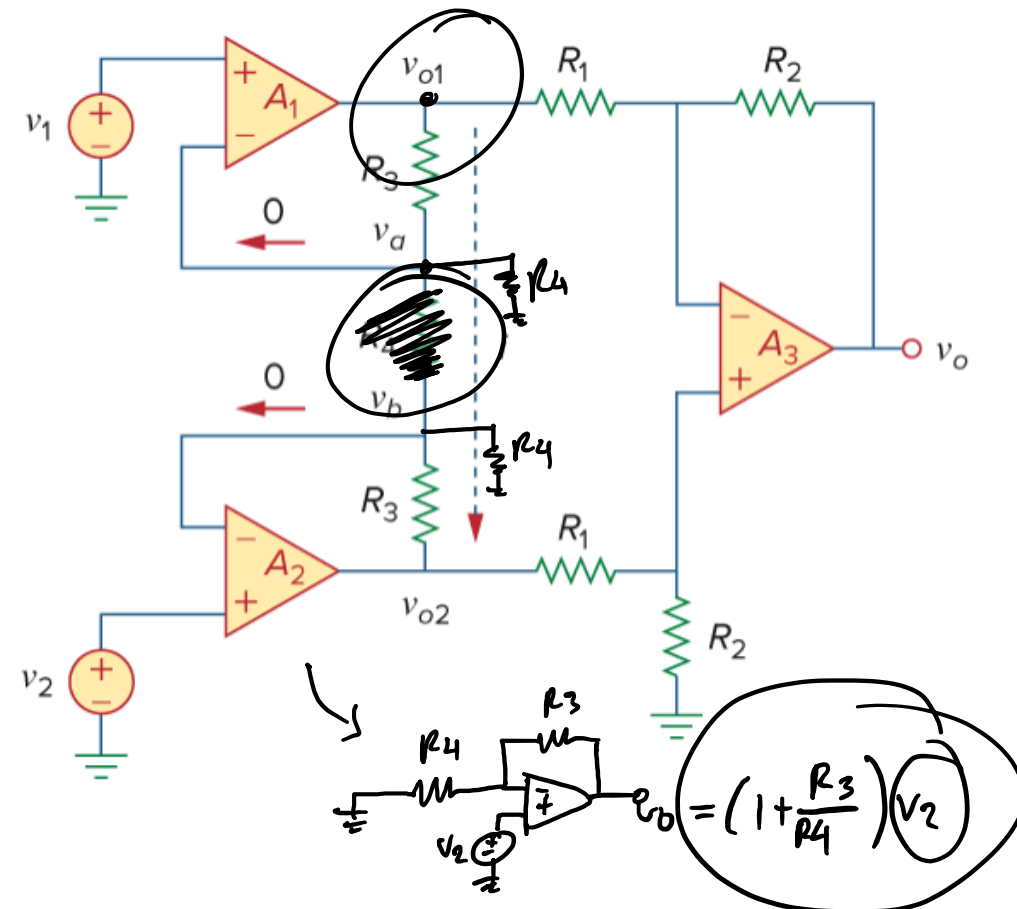

Instrumentation Amplifier



Now that we talked about it, check out:

https://en.wikipedia.org/wiki/Instrumentation_amplifier


Instrumentation Amplifiers

$$v_o = A_v(v_2 - v_1)$$


$$A_v = 1 + \frac{2R}{R_G}$$

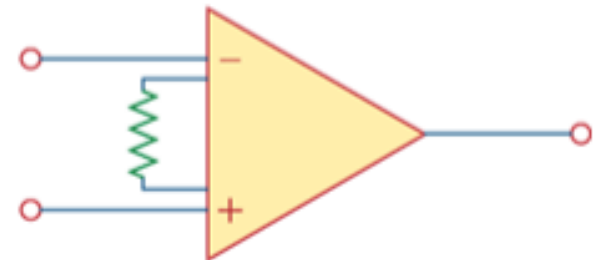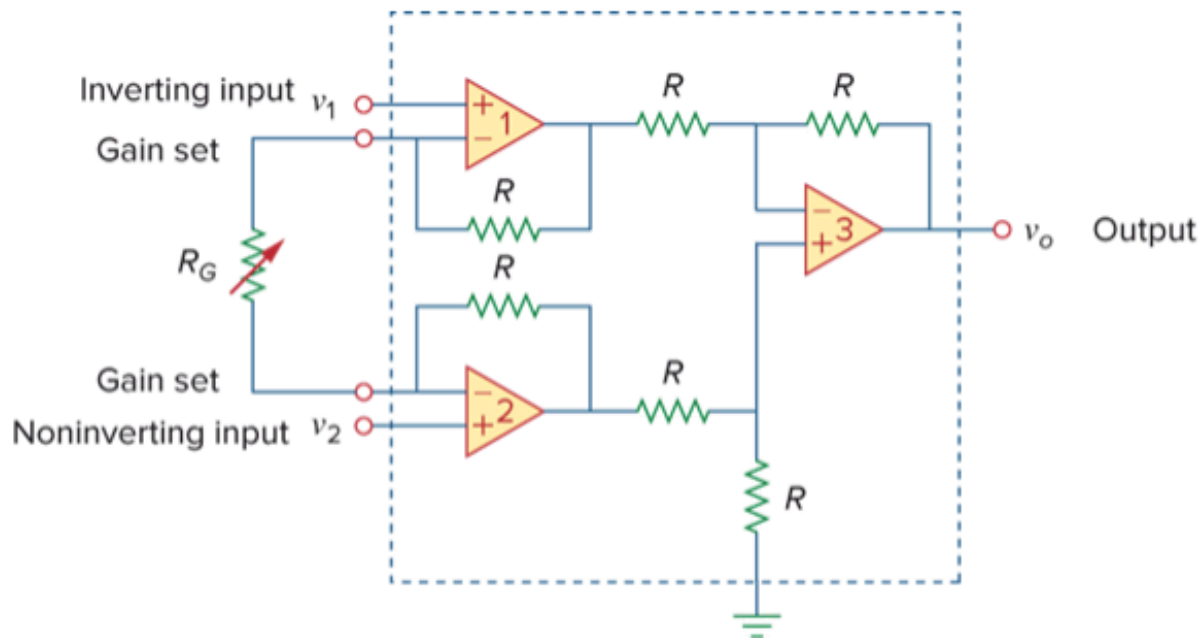


Instrumentation Amplifiers

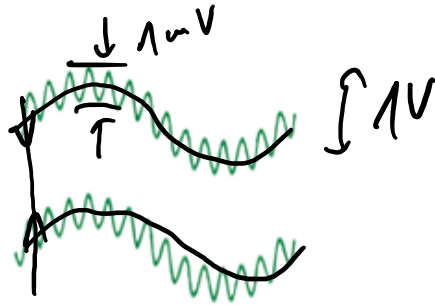

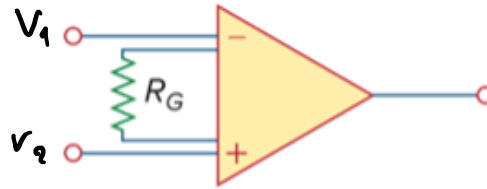Small differential signals riding on larger common-mode signals



Instrumentation amplifier

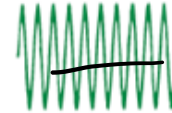

Amplified differential signal, no common-mode signal

