

EK 307: Electric Circuits

Fall 2017

Lecture 14

Oct 26, 2017


Prof. Miloš Popović

Department of Electrical and Computer Engineering

Boston University


Lecture 14: Today

1. Chapter 6: Capacitors

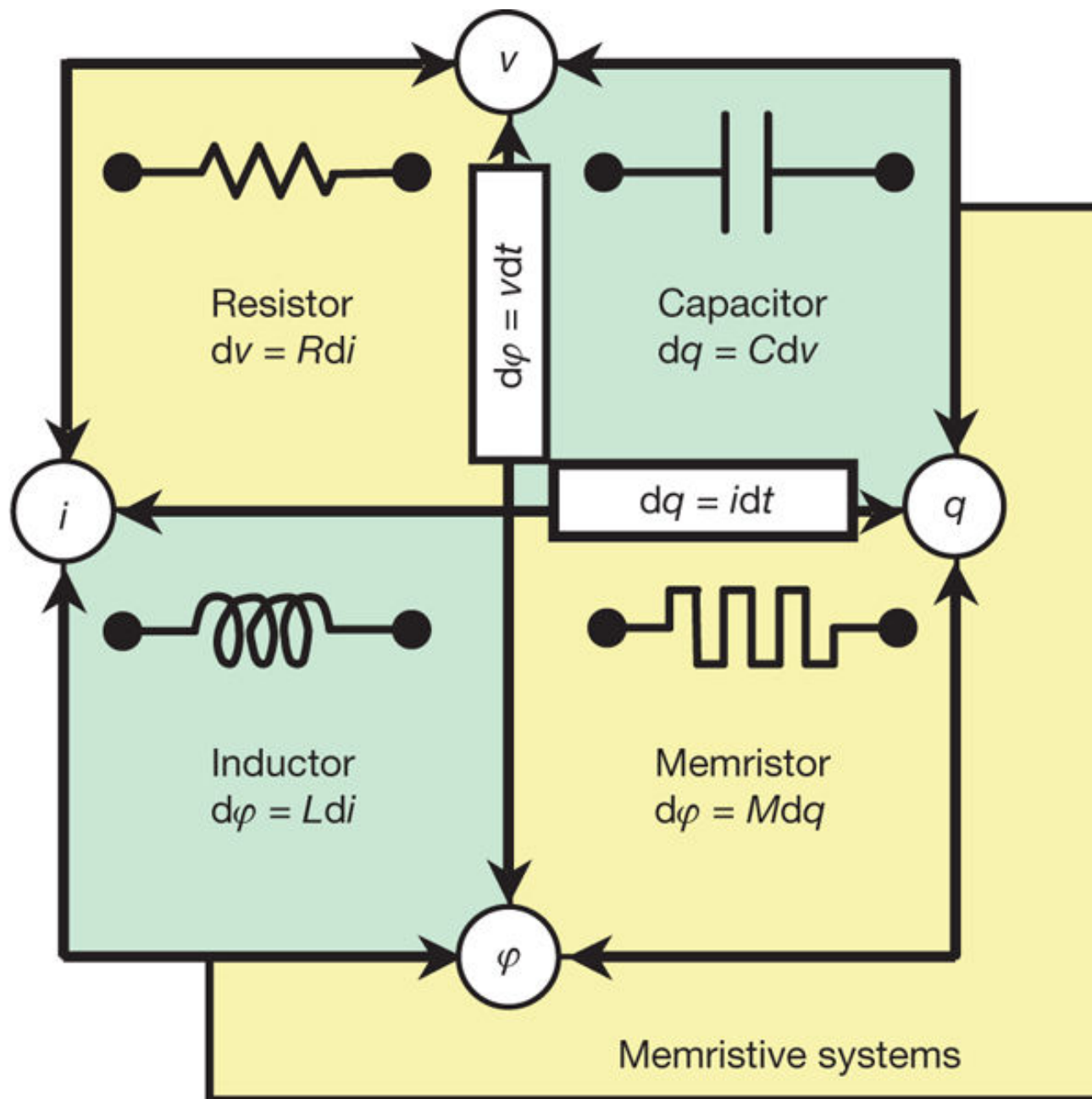


Chapter 6: Capacitors and Inductors

Capacitor

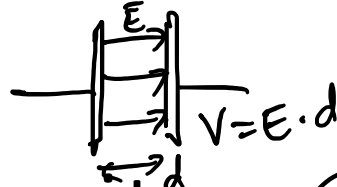

$$\frac{dq}{dt} =$$

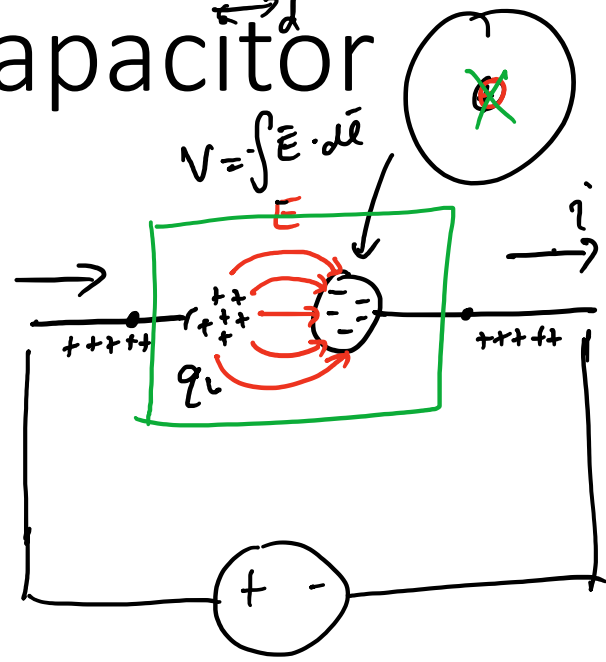

$$V = \int \vec{E} \cdot d\vec{e}$$

$$i = C \frac{dv}{dt}$$

$$\frac{dq}{dt} = C$$



$$Q = C v$$

$$\frac{v}{v} = \frac{C}{C} \rightarrow \frac{C}{C} = 1$$





$$P = vi$$

$$W = vIt$$

$$j =$$

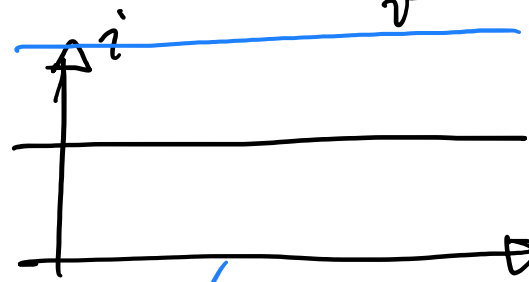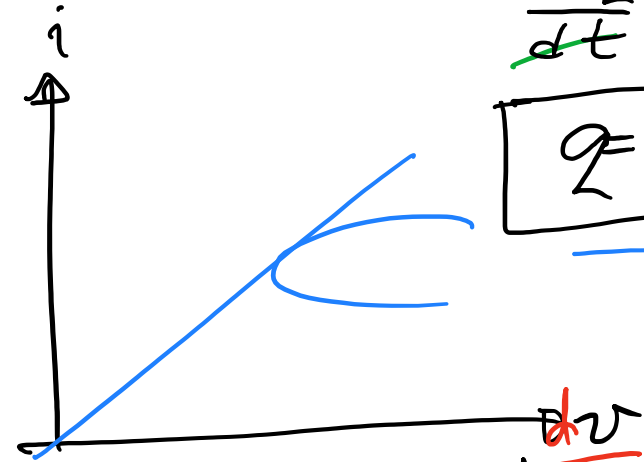



C

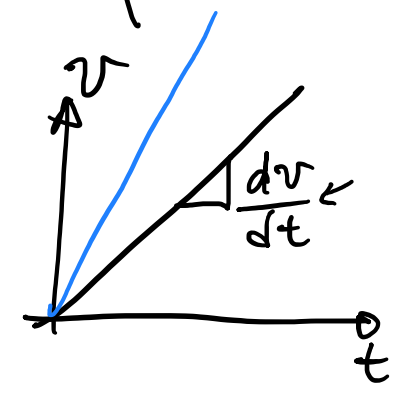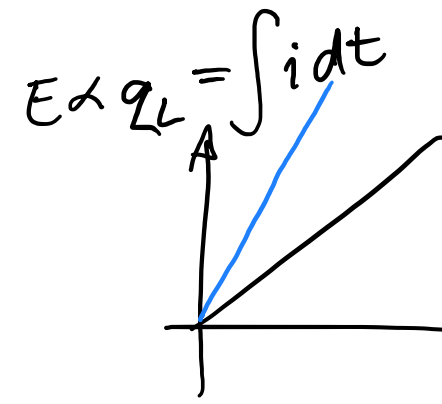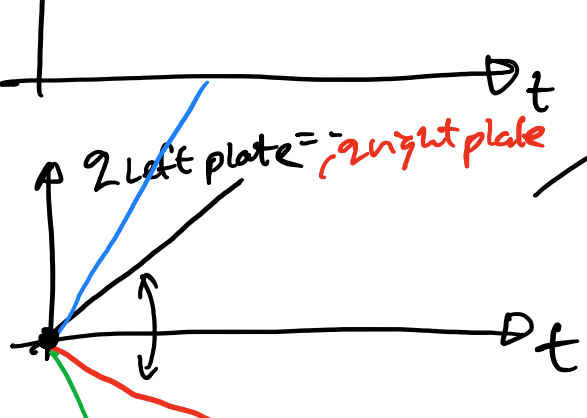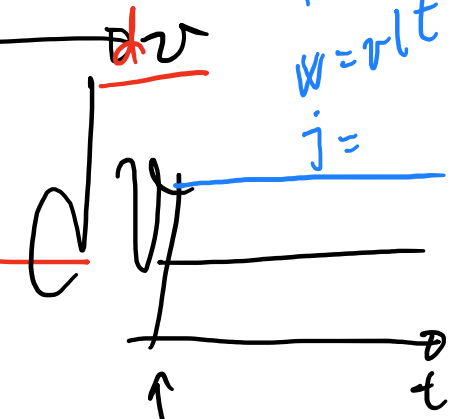

$$E \propto q_L = \int i dt$$

$\rightarrow$

Capacitor

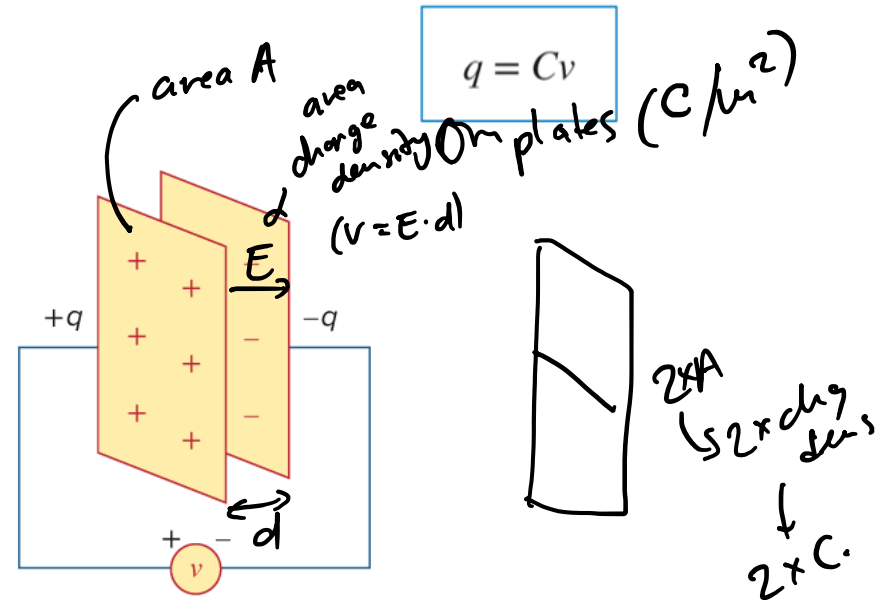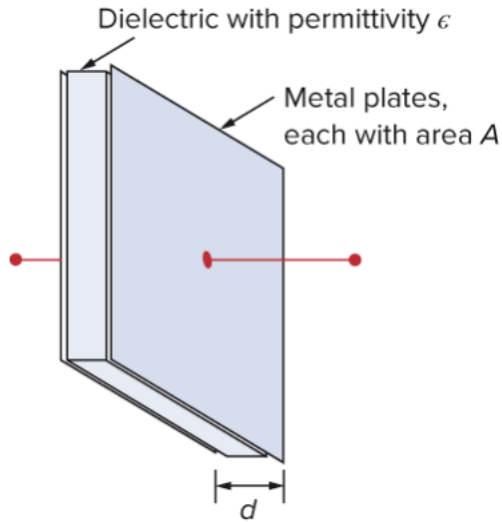

$$C = \frac{\epsilon A}{d}$$

1 Farad = 1 Coulomb/volt



Capacitor

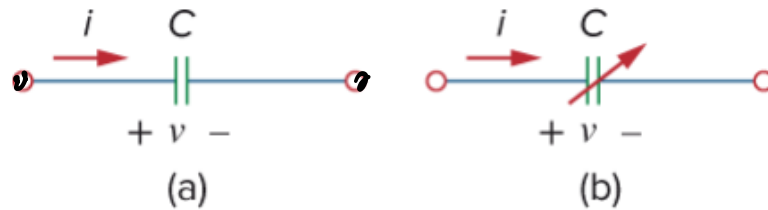






Figure 6.3 Circuit symbols for capacitors: (a) fixed capacitor, (b) variable capacitor.

Capacitor




$$q = Cv$$


$$i = \frac{dq}{dt}$$

$$i = C \frac{dv}{dt}$$

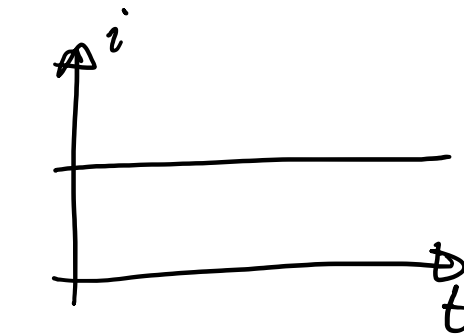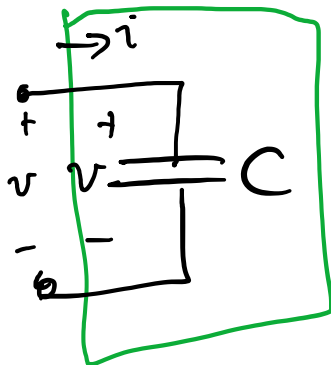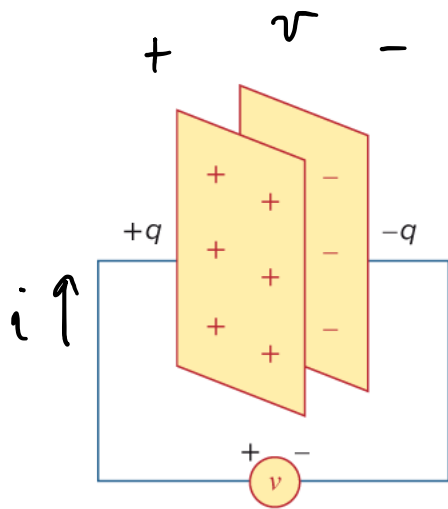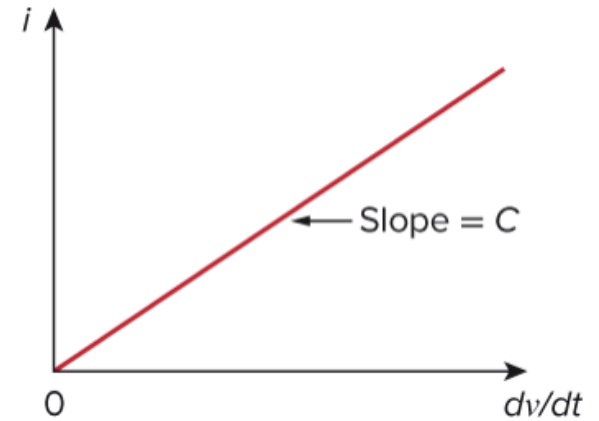


$$p = vi$$

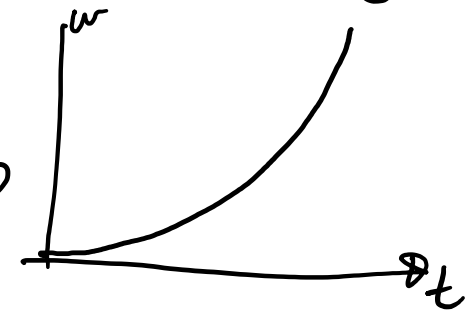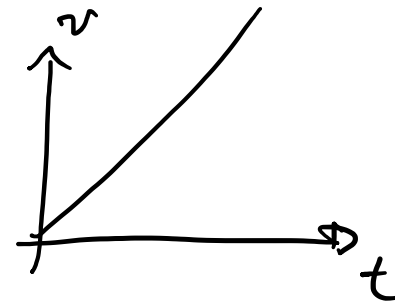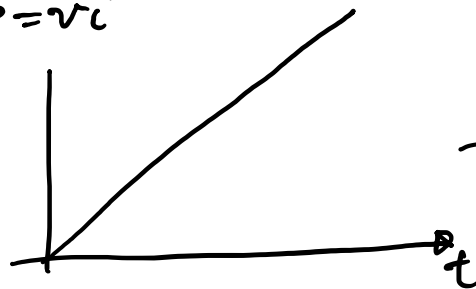


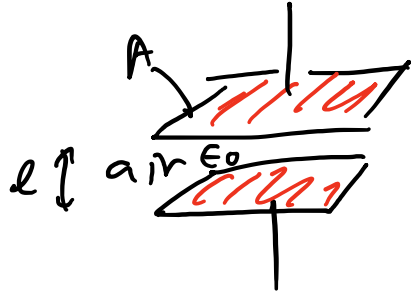

$$C_0 = \frac{\epsilon_0 A}{l}$$

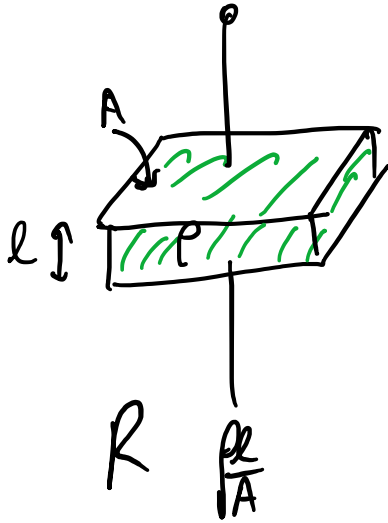
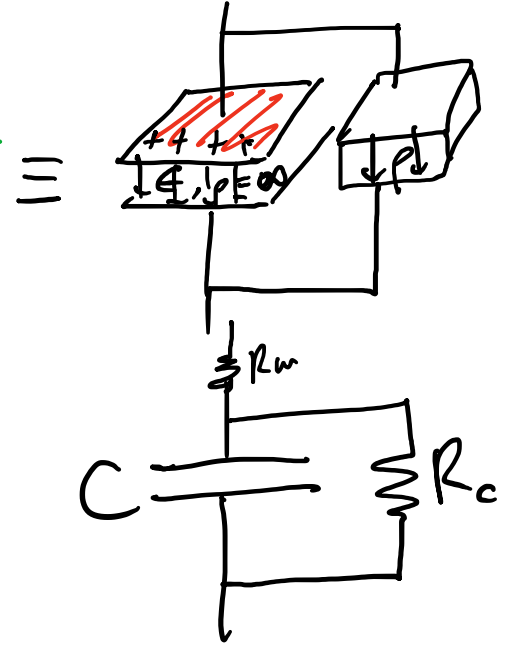
$$C = \frac{\epsilon A}{l}, R = \rho \frac{l}{A}$$




Capacitor

$$i = C \frac{dv}{dt}$$

$$q = Cv$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$
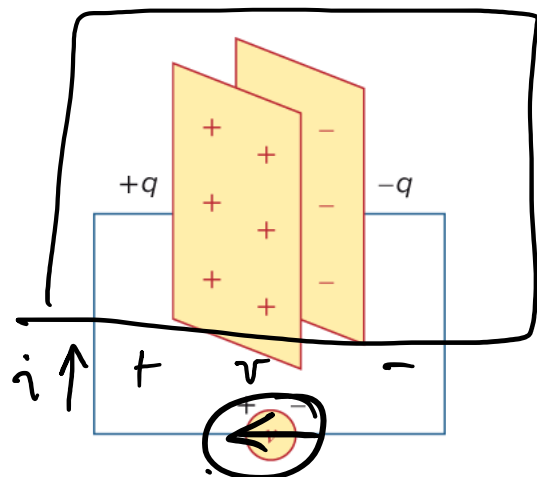
$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$



$$p = vi = Cv \frac{dv}{dt}$$

$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$

$$w = \frac{1}{2} C v^2$$


$$w = \frac{q^2}{2C}$$


$$i = C \frac{dv}{dt}$$

$$p = vi = vC \frac{dv}{dt}$$


$$w_e(t) = \int_0^t p(t') dt' = \int_0^t vC \frac{dv}{dt} dt = C \int_0^t v \frac{dv}{dt} dt = C \frac{1}{2} \int_0^t \left(\frac{d}{dt} v^2 \right) dt = \boxed{}$$
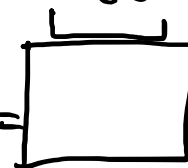
$$\frac{d}{dt} (v(t)^2) = 2v \frac{dv}{dt}$$



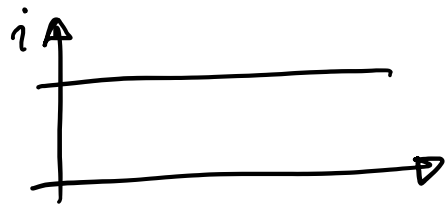

$$q = C \cdot \vartheta$$

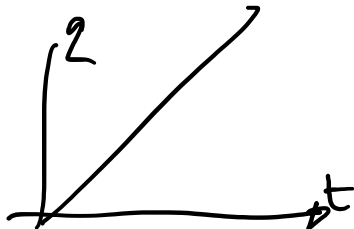

$$w_e = \frac{1}{2} C v^2 = \frac{1}{2} C ($$

$$C q^2 = \frac{1}{2C} (At)^2 = \frac{A^2}{2C} t^2$$




$$i = c \cdot \frac{dq}{dt}$$

$$q = At$$

Properties of a capacitor

1. A capacitor is an open circuit to dc.
2. The voltage on a capacitor cannot change abruptly.

$$i = C \frac{dv}{dt}$$

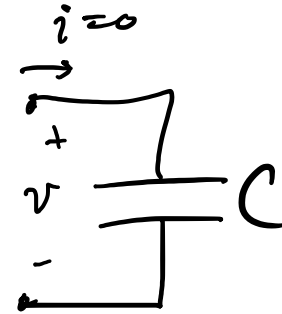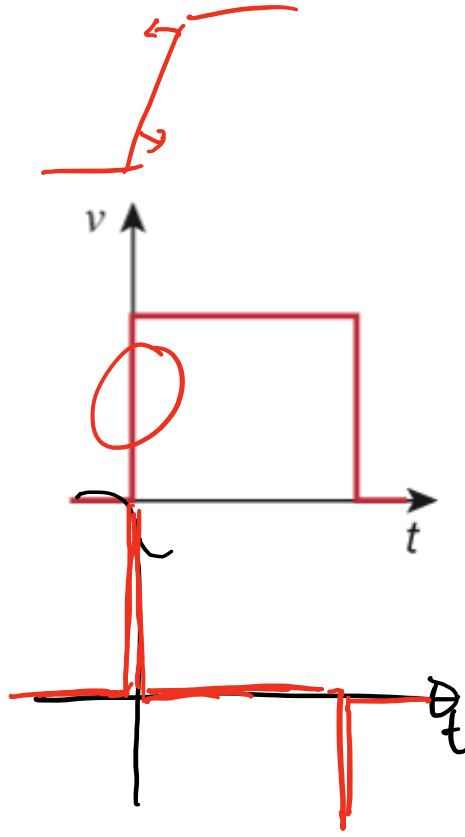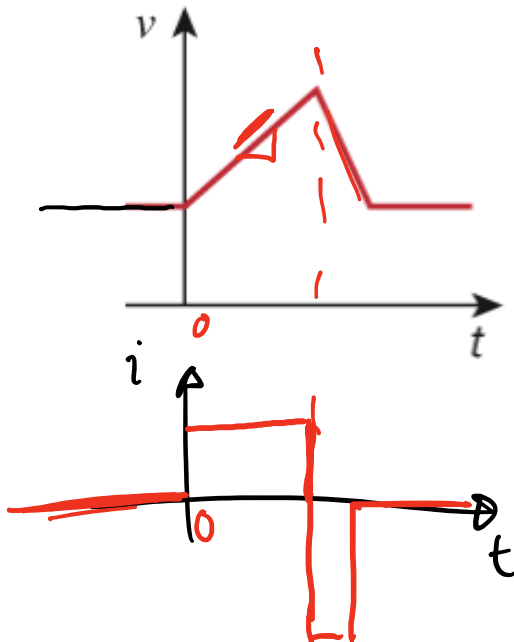




$$i = C \frac{dv}{dt} \rightarrow 0$$

DC: steady state

$$\frac{d}{dt} \Rightarrow 0$$


Properties of a capacitor

1. A capacitor is an open circuit to dc.
2. The voltage on a capacitor cannot change abruptly.
3. The ideal capacitor does not dissipate energy
4. Non-ideal capacitor may have leakage resistance

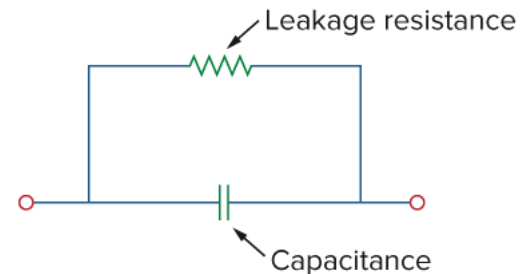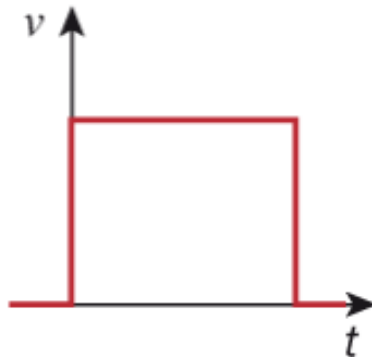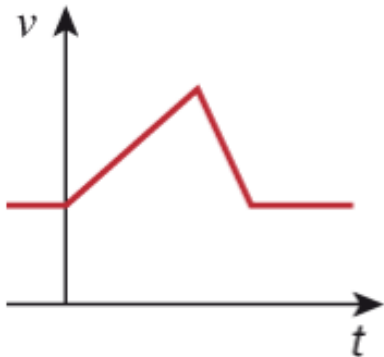

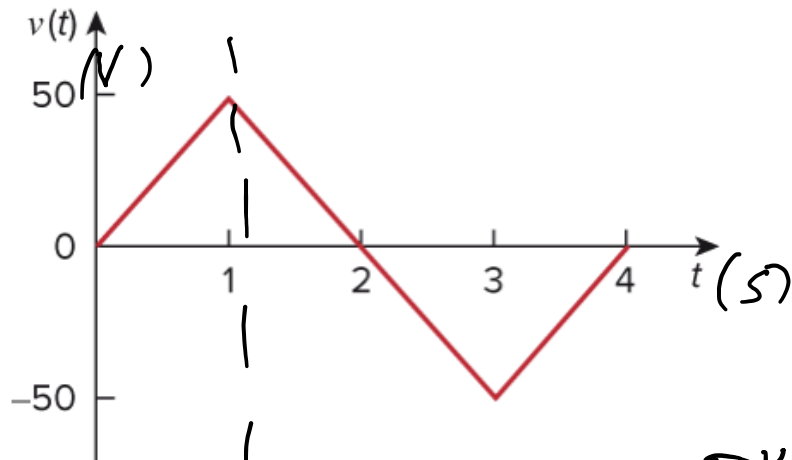Example 6.4

Determine the current through a $200\text{-}\mu\text{F}$ capacitor whose voltage is shown in **Fig. 6.9**.



$$Q = CV$$

$$[1C] = [1F][1V]$$


$$F = \frac{C}{V}$$

$$i = C \frac{dv}{dt} = C \frac{\Delta v}{\Delta t} = \frac{50V}{1s} 200\mu F = 10000 \mu \frac{VF}{s}$$

$$10000 \cdot 10^{-6}$$



$$= 10^{-2} \frac{VF}{s} = 10^{-2} \frac{C}{s} = 10^{-2} A$$

$$= 10 \text{ mA}$$

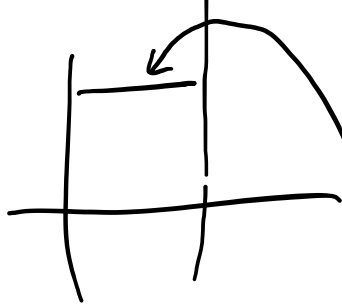

Practice Problem 6.5

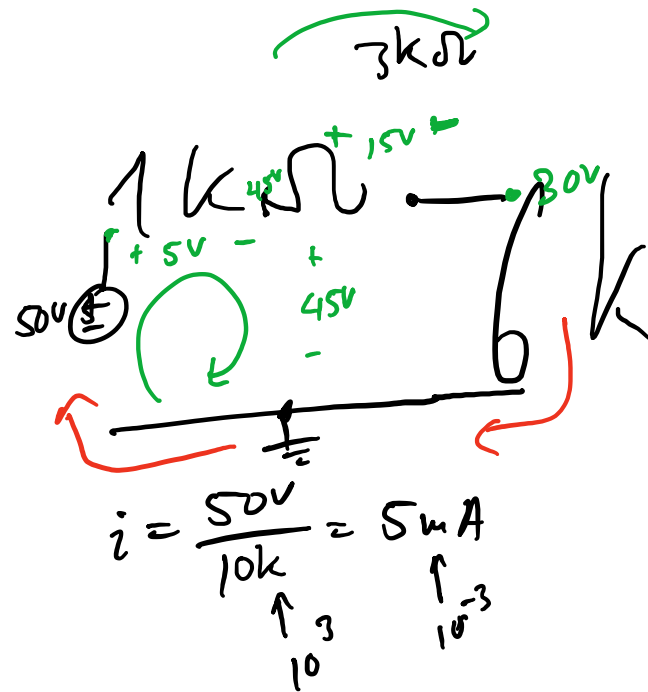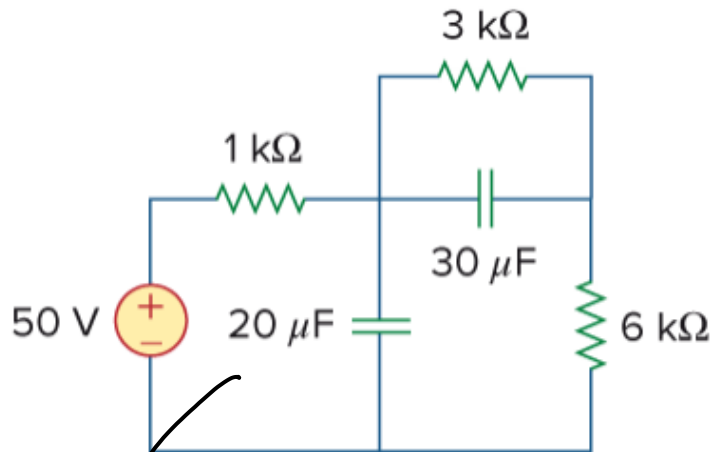Under dc conditions, find the energy stored in the capacitors in **Fig. 6.13**.



F
mF
μF
nF
pF
"puff"

$$w_e = \frac{1}{2} C v^2$$

$$= \frac{1}{2} 20 \mu F \cdot (45 V)^2$$

$$= 10 \cdot 10^{-6} F \cdot 2000 V^2$$

$$= 2 \cdot 10^4 \cdot 10^{-6} \cdot F V^2$$


$$= 0.02 \cdot F V^2$$

$$= 20 mJ$$

$$Q = C V \rightarrow F \cdot V \cdot V = \frac{F}{V} \cdot V \cdot \frac{J}{C}$$

Series and parallel


$$i = i_1 + i_2 + i_3 + \dots + i_N$$

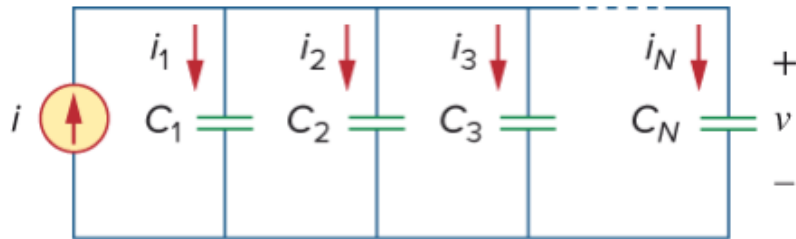

(a)



(b)

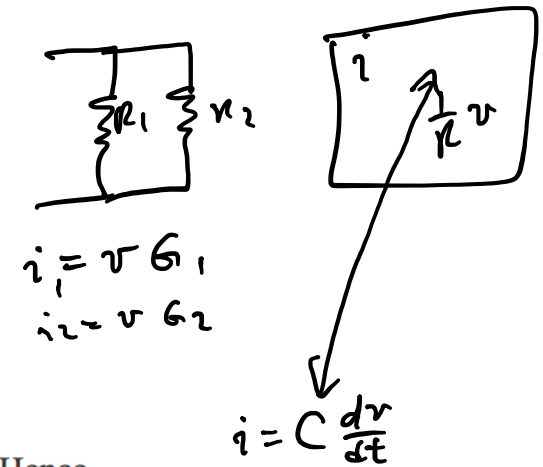

But $i_k = C_k dv/dt$. Hence,

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$


$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$

where


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

Series and parallel

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$

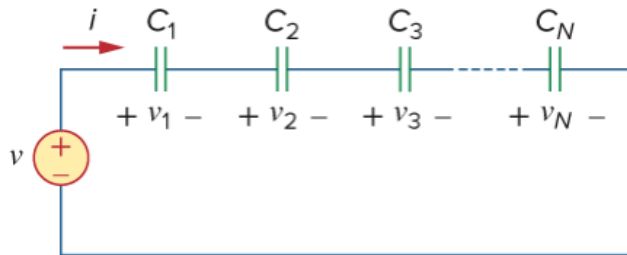

(a)

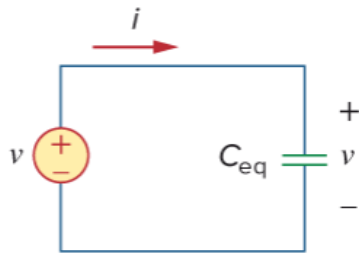

(b)

But $v_k = \frac{1}{C_k} \int_{t_0}^t i(\tau) d\tau + v_k(t_0)$. Therefore,

$$v = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) + \cdots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0)$$

$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \cdots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0) + \cdots + v_N(t_0)$$

$$= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

where

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots + \frac{1}{C_N}$$