

EK 307: Electric Circuits

Fall 2017

Lecture 17

Nov 7, 2017

Hayk Gevorgyan

Department of Electrical and Computer Engineering

Boston University


Last time (Lecture 16):



- **First-order circuits**
- **Source-free RC and RL circuits**
- **Singularity functions to represent step responses**
- **Discussed a driven RC circuit**

(covered Sections 7.1-7.4 and a little of 7.5)

Singularity functions: unit step, delta, ramp

$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$

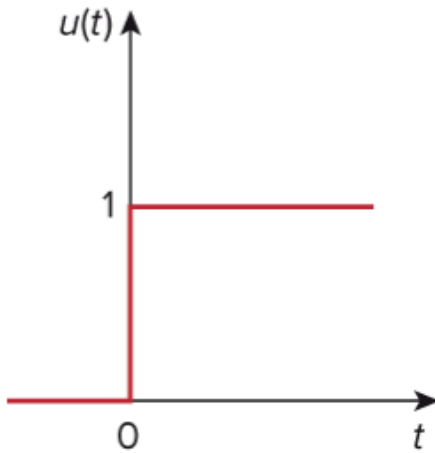

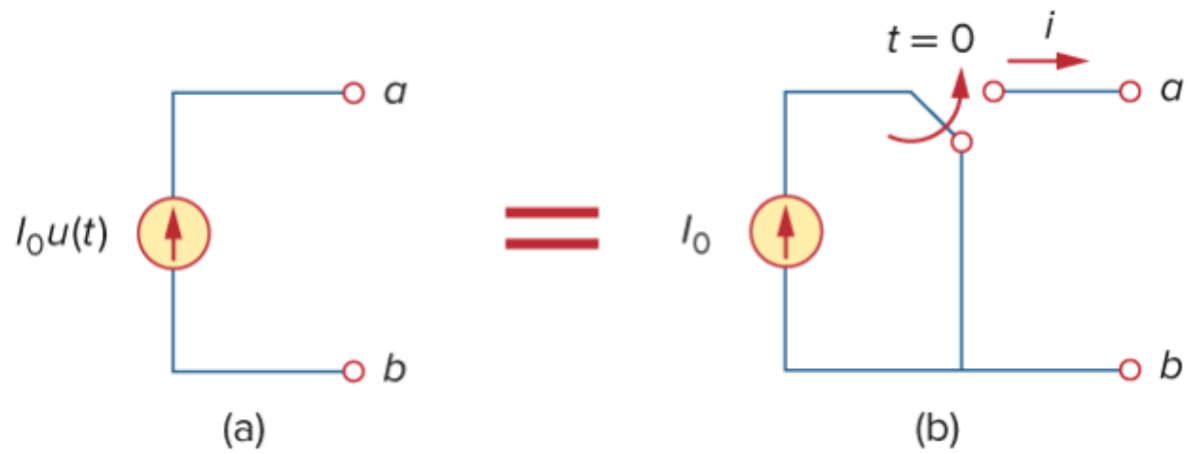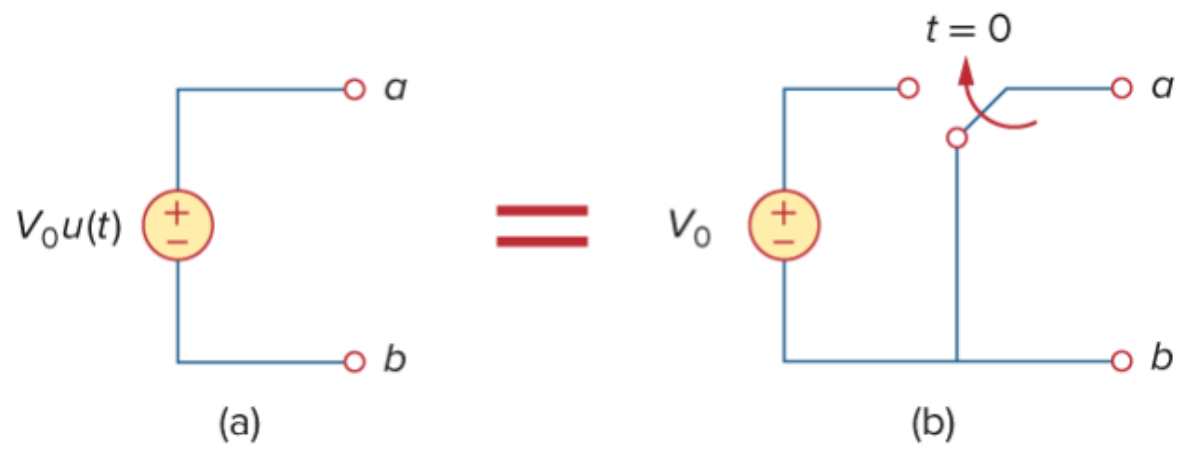

Lecture 17: Chapter 7: 1st order ccts

1. Driven RC and RL circuits
2. First-order op-amp circuits

(covering sections 7.5-7.7)



Step response

The **step response** of a circuit is its behavior when the excitation is the step function, which may be a voltage or a current source.


From last time: discussed physical intuition

$$v(0^-) = v(0^+) = V_0$$



Representation using switch:

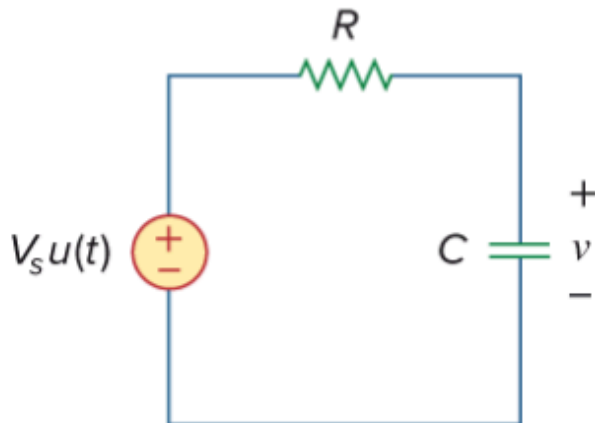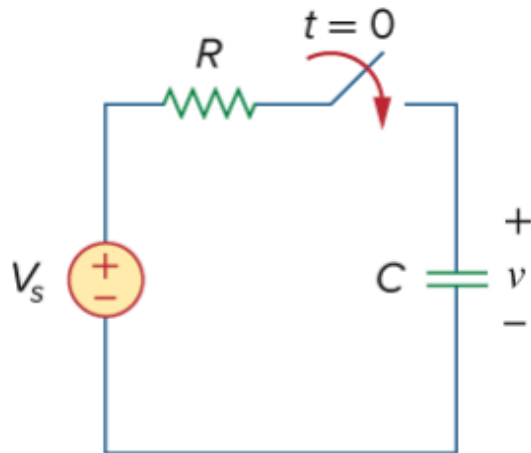


Representation using unit step function

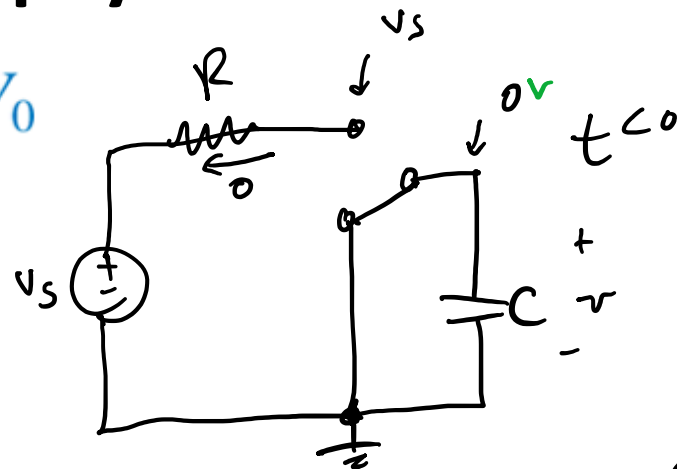

$$i = C \frac{dv}{dt}$$

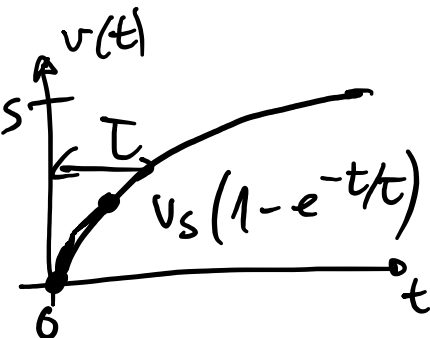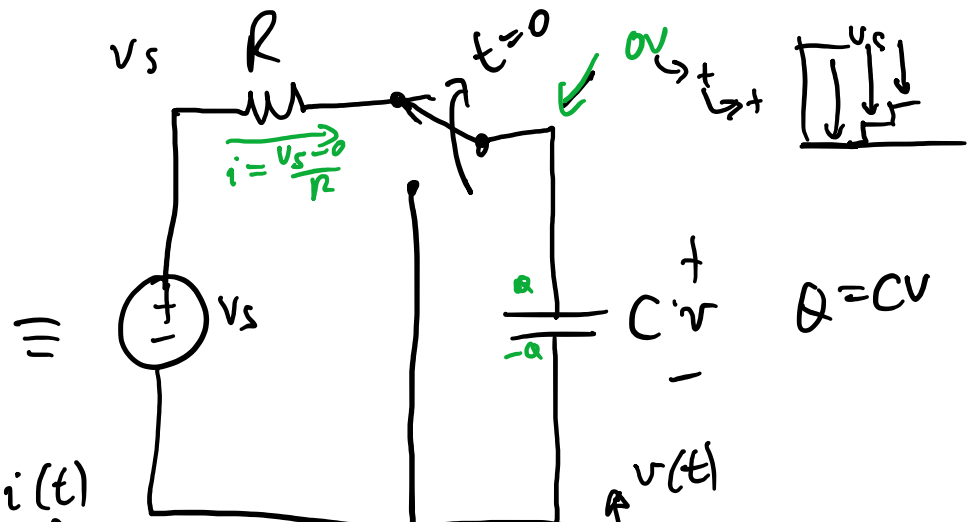

Solving for the step response

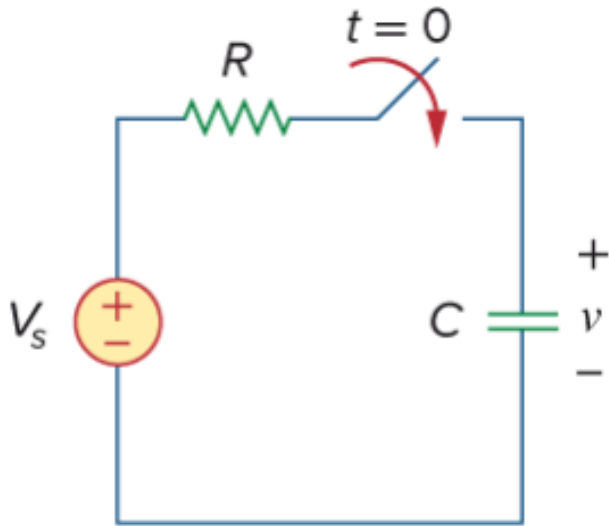

We write Kirchhoff's current law

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

or

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC} u(t)$$

where v is the voltage across the capacitor. For $t > 0$, **Eq. (7.41)** becomes

$$\frac{dv}{dt} + \frac{v}{RC} = \frac{V_s}{RC}$$

Rearranging terms gives

$$\frac{dv}{dt} = -\frac{v - V_s}{RC}$$

or


$$\frac{dv}{v - V_s} = -\frac{dt}{RC}$$

Integrating both sides and introducing the initial conditions,

$$\ln(v - V_s) \Big|_{V_0}^{v(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln(v(t) - V_s) - \ln(V_0 - V_s) = -\frac{t}{RC} + 0$$

Solving for the step response

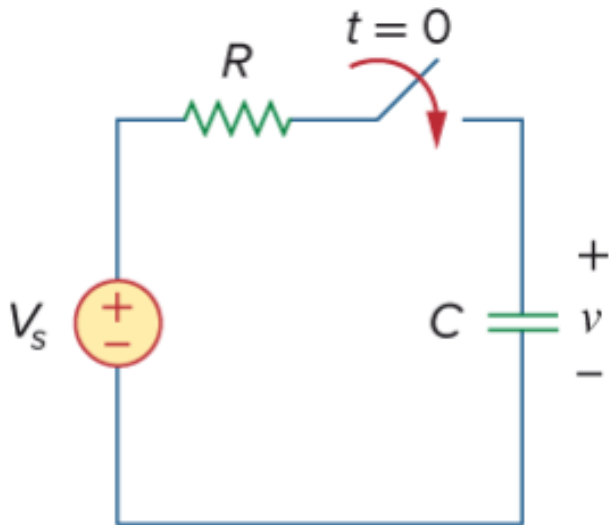

$$\ln \frac{v - V_s}{V_0 - V_s} = -\frac{t}{RC}$$

Taking the exponential of both sides

$$\frac{v - V_s}{V_0 - V_s} = e^{-t/\tau}, \quad \tau = RC$$

$$v - V_s = (V_0 - V_s)e^{-t/\tau}$$

or


$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad t > 0$$

Thus,

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$


This is known as the **complete (or total) response** of circuit to sudden turn-on of DC voltage source, assuming capacitor is initially charged.

Solving for the step response

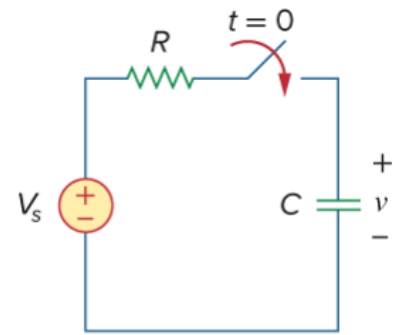


$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

Assuming that $V_s > V_0$:

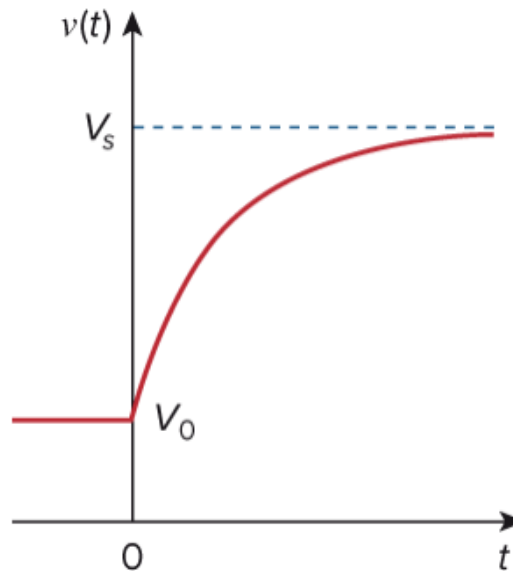

Solving for the step response

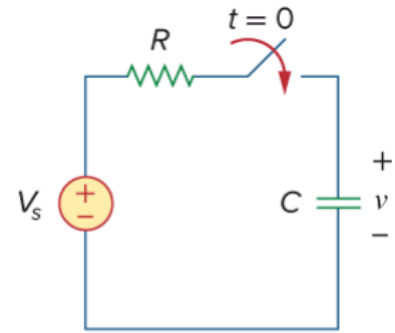

If capacitor is uncharged initially, then $V_0 = 0$ and

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$





$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases}$$


or

$$v(t) = V_s(1 - e^{-t/\tau})u(t)$$

Assuming that $V_s > V_0$:

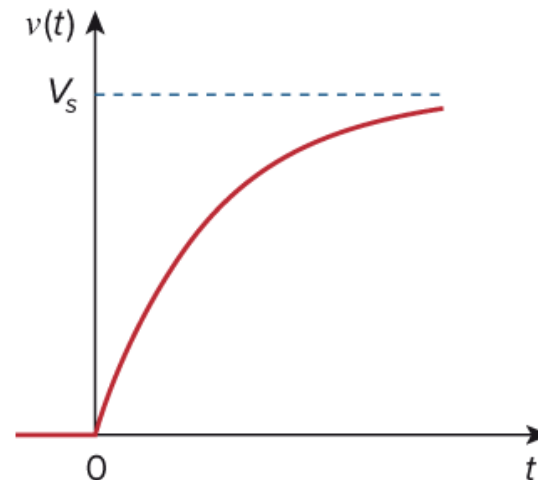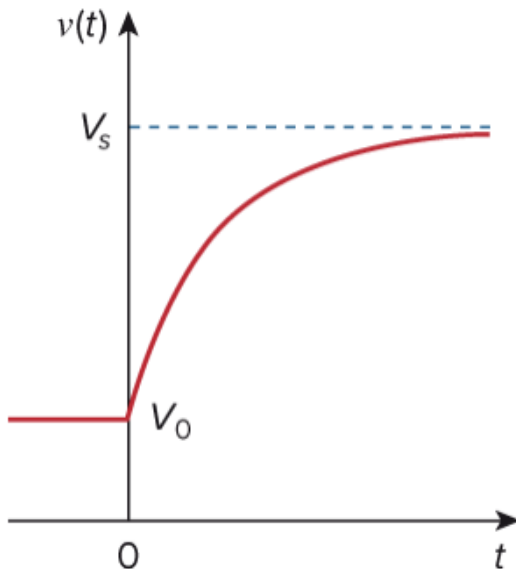

Solving for the step response

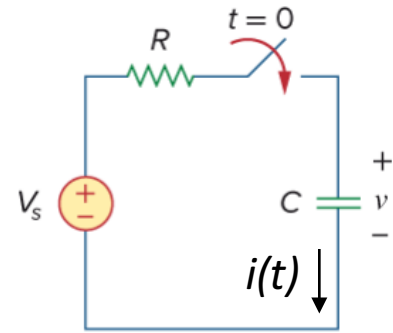


If capacitor uncharged initially, then $V_0 = 0$ and

$$v(t) = \begin{cases} 0, & t < 0 \\ V_s(1 - e^{-t/\tau}), & t > 0 \end{cases}$$

or

$$v(t) = V_s(1 - e^{-t/\tau})u(t)$$

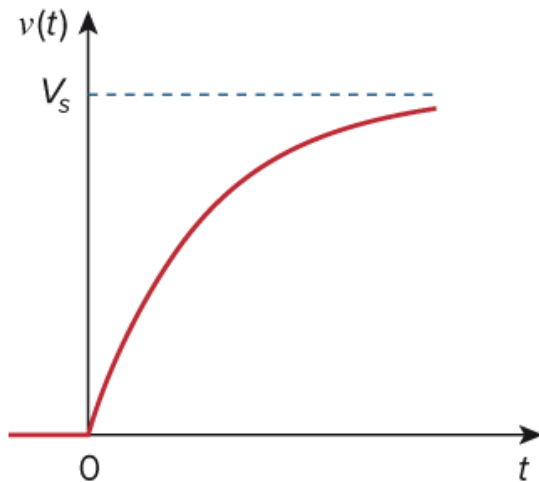


Voltage response

Current:

$$i(t) = C \frac{dv}{dt} = \frac{C}{\tau} V_s e^{-t/\tau}, \quad \tau = RC, \quad t > 0$$


or
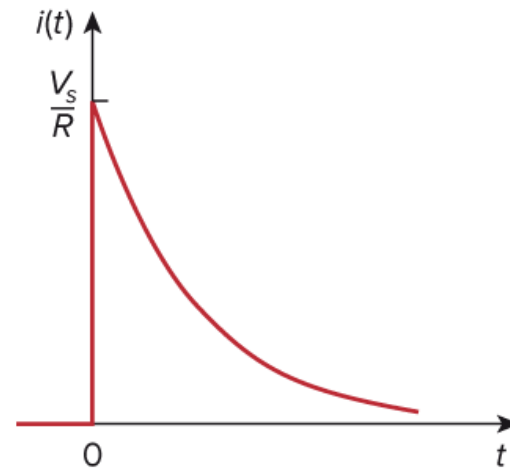
$$i(t) = \frac{V_s}{R} e^{-t/\tau} u(t)$$




Current response

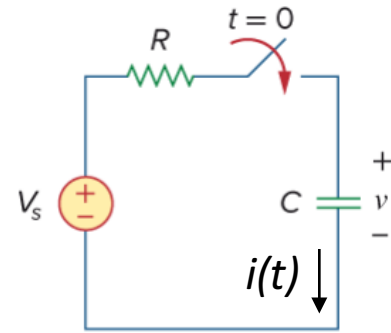Systematic shortcut method for step response of RC/RL circuit



$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

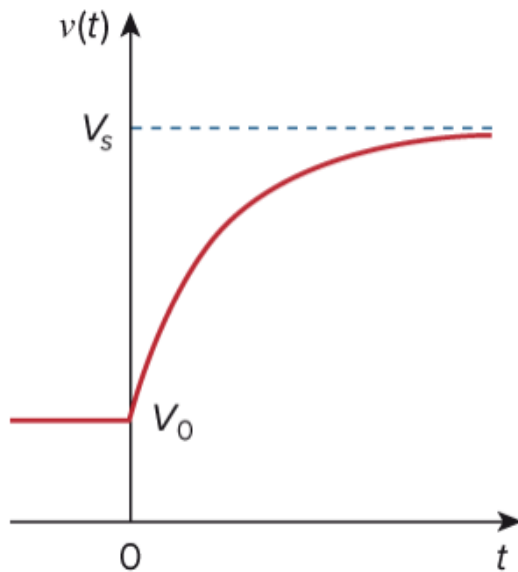Picture 1: Break down into natural and forced response



Voltage response


Complete response = natural response + forced response
stored energy independent source

$$v = v_n + v_f$$

$$v_n = V_0 e^{-t/\tau}$$


$$v_f = V_s(1 - e^{-t/\tau})$$

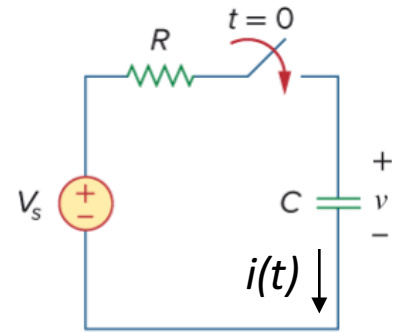Systematic shortcut method for step response of RC/RL circuit



$$v(t) = \begin{cases} V_0, & t < 0 \\ \boxed{V_s} + \boxed{(V_0 - V_s)e^{-t/\tau}}, & t > 0 \end{cases}$$

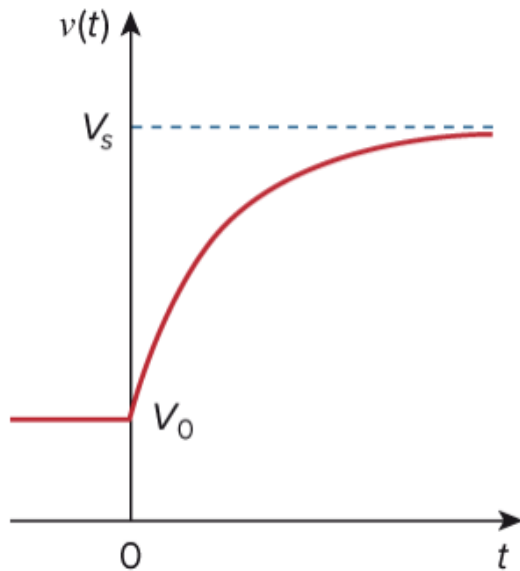Picture 2: Break down into **transient** + **steady state** responses




Voltage response

Complete response = transient response
temporary part + steady-state response
permanent part

The **transient response** is the circuit's temporary response that will die out with time.


The **steady-state response** is the behavior of the circuit a long time after an external excitation is applied.

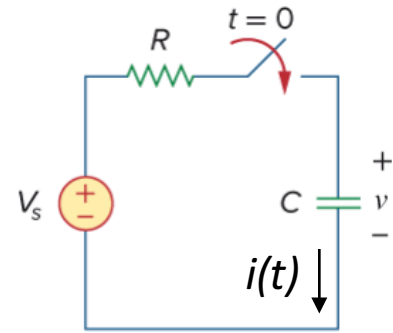Systematic shortcut method for step response of RC/RL circuit



$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau}, & t > 0 \end{cases}$$

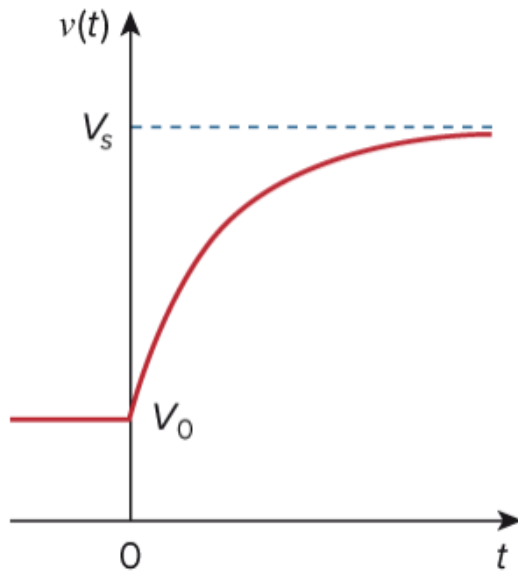Picture 2: Break down into **transient** + **steady state** responses



Voltage response


Complete response = transient response + steady-state response
temporary part permanent part

$$v = v_t + v_{ss}$$

$$v_t = (V_0 - V_s)e^{-t/\tau}$$

$$v_{ss} = V_s$$

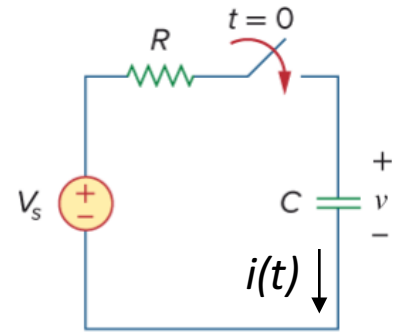
Systematic shortcut method for step response of RC/RL circuit



Either way, can write response for $t>0$ as:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$$

(For the capacitor voltage!)

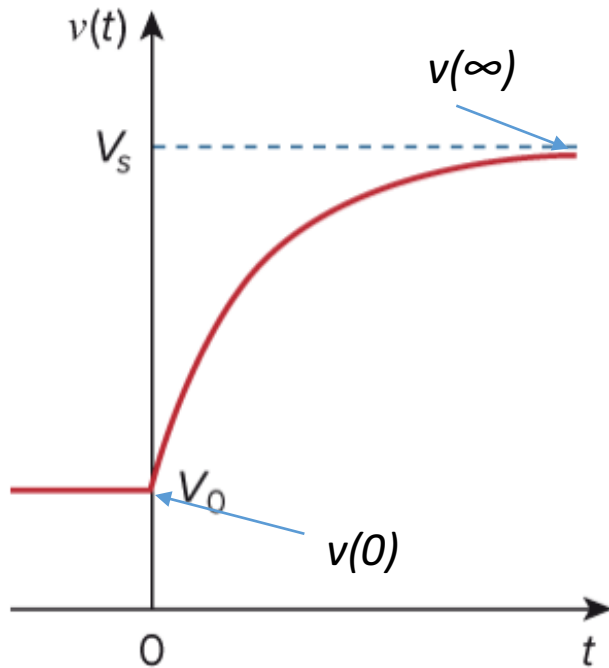



To find step response of RC circuit need 3 things:

1. Initial capacitor voltage, $v(0)$
2. Final capacitor voltage, $v(\infty)$
3. Time constant, τ

(Get #1 from cct at $t<0$, and #2,#3 from cct at $t>0$)

Practice Problem 7.10

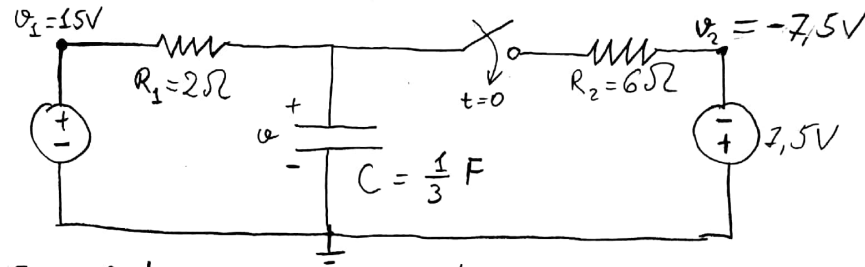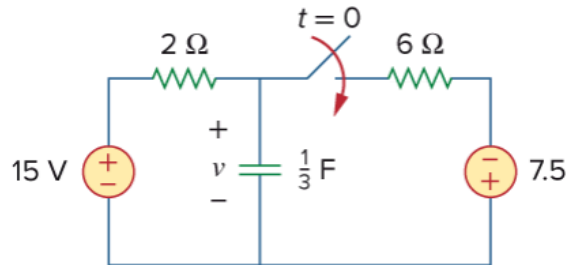Find $v(t)$ for $t > 0$ in the circuit of Fig. 7.44. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$.




Complete response = transient response + steady-state resp.

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

at $t = 0^-$ the switch is open. For dc voltage capacitor is open circuit, therefore

$$v(0) = v_1 = 15V$$

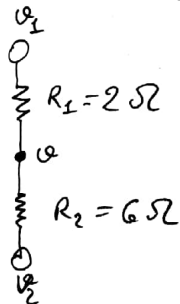at $t = \infty$ voltage on the capacitor is determined by voltage divider.




$$v(\infty) = v_2 + \frac{v_1 - v_2}{R_1 + R_2} =$$

$$= -7.5V + \frac{22.5V}{8\Omega} \cdot 6\Omega =$$

$$= -7.5V + 16.875V = 9.375V$$


Practice Problem 7.10

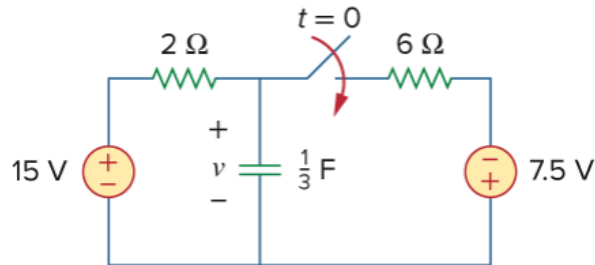Find $v(t)$ for $t > 0$ in the circuit of **Fig. 7.44**. Assume the switch has been open for a long time and is closed at $t = 0$. Calculate $v(t)$ at $t = 0.5$.



τ To find τ we need to find resistance seen by the capacitor i.e. Thevenin resistance.

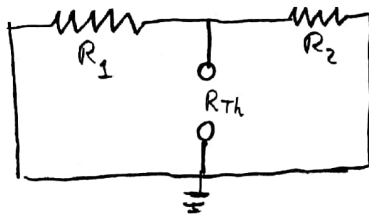Note, that output resistance of voltage source is 0.



$$R_T = \frac{R_1 R_2}{R_1 + R_2} \quad \tau = R_{Th} \cdot C = \frac{6 \cdot 2}{8} \cdot \frac{1}{3} \text{ s} = \frac{1}{2} \text{ s}$$




$v(t)$

$$v(t) = 9.375 \text{ V} + (15 - 9.375) e^{-2t} \text{ V} = (9.375 + 5.625 e^{-2t}) \text{ V}$$

$$v(0.5) = (9.375 + 2.0693) \text{ V} = 11.44 \text{ V}$$


Practice Problem 7.11

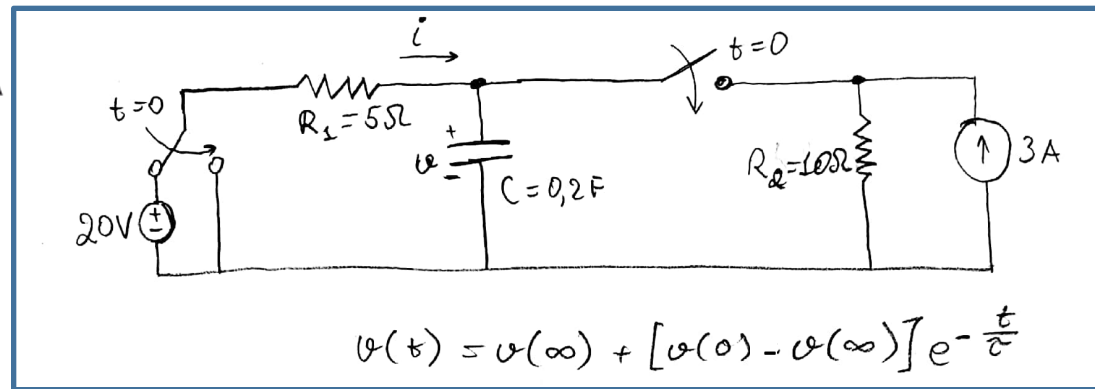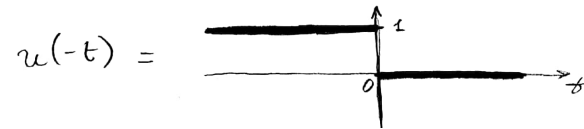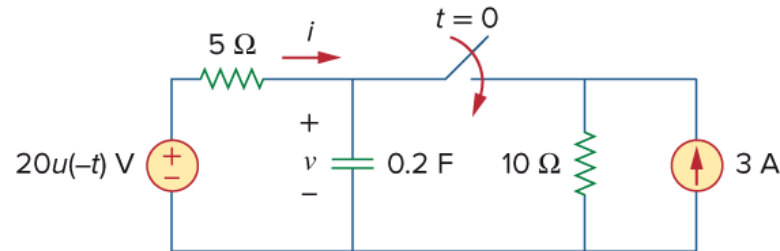The switch in **Fig. 7.47** is closed at $t = 0$. Find $i(t)$ and $v(t)$ for all time. Note that $u(-t) = 1$ for $t < 0$ and 0 for $t > 0$. Also, $u(-t) = 1 - u(t)$.



$t < 0$ For DC signal capacitor has infinite resistance.
 $\Rightarrow i(t) = 0 \Rightarrow v(t) = 20V, t < 0 \Rightarrow v(0) = 20V$

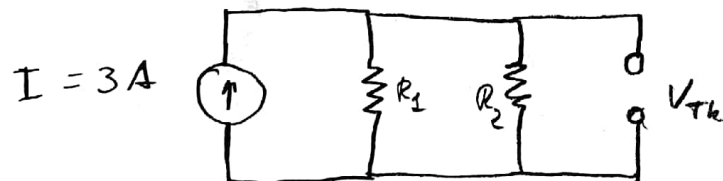
$t = \infty$ Infinitely long time after switches are turned, voltage on the capacitor can be found from equivalent circuit



$$v(\infty) = \frac{R_1 R_2}{R_1 + R_2} \cdot I = \frac{50}{15} \cdot 3V = 10V$$

Practice Problem 7.11

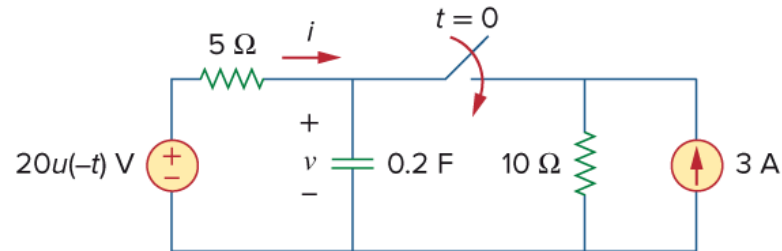The switch in **Fig. 7.47** is closed at $t = 0$. Find $i(t)$ and $v(t)$ for all time. Note that $u(-t) = 1$ for $t < 0$ and 0 for $t > 0$. Also, $u(-t) = 1 - u(t)$.



τ Output resistance of a current source is $\infty \Rightarrow$

\Rightarrow

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$


$$\tau = R_{Th} \cdot C = \frac{50}{15} \cdot \frac{1}{5} \text{ s} = \frac{10}{15} \text{ s}$$

$v(t), i(t)$

$t > 0 \quad v(t) = 10 \text{ V} + (20 - 10)e^{-1.5t} \text{ V} = 10(1 + e^{-1.5t}) \text{ V}$

$t > 0 \quad i(t) = -\frac{v(t)}{R_1} = -2(1 + e^{-1.5t}) \text{ A}$


Step Response of RL Circuits

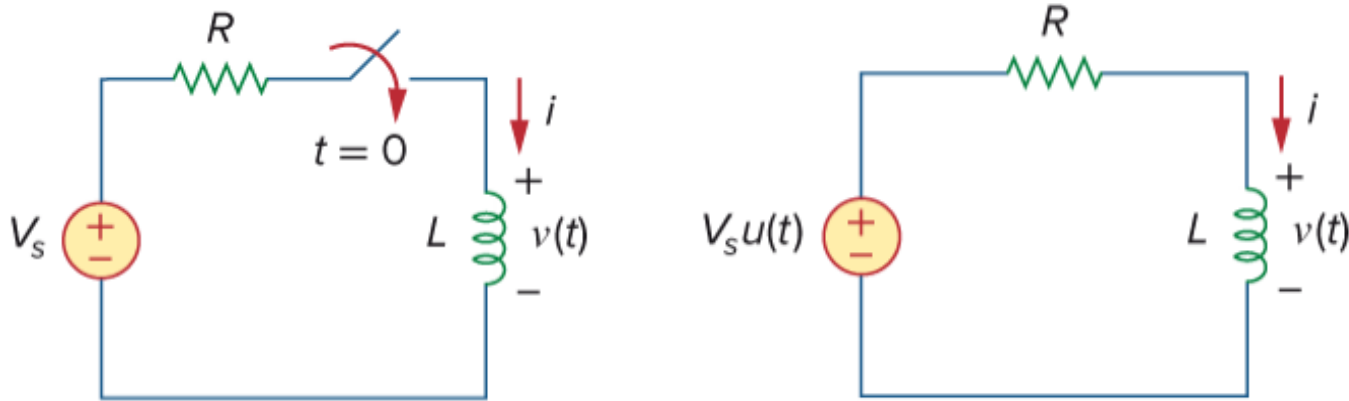

Same as RC, but here response is for inductor current (it's always the variable that stores energy – $\frac{1}{2}Cv^2$ for cap, $\frac{1}{2}Li^2$ for inductors)


$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$\tau = \frac{L}{R}$$


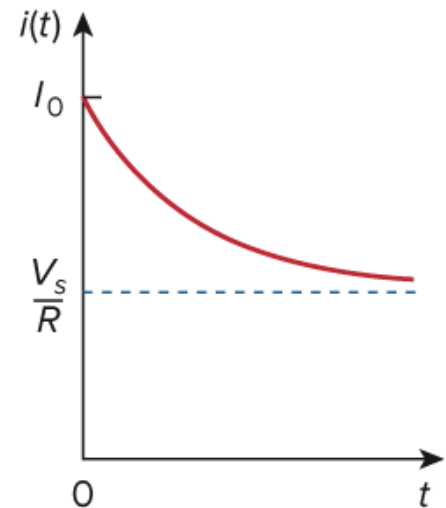


Step Response of RL Circuits
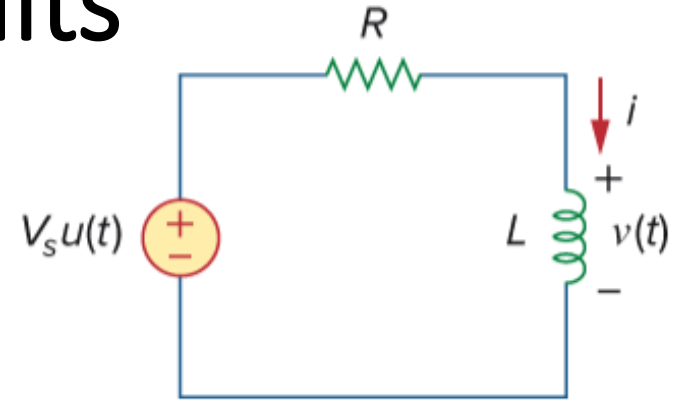
$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$





$$i(t) = \begin{cases} 0, & t < 0 \\ \frac{V_s}{R}(1 - e^{-t/\tau}), & t > 0 \end{cases}$$

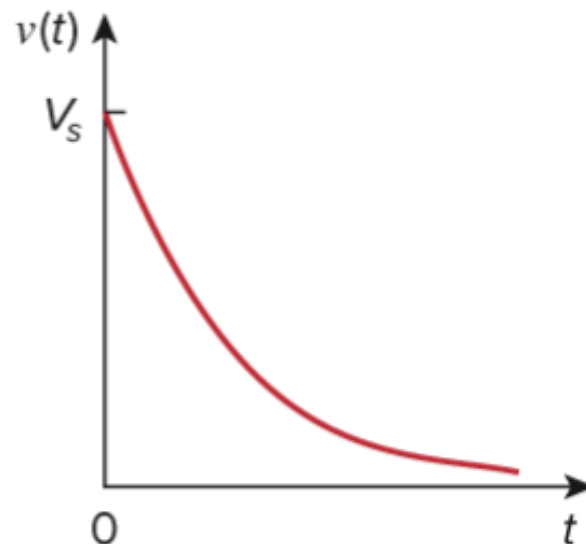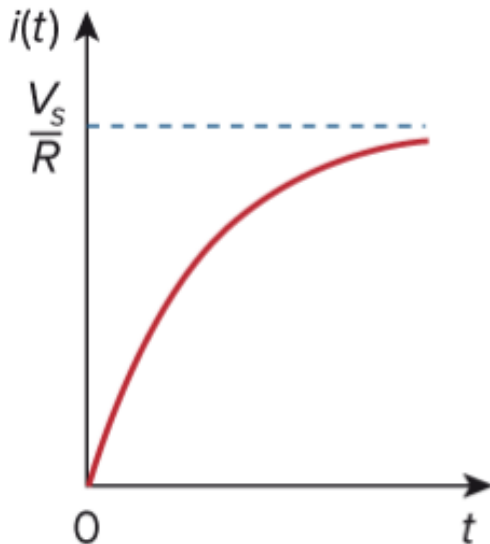


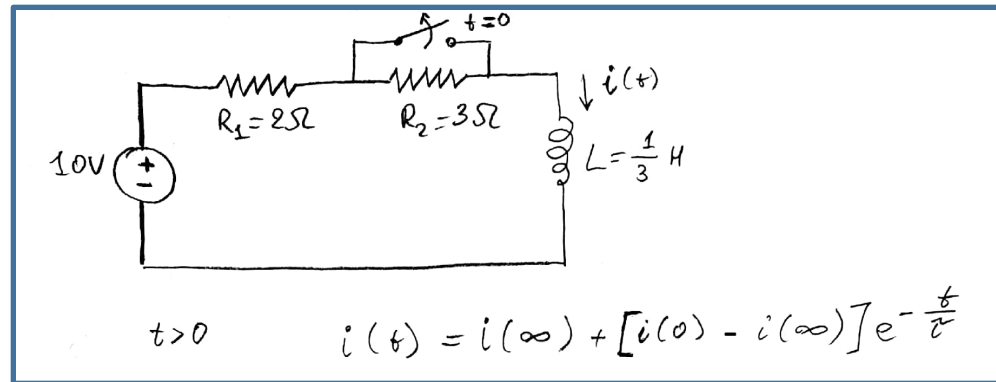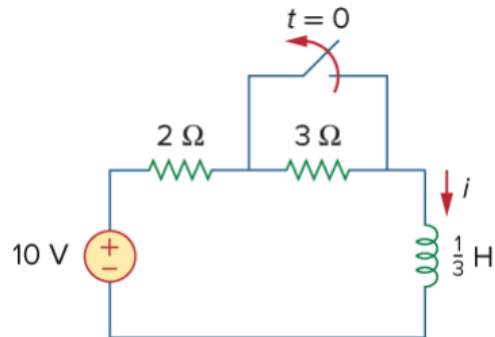Example 7.12

Find $i(t)$ in the circuit of **Fig. 7.51** for $t > 0$. Assume that the switch has been closed for a long time.



$t < 0$ equivalent circuit

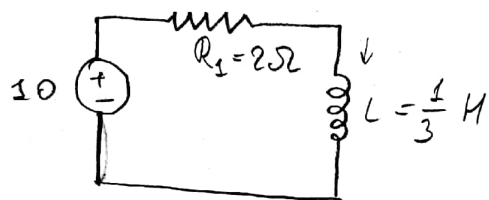


For DC current inductor is a short circuit \Rightarrow

$$\Rightarrow i(t) = \frac{10V}{2\Omega} = 5A, \quad t < 0$$

$$\Downarrow$$

$$i(0) = 5A$$


$t = \infty$

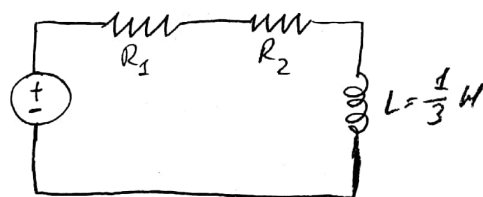


$$i(\infty) = \frac{10}{R_1 + R_2} = 2A$$

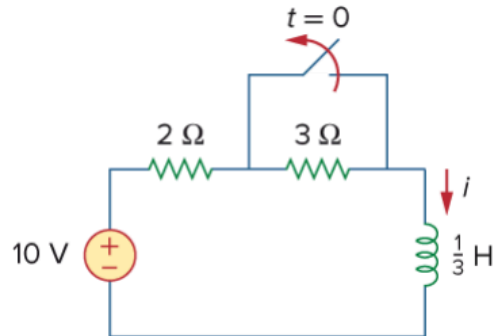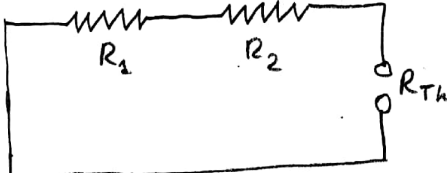Example 7.12

Find $i(t)$ in the circuit of **Fig. 7.51** for $t > 0$. Assume that the switch has been closed for a long time.



τ

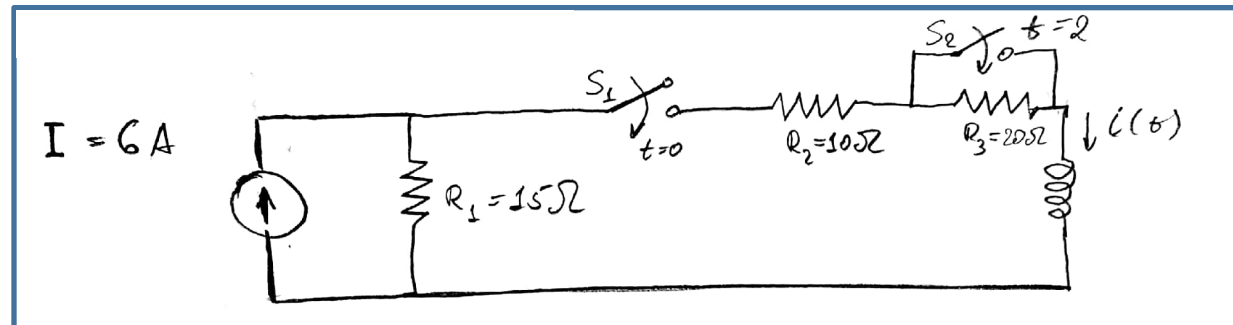
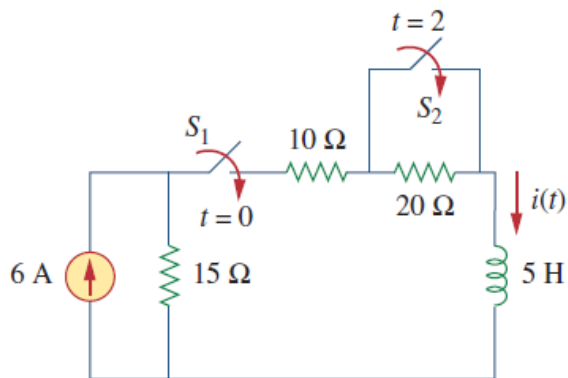

$$\tau = \frac{L}{R_{Th}} = \frac{L}{R_1 + R_2} = \frac{1}{3} \cdot \frac{1}{5} \text{ s} = \frac{1}{15} \text{ s}$$

$i(t)$

$$i(t) = 2 \text{ A} + (5 \text{ A} - 2 \text{ A}) e^{-15t} = (2 + 3e^{-15t}) \text{ A}$$


Practice Problem 7.13

Switch S_1 in Fig. 7.54 is closed at $t = 0$, and switch S_2 is closed at $t = 2$ s. Calculate $i(t)$ for all t . Find $i(1)$ and $i(3)$.



$t < 0$ All the current flows through R_1 , therefore
 $i(t) = 0, t < 0 \Rightarrow i(0) = 0$

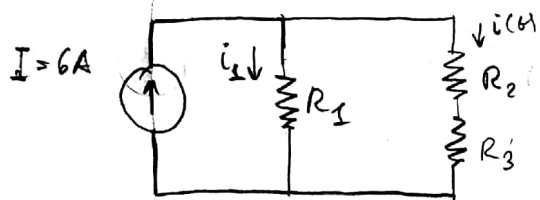$0 < t < 2$ equivalent circuit at $t \rightarrow \infty$, assuming S_2 switch stays open all the time.



$t \rightarrow \infty$

R_1 and series combination of R_2 and R_3 are connected in parallel, \Rightarrow

$$\Rightarrow i_1 R_1 = i(\infty)(R_2 + R_3) \quad \text{also} \quad i_1 + i(\infty) = I$$



$$\Downarrow$$

$$[I - i(\infty)] R_1 = i(\infty)(R_2 + R_3)$$

$$i(\infty) = \frac{I R_1}{R_1 + R_2 + R_3} = \frac{6 \cdot 15}{45} = 2 \text{ A}$$

Practice Problem 7.13

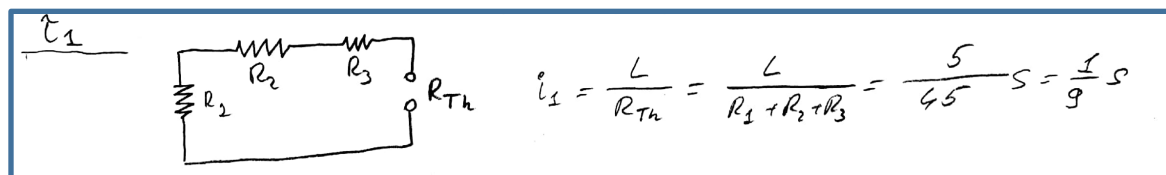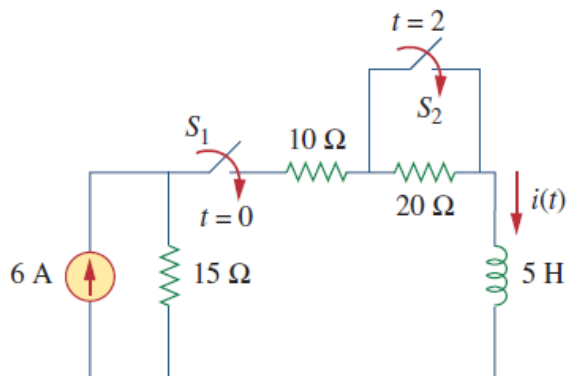Switch S_1 in Fig. 7.54 is closed at $t = 0$, and switch S_2 is closed at $t = 2$ s. Calculate $i(t)$ for all t . Find $i(1)$ and $i(3)$.




$i(t), 0 < t < 2$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

$$i(t) = 2A + (0 - 2)e^{-9t}A = 2(1 - e^{-9t})A$$

$t = 2 \text{ s} \gg \tau_1 \Rightarrow i(2) = 2A$

$t > 2$

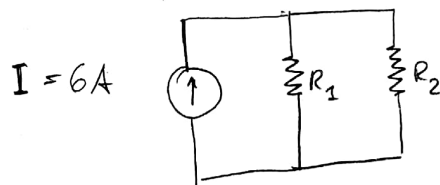

$$i(\infty) = \frac{I R_1}{R_1 + R_2} = \frac{6 \cdot 15}{25} A = 3.6 A$$

$$\tau_2 = \frac{L}{R_1 + R_2} = \frac{5}{25} \text{ s} = \frac{1}{5} \text{ s}$$

$i(t), t > 2$

$$i(t) = i(\infty) + [i(2) - i(\infty)]e^{-5(t-2)} = 3.6 - 1.6e^{-5(t-2)}$$

complete response

$$i(t) = \begin{cases} 0, & t < 0 \\ 2(1 - e^{-9t})A, & 0 < t < 2 \\ 3.6 - 1.6e^{-5(t-2)}A, & t > 2 \end{cases}$$

$$i(1) = 1.9938A \quad i(3) = 3.583A$$


First-order op-amp circuits

- Op-amp cct containing a storage element (C or L)
- Differentiators and integrators, already covered before, are examples of first-order op amp ccts
- For practical reasons, inductors are hardly ever used in op amp circuits because they are large.
- Therefore, the op amp circuits we consider here are of the *RC* type.

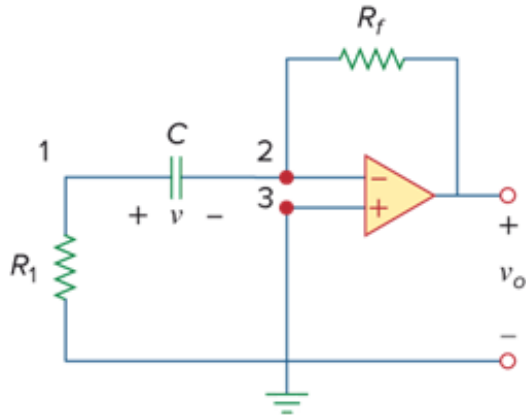
Example 7.14

For the op amp circuit in **Fig. 7.55(a)**, find v_o for $t > 0$, given that $v(0) = 3$ V.

Let $R_f = 80$ k Ω , $R_1 = 20$ k Ω , and $C = 5$ μ F.




(a)

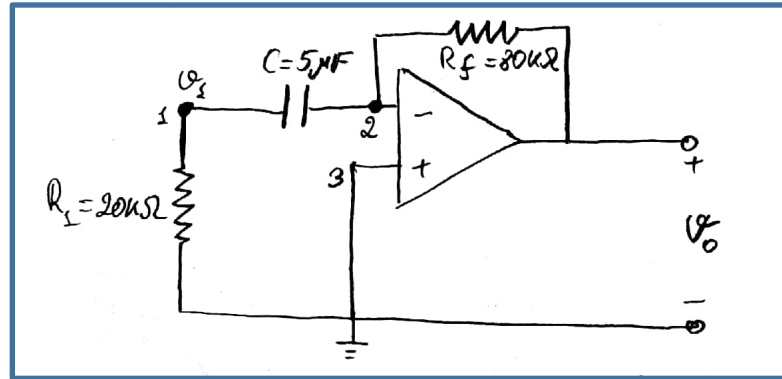

We write Kirchhoff's current law for point 1

$$\frac{0 - v_i}{R_i} = C \frac{dv_o}{dt}$$

op-amp equivalent circuit

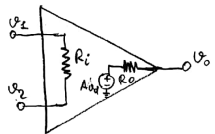

ideal op-amp

$$\begin{aligned} A &= \infty \\ R_i &= \infty \Omega \\ R_o &= 0 \Omega \\ i_1 &= i_2 = 0 \\ v_1 &= v_2 \end{aligned}$$


ideal op-amp $\Rightarrow v_1 = v_2 = 0 \Rightarrow v_i = 0 \Rightarrow$

$$\frac{dv_o}{dt} + \frac{v_o}{CR_i} = 0$$

$$v(t) = v_o e^{-\frac{t}{\tau}} \quad \tau = CR_i, \quad v_0 = v(0) = 3 \text{ V}$$

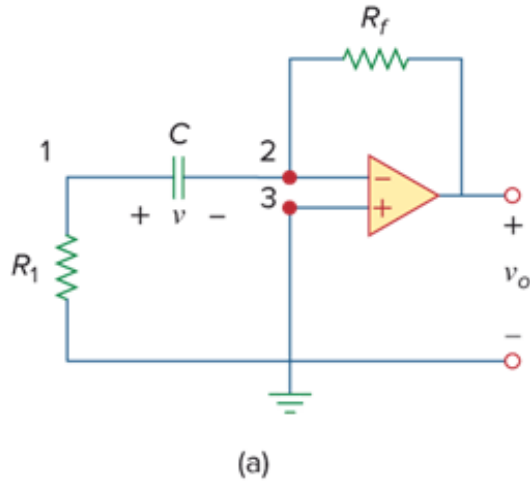Example 7.14

For the op amp circuit in **Fig. 7.55(a)**, find v_o for $t > 0$, given that $v(0) = 3 \text{ V}$.
Let $R_f = 80 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $C = 5 \mu\text{F}$.




KCL for point 2

$$C \frac{dv}{dt} = \frac{0 - v_o}{R_f} \Rightarrow v_o(t) = -CR_f \frac{dv}{dt}$$



$$v_o(t) = \frac{CR_f}{CR_1} V_0 e^{-\frac{t}{\tau}} = \frac{R_f}{R_1} V_0 e^{-\frac{t}{\tau}}$$

$$\tau = 5 \cdot 10^{-6} \text{ F} \cdot 20 \cdot 10^3 \Omega = 0,1 \text{ s}, \quad \frac{R_f}{R_1} = 4 \Rightarrow v_o(t) = 12 \text{ V} e^{-\frac{t}{0,1 \text{ s}}}$$

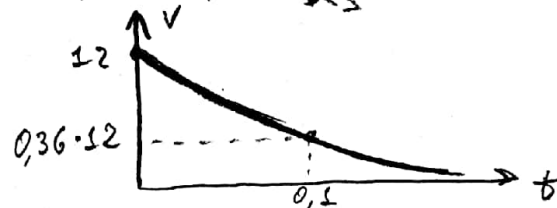

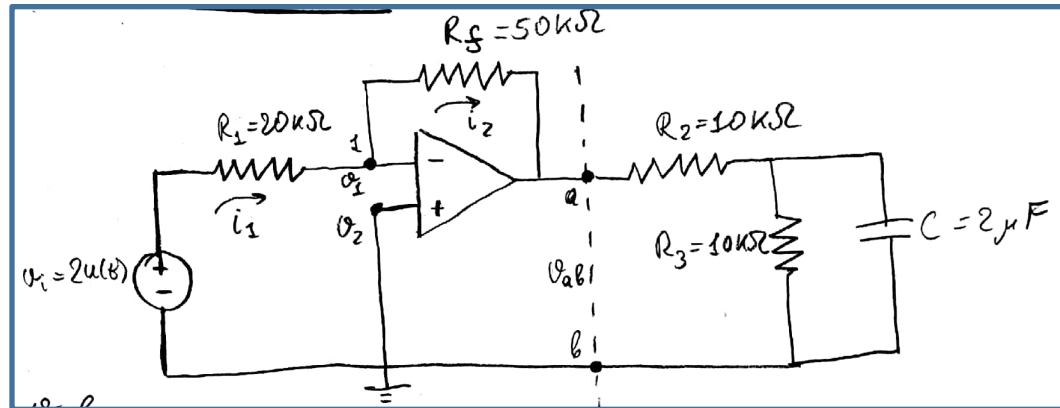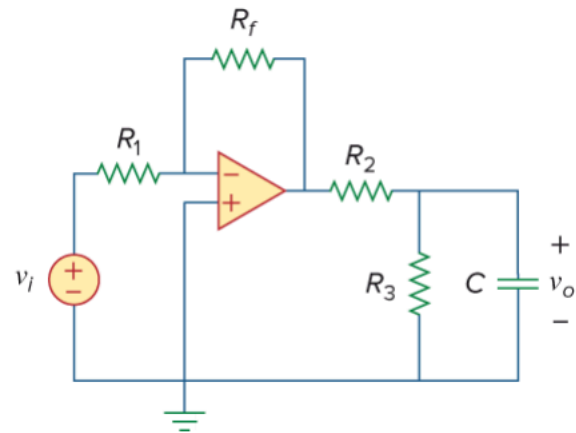Example 7.16

Find the step response $v_o(t)$ for $t > 0$ in the op amp circuit of Fig. 7.59. Let $v_i = 2u(t)$ V, $R_1 = 20 \text{ k}\Omega$, $R_f = 50 \text{ k}\Omega$, $R_2 = R_3 = 10 \text{ k}\Omega$, $C = 2 \mu\text{F}$.




v_{ab}

KCL for point 1

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_{ab}}{R_f}$$

$$v_1 = v_2 = 0 \Rightarrow \frac{v_i}{R_1} = -\frac{v_{ab}}{R_f} \Rightarrow v_{ab} = -\frac{R_f}{R_1} v_i$$



V_{th}

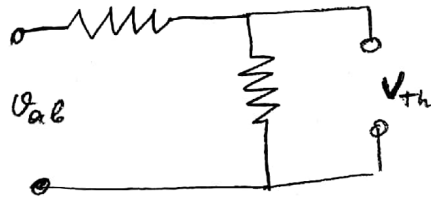


$$V_{th} = \frac{R_3}{R_2 + R_3} v_{ab} = -\frac{R_3}{R_2 + R_3} v_i$$

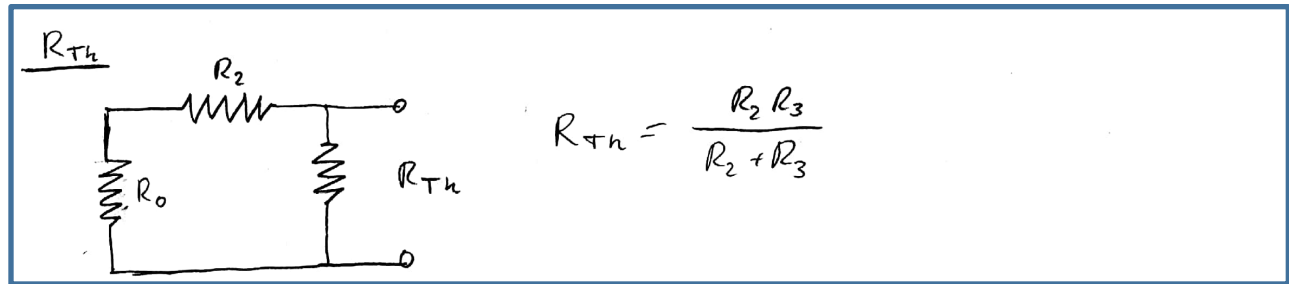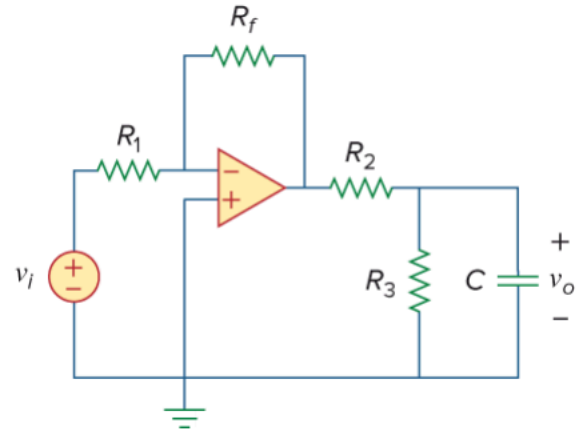Example 7.16

Find the step response $v_o(t)$ for $t > 0$ in the op amp circuit of Fig. 7.59. Let $v_i = 2u(t)$ V, $R_1 = 20 \text{ k}\Omega$, $R_f = 50 \text{ k}\Omega$, $R_2 = R_3 = 10 \text{ k}\Omega$, $C = 2 \mu\text{F}$.



equivalent circuit

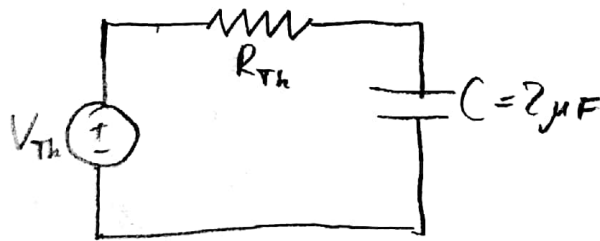

$$V_{Th} = -\frac{10}{20} \cdot \frac{50}{20} \cdot 2 u(t) = -2,5 u(t)$$

$$R_{Th} = \frac{R_2 R_3}{R_2 + R_3} = \frac{10 \cdot 10}{20} \text{ k}\Omega = 5 \text{ k}\Omega$$

$$\tau = R_{Th} \cdot C = 5 \cdot 10^3 \Omega \cdot 2 \cdot 10^{-6} \text{ F} = 0,01 \text{ s}$$

$$v_o(t) = v_o(\infty) + [v_o(0) - v_o(\infty)] e^{-\frac{t}{\tau}}, \quad t > 0$$

$$v_o(t) = -2,5 + [0 + 2,5] e^{-\frac{t}{0,01 \text{ s}}} = -2,5(1 - e^{-\frac{t}{0,01 \text{ s}}}) u(t)$$

