 


Self Checking Checkers


(Self-Checking Decoders for Error  
DETECTING / CORRECTING CODES)



$x = (v, R(v)) \in X$     -input code    FOR FAULT-FREE  $v, R(v)$   
 $z(x)$  output     $Z$  domain of  $z(x)$     range of  $z(x)$   
 $Z$  output code

Consider class  $F$  of faults in the checker

EX.  $F$  is SSFs.

 

DEF.1 Checker is fault-secure iff  
for  $\forall x \in X$  and  $\forall f \in F$

$Z_f(x) \notin Z$   
|  
Fault is detected  
by the checker

DEF.2 Checker is self-testing iff

For  $\forall f \in F \quad \exists x \in X : Z_f(x) \notin Z$   
 $\therefore$  there exists at least one fault-free  
 input which provokes a fault  $f \in F$  in  
 the checker and distorts the outputs of  
 the checker.

DEF 3 A circuit is a checker iff  
 for any  $x \notin X$   $z(x) \notin Z$   
 and  $x \in X$   $z(x) \in Z$ .


(This is also known as the code-disjoint  
 property)

DEF 4 A checker is self-checking iff  
 fault-secure and self-testing.

T1 A self-checking checker needs to have  
 at least two output lines, each of  
 which must take values 1 and 0  
 during normal operation.

 
EXAMPLES OF SELF CHECKING CHECKERS (SCC)

$X$  is an odd parity code of odd length  
 $(x_1, \dots, x_{2s+1}) \in X$  iff  $x_1 \oplus x_2 \oplus \dots \oplus x_{2s+1} = 1$



$F$  is a set of SSFs.

$Z = \{01, 10\}$

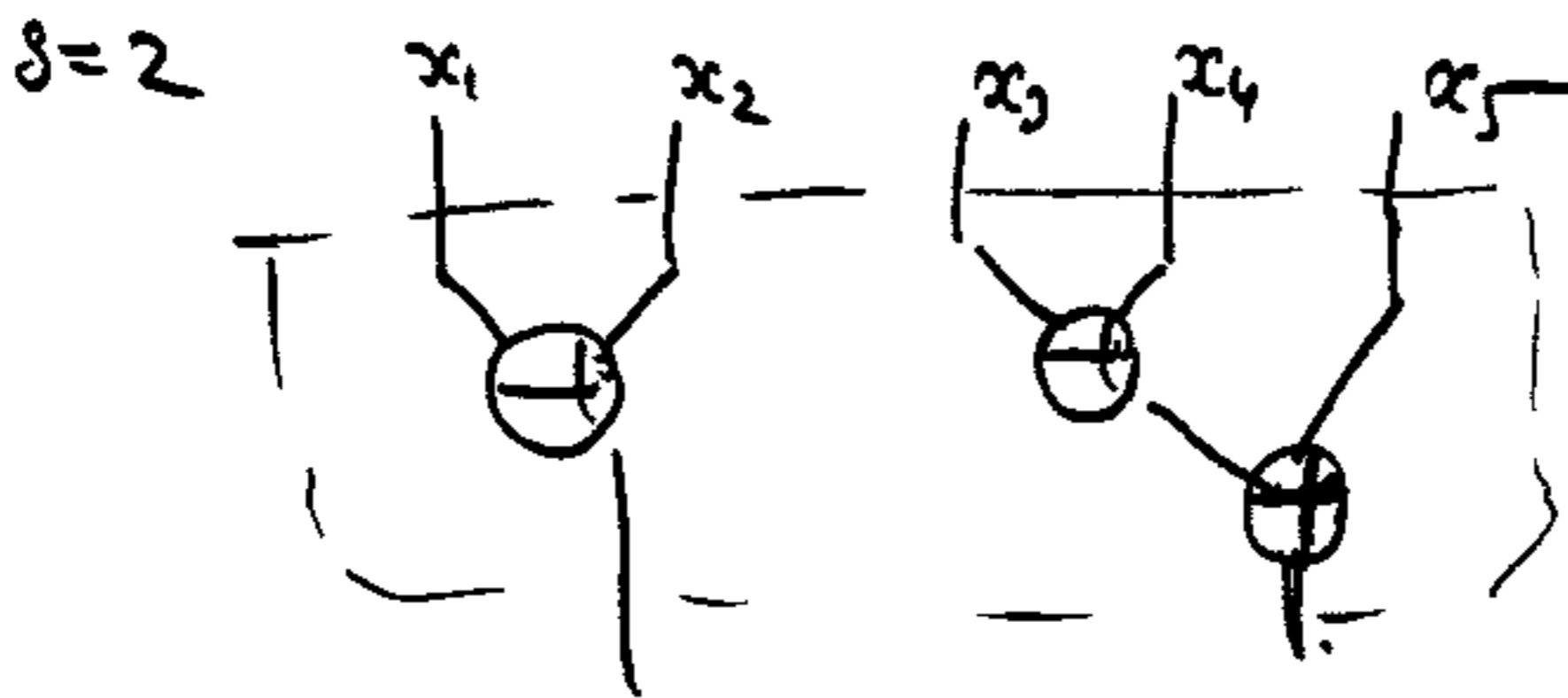


Self checking Checkers for  $K$  out of  $n$  codes and Berger codes can be found in: PRADHAN, FAULT TOLERANT COMPUTING vol 1, ch 5.

# Self-Testing Checker for

## PARITY VERIFICATION

Verify  $x_0 \oplus x_1 \oplus \dots \oplus x_{m-1} = 0 \Leftrightarrow x \in V$

Example  $m=8$

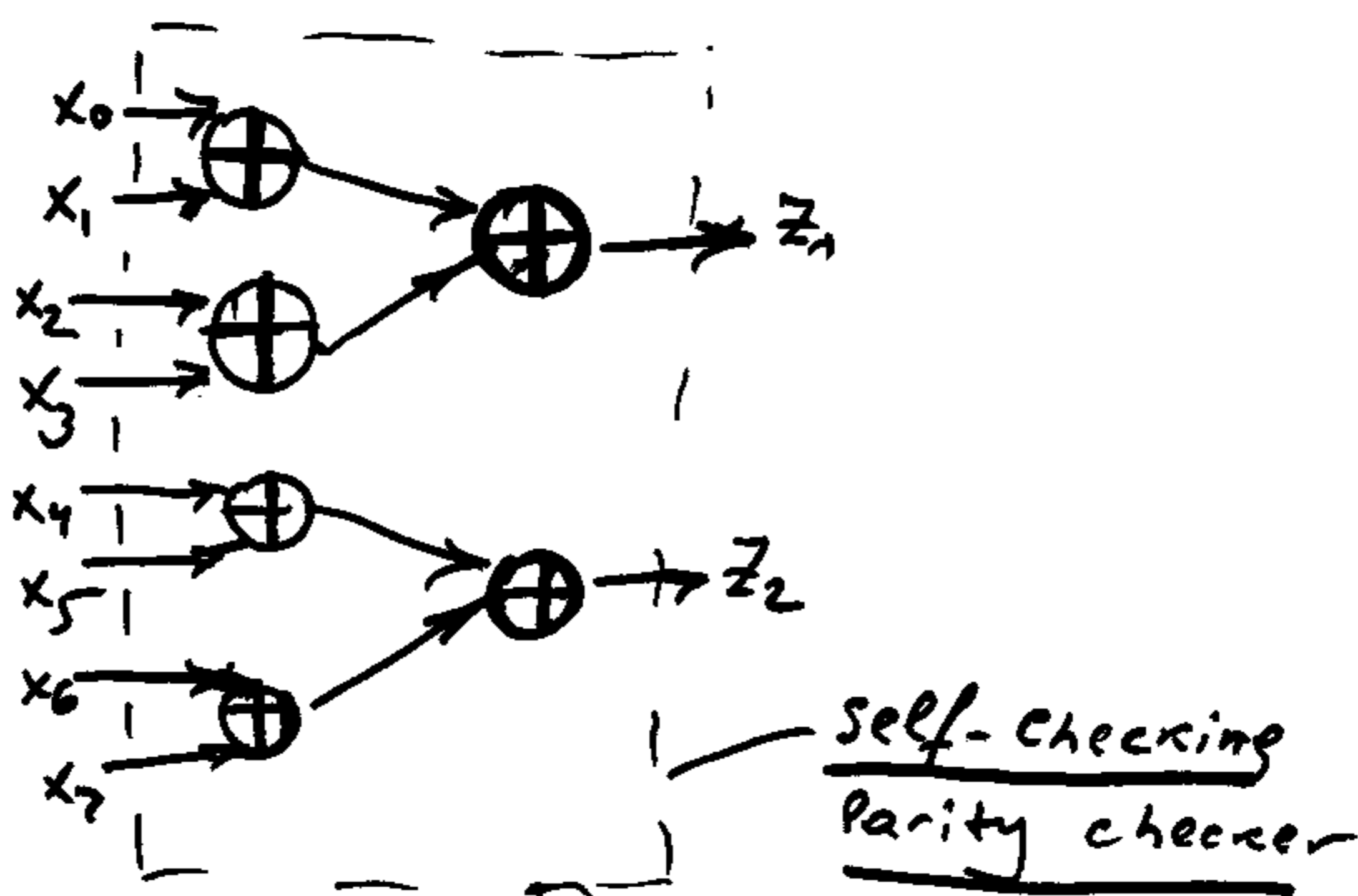

- 1) If  $x \in V$  and no faults in the checker  $\Rightarrow z_1 = z_2$
- 2) If  $x \notin V$  (odd number of ones in  $x$ ) and no faults in the checker  $z_1 \neq z_2$
- 3) If  $x \in V$  and there is a SSF in the checker then  $z_1 \neq z_2$ .

# TOTALLY SELF-CHECKING MATCH DETECTOR <sup>10/3/19</sup>


## MATCH DETECTOR

$$k=2$$

$$a = (a_0, a_1), \quad b = (b_0, b_1)$$

$$(a, b) \in C_{In} \Leftrightarrow a = b$$

$$C_{out} = \{01, 10\}$$

 

$$S_0 = 1 \quad a_0 = b_0 = a_1 = b_1$$


$$S_1 = 1 \quad a_0 = b_0 \neq a_1 = b_1$$

# DESIGN OF TOTALLY SELF-CHECKING CHECKERS (TSCC) 1980

Let  $f(x) = 1 \iff x \in C_{IN}$  - INPUT code  
 $x \in \{0, 1\}^n$

Represent  $f$  as  $h(x) \oplus g(x)$

Then

 

is a TSCC with  $C_{out} = \{01, 10\}$   
 iff  $C_{IN}$  is a test set for SSFs in  
 networks implementing  $h$  and  $g$ .

~~10/2~~  
10/2

DUAL-RAIL DESIGN OF  
TSCC with  $C_{out} = \{0, 1\}$


Let  $f(x) = 1 \iff x \in C_{in}$        $x \in \{0, 1\}^n$   
 $C_{in} \subseteq \{0, 1\}^n$

denote  $g(x) = \bar{f}(\bar{x})$

$\bar{x}$  - componentwise negation of  $x$

$g(x)$  called dual to  $f(x)$

$g(\bar{x}) = \text{NOT } f(x)$

 

$C_{IN}$  is a test for SSFs in  $f$  and  $g$

$f$  and  $g$  have the same complexity.

This approach is better than replication (duplication) of  $f$  (duplication does not provide for self-testing)



If  $f(x_1, x_2, \dots, x_n) = 1 \Leftrightarrow$

$(x_1, \dots, x_n) \in C_{IN}$  and all  $f$   
depends on all  $x_i$  and  $\bar{x}_i$  (non-unary  
 in all  $x_i$ )

then AND-XOR Reed-Muller  
 implementations of  $f$  and  $\mathcal{G}$   
 ( $\mathcal{G}$  is dual to  $f$ ) generates  
 a dual-rail TSCC for  $C_{IN}$   
 with  $C_{out} = \{01, 10\}$

Example 3 MR ( $\kappa=1$ )  
 $C_{IN} = \{000, 111\}$

$$f(x_1, x_2, x_3) = \bar{x}_1 \bar{x}_2 \bar{x}_3 + x_1 x_2 x_3 =$$

$$= (1 \oplus x_1)(1 \oplus x_2)(1 \oplus x_3) \oplus x_1 x_2 x_3 =$$

$$= 1 \oplus x_1 \oplus x_2 \oplus x_3 \oplus x_1 x_2 \oplus x_1 x_3 \oplus x_2 x_3$$

$$\mathcal{G}(x_1, x_2, x_3) = \bar{x}_1 \oplus \bar{x}_2 \oplus \bar{x}_3 \oplus \bar{x}_1 \bar{x}_2 \oplus \bar{x}_1 \bar{x}_3 \oplus \bar{x}_2 \bar{x}_3$$

